

EE 459/500 – HDL Based Digital Design with Programmable Logic


Lecture 11 FSM, ASM, FSMD, ASMD

*Read before class:
Chapters 4,5 from textbook*

Overview

- Finite State Machines (FSMs)
 - State Graphs: general form
 - Algorithmic State Machine (ASM) charts
- Finite State Machines with Datapath (FSMD)
- Algorithmic State Machine with Datapath (ASMD)

FSM – general form

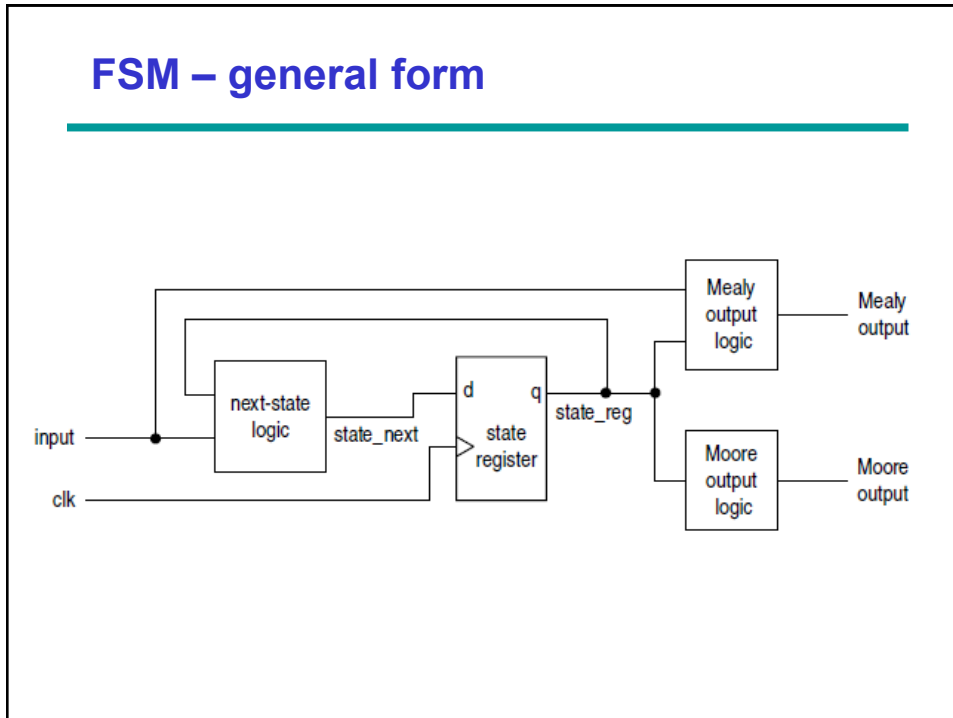


State Graph \leftrightarrow ASM chart


- State diagram:
 - **Nodes:** unique states of the FSM
 - **Transitional arcs:** labeled with the condition that causes the transition
- Algorithmic State Machine (ASM) chart is an alternative representation
 - Composed of a network of **ASM blocks**
 - ASM block:
 - **State box:** represents a state in the FSM
 - Optional network of **decision boxes** and **conditional output boxes**
- A state diagram can be converted to an ASM chart and vice-versa

State Graph \leftrightarrow ASM chart

State of State Graph


 


ASM Block

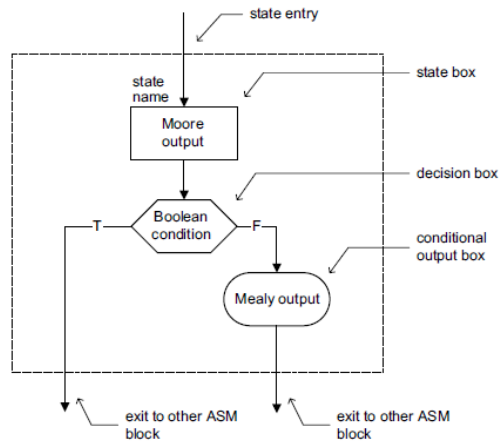

Example

Somewhat easier to write VHDL code for!

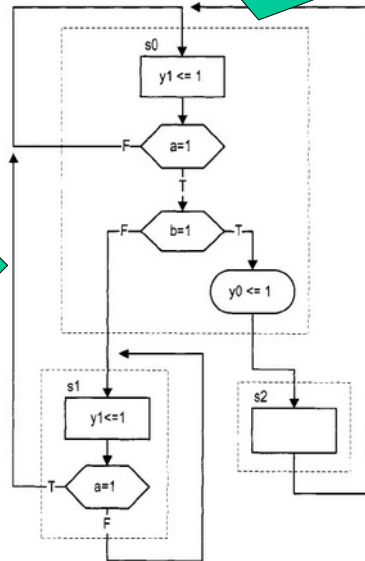 

VHDL code of example

```
library ieee;
use ieee.std_logic_1164.all;

entity fsm_eg is
  port(
    clk, reset: in std_logic;
    a, b: in std_logic;
    y0, y1: out std_logic
  );
end fsm_eg;

architecture two_seg_arch of fsm_eg is
  type eg_state_type is (s0, s1, s2);
  signal state_reg, state_next: eg_state_type;

begin

  -- state register
  process(clk,reset)
  begin
    if (reset='1') then
      state_reg <= s0;
    elsif (clk'event and clk='1') then
      state_reg <= state_next;
    end if;
  end process;


```

VHDL code of example

```
-- next-state/output logic
process(state_reg,a,b)
begin
  state_next <= state_reg; -- default back to same state
  y0 <= '0'; -- default 0
  y1 <= '0'; -- default 0
  case state_reg is
    when s0 =>
      y1 <= '1';
      if a='1' then
        if b='1' then
          state_next <= s2;
          y0 <= '1';
        else
          state_next <= s1;
        end if;
      -- no else branch
      end if;
    when s1 =>
      y1 <= '1';
      if (a='1') then
        state_next <= s0;
      -- no else branch
      end if;
    when s2 =>
      state_next <= s0;
  end case;
end process;
end two_seg_arch;
```

Overview


- Finite State Machines (FSMs)
 - State Graphs: general form
 - Algorithmic State Machine (ASM) charts
- **Finite State Machines with Datapath (FSMD)**
- ASM with Datapath (ASMD)

Finite State Machine with Data-path (FSMD)

- Combine an FSM and regular sequential circuits
- The FSM is called **control-path**; examines the external commands and status and generates control signals to specify operation of regular sequential circuits, which are known collectively as **data-path**
- FSMD used to implement systems described by **RT (register transfer) methodology**:
 - Operations are specified as data manipulation and transfer among a collection of registers


Block diagram of FSMD

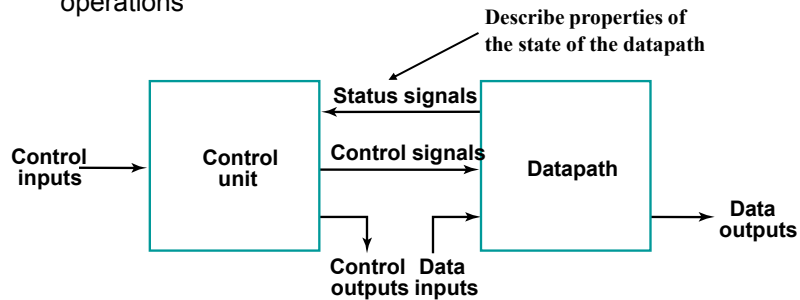- Datapath - performs data transfer and processing operations
- Control Unit - Determines the enabling and sequencing of the operations



- The control unit receives:
 - External control inputs
 - Status signals
- The control unit sends:
 - Control signals
 - Control outputs

Block diagram of FSMD (detailed)

 


Register Transfer Operations

- Register Transfer Operations - the movement and processing of data stored in registers
- Three basic components:
 - A set of registers (operands)
 - Transfer operations
 - Control of operations
- Elementary operations - called *microoperations*
 - load, count, shift, add, bitwise "OR", etc.
- Notation: $r_{dest} \leftarrow f(r_{src1}, r_{src2}, \dots, r_{srcn})$

Register Notation

 
- Letters and numbers – register (e.g. R2, PC, IR)
- Parentheses () – range of register bits (e.g. R1(1), PC(7:0), AR(L))



- Arrow (\leftarrow) – data transfer (ex. $R1 \leftarrow R2$, $PC(L) \leftarrow R0$)
- Brackets [] – Specifies a memory address (ex. $R0 \leftarrow M[AR]$, $R3 \leftarrow M[PC]$)
- Comma – separates parallel operations

Conditional Transfer

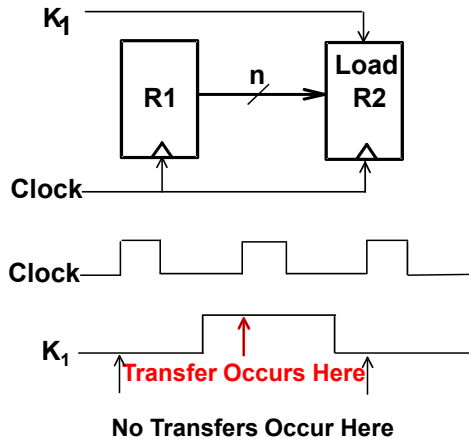- If $(K_1 = 1)$ then $(R2 \leftarrow R1)$
 $\Leftrightarrow K_1: (R2 \leftarrow R1)$
where K_1 is a control expression specifying a conditional execution of the microoperation.



Microoperations

- Logical groupings:
 - Transfer - move data from one set of registers to another
 - Arithmetic - perform arithmetic on data in registers
 - Logic - manipulate data or use bitwise logical operations
 - Shift - shift data in registers

Arithmetic operations

+ Addition
- Subtraction
* Multiplication
/ Division

Logical operations

∨ Logical OR
∧ Logical AND
⊕ Logical Exclusive OR
- Not

Example Microoperations

- $R1 \leftarrow R1 + R2$
 - Add the content of R1 to the content of R2 and place the result in R1.
- $PC \leftarrow R1 * R6$
- $R1 \leftarrow R1 \oplus R2$
- $(K1 + K2): R1 \leftarrow R1 \vee R3$
 - On condition $K1$ OR $K2$, the content of R1 is Logic bitwise ORed with the content of R3 and the result placed in R1.
 - NOTE: "+" (as in $K_1 + K_2$) means "OR." In $R1 \leftarrow R1 + R2$, + means "plus".

Arithmetic Microoperations

Symbolic Designation	Description
$R0 \leftarrow R1 + R2$	Addition
$R0 \leftarrow \overline{R1}$	Ones Complement
$R0 \leftarrow \overline{R1} + 1$	Two's Complement
$R0 \leftarrow R2 + \overline{R1} + 1$	R2 minus R1 (2's Comp)
$R1 \leftarrow R1 + 1$	Increment (count up)
$R1 \leftarrow R1 - 1$	Decrement (count down)

- Any register may be specified for source 1, source 2, or destination.
- These simple microoperations operate on the whole word

Logical Microoperations

Symbolic Designation	Description
$R0 \leftarrow \overline{R1}$	Bitwise NOT
$R0 \leftarrow R1 \vee R2$	Bitwise OR (sets bits)
$R0 \leftarrow R1 \wedge R2$	Bitwise AND (clears bits)
$R0 \leftarrow R1 \oplus R2$	Bitwise EXOR (complements bits)

Shift Microoperations


- Let R2 = 11001001

Symbolic Designation	Description	R1 content
$R1 \leftarrow sl R2$	Shift Left	10010010
$R1 \leftarrow sr R2$	Shift Right	01100100

- Note: These shifts "zero fill". Sometimes a separate flip-flop is used to provide the data shifted in, or to "catch" the data shifted out.
- Other shifts are possible (rotates, arithmetic)

Example

- $a \leftarrow a - b + 1$

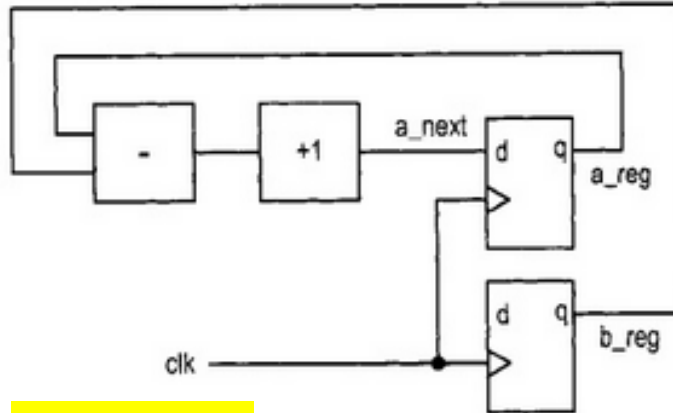

Block diagram


Overview

- Finite State Machines (FSMs)
 - State Graphs: general form
 - Algorithmic State Machine (ASM) charts
- Finite State Machines with Datapath (FSMD)
- Algorithmic State Machine with Datapath (ASMD)

Algorithmic State Machine with Data-path (ASMD)


- Extend ASM chart to incorporate RT operations and call it ASMD (ASM with data-path):

ASMD segment

 


Block diagram:

Implementing the RT operations

 


Location of RT operation inside ASM block

ASM block

 

Block diagram

 


Decision box with a register

- RT operation in an ASMD chart is controlled by an embedded clock signal
- Destination register is updated **when the machine exits the current ASMD block**, but not within the block!
- Example: $r \leftarrow r - 1$ means
 - $r_next \leq r_reg - 1$;
 - $r_reg \leq r_next$ at the rising edge of the clock (when machine exits current block)

Example

- Fibonacci number circuit
- A sequence of integers
- $fib(i) =$
 - 0, if $i = 0$
 - 1 if $i = 1$
 - $fib(i-1) + fib(i-2)$, if $i > 1$

ASMD chart

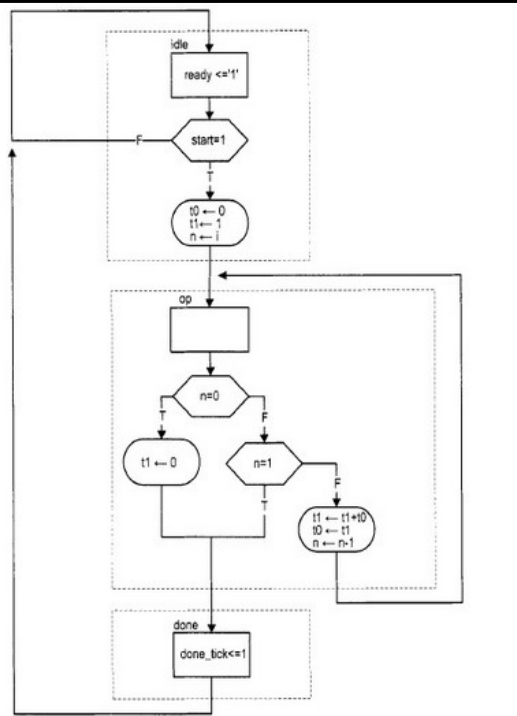

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity fib is
  port(
    clk, reset: in std_logic;
    start: in std_logic;
    i: in std_logic_vector(4 downto 0);
    ready, done_tick: out std_logic;
    f: out std_logic_vector(19 downto 0)
  );
end fib;

architecture arch of fib is
  type state_type is (idle,op,done);
  signal state_reg, state_next: state_type;
  signal t0_reg, t0_next, t1_reg, t1_next: unsigned(19 downto 0);
  signal n_reg, n_next: unsigned(4 downto 0);

begin

  -- fsmd state and data registers
  process(clk,reset)
  begin
    if reset='1' then
      state_reg <= idle;
      t0_reg <= (others=>'0');
      t1_reg <= (others=>'0');
      n_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      state_reg <= state_next;
      t0_reg <= t0_next;
      t1_reg <= t1_next;
      n_reg <= n_next;
    end if;
  end process;

```

VHDL code

```

-- fsmd next-state logic
process(state_reg,n_reg,t0_reg,t1_reg,start,i,n_next)
begin
  ready <='0';
  done_tick <= '0';
  state_next <= state_reg;
  t0_next <= t0_reg;
  t1_next <= t1_reg;
  n_next <= n_reg;
  case state_reg is
    when idle =>
      ready <= '1';
      if start='1' then
        t0_next <= (others=>'0');
        t1_next <= (0=>'1', others=>'0');
        n_next <= unsigned(i);
        state_next <= op;
      end if;
    when op =>
      if n_reg=0 then
        t1_next <= (others=>'0');
        state_next <= done;
      elsif n_reg=1 then
        state_next <= done;
      else
        t1_next <= t1_reg + t0_reg;
        t0_next <= t1_reg;
        n_next <= n_reg - 1;
      end if;
    when done =>
      done_tick <= '1';
      state_next <= idle;
  end case;
end process;

-- output
f <= std_logic_vector(t1_reg);

end arch;

```

Summary

- Algorithmic State Machine charts are somewhat more convenient to use to write behavioral VHDL code
- Finite State Machines with Datapath (FSMD) and Algorithmic State Machine with Datapath (ASMD) are useful when we care about the internal structure of the circuit (e.g., we want the synthesis tool to preserve the pipeline structure)