

## ECE-470 Digital Design II Compression Techniques


1

## Overview

- Motivation
- Basics
- Ones-Count compression
- Transition-Count compression
- Parity checking
- Syndrome checking
- Signature analysis
- Summary

2

### Motivation

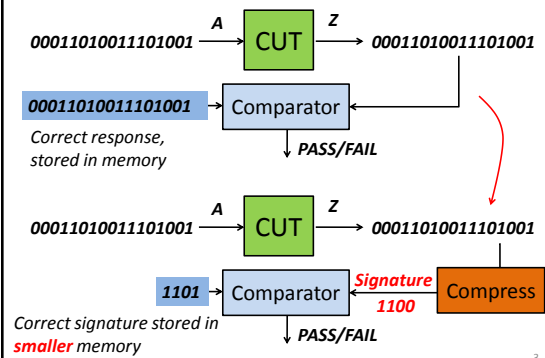

3

### Key Points

- Memory savings should overcome the extra hardware to implement the compression unit
- The compression unit could be implemented together with the CUT, achieving built-in self-test (BIST): to be discussed in a later lecture

4


### Compression Unit Requirements

- Should not introduce big signal delays
- Length of signature should be a logarithmic factor of the length of the output response length
- If response of faulty CUT is different from correct response, the faulty signature should also be different from the good signature. No **error masking** (otherwise faulty response is an **alias** of the correct output response)

5
 
### 1. Ones-Count Compression

- Signature:  $1C(R) = \sum r_i$
- Compressor: simple counter
- Degree of compression:  $\lceil \log_2(m+1) \rceil$



6

## Ones-Count Compression

- Separate counter for each PO for multi-output circuits, or
- Parallel-to-serial converter first, then a single counter
- **Theorem 1:** Masking probability for ones-count compression for a combinational circuit approaches  $(\pi m)^{-1/2}$

7


## Ones-Count Compression

- **Theorem 2:** When applying ones counting and the test set  $T'(C)$  to  $C$ , no error masking occurs for any fault in  $F$
- Where:
  - $C$ : combinational circuit, with  $F$  faults of interest
  - $T = \{T_0, T_1\}$  set of  $m$  test vectors that detect  $F$
  - $T'(C)$ : test set with one copy of every pattern in  $T_0$  and  $|T_0| + 1$  copies of every pattern in  $T_1$
  - For all tests in  $T_0$ , the fault free response is 0; for all tests in  $T_1$ , the fault free response is 1

8
 
## 2. Transition-Count Compression

- Signature:  $TC(R) = \sum (r_i \text{ XOR } r_{i+1})$
- Compressor: transition detector (TD) and a counter with  $\lceil \log_2 m \rceil$  stages
- Degree of compression:  $\lceil \log_2(m-1) \rceil$



9

## Transition-Count Compression

- Sensitive to the order of bits
- Does not guarantee detecting all single-bit errors
- **Theorem 1:** In an arbitrary  $m$ -bit sequence, the probability of a single-bit error being masked is  $(m-2)/2m$
- **Theorem 2:** Masking probability for transition-count compression for a combinational circuit approaches  $(\pi m)^{-1/2}$

10


## Transition-Count Compression

- **Theorem 3:** Let  $T$  be single-fault test for irredundant single-out circuit  $C$ . Let  $T_0(T_1)$  be all tests in  $T$  producing output 0(1). Construct test sequence  $X = t(1) t(2) \dots t(p)$ :
  - $X$  contains every element in  $T$
  - $X$  is alternating sequence of tests from  $T_0$  and  $T_1$ . If  $|T_0| \geq |T_1|$ ,  $t(1) \in T_0$ , otherwise  $t(1) \in T_1$ . If  $t(i) \in T_d$ , select  $t(i+1) \in \bar{T}_d$  for  $1 \leq i \leq p-1$
  - Resulting sequence is a single-fault transition-count (TC) test for  $C$

11
 
## 3. Parity-Check Compression

- Signature:  $p(R) = \text{parity of circuit response}$
- Compressor: simple parity checker (LFSR)



12

## Parity-Check Compression

- Initial state of DFF is 0, signature is 0 if parity is even, 1 if parity is odd
- Probability of masking approaches 1/2
- Extension to multiple-output circuits:
  - Use multi-input XOR gate
  - Use separate parity checker for each output

13


## 4. Syndrome Testing

- Uses exhaustive testing: applying all  $2^n$  test vectors
- Signature (syndrome) S**: normalized number of 1's in the output response stream,  $S = K/2^n$
- It is a special case of 1's counting
- Examples:
  - $S(3\text{-input AND}) = 1/8$
  - $S(3\text{-input OR}) = 7/8$
- Syndrome  $S$  is a functional property of circuit implementing function  $f$

14
 
## Syndrome Testing

- It is of interest because of the concept of syndrome testability
- Syndrome testability**: any function  $f$  can be realized such that all single stuck-at faults are syndrome detectable



Gate type for C3	Syndrome S3
OR	$S1 + S2 - S1S2$
AND	$S1S2$
NAND	$1 - S1S2$
NOR	$1 - (S1 + S2 + S1S2)$
XOR	$S1 + S2 - 2S1S2$

15

## Syndrome Testing

- Definition**: A realization  $C$  of a function  $f$  is said to be syndrome-testable if no single stuck-at fault causes the circuit to have the same syndrome as the fault-free circuit
- Lemma**: A two level irredundant circuit that realizes a unate function (a function  $f$  is unate in  $x_i$  if there exists a sum of product expression for  $f$  where  $x_i$  appears only in uncomplemented form) in all its variables is syndrome testable
- Lemma**: Every two-level irredundant combinational circuit can be made syndrome testable by adding control inputs to the AND gates
- Lemma**: Every fanout-free irredundant combinational circuit composed of AND, OR, NAND, NOR, and NOT gates is syndrome testable

16

## 5. Signature Analysis

- Compression technique based on the concept of cyclic redundancy checking (CRC)
- Implemented using linear feedback shift registers (LFSRs), utilized for:
  - Generate pseudorandom sequences
  - Compression of circuit out response, known as **signature analysis**

17


## Linear Feedback Shift Registers (LFSR)

- A generating function can be associated with an LFSR's output sequence:
 
$$G(x) = a_0 + a_1 x + a_2 x^2 + \dots + a_m x^m + \dots$$

$$\{a_m\} = a_0, a_1, a_2, \dots$$
 output sequence generated by LFSR
- Two types of LFSRs:
  - External XOR
  - Internal XOR

18
 
### LFSR Type 1: External XOR (autonomous circuit; clock is only input)




Initial  
Current

$a_m$	$a_{m-1}$	$a_{m-2}$	$a_{m-3}$	$a_{m-n-1}$	$a_{m-n}$
-------	-----------	-----------	-----------	-------------	-----------

19

### LFSR Type 2: Internal XOR

 

Initial  
Current

$a_{m-1}$	$a_{m-2}$	$a_{m-3}$	$a_{m-n-1}$	$a_{m-n}$
-----------	-----------	-----------	-------------	-----------

20

### Linear Feedback Shift Registers (LFSR)

- Note that: 
$$a_m = \sum_{i=1}^n c_i a_{m-i}$$
- Operation of the LFSR can be defined by a recurrence relation:  

$$G(x) = \sum_{i=1}^n c_i x^i G(x) + \sum_{i=1}^n c_i x^i (a_{-i} x^{-i} + \dots + a_{-1} x^{-1})$$

$$G(x) = \frac{\sum_{i=1}^n c_i x^i (a_{-i} x^{-i} + \dots + a_{-1} x^{-1})}{1 + \sum_{i=1}^n c_i x^i}$$
- $G(x)$  is a function of the initial state  $a_{-1}, a_{-2}, \dots, a_{-n}$  and the feedback coefficients  $c_1, c_2, \dots, c_n$

21

### Linear Feedback Shift Registers (LFSR)

- The denominator is the **characteristic polynomial** of sequence  $\{a_m\}$  and of the LFSR:  

$$P(x) = 1 + c_1 x + c_2 x^2 + \dots + c_n x^n$$
- Note again:** characteristic polynomial and the initial states characterize the cyclic nature of the LFSR
- Reciprocal polynomial:**  

$$P^*(x) = c_n + c_{n-1} x + c_{n-2} x^2 + \dots + c_1 x^{n-1} + x^n$$

$$P^*(x) = x^n P(1/x)$$


22

### Linear Feedback Shift Registers (LFSR)

- Given a characteristic polynomial, it is easy to implement a type 1 LFSR to realize it
- Associate  $x^i$  with  $Q_i$ , the  $P(x)$  can be read off directly from the diagram of the LFSR
- Associate  $x^i$  with  $Q_{n-i}$  and label input of first FF as  $Q_0$ , then  $P^*(x)$  can be read off directly from the diagram of the LFSR

23


### Type 1, external XOR

 

$$P(x) = 1 + c_1 x + c_2 x^2 + \dots + c_n x^n$$

24

### Type 1, external XOR

 

$$P^*(x) = 1 + c_{n-1}x + c_{n-2}x^2 + \dots + c_1x^{n-1} + x^n$$

25

### Periodicity of LFSR

- **Theorem:** If the initial state of an LFSR is zero except  $a_{-n} = 1$ , then the LFSR sequence  $\{a_m\}$  is periodic with a period that is the smallest integer  $k$  for which  $P(x)$  divides  $(1-x^k)$
- If period is  $2^n-1$  then LFSR generates a maximum length sequence
- In this case, the characteristic polynomial is called **primitive polynomial**

26


### Maximum -length Sequences

- Sequences generated by LFSR with primitive polynomial are called **pseudorandom sequences**
- Any string of  $2^n-1$  consecutive outputs is called an **m-sequence**:
  - Number of 1's in an m-sequence differs from the number of 0's by one
  - An m-sequence produces an equal number of runs of 1's and 0's
  - One half of the runs have length 1, one forth have length 2, one eighth have length 3, etc.
- **Randomness of LFSR makes them good for generating test sequences in BIST circuits**

27
 
### 5. Single-Input LFSRs as Signature Analyzers

- Signature analyzer is a type 2 single-input LFSR
- Smallest degree of masking makes this approach most popular in practice. The structure of the LFSR distributes all possible input bit streams evenly over all possible signatures.
- *Remainder left in the register (after completion of test) represents the signature*




$$G(x) = Q(x)P^*(x) + R(x)$$

Initial state:  $I(x) = 0$ ; Final state:  $R(x)$

28

### Multiple-Input LFSR as Signature Analyzers: MISR

- Used for multi-output circuits

 

29

### LFSR as Signature Analyzers

- Signature analysis is the most popular method employed for test data compression because produces a small degree of masking
- One can decrease probability of masking by increasing the length of LFSR or changing the characteristic polynomial
- Functional registers are often modified to work as LFSR as well

30

## Summary

- Compression techniques are widely used, esp. because their use in self-testing techniques
- All Boolean functions can be implemented by a circuit that is syndrome testable
- Signature analysis is the most popular test data compression technique due to low error masking probability

31