

EECE-4740/5740 Advanced VHDL and FPGA Design
Lecture 4

FSM, ASM, FSMD, ASMD

Cristinel Ababei
Dept. of Electrical and Computer Engr.
Marquette University

1

Overview


- **Finite State Machine (FSM) Representations:**
 1. **State Graphs**
 2. **Algorithmic State Machine (ASM) Charts**
- Finite State Machines with Datapath (FSMD)
- Algorithmic State Machine with Datapath (ASMD)

- Examples
 - Example 1 – period counter
 - Example 2 – division circuit
 - Example 3 – binary-2-BCD converter
 - Example 4 – low-frequency counter
 - Example 5 – multiplier

2

FSM – general form

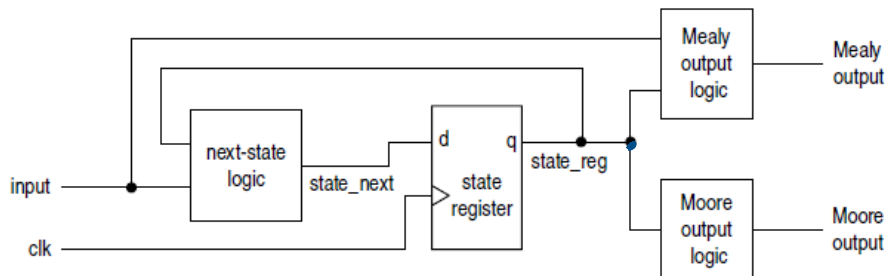- In practice, main application of an FSM is to act as **controller** of a large digital system
- It examines external commands and status and activates proper control signals to control operation of a **data path** (composed of regular sequential and combinational components)



3

State Graph \leftrightarrow ASM Chart

- **State graph or state diagram:**
 - **Nodes:** unique states of the FSM
 - **Transitional arcs:** labeled with the condition that causes the transition
- **Algorithmic State Machine (ASM) chart** is an alternative representation
 - Composed of a network of **ASM blocks**
 - ASM block:
 - **State box:** represents a state in the FSM
 - Optional network of **decision boxes** and **conditional output boxes**
 - More descriptive for applications with complex transition conditions and actions!
- A state diagram can be converted to an ASM chart and vice-versa

4


ASM Charts

- **Algorithmic State Machine (ASM) Chart** is a popular high-level flowchart-like graphical model (or notation) to **specify the (hardware) algorithms in digital systems**.
- Major differences from flowcharts are:
 - ❖ uses 3 types of boxes: state box (similar to operation box), decision box, and conditional box
 - ❖ contains exact (or precise) timing information; flowcharts impose a relative timing order for the operations.
- From the ASM chart it is possible to obtain
 - ❖ the control
 - ❖ the architecture (data processor)

5

Components of ASM Charts

 
- The **state box** is rectangular in shape. It has at most one entry point and one exit point and is used to specify one or more operations which could be simultaneously completed in one **clock cycle**.



6

Components of ASM Charts

 
- The **decision box** is diamond in shape. It has one entry point but multiple exit points and is used to specify a number of alternative paths that can be followed.



7

Components of ASM Charts

 
- The **conditional box** is represented by a rectangle with rounded corners. It always follows a decision box and contains one or more *conditional operations* that are only invoked when the path containing the conditional box is selected by the decision box.




8

State Graph \leftrightarrow ASM Chart

State of State Graph

 


ASM Block

 

9

Example

Easier to write VHDL!

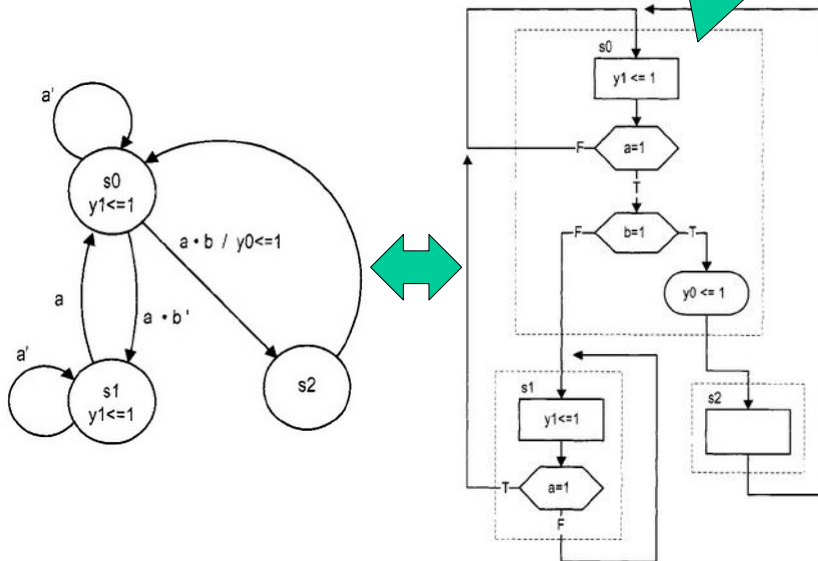

10

VHDL code

```
library ieee;
use ieee.std_logic_1164.all;

entity fsm_eg is
  port(
    clk, reset: in std_logic;
    a, b: in std_logic;
    y0, y1: out std_logic
  );
end fsm_eg;

architecture two_seg_arch of fsm_eg is
  type eg_state_type is (s0, s1, s2);
  signal state_reg, state_next: eg_state_type;

begin

  -- state register
  process(clk,reset)
  begin
    if (reset='1') then
      state_reg <= s0;
    elsif (clk'event and clk='1') then
      state_reg <= state_next;
    end if;
  end process;
```

11


VHDL code

```
-- next-state/output logic
process(state_reg,a,b)
begin
  state_next <= state_reg; -- default back to same state
  y0 <= '0'; -- default 0
  y1 <= '0'; -- default 0
  case state_reg is
    when s0 =>
      y1 <= '1';
      if a='1' then
        if b='1' then
          state_next <= s2;
          y0 <= '1';
        else
          state_next <= s1;
        end if;
      -- no else branch
    end if;
    when s1 =>
      y1 <= '1';
      if (a='1') then
        state_next <= s0;
      -- no else branch
    end if;
    when s2 =>
      state_next <= s0;
  end case;
end process;
end two_seg_arch;
```


12

 Example: Rising-edge detector

- Generates a short, one-clock-cycle pulse (called a tick) when input signal changes from '0' to '1'
- Here: Mealy machine
- Assignment: Moore machine
- See more examples in Ch.5 of P.Chu's book (e.g., debouncing circuit)



(a) State diagram

 

(b) ASM chart

13

VHDL code

```

library ieee;
use ieee.std_logic_1164.all;

entity edge_detect is
  port(
    clk, reset: in std_logic;
    level: in std_logic;
    tick: out std_logic
  );
end edge_detect;

architecture MEALY_ARCHITECTURE of edge_detect is

  type state_type is (S0, S1);
  signal state_current, state_next : state_type;

begin

  -- state register; process #1
  process (clk , reset)
  begin
    if (reset = '1') then
      state_current <= S0;
    elsif (clk' event and clk = '1') then
      state_current <= state_next;
    end if;
  end process;

```

14

VHDL code

```
-- next state and output logic; process #2
process (state_current, level)
begin
    state_next <= state_current;
    tick <= '0';
    case state_current is
        when S0 =>
            if level = '1' then
                state_next <= S1;
                tick <= '1';
            end if;
        when S1 =>
            if level = '0' then
                state_next <= S0;
            end if;
    end case;
end process;
end MEALY_ARCHITECTURE;
```

15

Overview

- Finite State Machine (FSM) Representations:
 1. State Graphs
 2. Algorithmic State Machine (ASM) Charts
- **Finite State Machines with Datapath (FSMD)**
- **Algorithmic State Machine with Datapath (ASMD)**

- Examples
 - Example 1 – period counter
 - Example 2 – division circuit
 - Example 3 – binary-2-BCD converter
 - Example 4 – low-frequency counter
 - Example 5 – multiplier

16


Finite State Machine with Data-path (FSMD): Enabler of RT design methodology

- **FSMD = FSM +
Regular Sequential Circuits +
Combinational Circuits**
- The FSM is called **control-path (control logic)**; the rest is called **data-path**
- FSMD used to implement systems described by **register transfer (RT) methodology**

17

Conceptual block diagram of FSMD

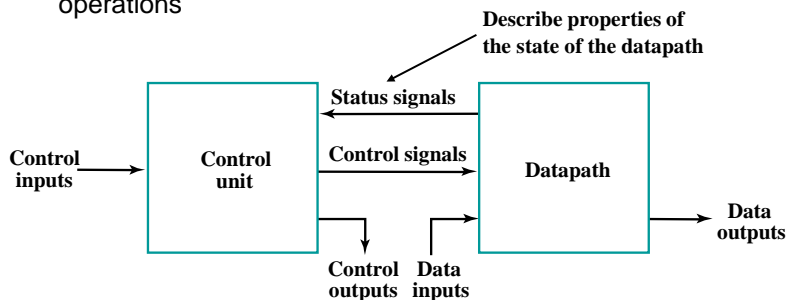
- **Datapath** - performs **data transfer** and **processing** operations
- **Control Unit** - Determines the enabling and sequencing of the operations



- The control unit receives:
 - External control inputs
 - Status signals
- The control unit sends:
 - Control signals
 - Control outputs

18

Block diagram of FSMD (detailed)

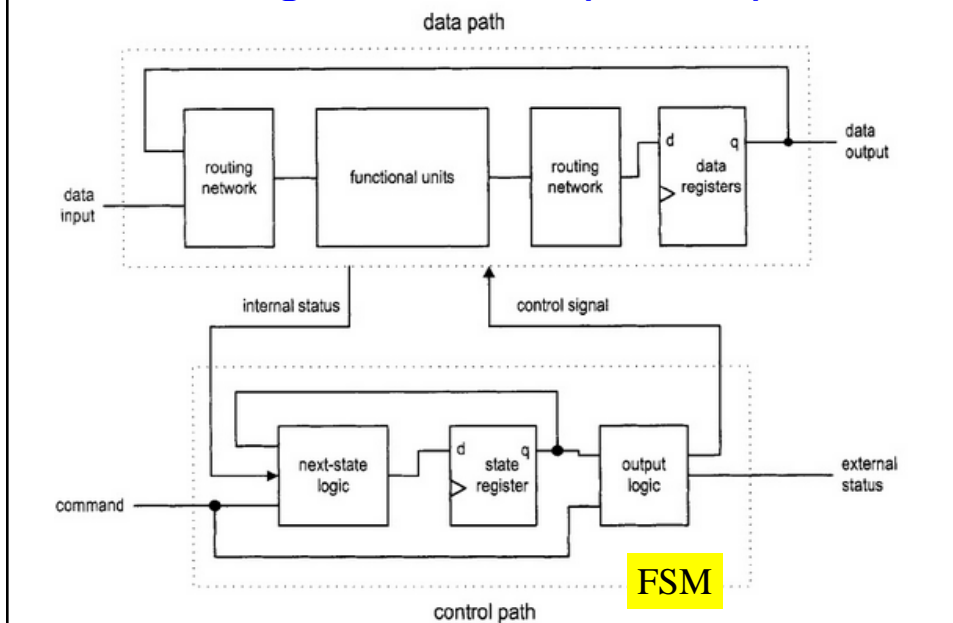

19

RT Design Methodology

- RT operations are specified as data manipulation and transfer among a collection of registers
- A circuit based on RT methodology specifies which RT operations should be executed in each step
- RT operations are done in a clock-by-clock basis; so, timing is similar to a state transition of a FSM
- Hence, FSM is natural choice to specify the sequencing of an RT algorithm
- **Extend ASM chart to incorporate RT operations and call it ASMD (ASM with datapath) chart**

20


RT Operations (8 slides; can be skipped)

- Register Transfer Operations - the movement and processing of data stored in registers
- Three basic components:
 - A set of registers (operands)
 - Transfer operations
 - Control of operations
- Elementary operations - called **microoperations**
 - load, count, shift, add, bitwise "OR", etc.
- Notation: $r_{dest} \leftarrow f(r_{src1}, r_{src2}, \dots, r_{srcn})$

21

Register Notation

 - Letters and numbers – register (e.g. R2, PC, IR)
- Parentheses () – range of register bits (e.g. R1(1), PC(7:0), AR(L))




- Arrow (\leftarrow) – data transfer (ex. $R1 \leftarrow R2$, $PC(L) \leftarrow R0$)
- Brackets [] – Specifies a memory address (ex. $R0 \leftarrow M[AR]$, $R3 \leftarrow M[PC]$)
- Comma – separates parallel operations

22

Conditional Transfer

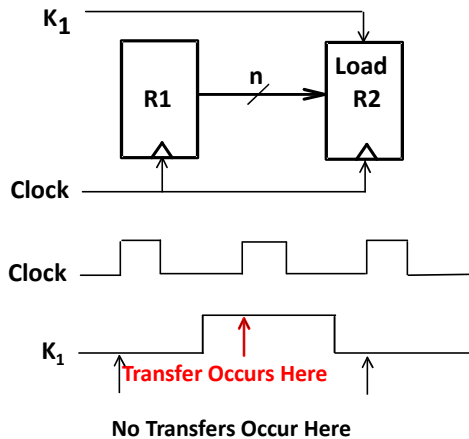- If $(K_1 = 1)$ then $(R2 \leftarrow R1)$
 $\Leftrightarrow K_1: (R2 \leftarrow R1)$
 where K_1 is a control expression specifying a conditional execution of the microoperation.



23

Microoperations

- Logical groupings:
 - Transfer - move data from one set of registers to another
 - Arithmetic - perform arithmetic on data in registers
 - Logic - manipulate data or use bitwise logical operations
 - Shift - shift data in registers

Arithmetic operations

+ Addition
 - Subtraction
 * Multiplication
 / Division

Logical operations

∨ Logical OR
 ∧ Logical AND
 ⊕ Logical Exclusive OR
 - Not

24

Example Microoperations

- $R1 \leftarrow R1 + R2$
 - Add the content of R1 to the content of R2 and place the result in R1.
- $PC \leftarrow R1 * R6$
- $R1 \leftarrow R1 \oplus R2$
- $(K1 + K2): R1 \leftarrow R1 \vee R3$
 - On condition K1 OR K2, the content of R1 is Logic bitwise ORed with the content of R3 and the result placed in R1.
 - NOTE: "+" (as in $K_1 + K_2$) means "OR." In $R1 \leftarrow R1 + R2$, + means "plus".

25

Arithmetic Microoperations

Symbolic Designation	Description
$R0 \leftarrow R1 + R2$	Addition
$R0 \leftarrow \overline{R1}$	Ones Complement
$R0 \leftarrow \overline{R1} + 1$	Two's Complement
$R0 \leftarrow R2 + \overline{R1} + 1$	R2 minus R1 (2's Comp)
$R1 \leftarrow R1 + 1$	Increment (count up)
$R1 \leftarrow R1 - 1$	Decrement (count down)

- Any register may be specified for source 1, source 2, or destination.
- These simple microoperations operate on the whole word

26

Logical Microoperations

Symbolic Designation	Description
$R0 \leftarrow \overline{R1}$	Bitwise NOT
$R0 \leftarrow R1 \vee R2$	Bitwise OR (sets bits)
$R0 \leftarrow R1 \wedge R2$	Bitwise AND (clears bits)
$R0 \leftarrow R1 \oplus R2$	Bitwise EXOR (complements bits)

27

Shift Microoperations

- Let R2 = 11001001

Symbolic Designation	Description	R1 content
$R1 \leftarrow sl R2$	Shift Left	10010010
$R1 \leftarrow sr R2$	Shift Right	01100100


- Note: These shifts "zero fill". Sometimes a separate flip-flop is used to provide the data shifted in, or to "catch" the data shifted out.
- Other shifts are possible (rotates, arithmetic)

28


Algorithmic State Machine with Data-path (ASMD)

- Extend ASM chart to incorporate RT operations → ASMD (ASM with datapath) chart

ASMD segment

 

 
Block diagram: implementation of RT operations (likely synthesized by CAD tool for you or directly specified as structural description)




29

Location of RT operation inside ASM block

ASM block

 

 Block diagram: implementation of RT operations (likely synthesized by CAD tool for you or directly specified as structural description)



30

Decision Box with a Register

- RT operation in an ASMD chart is controlled by an embedded clock signal
- Destination register is updated **when the machine exits the current ASMD block**, but not within the block!
- Example: $r \leftarrow r - 1$ means:
 - $r_next \leq r_reg - 1$;
 - $r_reg \leq r_next$ at the rising edge of the clock (when machine exits current block)


31

Example of ASMD description

- **Fibonacci number circuit**
 - **Page 140 in Textbook**
- A sequence of integers
- $\text{fib}(i) =$
$$\begin{cases} 0, & \text{if } i = 0 \\ 1, & \text{if } i = 1 \\ \text{fib}(i-1) + \text{fib}(i-2), & \text{if } i > 1 \end{cases}$$

32

ASMD chart

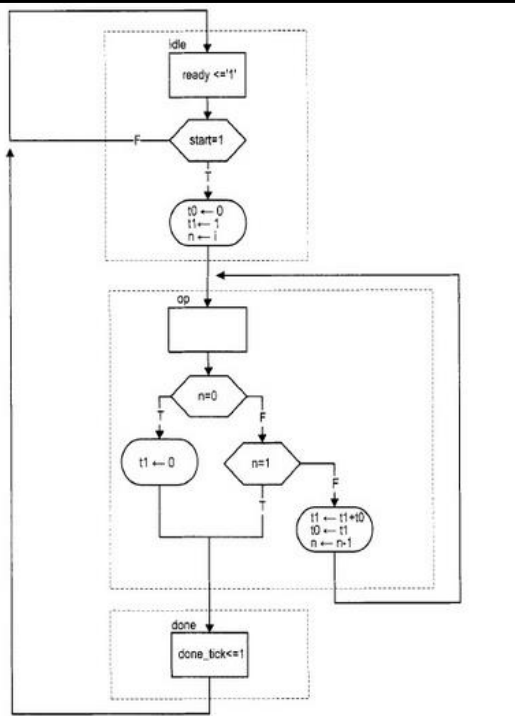

33

VHDL code

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity fib is
  port(
    clk, reset: in std_logic;
    start: in std_logic;
    i: in std_logic_vector(4 downto 0);
    ready, done_tick: out std_logic;
    f: out std_logic_vector(19 downto 0)
  );
end fib;

architecture arch of fib is
  type state_type is (idle,op,done);
  signal state_reg, state_next: state_type;
  signal t0_reg, t0_next, t1_reg, t1_next: unsigned(19 downto 0);
  signal n_reg, n_next: unsigned(4 downto 0);

begin

  -- fsmd state and data registers
  process(clk,reset)
  begin
    if reset='1' then
      state_reg <= idle;
      t0_reg <= (others=>'0');
      t1_reg <= (others=>'0');
      n_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
      state_reg <= state_next;
      t0_reg <= t0_next;
      t1_reg <= t1_next;
      n_reg <= n_next;
    end if;
  end process;

```

34

```

-- fsmd next-state logic
process (state_reg, n_reg, t0_reg, t1_reg, start, i, n_next)
begin
    ready <= '0';
    done_tick <= '0';
    state_next <= state_reg;
    t0_next <= t0_reg;
    t1_next <= t1_reg;
    n_next <= n_reg;
    case state_reg is
        when idle =>
            ready <= '1';
            if start='1' then
                t0_next <= (others=>'0');
                t1_next <= (0=>'1', others=>'0');
                n_next <= unsigned(i);
                state_next <= op;
            end if;
        when op =>
            if n_reg=0 then
                t1_next <= (others=>'0');
                state_next <= done;
            elsif n_reg=1 then
                state_next <= done;
            else
                t1_next <= t1_reg + t0_reg;
                t0_next <= t1_reg;
                n_next <= n_reg - 1;
            end if;
        when done =>
            done_tick <= '1';
            state_next <= idle;
        end case;
    end process;

-- output
f <= std_logic_vector(t1_reg);

end arch;

```

35

Overview

- Finite State Machine (FSM) Representations:
 1. State Graphs
 2. Algorithmic State Machine (ASM) Charts
- Finite State Machines with Datapath (FSMD)
- Algorithmic State Machine with Datapath (ASMD)

- Examples
 - Example 1 – period counter
 - Example 2 – division circuit
 - Example 3 – binary-2-BCD converter
 - Example 4 – low-frequency counter
 - Example 5 – multiplier


36

Example 1: Period Counter

- Measure the period of a periodic input waveform
- Solution:
 - Count the number of clock cycles between two rising edges of the input signal
 - Use a **rising-edge detection** circuit (discussed earlier)
 - Frequency of clock signal is known \rightarrow easy to find the period of input signal: $N \cdot 1/f_{CLK}$
 - Assume: $T_{CLK} = (1/f_{CLK}) = 20 \text{ ns}$
 - Register t counts for 50,000 clock cycles from 0 to 49,999 then wraps around; it takes 1ms to circulate through 50,000 cycles
 - Register p counts in terms of milliseconds

37

ASMD chart

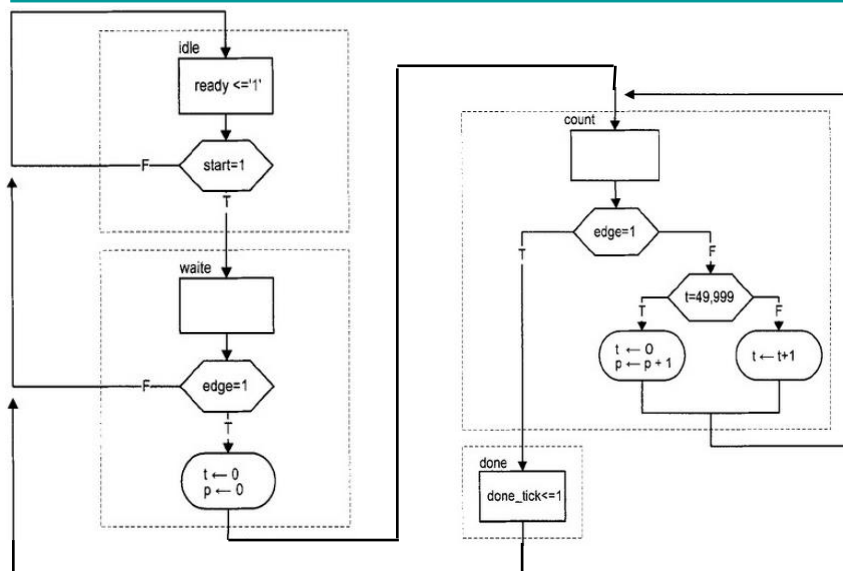

38

VHDL code

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity period_counter is
  port(
    clk, reset: in std_logic;
    start, si: in std_logic;
    ready, done_tick: out std_logic;
    prd: out std_logic_vector(9 downto 0)
  );
end period_counter;

architecture arch of period_counter is

  constant CLK_MS_COUNT: integer := 50000; -- 1 ms tick
  type state_type is (idle, waite, count, done);
  signal state_reg, state_next: state_type;
  signal t_reg, t_next: unsigned(15 downto 0); -- up to 50000
  signal p_reg, p_next: unsigned(9 downto 0); -- up to 1 sec
  signal delay_reg: std_logic;
  signal edge: std_logic;
```

39

```
begin

  -- state and data register
  process(clk,reset)
  begin
    if reset='1' then
      state_reg <= idle;
      t_reg <= (others=>'0');
      p_reg <= (others=>'0');
      delay_reg <= '0';
    elsif (clk'event and clk='1') then
      state_reg <= state_next;
      t_reg <= t_next;
      p_reg <= p_next;
      delay_reg <= si;
    end if;
  end process;

  -- edge detection circuit
  edge <= (not delay_reg) and si;
```

40

```

-- FSMD next-state logic/DATAPATH operations
process (start, edge, state_reg, t_reg, t_next, p_reg)
begin
  ready <= '0';
  done_tick <= '0';
  state_next <= state_reg;
  p_next <= p_reg;
  t_next <= t_reg;
  case state_reg is
    when idle =>
      ready <= '1';
      if (start='1') then
        state_next <= waite;
      end if;
    when waite => -- wait for the first edge
      if (edge='1') then
        state_next <= count;
        t_next <= (others=>'0');
        p_next <= (others=>'0');
      end if;
    when count =>
      if (edge='1') then -- 2nd edge arrived
        state_next <= done;
      else -- otherwise count
        if t_reg = CLK_MS_COUNT-1 then -- 1ms tick
          t_next <= (others=>'0');
          p_next <= p_reg + 1;
        else
          t_next <= t_reg + 1;
        end if;
      end if;
    when done =>
      done_tick <= '1';
      state_next <= idle;
    end case;
  end process;
  prd <= std_logic_vector(p_reg);
end arch;

```

41

Overview

- Finite State Machine (FSM) Representations:
 1. State Graphs
 2. Algorithmic State Machine (ASM) Charts
- Finite State Machines with Datapath (FSMD)
- Algorithmic State Machine with Datapath (ASMD)

- Examples
 - Example 1 – period counter
 - **Example 2 – division circuit**
 - Example 3 – binary-2-BCD converter
 - Example 4 – low-frequency counter
 - Example 5 – multiplier

42

Example 2: Division circuit (more complex)

- **Division algorithm** of 4-bit unsigned integers:
 - (1) Double the dividend width - by appending 0's in front and align the divisor to leftmost bit of extended dividend
 - (2) If corresponding dividend bits are \geq to divisor, subtract divisor from dividend and make corresponding quotient bit 1. Otherwise, keep original dividend bits and make quotient bit 0.
 - (3) Append one additional dividend bit to previous result and shift divisor to right 1 position
 - (4) Repeat (2) and (3) until all dividend bits are used

43

Division of two 4-bit unsigned integers

1 2 3 4 5


divisor

```
0010 / 00001101 — dividend
      0000
      ----
      0001
      0000
      ----
      0011
      0010
      ----
      0010
      0010
      ----
      0001 — remainder
```

00110 — quotient

44

Sketch of Datapath of Division circuit

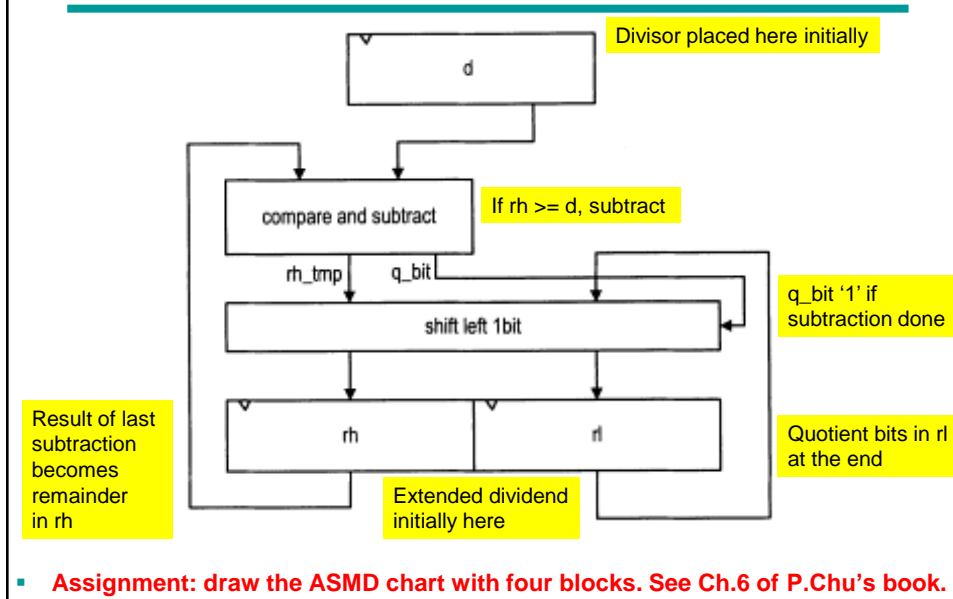

45

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
```

VHDL code

```
entity div is
  generic(
    W: integer:=8;
    CBIT: integer:=4 -- CBIT=log2(W)+1
  );
  port(
    clk, reset: in std_logic;
    start: in std_logic;
    dvsr, dvnd: in std_logic_vector(W-1 downto 0);
    ready, done_tick: out std_logic;
    quo, rmd: out std_logic_vector(W-1 downto 0)
  );
end div;

architecture arch of div is

  type state_type is (idle,op,last,done);
  signal state_reg, state_next: state_type;
  signal rh_reg, rh_next: unsigned(W-1 downto 0);
  signal rl_reg, rl_next: std_logic_vector(W-1 downto 0);
  signal rh_tmp: unsigned(W-1 downto 0);
  signal d_reg, d_next: unsigned(W-1 downto 0);
  signal n_reg, n_next: unsigned(CBIT-1 downto 0);
  signal q_bit: std_logic;
```

46

```

begin

    -- fsmd state and data registers
    process(clk,reset)
    begin
        if reset='1' then
            state_reg <= idle;
            rh_reg <= (others=>'0');
            rl_reg <= (others=>'0');
            d_reg <= (others=>'0');
            n_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            state_reg <= state_next;
            rh_reg <= rh_next;
            rl_reg <= rl_next;
            d_reg <= d_next;
            n_reg <= n_next;
        end if;
    end process;

```

47

```

-- fsmd next-state logic and data path logic
process(state_reg,n_reg,rh_reg,rl_reg,d_reg,
        start,dvsr,dvnd,q_bit,rh_tmp,n_next)
begin
    ready <='0';
    done_tick <= '0';
    state_next <= state_reg;
    rh_next <= rh_reg;
    rl_next <= rl_reg;
    d_next <= d_reg;
    n_next <= n_reg;
    case state_reg is
        when idle =>
            ready <= '1';
            if start='1' then
                rh_next <= (others=>'0');
                rl_next <= dvnd; -- dividend
                d_next <= unsigned(dvsr); -- divisor
                n_next <= to_unsigned(W+1, CBIT); -- index
                state_next <= op;
            end if;
        when op =>
            -- shift rh and rl left
            rl_next <= rl_reg(W-2 downto 0) & q_bit;
            rh_next <= rh_tmp(W-2 downto 0) & rl_reg(W-1);
            --decrease index
            n_next <= n_reg - 1;
            if (n_next=1) then
                state_next <= last;
            end if;
        when last => -- last iteration
            rl_next <= rl_reg(W-2 downto 0) & q_bit;
            rh_next <= rh_tmp;
            state_next <= done;
        when done =>
            state_next <= idle;
            done_tick <= '1';
    end case;
end process;

```

48


```

-- compare and subtract
process(rh_reg, d_reg)
begin
  if rh_reg >= d_reg then
    rh_tmp <= rh_reg - d_reg;
    q_bit <= '1';
  else
    rh_tmp <= rh_reg;
    q_bit <= '0';
  end if;
end process;

-- output
quo <= r1_reg;
rmd <= std_logic_vector(rh_reg);

end arch;

```

49

Overview

- Finite State Machine (FSM) Representations:
 1. State Graphs
 2. Algorithmic State Machine (ASM) Charts
- Finite State Machines with Datapath (FSMD)
- Algorithmic State Machine with Datapath (ASMD)

- Examples
 - Example 1 – period counter
 - Example 2 – division circuit
 - **Example 3 – binary-2-BCD converter**
 - Example 4 – low-frequency counter
 - Example 5 – multiplier

50

Example 3: Binary-to-BCD converter

- A decimal number is represented as sequence of 4-bit BCD digits
- Conversion can be processed by a special BCD register, which is divided into 4-bit groups internally
- Shifting a BCD sequence to left requires adjustment of if a BCD digit is $> 9_{10}$ after shifting
 - Example: If a BCD sequence is “0001 0111” (i.e., 17_{10}), it should become “0011 0100” (i.e., 34_{10}) rather than “0010 1110”
- Example:
 - Binary: 001000000000
 - BCD: 0101 0001 0010
 - Decimal: 5 1 2
- **Read section 6.3.3 in P.Chu's book for details on algorithm**
- **Assignment: Draw a sketch of the datapath. Draw the ASMD chart.**

51

VHDL code

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity bin2bcd is
  port(
    clk: in std_logic;
    reset: in std_logic;
    start: in std_logic;
    bin: in std_logic_vector(12 downto 0);
    ready, done_tick: out std_logic;
    bcd3,bcd2,bcd1,bcd0: out std_logic_vector(3 downto 0)
  );
end bin2bcd ;

architecture arch of bin2bcd is
  type state_type is (idle, op, done);
  signal state_reg, state_next: state_type;
  signal p2s_reg, p2s_next: std_logic_vector(12 downto 0);
  signal n_reg, n_next: unsigned(3 downto 0);
  signal bcd3_reg,bcd2_reg,bcd1_reg,bcd0_reg: unsigned(3 downto 0);
  signal bcd3_next,bcd2_next,bcd1_next,bcd0_next: unsigned(3 downto 0);
  signal bcd3_tmp,bcd2_tmp,bcd1_tmp,bcd0_tmp: unsigned(3 downto 0);
```

52

```

begin

-- state and data registers
process (clk,reset)
begin
  if reset='1' then
    state_reg <= idle;
    p2s_reg <= (others=>'0');
    n_reg <= (others=>'0');
    bcd3_reg <= (others=>'0');
    bcd2_reg <= (others=>'0');
    bcd1_reg <= (others=>'0');
    bcd0_reg <= (others=>'0');
  elsif (clk'event and clk='1') then
    state_reg <= state_next;
    p2s_reg <= p2s_next;
    n_reg <= n_next;
    bcd3_reg <= bcd3_next;
    bcd2_reg <= bcd2_next;
    bcd1_reg <= bcd1_next;
    bcd0_reg <= bcd0_next;
  end if;
end process;

```

53

```

-- fsmd next-state logic / data path operations
process (state_reg,start,p2s_reg,n_reg,n_next,bin,
        bcd0_reg,bcd1_reg,bcd2_reg,bcd3_reg,
        bcd0_tmp,bcd1_tmp,bcd2_tmp,bcd3_tmp)
begin
  state_next <= state_reg;
  ready <= '0';
  done_tick <= '0';
  p2s_next <= p2s_reg;
  bcd0_next <= bcd0_reg;
  bcd1_next <= bcd1_reg;
  bcd2_next <= bcd2_reg;
  bcd3_next <= bcd3_reg;
  n_next <= n_reg;
  case state_reg is
    when idle =>
      ready <= '1';
      if start='1' then
        state_next <= op;
        bcd3_next <= (others=>'0');
        bcd2_next <= (others=>'0');
        bcd1_next <= (others=>'0');
        bcd0_next <= (others=>'0');
        n_next <= "1101"; -- index
        p2s_next <= bin; -- input shift register
        state_next <= op;
      end if;
    when op =>
      -- shift in binary bit
      p2s_next <= p2s_reg(11 downto 0) & '0';
      -- shift 4 BCD digits
      bcd0_next <= bcd0_tmp(2 downto 0) & p2s_reg(12);
      bcd1_next <= bcd1_tmp(2 downto 0) & bcd0_tmp(3);
      bcd2_next <= bcd2_tmp(2 downto 0) & bcd1_tmp(3);
      bcd3_next <= bcd3_tmp(2 downto 0) & bcd2_tmp(3);
      n_next <= n_reg - 1;
      if (n_next=0) then
        state_next <= done;
      end if;
    when done =>
      state_next <= idle;
      done_tick <= '1';
  end case;
end process;

```

54

```
-- data path function units
bcd0_tmp <= bcd0_reg + 3 when bcd0_reg > 4 else
    bcd0_reg;
bcd1_tmp <= bcd1_reg + 3 when bcd1_reg > 4 else
    bcd1_reg;
bcd2_tmp <= bcd2_reg + 3 when bcd2_reg > 4 else
    bcd2_reg;
bcd3_tmp <= bcd3_reg + 3 when bcd3_reg > 4 else
    bcd3_reg;

-- output
bcd0 <= std_logic_vector(bcd0_reg);
bcd1 <= std_logic_vector(bcd1_reg);
bcd2 <= std_logic_vector(bcd2_reg);
bcd3 <= std_logic_vector(bcd3_reg);

end arch;
```

55

Overview

- Finite State Machine (FSM) Representations:
 1. State Graphs
 2. Algorithmic State Machine (ASM) Charts
- Finite State Machines with Datapath (FSMD)
- Algorithmic State Machine with Datapath (ASMD)

- Examples
 - Example 1 – period counter
 - Example 2 – division circuit
 - Example 3 – binary-2-BCD converter
 - **Example 4 – low-frequency counter**
 - Example 5 – multiplier


56

Example 4: Accurate low-frequency counter

- **Measure frequency of a periodic input waveform**
- One way:
 - Count number of input pulses in a fixed amount of time, say 1 sec
 - Not working for low-frequency signals; example 2 Hz
- Another way:
 1. Measure period of signal
 2. Take reciprocal ($f=1/T$)
 3. Convert binary number to BCD format
- Assume: frequency of input signal is between 1-10 Hz ($T = 100...1000$ ms)
- Structural description:
 - Instantiate a period counter, a division circuit, and a binary-3-BCD converter
 - Create a new ASM chart for master control


57

Block diagram

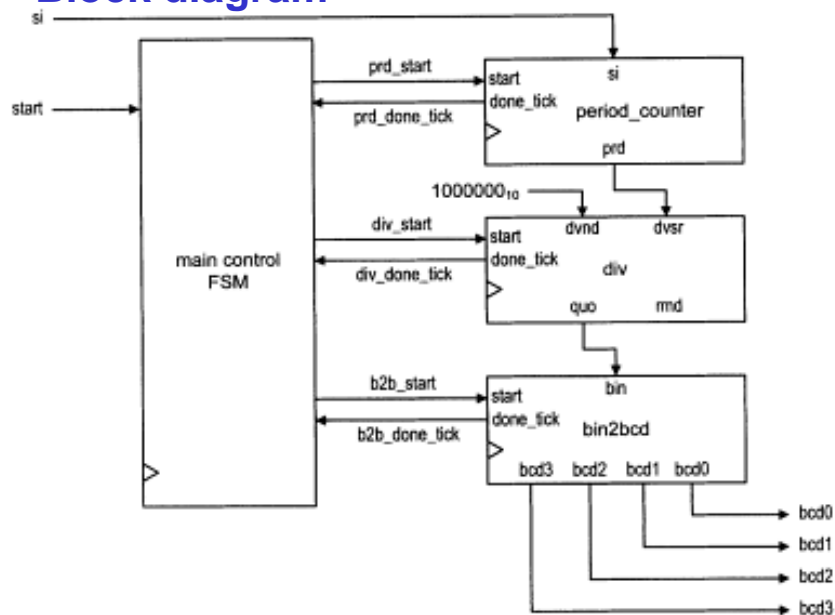

58

ASM chart of master control

 

59

VHDL code

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity low_freq_counter is
  port(
    clk, reset: in std_logic;
    start: in std_logic;
    si: in std_logic;
    bcd3, bcd2, bcd1, bcd0: out std_logic_vector(3 downto 0)
  );
end low_freq_counter;

architecture arch of low_freq_counter is

  type state_type is (idle, count, frq, b2b);
  signal state_reg, state_next: state_type;
  signal prd: std_logic_vector(9 downto 0);
  signal dvsr, dvnd, quo: std_logic_vector(19 downto 0);
  signal prd_start, div_start, b2b_start: std_logic;
  signal prd_done_tick, div_done_tick, b2b_done_tick: std_logic;

begin

```

60

```

=====
-- component instantiation
=====

-- instantiate period counter
prd_count_unit: entity work.period_counter
port map(clk=>clk, reset=>reset, start=>prd_start, si=>si,
         ready=>open, done_tick=>prd_done_tick, prd=>prd);

-- instantiate division circuit
div_unit: entity work.div
generic map(W=>20, CBIT=>5)
port map(clk=>clk, reset=>reset, start=>div_start,
         dvsr=>dvsr, dvnd=>dvnd, quo=>quo, rmd=>open,
         ready=>open, done_tick=>div_done_tick);

-- instantiate binary-to-BCD convertor
bin2bcd_unit: entity work.bin2bcd
port map
  (clk=>clk, reset=>reset, start=>b2b_start,
   bin=>quo(12 downto 0), ready=>open,
   done_tick=>b2b_done_tick,
   bcd3=>bcd3, bcd2=>bcd2, bcd1=>bcd1, bcd0=>bcd0);

-- signal width extension
dvnd <= std_logic_vector(to_unsigned(1000000, 20));
dvsr <= "00000000000" & prd;

```

61

```

=====
-- Master FSM
=====

process(clk,reset)
begin
  if reset='1' then
    state_reg <= idle;
  elsif (clk'event and clk='1') then
    state_reg <= state_next;
  end if;
end process;

```

62

```

process(state_reg,start,
        prd_done_tick,div_done_tick,b2b_done_tick)
begin
    state_next <= state_reg;
    prd_start <='0';
    div_start <='0';
    b2b_start <='0';
    case state_reg is
        when idle =>
            if start='1' then
                state_next <= count;
                prd_start <='1';
            end if;
        when count =>
            if (prd_done_tick='1') then
                div_start <='1';
                state_next <= frq;
            end if;
        when frq =>
            if (div_done_tick='1') then
                b2b_start <='1';
                state_next <= b2b;
            end if;
        when b2b =>
            if (b2b_done_tick='1') then
                state_next <= idle;
            end if;
    end case;
end process;
end arch;

```

63

Overview

- Finite State Machine (FSM) Representations:
 1. State Graphs
 2. Algorithmic State Machine (ASM) Charts
- Finite State Machines with Datapath (FSMD)
- Algorithmic State Machine with Datapath (ASMD)

- Examples
 - Example 1 – period counter
 - Example 2 – division circuit
 - Example 3 – binary-2-BCD converter
 - Example 4 – low-frequency counter
 - **Example 5 – multiplier**


64

Example 5: Add-and-shift Multiplier

- Multiplier for unsigned numbers
- See Section 4.8 in C.H.Roth book

$$\begin{array}{r}
 \text{Multiplicand} \longrightarrow 1\ 1\ 0\ 1\ (13) \\
 \text{Multiplier} \longrightarrow 1\ 0\ 1\ 1\ (11) \\
 \hline
 \text{Partial products} \left. \vphantom{\begin{array}{l} \text{Multiplicand} \\ \text{Multiplier} \end{array}} \right\} \begin{array}{r}
 \longrightarrow 1\ 1\ 0\ 1 \\
 \longrightarrow 1\ 1\ 0\ 1 \\
 \longrightarrow 1\ 0\ 0\ 1\ 1\ 1 \\
 \longrightarrow 0\ 0\ 0\ 0 \\
 \longrightarrow 1\ 0\ 0\ 1\ 1\ 1 \\
 \longrightarrow 1\ 1\ 0\ 1 \\
 \hline
 1\ 0\ 0\ 0\ 1\ 1\ 1\ 1\ (143)
 \end{array}
 \end{array}$$

65

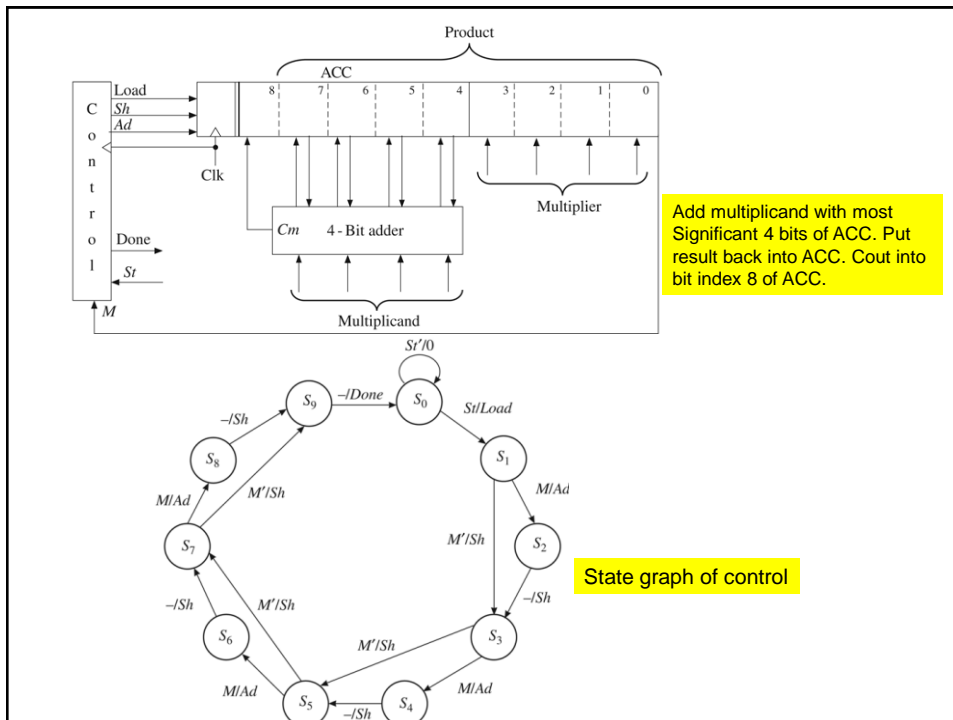

66

Summary

- State graphs and ASM charts are graphical models for FSMs
- ASM charts are somewhat more convenient to write VHDL code from
- **Finite State Machines with Datapath, FSMDs (particularly, Algorithmic State Machine with Datapath, ASMD – as a form of FSMD) are great for RT design methodology**
- They are useful when we care about the internal structure of the circuit
- Try to reuse developed components to implement larger designs

67

Credits

- Chapters 5,6 of Pong P. Chu, FPGA Prototyping by VHDL, 2008
- Chapter 5 from Jr. Charles H. Roth and Lizy K. John, Digital Systems Design Using VHDL, 2007.

68