


1 AC power

We'll apply phasor techniques to the study of ac power.

Definitions

- (a) Instantaneous power - delivered to a device is given by the product of the instantaneous voltage across the device and the instantaneous current through it.

$$p(t) \triangleq v(t) \cdot i(t) \quad (1)$$

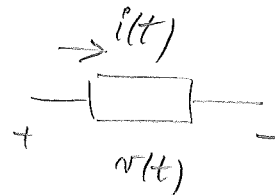(b) Average power

- Obtained for a time interval t_1 to t_2 by integrating the instantaneous power $p(t)$ and by dividing by the length of the interval:

$$P \triangleq \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt \quad (2)$$

- In the particular case that $p(t)$ is periodic with period T , the average power can be computed as:

$$P = \frac{1}{T} \int_{t_x}^{t_x + T} p(t) dt \quad (2') \quad \text{where } t_x \text{ is arbitrary.}$$

Sinusoidal steady state power ("ac power") (forcing function is a sinusoid)

$$v(t) = V_{ac} \cos(\omega t + \theta)$$

$$i(t) = I_{ac} \cos(\omega t + \phi)$$

$$p(t) = v(t) \cdot i(t) = V_{ac} \cdot I_{ac} \cdot \cos(\omega t + \theta) \cdot \cos(\omega t + \phi)$$

Use trig. identity $\cos a \cdot \cos b = \frac{1}{2} [\cos(a-b) + \cos(a+b)]$ to get:


$$p(t) = \frac{1}{2} V_{m} I_{m} \cos(\theta - \phi) + \frac{1}{2} V_{m} I_{m} \cos(2\omega t + \theta + \phi) \quad (3)$$

Average power:

time independent!

time dependent!
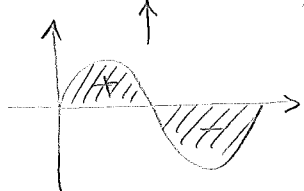
$$P = \frac{1}{T} \int_{t_x}^{t_x+T} \frac{1}{2} V_{m} I_{m} \cos(\theta - \phi) dt + 0 = \frac{1}{T} (t_x+T - t_x) \frac{1}{2} V_{m} I_{m} \cos(\theta - \phi)$$





$$P = \frac{1}{2} V_{m} I_{m} \cos(\theta - \phi) = \left(\frac{1}{\sqrt{2}} V_{m}\right) \cdot \left(\frac{1}{\sqrt{2}} I_{m}\right) \cdot \cos(\theta - \phi) = V_{rms} \cdot I_{rms} \cdot \cos(\theta - \phi)$$

[W] watts



$rms \equiv$ root-mean-square.

Example general

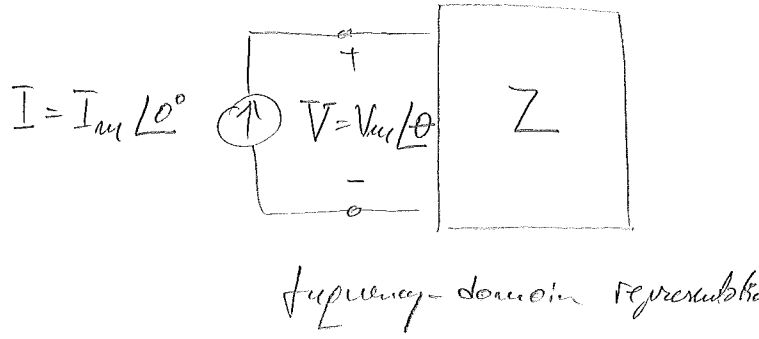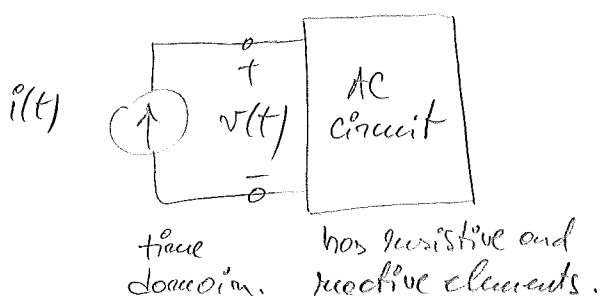

$$i(t) = I_m \cos \omega t ; \quad v(t) = V_m \cos(\omega t + \theta)$$

$$\phi = 0^\circ$$

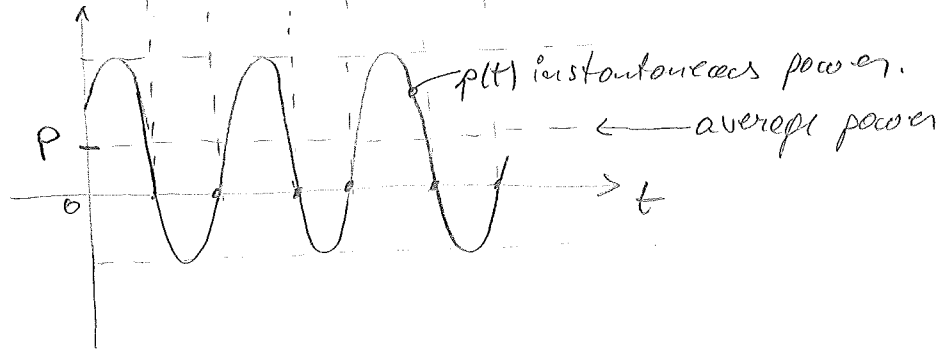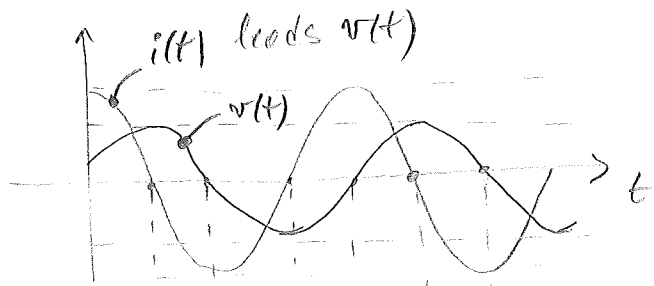

we will want to find it out.

We identify three important cases:

Case 1: $\theta - \phi = 0^\circ$ \Rightarrow v and i are in phase with each other as in a purely resistive load!

$$(3) \Rightarrow \boxed{p(t) = \frac{1}{2} V_m I_m [1 + \cos 2\omega t]} \quad (5)$$

Note: it alternates between 0 and $V_m I_m$ and so always positive!

In this case 1, expression (4) reaches its maximum denoted $S = \frac{1}{2} V_m I_m = V_{rms} \cdot I_{rms}$ and called the

(6) apparent power

Even though S has the same dimension as P , S is expressed in VA (volt amperes) to distinguish it from P .

Case 2: $\theta - \phi = \pm 90^\circ$: condition arises when circuit is purely reactive.

Because $\cos(\pm 90^\circ) = 0$:

$$(3) \Rightarrow \boxed{p(t) = \frac{1}{2} V_m I_m \cos(2\omega t \pm 90^\circ)} \quad (7)$$

whose average is zero! which confirms that purely reactive loads dissipate no power: the energy absorbed during a positive alternation of $p(t)$ is returned to the source during the subsequent negative alternation!

Case 3 circuit is partly resistive, partly reactive

$$\Rightarrow 0 \leq \cos(\theta - \phi) \leq 1$$

$$\Rightarrow \boxed{0 \leq P \leq S} \quad (8)$$

Definitions: The term $\cos(\theta - \phi)$ is called "power factor" (pf)

$$pf = \cos(\theta - \phi) \quad (9)$$

↑ called "pf angle"



OBS: Because $\cos(\theta - \phi) = \cos[-(\theta - \phi)]$ the power factor is the same whether current lags or leads the voltage!

- Power factor pf is given by:

$$pf = \frac{\text{average power}}{\text{apparent power}} = \frac{\frac{1}{2} V_{rms} I_{rms} \cos(\theta - \phi)}{\frac{1}{2} V_{rms} I_{rms}} = \cos(\theta - \phi)$$

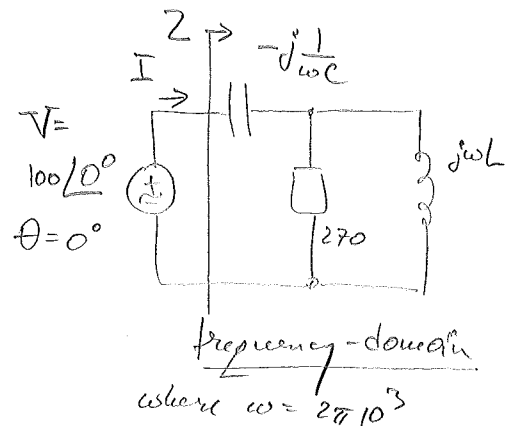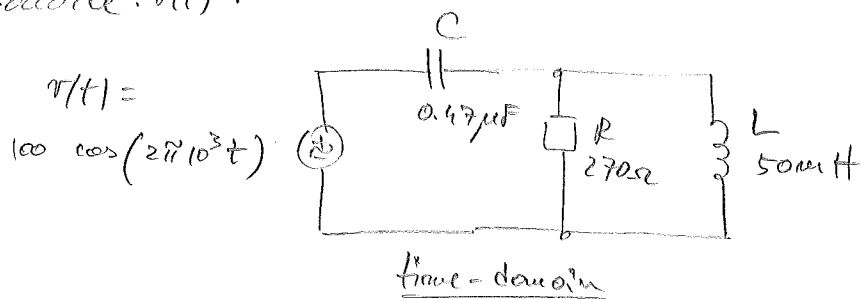Example:

Find apparent power as well as avg. power delivered by the source. $v(t)$:



We need to find V_{rms} , I_{rms} , and $\theta - \phi$

$$V_{rms} = 100 \text{ V}, \quad \theta = 0^\circ$$

$$I = \frac{V}{Z} \quad \text{where} \quad Z = Z_C + Z_R \parallel Z_L$$
$$= -j \frac{1}{\omega C} + \frac{j\omega L R}{R + j\omega L} = \frac{-j1}{2\pi \cdot 10^3 \times 0.47 \times 10^{-6}} + \frac{j2\pi \cdot 10^3 \times 0.05 \times 270}{270 + j2\pi \cdot 10^3 \times 0.05}$$
$$= 155.5 - j205.2 = 257.3 \angle -52.88^\circ \Omega \quad (\text{capacitive load})$$

$$\text{Then: } I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{257.3 \angle -52.88^\circ} = 0.3866 \angle 52.88^\circ \text{ A}$$

Apparent power: $S = \frac{1}{2} \times 100 \times 0.3866 = 19.43 \text{ VA}$

Power factor: $pf = \cos(0^\circ - 52.88^\circ) = \cos(52.88^\circ) = 0.6035$

Average power: $P = 19.43 \times 0.6035 = 11.72 \text{ W}$