
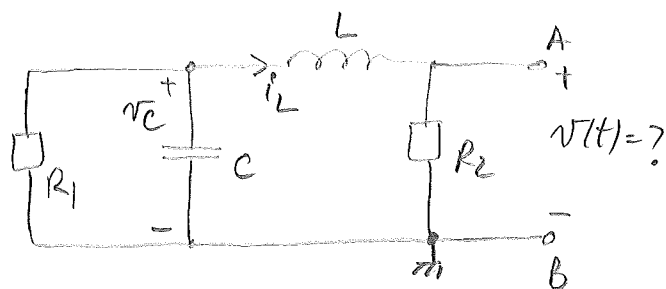


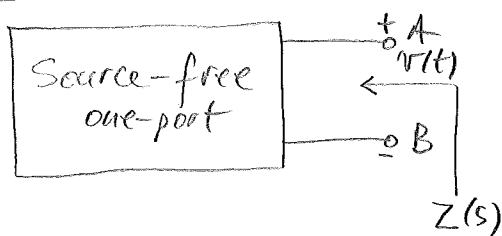Example 1

Given source free circuit with initial conditions: $v_C(0^-) = 10\text{ V}$ and $i_L(0^-) = 0$, find $v(t \geq 0) = ?$.



$$\begin{aligned} R_1 &= 2\text{ k} \\ C &= 5\text{ nF} \\ L &= 1\text{ mH} \\ R_2 &= 0.5\text{ k} \end{aligned}$$

Solution

The poles of $Z(s)$ determine the functional form of the open-circuit voltage $v(t)$!

That is because $Z(s) = \frac{V(s)}{I(s)}$ and thus we "look" at $Z(s)$ some way as we looked at $H(s)$ in previous two lectures:

$$V(s) = Z(s) \cdot I(s)$$

↑ When zero at the limit, $Z(s)$ is infinity, which corresponds to the poles of it!

- In our case:

$$Z(s) = R_2 \parallel \left[sL + \left(R_1 \parallel \frac{1}{sC} \right) \right]$$

$$Z(s) = \frac{R_2(R_1 L C s^2 + L s + R_1)}{R_1 L C s^2 + (R_1 R_2 C + L) s + (R_1 + R_2)}$$

- Let's try the asymptotic checks:

$$Z(0) = R_1 \parallel R_2 \quad \text{confirmed!}$$

$$Z(\infty) = R_2 \quad \text{confirmed!}$$

$$Z(s) = 500 \cdot \frac{s^2 + 10^5 s + 20 \times 10^{10}}{s^2 + 6 \times 10^5 s + 25 \times 10^{10}} \quad [\Omega]$$

- Conjugate pole-pair: $p_{1,2} = (-3 \pm j4) \cdot 10^5$ complex NP/s

- From previous lecture, we know:

$$v(t) = 2 \cdot A \cdot e^{-3 \times 10^5 t} \times \cos(4 \times 10^5 t + \theta) \quad (1)$$

- We now wish to find A and θ on the basis of initial conditions.

- On one hand observe:

$$v = R_2 \cdot i_L$$

$$v(0) = R_2 \cdot i_L(0) = R_2 \cdot 0 = 0$$

1st initial condition

- On other hand, equation (1):

$$v(0) = 2 \cdot A \cdot e^0 \cdot \cos(0 + \theta) = 2A \cos \theta$$

$$\Rightarrow 2A \cos \theta = 0 \quad (2)$$

- Because we seek a solution with $A \neq 0$, we must have:

$$\cos \theta = 0 \Rightarrow \theta = 90^\circ$$

- Hence:

$$v(t) = 2A e^{-3 \times 10^5 t} \cdot \sin(4 \times 10^5 t) \quad (3)$$

- For inductances:

$$v_C - v = L \frac{di_L}{dt}$$

$$\frac{v_C - v}{L} = \frac{d}{dt} \left(\frac{v}{R_2} \right) \Rightarrow \frac{R_2}{L} (v_C - v) = \frac{dv}{dt} \quad (4)$$


So, second initial condition:

$$\frac{dv(0)}{dt} = \frac{R_2}{L} [v_C(0) - v(0)] = \frac{500}{10^{-3}} (10 - 0) = 5 \times 10^6$$

But using equation (3): $\frac{dv(0)}{dt} = 2A (-3 \times 10^5 \cdot e^0 \cdot \sin 0 + 4 \times 10^5 \cdot e^0 \cdot \cos 0) = 8 \times 10^5 \times A$

$$\Rightarrow 8 \times 10^5 \times A = 5 \times 10^6 \Rightarrow \boxed{A = 6.25} \text{ [V]} \quad (5)$$
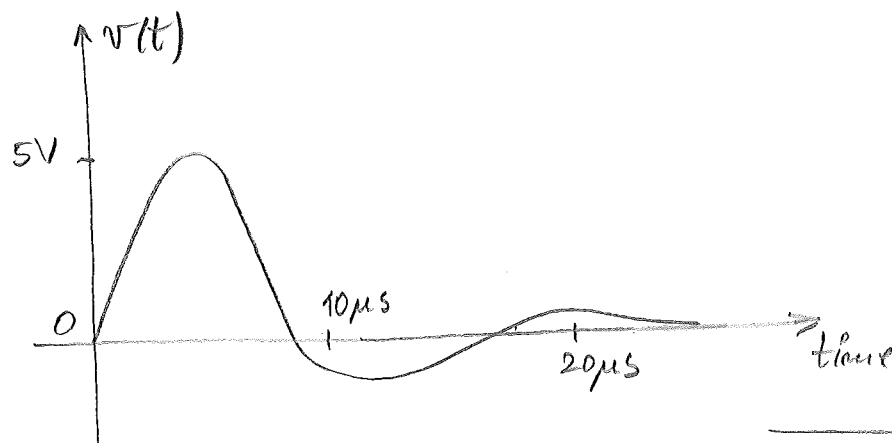
$$\text{So, finally: } \boxed{v(t) = 12.5 \times e^{-3 \times 10^5 t} \times \sin(4 \times 10^5 t)} \text{ [V]}$$



IMPORTANT DISCUSSION

- This example is done without using or having any knowledge about Laplace transforms. Because of that we had to do extra work to find constants \boxed{A} and $\boxed{\theta}$! This extra work may become tedious and time consuming in general.
- That is why Laplace transform-based analysis should be preferred because Laplace transform takes initial conditions into account automatically!
- For more info on the subtle differences between these two approaches, see the "STORY OF \boxed{S} " lecture notes at the end of the semester!