
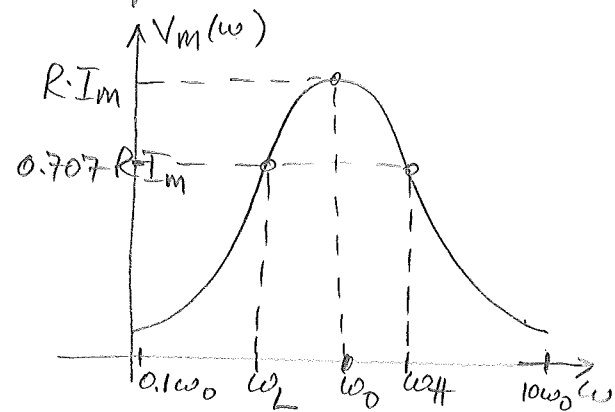

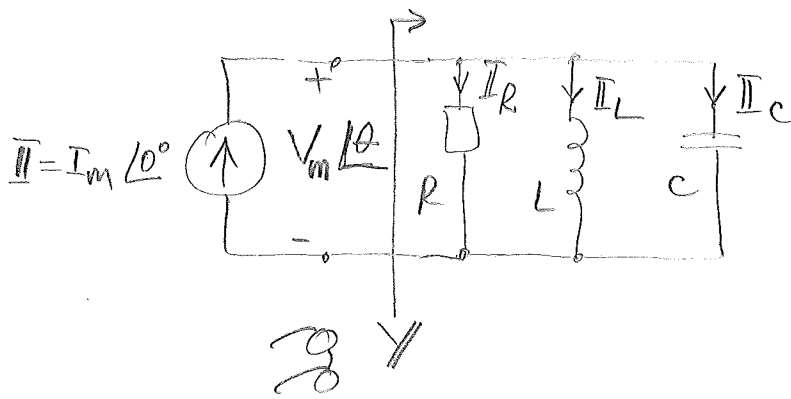
## 2 Parallel Resonance

- Capacitance & inductance connected in parallel.



$$Y = G + j\left(\omega C - \frac{1}{\omega L}\right) \quad (1)$$

Doing a similar analysis as for the series resonance we can derive:

$$Y = G \left[ 1 + jQ \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] \quad (2)$$

$$\text{where } \omega_0 = \frac{1}{\sqrt{LC}} \text{ is}$$

the "resonance frequency"

$$Q = R \sqrt{\frac{C}{L}} \quad (3) \text{ is the "quality factor" of the parallel RLC circuit!}$$

$$V = Z \cdot I = \frac{1}{Y} \cdot I = \frac{I_m}{G \left[ 1 + jQ \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]} \Rightarrow \quad (4)$$

$$\Rightarrow \begin{cases} V_m(\omega) = R I_m \cdot \frac{1}{\sqrt{1 + Q^2 \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}} & (5) \leftarrow \text{Has peak value: } V_{m(\max)} = R \cdot I_m \\ \angle V = \theta(\omega) = -\tan^{-1} \left[ Q \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] & (6) \end{cases}$$

- (1)  $\omega < \omega_0 \Rightarrow L$  dominates  $\Rightarrow$  parallel RLC is inductive
- (2)  $\omega > \omega_0 \Rightarrow C$  dominates  $\Rightarrow$  " " capacitive.
- (3)  $\omega = \omega_0$   $\Rightarrow \omega C = \frac{1}{\omega L} \Rightarrow Y$  is purely conductive:  $Y = G + j0$   
 Resonance  $\Rightarrow L \& C$  combination effectively behave as an open circuit!

$V_m$  is maximized at resonance, and average power dissipated by R:

$$P_{max} = \frac{1}{2} R I_m^2 = R I_{rms}^2$$

Frequencies at which P is down to half its maximum value are the "half power frequencies"  $\omega_L, \omega_H$ , and the

"half power bandwidth"  $BW = \omega_H - \omega_L$  is such that:

$$Q = \frac{\omega_0}{BW} \quad (7)$$

$$(7) + (3) \Rightarrow BW = \frac{1}{RC} \quad (8)$$

NOTE: In a parallel RLC circuit  $\omega_0$  is set by L, C and bandwidth BW is set by R, C!

Following the same line as in series RLC we can derive that in a parallel RLC circuit, we have:

|  |                   |   |
|--|-------------------|---|
| $\left\{ \begin{array}{l} I_R = \frac{V_m}{R} \angle \theta \\ I_C = \omega C V_m \angle \theta + 90^\circ \\ I_L = \frac{1}{\omega L} V_m \angle \theta - 90^\circ \end{array} \right.$ | and at resonance: | $\left\{ \begin{array}{l} V = R \cdot I_m \angle 0^\circ \\ I_R = I_m \angle 0^\circ \\ I_C = Q I_m \angle +90^\circ \\ I_L = Q I_m \angle -90^\circ \end{array} \right.$ |
|--|-------------------|---|

Note: If  $Q > 1 \Rightarrow$  current peak amplitudes  $> I_m$   
This is called "resonant current rise"!

- "Maximum stored energy" at resonance:  $w_L(t) + w_C(t)$

- "Power dissipated per cycle" at resonance:  $w_R(\text{cycle})$


$$\begin{aligned} w_L(t) + w_C(t) &= \frac{Q}{\omega_0} R \cdot I_{rms}^2 \\ w_R(\text{cycle}) &= \frac{2\pi}{\omega_0} R I_{rms}^2 \end{aligned} \quad \Rightarrow$$

$$\Rightarrow Q = 2\pi \cdot \frac{\text{maximum stored energy}}{\text{energy dissipated per cycle}} \quad (9)$$
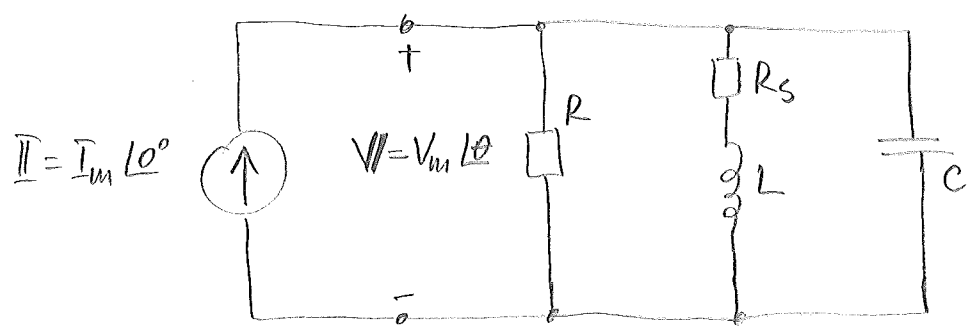
### 3 Practical Resonant Circuits

- A class of circuits called tuned circuits such as tuned oscillators and tuned amplifiers in radio communications!

- L is the least ideal  $\Rightarrow$  modeled in series with a "stray" resistance.



A practical tank circuit.

$$Y = \frac{1}{R} + j\omega C + \frac{1}{R_S + j\omega L}$$

$$Y = \frac{1}{R} + \frac{R_S}{R_S^2 + (\omega L)^2} + j\omega \left( C - \frac{L}{R_S^2 + (\omega L)^2} \right)$$

- We are interested in  $\omega_{res} \neq 0$ , which makes the circuit resonant, (makes  $Y$  purely real): it is the frequency that makes:

$$C - \frac{L}{R_S^2 + (\omega_{res} L)^2} = 0$$

$$\Rightarrow \omega_{res} = \sqrt{\frac{1}{LC} - \frac{R_S^2}{L^2}} \quad (10)$$

- In the limit  $R_S \rightarrow 0 \Rightarrow \omega_{res} \rightarrow \frac{1}{\sqrt{LC}}$

- But, the effect of  $R_S \neq 0$  is that  $\omega_{res} < \frac{1}{\sqrt{LC}}$  a downshift in the resonance frequency!

- An appropriate figure of merit for a practical inductor is the "quality factor of the inductor" defined:


$$Q_{coil} \triangleq \frac{|Z_L(\omega_{res})|}{R_S} = \frac{\omega_{res} L}{R_S} \quad (11)$$

- when  $\omega_{res} \rightarrow \frac{1}{\sqrt{LC}}$  we can approximate  $R_S = \omega_{res} L / Q_{coil} \approx \frac{1}{\sqrt{LC}} \cdot \frac{L}{Q_{coil}}$

So:

$$\omega_{res} = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{1}{2Q_{coil}^2}} \quad (12)$$

Example 1:

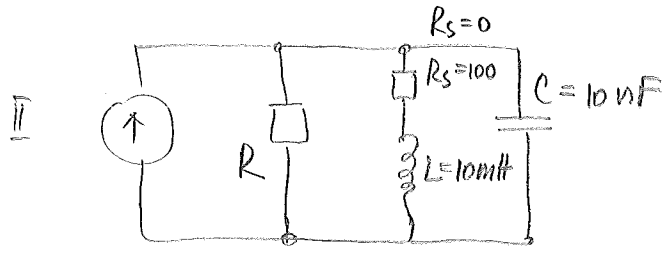

Case 1:  $R_s = 0$   
 Case 2:  $R_s = 100 \Omega$   
 Find  $\omega_{res} = ?$   
 $Q_{coil} = ?$

Case 1:  $R_s = 0$

Use eq. (11):  $Q_{coil} = \frac{\omega_{res} L}{R_s} = \infty$

Use eq. (12):  $\omega_{res} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 10^{-8}}} = 10^5 \frac{\text{rad}}{\text{s}}$



Case 2:  $R_s = 100 \Omega$

$Q_{coil} = \frac{\omega_{res} L}{R_s} \approx \frac{10^5 \times 10^{-2}}{100} = 10$

$\omega_{res} = \frac{1}{\sqrt{LC}} \times \sqrt{1 - \frac{1}{Q_{coil}^2}} = 10^5 \sqrt{1 - \frac{1}{10^2}} = 99,499 \frac{\text{rad}}{\text{s}}$  indicating

a 0.5% frequency downshift!

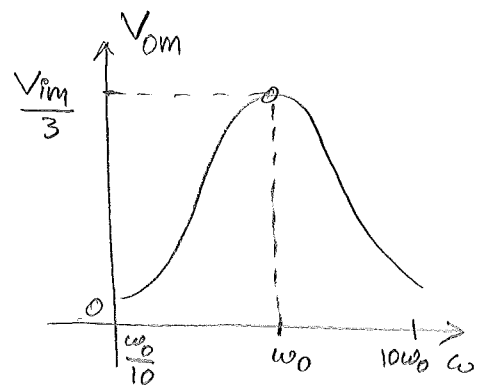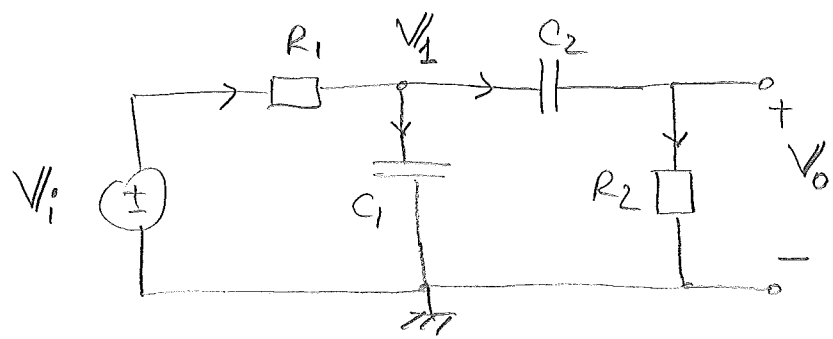Example 2: A passive inductorless Band-Pass circuit



(1)  $\frac{V_i - V_1}{R_1} = \frac{V_1}{\frac{1}{j\omega C_1}} + \frac{V_1 - V_o}{\frac{1}{j\omega C_2}}$

$$(2) \quad \frac{V_2 - V_0}{\frac{1}{j\omega C_2}} = \frac{V_0}{R_2}$$

(6)

$$(1) + (2) \Rightarrow \left( V_0 = \frac{j\omega R_2 C_2}{1 + j\omega(R_1 C_1 + R_2 C_2 + R_1 C_2) - \omega^2 R_1 R_2 C_1 C_2} \cdot V_i \right) \quad (3)$$

can be manipulated into standard band-pass form:

$$(4) \quad \left( V_0 = \frac{A}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)} \cdot V_i \right) \quad \text{where:} \quad \left\{ \begin{array}{l} A = \frac{1}{1 + \frac{R_1}{R_2} \left(1 + \frac{C_1}{C_2}\right)} \\ \omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \\ Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 C_1 + R_2 C_2 + R_1 C_2} \end{array} \right.$$

Note:


- Because  $A \leq 1 \Rightarrow$  no matter values of  $R_1, R_2, C_1, C_2$  we always have:

$$V_{om(max)} \leq V_{im}$$

- Our circuit is incapable of resonance signal rise!

$$\text{- Let } \left\{ \begin{array}{l} R_1 = R_2 = R \\ C_1 = C_2 = C \end{array} \right. \Rightarrow \left\{ \begin{array}{l} A = \frac{1}{3} \\ \omega_0 = \frac{1}{RC} \\ Q = \frac{1}{3} \end{array} \right.$$

Example 3: KRC circuit

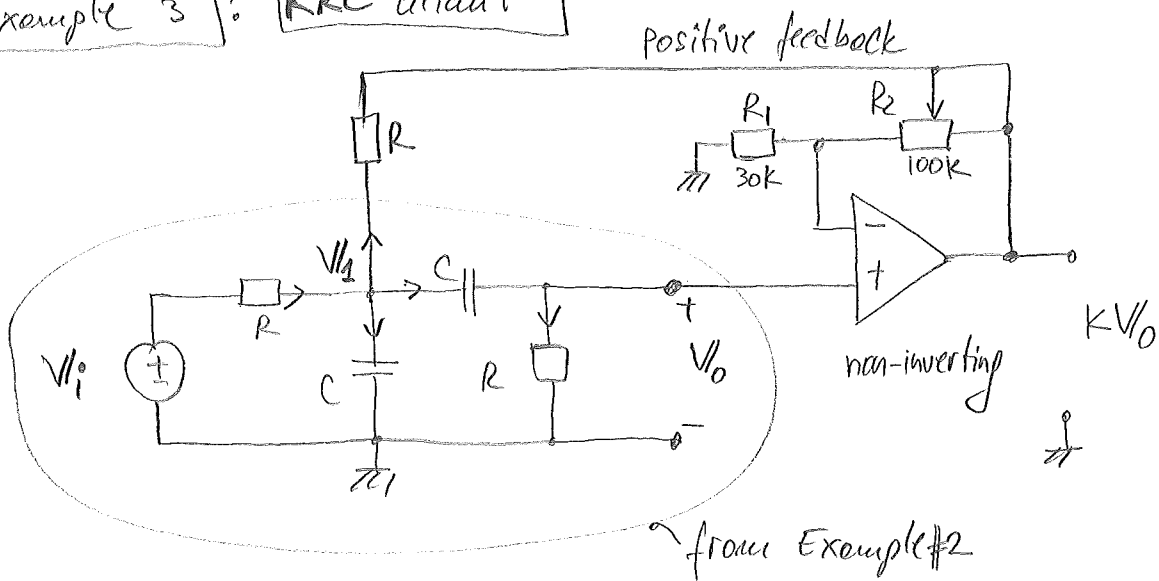

- $V_0$  is amplified by  $K = 1 + \frac{R_2}{R_1}$  and then re-injected via an additional  $R$  into circuit itself!
- Due to the positive feedback action by OpAmp, it is possible to bolster both  $A$  &  $Q$ .

$$\begin{cases} \text{(1)} & \frac{V_i - V_1}{R} - \frac{V_1}{\frac{1}{j\omega C}} + \frac{V_1 - V_0}{\frac{1}{j\omega C}} + \frac{V_1 - KV_0}{R} \\ \text{(2)} & \frac{V_1 - V_0}{\frac{1}{j\omega C}} = \frac{V_0}{R} \end{cases} \Rightarrow$$

$$\Rightarrow V_0 = \frac{j\omega RC}{2 - (\omega RC)^2 + (4-K)j\omega RC} \cdot V_i \quad (3)$$

which when put into the band-pass form (eq. 4 in Example 2) we get:

$$A = \frac{1}{4-K} \quad \omega_0 = \frac{\sqrt{2}}{RC} \quad Q = \frac{\sqrt{2}}{4-K}$$

↑  
still set by RC

controlled by  $K$ : very to achieve wide range of  $A, Q$   
 In the limit  $K \rightarrow 4 \Rightarrow A = \infty, Q = \infty \Rightarrow$  oscillation!!!!