
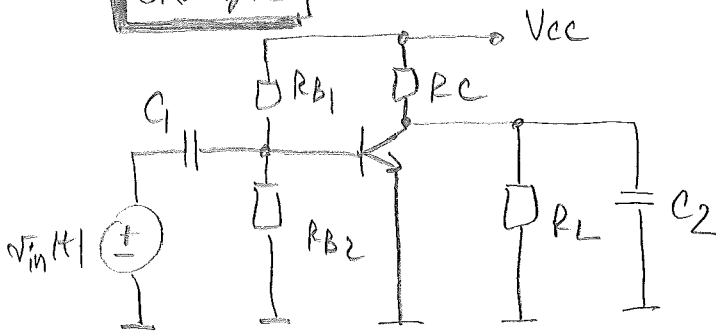


## Example

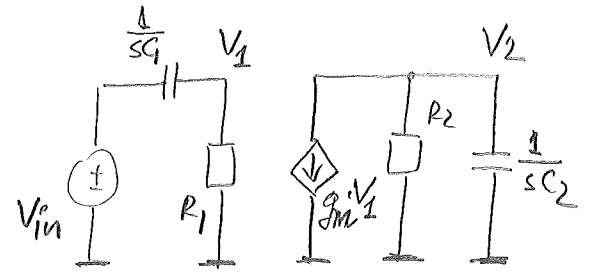

small  
signal  
analysis



where:  $\begin{cases} R_1 \triangleq R_{B1} \parallel R_{B2} \parallel r_{\pi} \\ R_2 \triangleq R_C \parallel R_L \end{cases}$

$$\begin{cases} \frac{V_{in} - V_1}{\frac{1}{sC_1}} = \frac{V_1}{R_1} \Rightarrow sC_1 V_{in} = V_1 (sC_1 + G_1) \Rightarrow \frac{V_1}{V_{in}} = \frac{sC_1}{sC_1 + G_1} \\ g_m V_1 + \frac{V_2}{R_2} + \frac{V_2}{\frac{1}{sC_2}} = 0 \Rightarrow g_m V_1 = -V_2 (sC_2 + G_2) \end{cases} \Rightarrow \text{eliminate } V_1$$

$$\Rightarrow H(s) = \frac{V_2}{V_{in}} = - \frac{sC_1 \cdot g_m}{(sC_1 + G_1)(sC_2 + G_2)}$$


$$H(s) = \frac{-\frac{g_m \cdot s}{C_2}}{\left(s + \frac{G_1}{C_1}\right) \left(s + \frac{G_2}{C_2}\right)}$$

of the form:

$$H(s) = \frac{-K \cdot s}{(s+a)(s+b)}$$

Assume:  $a < b$ ,  $a, b > 0$ ,  $K > 0$

Magnitude Bode diagram:

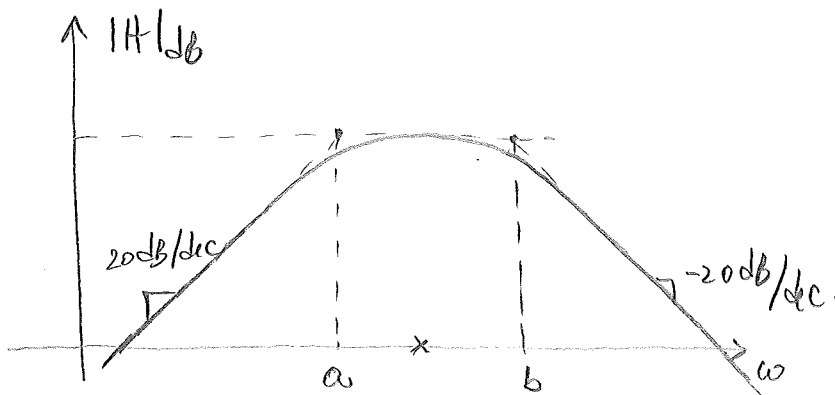


$$H(j\omega) = \frac{-K j\omega}{(j\omega + a)(j\omega + b)}$$

$\omega \rightarrow 0$ : derivator

$\omega \rightarrow \infty$ : integrator

- Consider the response to this signal:

$$v_{in}(t) = E [u(t) - u(t - T_0)]$$

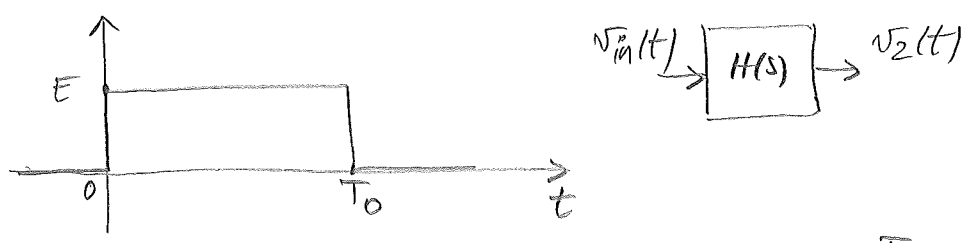

$$V_{in}(s) = E \left( \frac{1}{s} - \frac{1}{s} e^{-sT_0} \right) = \frac{E}{s} (1 - e^{-sT_0})$$

$$V_2(s) = H(s) \cdot V_{in}(s) = \underbrace{\frac{E}{s} (1 - e^{-sT_0})}_{=V_{in}(s)} \cdot \underbrace{\frac{-k}{(s+a)(s+b)}}_{=H(s)}$$


take it separately:

$$H(s) = \frac{-k}{(s+a)(s+b)} = \frac{-\frac{k}{b-a}}{s+a} + \frac{-\frac{k}{a-b}}{s+b} = \frac{-k}{b-a} \left[ \frac{1}{s+a} - \frac{1}{s+b} \right]$$

$$\Rightarrow V_2(s) = -\frac{Ek}{b-a} \cdot (1 - e^{-sT_0}) \cdot \left( \frac{1}{s+a} - \frac{1}{s+b} \right)$$

$$\Rightarrow v_2(t) = -\frac{Ek}{b-a} \left[ e^{-at} - e^{-bt} \right] u(t) + \frac{Ek}{b-a} \left[ e^{-a(t-T_0)} - e^{-b(t-T_0)} \right] u(t-T_0)$$

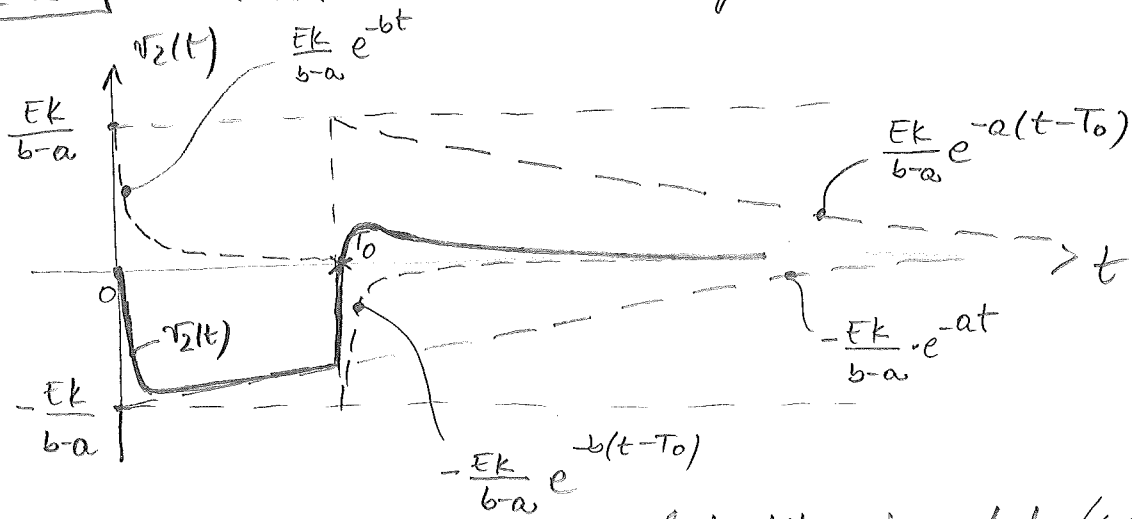
Case 1 Assume:  $a \ll b \Rightarrow$  large bandwidth!




NOTE:  $a \rightarrow 0$   $b \rightarrow \infty$  output will look like input! (with minus)

**Case 2**

$a, b$  both very large:

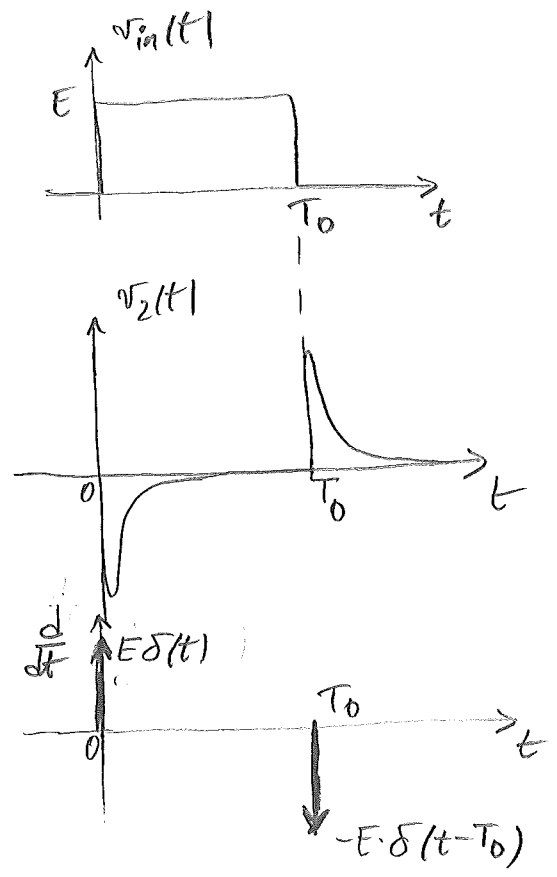


**ideal**

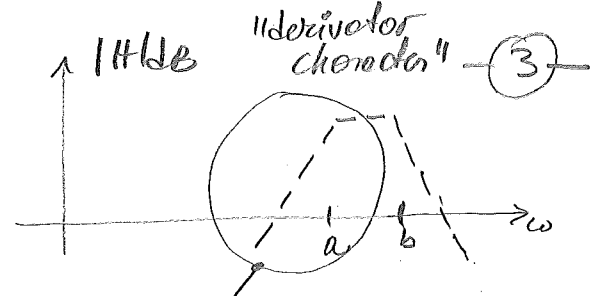


Looks more like derivative!  
Hence output will look more like:

**Case 3**

$a, b$  both very small:

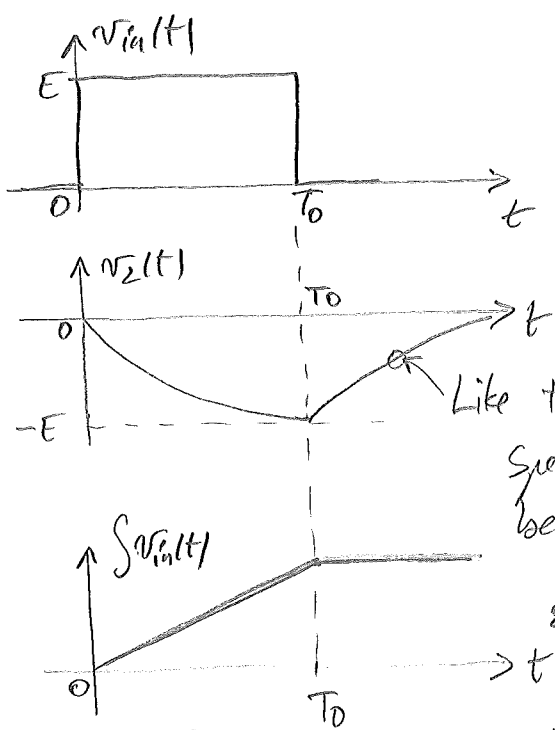

**ideal**

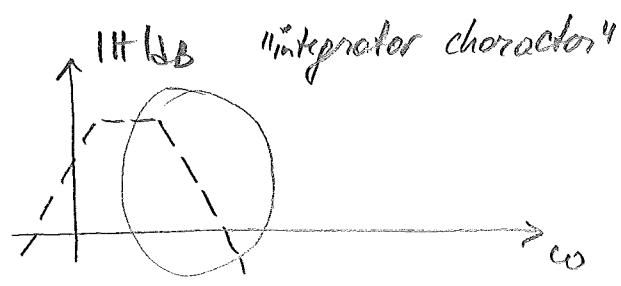

Looks more like integrator!  
So, output:

Like this because there is part of the spectrum where the circuit does not behave like an (ideal) integrator!

**QUESTION**

what is output for input:

