

### 3 Hybrid parameters (the "h parameters")

$$(1) \begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 \\ I_2 = h_{21} I_1 + h_{22} V_2 \end{cases} \Rightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = [h] \cdot \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


$$(2) h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} : \text{short-circuit input impedance} \quad [\Omega]$$

$$(3) h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} : \text{short-circuit forward current gain}$$


$$(4) h_{12} = \left. \frac{V_1}{V_2} \right|_{I_2=0} : \text{open-circuit reverse voltage gain}$$

$$(5) h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} : \text{open-circuit output admittance} \quad [\Omega^{-1}]$$

**Example** Find h parameters.

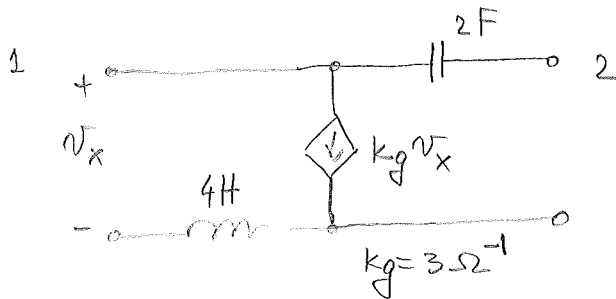

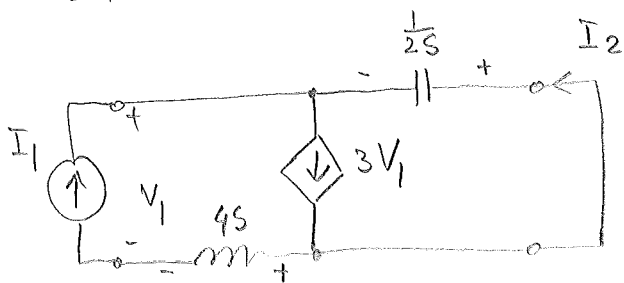- To find  $h_{11}$  and  $h_{21}$  we use the circuit with the output short-circuited:




$$\begin{cases} \text{KCL: } I_1 + I_2 = 3V_1 \\ \text{KVL: } V_1 + \frac{1}{2S} I_2 = 4S I_1 \end{cases} \Rightarrow \begin{matrix} \text{eliminate} \\ I_2 \text{ or } V_1 \end{matrix}$$

$$\begin{matrix} I_2 \\ \Rightarrow \end{matrix} \quad V_1 = \frac{8S^2 + 1}{2S + 3} I_1$$

$$\begin{matrix} V_1 \\ \Rightarrow \end{matrix} \quad I_2 = \frac{2S(12S - 1)}{2S + 3} I_1$$

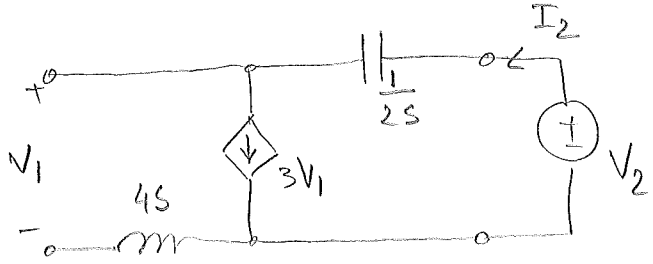- To find  $h_{12}$  and  $h_{22}$  we use the circuit with the input port as open-circuit:



$$\begin{cases} I_2 = 3V_1 \\ V_2 - V_1 = \frac{1}{2S} \cdot I_2 \end{cases} \Rightarrow \boxed{V_1 = \frac{2S}{2S+3} V_2} \text{ by } I_2 \text{ elimination}$$


$$\Rightarrow \boxed{I_2 = \frac{6S}{2S+3} V_2} \text{ by } V_1 \text{ elimination.}$$

- Finally:  $[h] = \begin{bmatrix} \frac{8S^2+1}{2S+3} \Omega & \frac{2S}{2S+3} \\ \frac{2S(2S-1)}{2S+3} & \frac{6S}{2S+3} S^{-1} \end{bmatrix}$

**NOTE:**  $h$  parameters can be added directly when 2 ports are connected in series at the input or in parallel at the output; not used after!
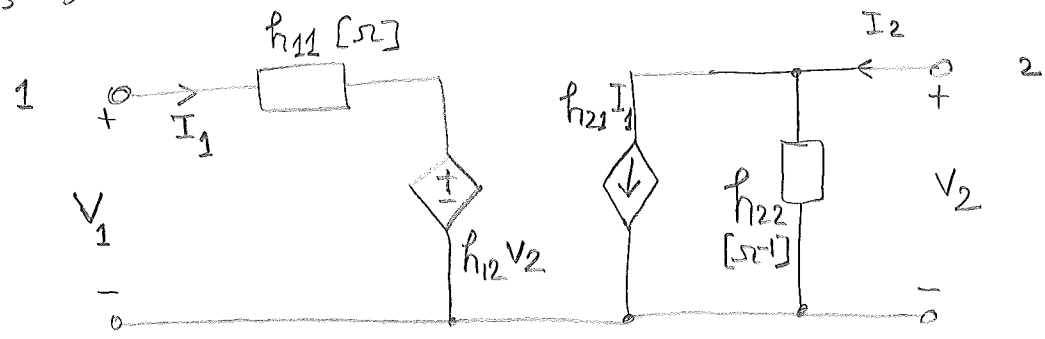
### Models of $h$ parameters


- Given a set of  $h$  parameters, a circuit that realizes them is shown below:



**Note:** This circuit is used to model the small-signal behavior of BJT's!

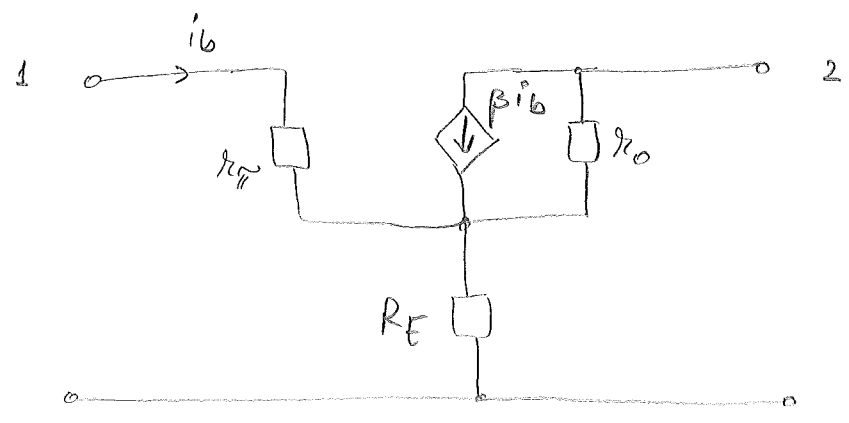**Example**

For the small-signal model of a common-emitter (CE) BJT amplifier, find its h parameters.





Solution: utilize techniques similar to the previous example to derive:

$$[h_e] = \begin{bmatrix} h_{ie} & h_{re} \\ h_{fe} & h_{oe} \end{bmatrix} = \begin{bmatrix} r_{\pi} + (\beta + 1)(R_E \parallel r_o) & \frac{R_E}{R_E + r_o} \\ \beta - (\beta + 1) \frac{R_E}{R_E + r_o} & \frac{1}{R_E + r_o} \end{bmatrix}$$

[e] stands for common emitter

$$h_{ie} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

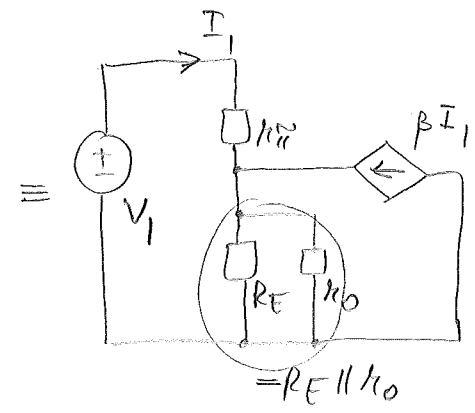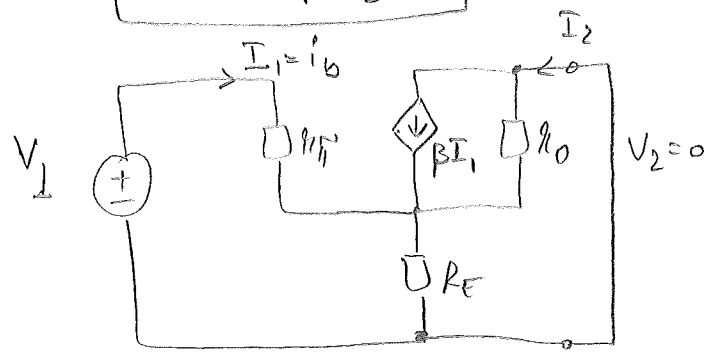

$$V_1 = r_{\pi} \cdot I_1 + (R_E \parallel r_o) (\cdot I_1 + \beta I_1)$$

$$V_1 = \left[ r_{\pi} + (\beta + 1)(R_E \parallel r_o) \right] I_1$$

$$\Rightarrow h_{ie} = \frac{V_1}{I_1} \Big|_{V_2=0} = r_{\pi} + (\beta + 1)(R_E \parallel r_o)$$

DIY:  $h_{re}, h_{fe}, h_{oe}$  !