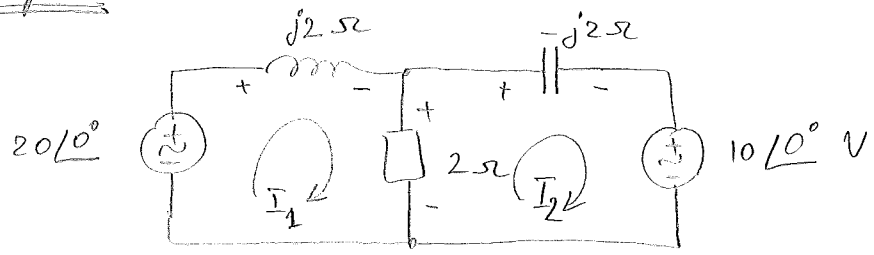


Example:



Find avg. power absorbed by each of the passive elements.

Solution:

- Avg. power absorbed by inductor & capacitor (are purely reactive elements) is zero: see case 2 in last lecture!
- use mesh analysis to find current thru resistance 2Ω:

$$\begin{cases} j2 \cdot I_1 + 2(I_1 - I_2) = 20 \\ 2(I_1 - I_2) = -j2 I_2 + 10 \end{cases} \Rightarrow \begin{cases} (2+j2) I_1 - 2 I_2 = 20 \\ 2 I_1 + (-2+j2) I_2 = 10 \end{cases}$$

where:  $Ax = b$

$$A = \begin{bmatrix} 2+j2 & -2 \\ 2 & -2+j2 \end{bmatrix} \quad b = \begin{bmatrix} 20 \\ 10 \end{bmatrix} \quad X = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Solve system to get:

$$\begin{cases} I_1 = 5 - j10 = 11.18 \angle -63.43^\circ \text{ A} \\ I_2 = 5 - j5 = 7.071 \angle -45^\circ \text{ A} \end{cases}$$

The net equivalent current thru 2Ω is:


$$I_1 - I_2 = -j5 = 5 \angle -90^\circ \text{ A}$$

||  
I<sub>in</sub>

Hence average power absorbed by resistor is:

$$P_R = \frac{1}{2} V_{in} I_{in} = \frac{1}{2} R I_{in}^2 = \frac{V_{in}^2}{2R} = \frac{1}{2} \times 2 \times 25 = 25 \text{ [W]}$$

# 2 Power and impedance

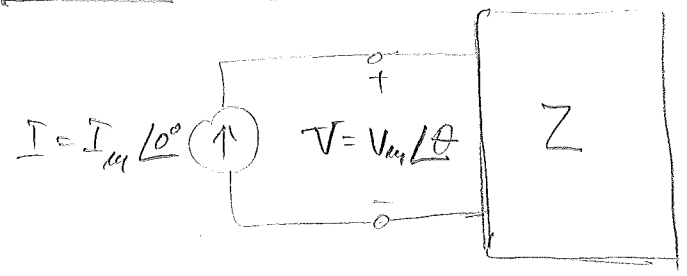

$$Z = \frac{V}{I} = |Z| \angle \theta$$

frequency-domain  
circuit representation.

$$i(t) = I_m \cos(\omega t) \quad v(t) = V_m \cos(\omega t + \theta)$$

$\phi = 0^\circ$   
current used as  
reference.

$$\theta - \phi = \theta - 0^\circ = \theta = \phi_Z$$

Therefore, equation (4) (see last lecture) can be written as:


$$P = \frac{1}{2} V_m I_m \cos \theta = V_{rms} \cdot I_{rms} \cdot \cos \theta = V_{rms} \cdot I_{rms} \cos(\phi_Z) \Rightarrow$$

with  $V_{rms} = |Z| \cdot I_{rms}$

$$\Rightarrow P = |Z| \cdot I_{rms}^2 \cdot \cos(\phi_Z) = I_{rms}^2 \cdot \left[ |Z| \cdot \cos(\phi_Z) \right] = R(\omega) \cdot I_{rms}^2 = R(\omega)$$

$$(1) \quad P = R(\omega) I_{rms}^2 = \frac{(V_{rms} \cdot \cos \theta)^2}{R(\omega)}$$

↑  
prove it on your own.

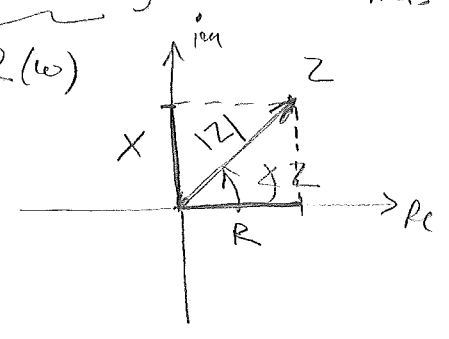


**OBS:**  $R(\omega)$  (of an impedance) represents the ability of a circuit to dissipate power in response to ac current!

Example:

A circuit is connected to the 120 V (rms), 60 Hz household ac line and dissipates an average power of 1 kW with a power factor  $pf = 0.75$ . Find the simple series and parallel equivalents of the circuit, knowing in class the assignment.


that the  $pf$  is a "leading  $pf$ "  $\equiv$  current  $i$  leads voltage  $v$

(a)

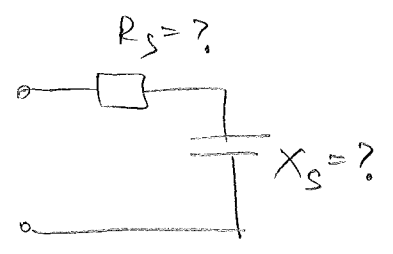

$\varphi = \theta - \phi < 0$   
OBS: this is a capacitive impedance.

A "visual":

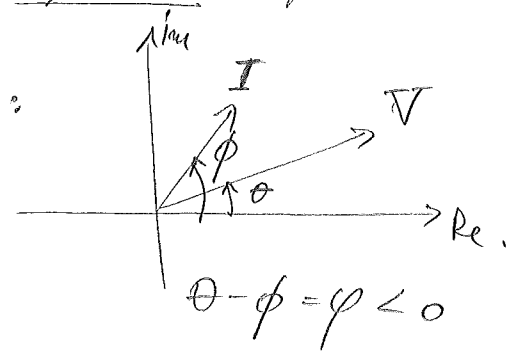

For simplicity assume current as reference with  $\phi = 0^\circ$ . Then:

$$\varphi = \theta = -\cos^{-1} pf = -\cos^{-1} 0.75 = -41.41^\circ$$


$Z = R + jX$  we have:

$$Eq. (11) \Rightarrow R = \frac{(V_{rms} \cos \theta)^2}{P} = \frac{(120 \times 0.75)^2}{10^3} = 8.1 \Omega$$


$$X = R \tan \theta = 8.1 \times \tan(-41.41^\circ) = -7.14 \Omega$$

The equivalent series circuit:
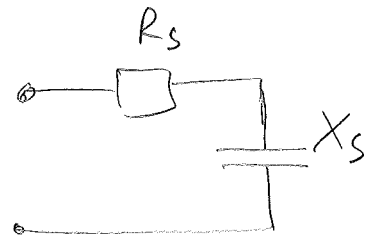
$$\text{is obviously } \begin{cases} R = R_s \\ X = X_s \end{cases}$$



(b)

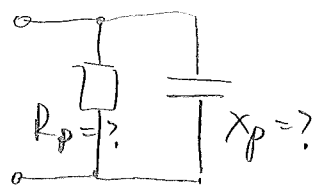


Hint: convert from above or work with admittance:  $Y = G + jB$
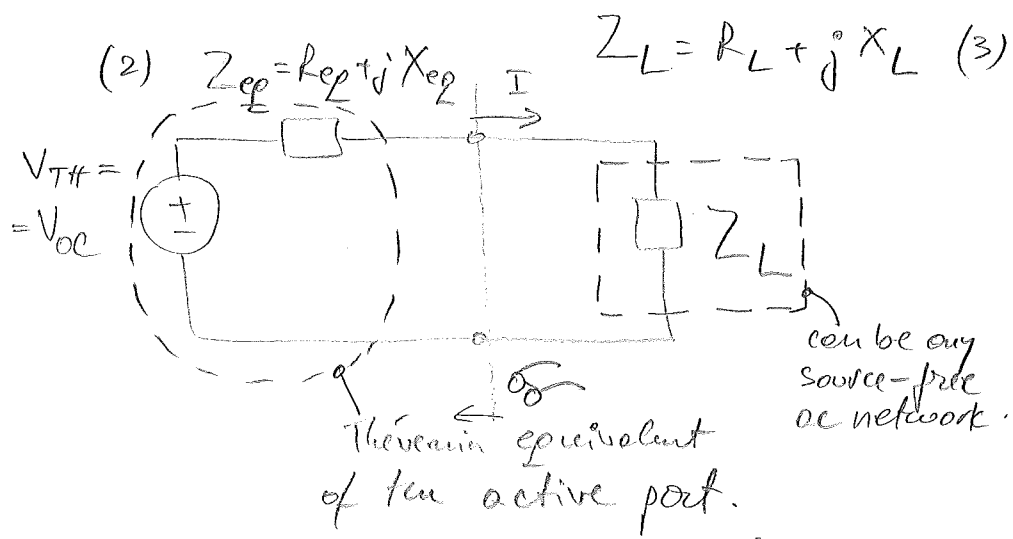
### 3 Maximum power transfer

Reminder: for resistive circuits we found that power transfer is maximized when the load is made equal to the source resistance. (condition called matching)

Now - what is the condition for an active ac port driving a load impedance:



$R_L = ?$ ,  $X_L = ?$  that maximize power transfer to the load!

The load power is  $P_L = R_L \cdot I_{rms}^2 = \frac{1}{2} R_L I_{rms}^2$  (see eq. (1))

where  $I_{rms} = \left| \frac{V_{oc}}{Z_{eq} + Z_L} \right|$

$$\Rightarrow P_L = \frac{1}{2} R_L \cdot \frac{|V_{oc}|^2}{(R_{eq} + R_L)^2 + (X_{eq} + X_L)^2}$$

any non-zero value would only reduce  $P_L$ . Eliminate this term by imposing:

(4)  $X_L = -X_{eq}$

so, we're left with:

$$P_L = \frac{1}{2} R_L \cdot \frac{|V_{oc}|^2}{(R_{eq} + R_L)^2}$$

← problem of finding the condition for  $R_L$  that maximizes  $P_L$ . We have shown in EE-206 that

$R_L = R_{eq}$  (5)

$$\Rightarrow R_L + jX_L = R_{eq} - jX_{eq}$$

$$\boxed{Z_L = Z_{eq}^*} \quad (6)$$

▷ Power transfer from an active ac port (in particular an ac source in series w/ an impedance) to a load is maximized when the load impedance is made equal to the complex conjugate of the equivalent impedance of the port!


▷ when this condition is met, the load is said to be matched to the ac port.

▷ Physically, the two reactances cancel each other, in effect forming a short-circuit. In this case the ac port and matched load form a resonant circuit!

▷ Maximum average power:

$$\boxed{P_{L(max)} = \frac{1}{2} |V_{oc}|^2 \cdot \frac{R_{eq}}{(R_{eq} + R_{eq})^2} = \frac{1}{8} \frac{|V_{oc}|^2}{R_{eq}}} \quad (7)$$

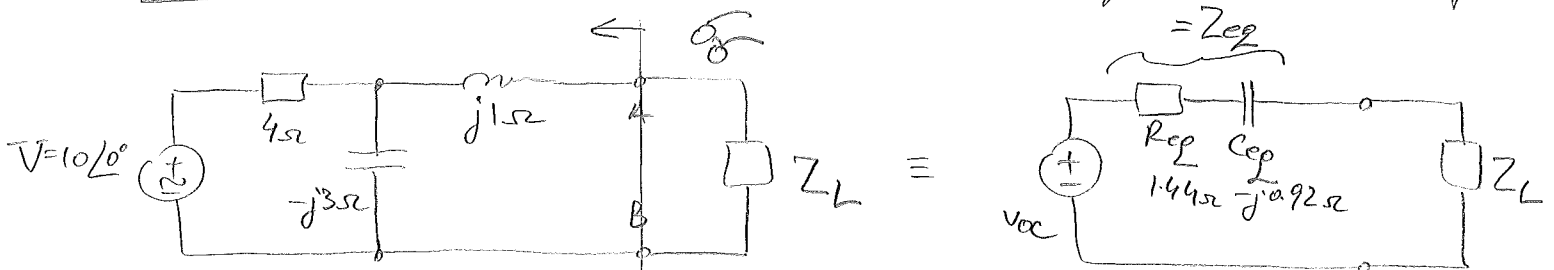Example: Find the load that will receive maximum power. Find that power.



(a)  $Z_{eq}$  Thèvenin equivalent = ?

$$V_{oc} = \frac{-j^3}{4 - j^3} \cdot 10 \angle 0^\circ = 6 \angle -53.13^\circ \text{ V}$$

$$Z_{eq} = j1 + [4 \parallel (-j^3)] = \dots = 1.44 - j0.92$$

$$\Rightarrow \boxed{Z_L = 1.44 + j0.92}$$

(b) (7)  $\Rightarrow$  
$$\boxed{P_{L(max)} = \frac{1}{8} \frac{|V_{oc}|^2}{R_{eq}} = \frac{1}{8} \times \frac{6^2}{1.44} = 3.125 \text{ W}}$$