

## 5 Power factor correction

- $P(t)$  does not contribute to average power (see figure 1)
- But it places an additional burden upon the source, which besides supplying the noted real power, must also contend with reactive power exchanges.
  - This burden is especially undesired in generation & distribution of industrial power:

$$(11) \quad \boxed{I_{rms} = \frac{P}{V_{rms} \times pf}}$$

see lecture #1  
center (eq. 4)

reveals that the current needed to supply a specified ac power at the rated line voltage is inversely proportional to pf of the load.

- (1)  $\Rightarrow$  lower pf's require greater current-carrying capacity be built into system.
- (2)  $\Rightarrow$  larger currents  $\Rightarrow$  greater ohmic losses in the power line resistance  $\Rightarrow$  lower efficiency

Example: Assume  $\varphi = \pm 45^\circ \Rightarrow pf = \cos 45^\circ = \frac{1}{\sqrt{2}} = 0.707$

$$(11) \Rightarrow \dot{I}_{rms}(pf=0.707) = \sqrt{2} \dot{I}_{rms}(pf=1) = 1.414 \dot{I}_{rms}(pf=1)$$

i.e.: current capacity must be increased by 41.4% to accommodate the same reactive power exchanges as when  $pf=1$  !


Also:

$$R_{line} \cdot \dot{I}_{rms}(pf=0.707)^2 = 2 \times R_{line} \times \dot{I}_{rms}(pf=1)^2$$

indicating a doubling in line-power loss due to reactive exchanges!

**[OBS]**: To optimize power generation & distribution, it is desirable to have  $pf \rightarrow 1$  or  $\varphi \rightarrow 0$ . In that case we have  $Q \rightarrow 0$ ,  $P(t) \rightarrow 0$ ,  $p(t) \rightarrow P_R(t)$

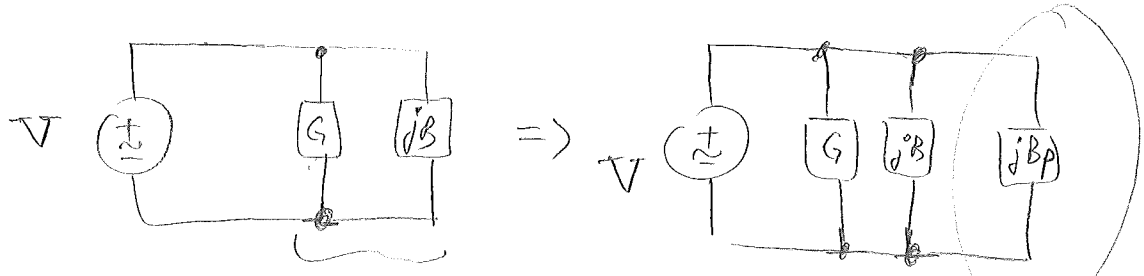- Such a condition is met by connecting a suitable reactive element at the load end so that reactive power is exchanged between load and this element, rather than between load and source! (parallel connection is preferred)
- This procedure is called "power-factor correction"!



$$Y = G + jB$$

- Using eq. (5):  $P = R(\omega) \cdot I_{rms}^2$  and

Also knowing:  $R = \frac{G}{G^2 + B^2}$      $X = \frac{-B}{G^2 + B^2}$

we get:  $\begin{cases} P = G V_{rms}^2 \\ Q = -B V_{rms}^2 \end{cases}$

- Now, find an element with susceptance  $B_p$ , which connected in || with load will raise the power-factor of the composite.

admittance:  $Y + jB_p = G + j(B + B_p)$  to unity. That is equivalent to imposing  $j(B + B_p) = 0 \Rightarrow B_p = -B$  (12)

- Composite admittance becomes purely resistive:  $Y + jB_p = G$   
 $\Rightarrow Q = 0 \Rightarrow$  the source no longer has to contend with reactive exchanges, and supplies now only real power  $p(t) = p_R(t)$ .

**OBS:** Physically: combination of parallel equal but opposite reactances (susceptances) acts as an open circuit! phenomenon called resonance.  
 Δ To raise pf to unity, the load must be made resonant!

- In practical situations a pf close to 1 is sufficient.
- Given a load  $Z = R + jX$ , find a reactance  $X_p$  connected in // with  $Z$  to raise the composite load  $jX_p || Z$  to a new value  $Pf_{new} = \cos[\angle(jX_p || Z)]$

$$X_p = \frac{R^2 + X^2}{R \cdot \tan[\pm \cos^{-1}(Pf_{new})] - X} \quad (13)$$

+ sign if  $Pf_{new}$  is lagging  
 - sign if  $Pf_{new}$  is leading.

- An alternate form: multiply with  $I_{rms}^2$  num. and denom. :  
 observing that:  $V_{rms}^2 = (R^2 + X^2) \cdot I_{rms}^2$   
 & using:  $P = R I_{rms}^2$ ;  $Q = X I_{rms}^2$

$$X_p = \frac{V_{rms}^2 / P}{\tan(\pm \cos^{-1} Pf_{new}) - \tan(\pm \cos^{-1} Pf_{old})} \quad (14)$$

also recall:

$$X_p = -\frac{1}{\omega C}$$

Example 1


Source 220 V(rms), 60 Hz  
 industrial load consumes  $P = 50 \text{ kW}$ ;  $pf = 0.7$  lagging.

Find a suitable bank of parallel capacitors to ensure  $pf = 0.95$  lagging  
 what current must these capacitor be able to withstand?

$$(14) \Rightarrow X_p = \frac{\frac{220^2}{50 \times 10^3}}{\tan(\cos^{-1} 0.95) - \tan(\cos^{-1} 0.75)} = -1.75 \Omega$$

$\Rightarrow$  We need  $C_p$  such that:  $\frac{1}{\omega C_p} = X_p$
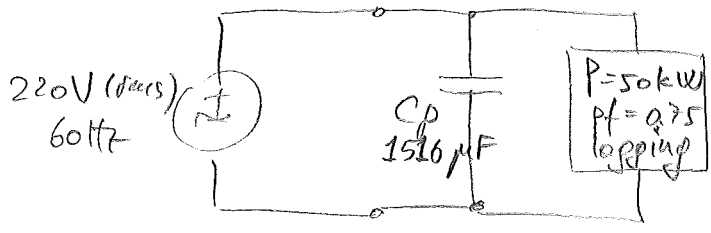
$$\text{or } C_p = -\frac{1}{\omega X_p} = -\frac{1}{2\pi 60 \times (-1.75)} = 1516 \mu\text{F}$$



By Ohm's law, current thru capacitor bank:

$$I_{rms} = \frac{V_{rms}}{|Z_{Cp}|} = \frac{220}{1.750} = 125.7 \text{ A}$$

← must be kept in mind when specifying Cp!

