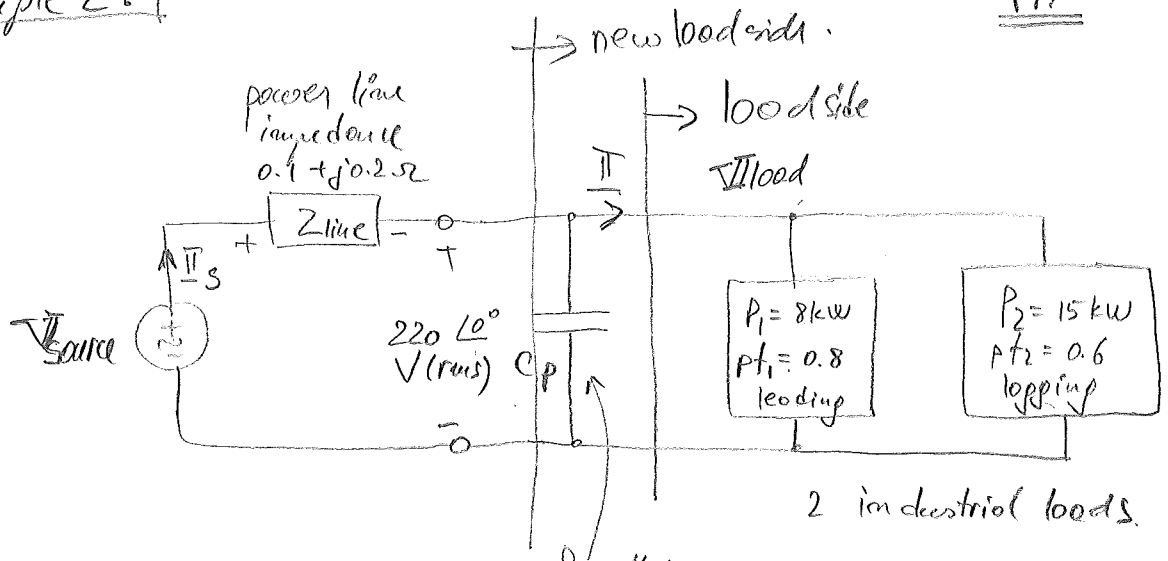


Example 2:



Parallel capacitance bank C_p used to correct power factor.

- (a) Assuming $C_p = 0$ find voltage and current capacity required to ensure 220 V (rms) across the load. Find efficiency of the system.
- (b) Specify a suitable value for C_p to ensure $pf = 0.95$ lagging. Re-compute source capacity and efficiency and compare w/ the uncorrected case.

(a) At the load we have (eq. 7):

$$Q_1 = P_1 \cdot \tan \phi_1 = 8 \tan (-\cos^{-1} 0.8) = -6 \text{ kVAR}$$

$$Q_2 = P_2 \cdot \tan \phi_2 = 15 \tan (\cos^{-1} 0.6) = 20 \text{ kVAR}$$

By "ac power conservation principle"

$$S_{\text{load}} = S_1 + S_2 = (8 - j6) + (15 + j20) = 23 + j14 \text{ kVA}$$

$$= P_{\text{load}} + j Q_{\text{load}}$$

Also

$$I_{\text{rms}} = (I_{\text{rms}}^*)^* \cdot \frac{(10)}{220} \left(\frac{S_{\text{load}}}{V_{\text{rms}}} \right)^* = \frac{(23 - j14) \times 10^3}{220}$$

$$= 104.5 - j63.64 = 122.4 \angle -31.33^\circ \text{ A}$$

By KVL:

$$\begin{aligned}
 \overset{\text{phasor}}{\rightarrow} \mathbf{V}_{s(\text{rms})} &= 220 \angle 0^\circ + Z_{\text{line}} \cdot \mathbf{I}_{\text{rms}} \\
 &= 220 + (0.1 + j0.2)(104.5 - j63.64) \\
 &= 243.2 + j14.53 \text{ V} \\
 &= \underline{243.6 \angle 3.42^\circ} \text{ V}
 \end{aligned}$$

By eq. 10:

$$\begin{aligned}
 S_{\text{source}} &= \mathbf{V}_{s(\text{rms})} \cdot \mathbf{I}_{\text{rms}}^* = (243.6 \angle 3.42^\circ) \times (122.4 \angle 31.33^\circ) \\
 &= 29.82 \angle 34.75^\circ = 24.50 + j17.00 \text{ kVA} \\
 &= P_{\text{source}} + jQ_{\text{source}}.
 \end{aligned}$$

Finally, the efficiency of the system:

$$\boxed{\eta = \frac{P_{\text{load}}}{P_{\text{source}}} = \frac{23}{24.50} = 93.9\%}$$

(b) Before power-factor correction:

$$\begin{aligned}
 \text{pf} &= \cos \varphi = \cos \left(\tan^{-1} \left(\frac{14}{23} \right) \right) = 0.854 \\
 &= \frac{P_{\text{load}}}{Q_{\text{load}}}
 \end{aligned}$$

- To raise pf to 0.95 we need $C_p = -\frac{1}{\omega X_p}$, where X_p is found with equation (14). Hence:

$$C_p = -\frac{\tan(\cos^{-1} 0.95) - \tan(\cos^{-1} 0.84)}{377 \times 220^2 / (23 \times 10^3)} = 353 \mu\text{F}$$

- with C_p in place, complex power of the load becomes (eq. (17)):

$$S_{\text{load}} = 23 + j23 \tan(\cos^{-1} 0.95) = 23 + j7.56 \text{ kVA}.$$

- Repeating calculations we find:

all phasors

$$I_{rms} = 110.0 \angle -18.20^\circ \text{ A}$$

$$V_{S(rms)} = 238.0 \angle 4.21^\circ \text{ V}$$

$$S_{source} = 24.21 + j9.98 \text{ kVA}$$

$$\eta = 95\%$$

- In summary, with C_p in place, the required source capacity is decreased from 243.6V, 122.4A to 238.0V, 110.0A (rms)

- Also, system efficiency is increased from 93.9% to 95%!

