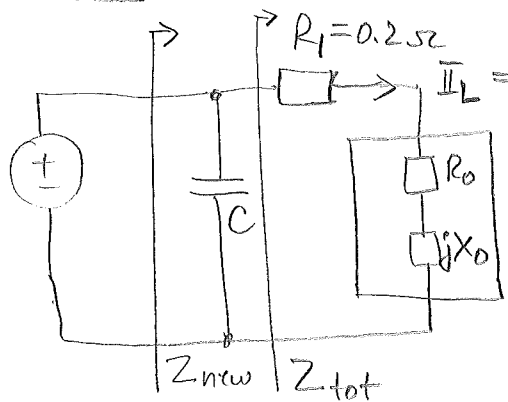


Problem 46 Ch. 11

Given:

V_s
60V



$I_L = |I_{L(rms)}| \angle 0^\circ$ ← assume for convenience

Load:
 $Z_L = R_0 + jX_0$

Apparent power: $S_0 = |P_0| = 10^3 [VA]$

pf = 0.8 lagging


Find: $C = ?$ such that the source power-factor $pf_{new} = 0.9$ lagging.
 ↑
 very important
 not of the load!

Solution:

- From first lecture on "ac power" Recall:

power-factor $pf = \cos \phi = \frac{\text{average power}}{\text{apparent power}} = \frac{P_0}{S_0}$


- power triangle of the load:

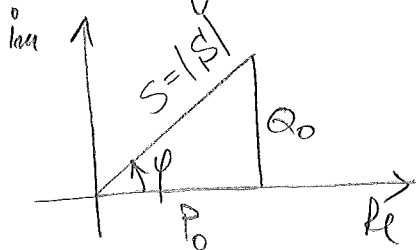

- impedance triangle of the load.


Recall:

$P_0 = R_0 \cdot |I_{L(rms)}|^2$
 $Q_0 = X_0 \cdot |I_{L(rms)}|^2$

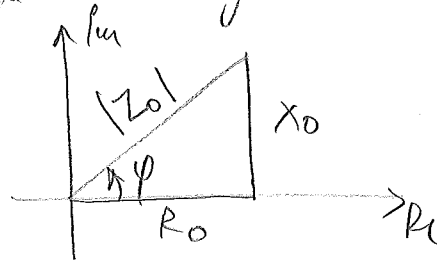

$P_0 = S_0 \times pf = 10^3 \times 0.8 = 8000 [W]$

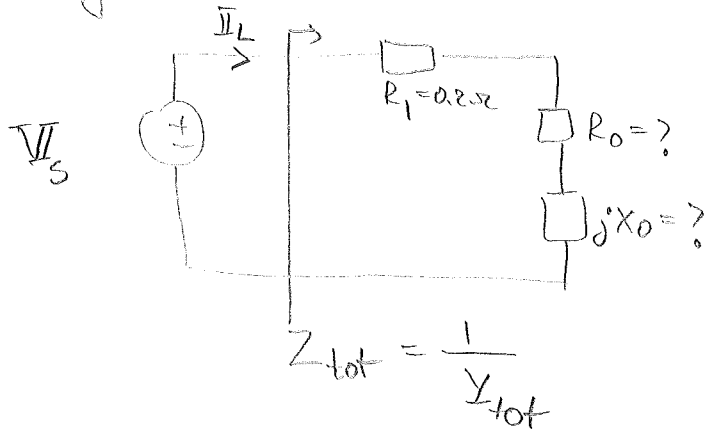- Our goal is to find Z_{tot} or Y_{tot} :



$P_{tot} = P_1 + P_0 = R_1 |I_{L(rms)}|^2 + P_0$
 $= 0.2 \times 40^2 + 8000 = 320 + 8000$
 $= 8320 [W]$

- Use relationship between power-triangle and impedance-triangle:

$$R_o = \frac{P_o}{|I_L(mA)|^2} = \frac{8000}{40^2} = 5.52$$

$$X_o = R_o \tan \phi = R_o \cdot \tan(\overset{\text{lagging}}{\cos^{-1} 0.8}) = 5 \cdot \tan(36.87^\circ) = 3.75 \Omega$$

$\cos^{-1} \text{pt}$ because $\text{pt} \triangleq \cos \phi$

$$\Rightarrow Z_o = 5 + j3.75 \Omega$$

- Hence, $Z_{tot} = (R_1 + R_o) + jX_o = 5.2 + j3.75 \Rightarrow \text{pt}_{old} = \cos(35.79^\circ) = 0.811$


$$\Rightarrow Y_{tot} = \frac{1}{Z_{tot}} = \frac{1}{5.2 + j3.75} = 0.126 - j0.091$$

↑ of source V_s !!!
not of Load.

- Now, we can find V_s which creates I_L thru Z_{tot} !

$$V_s = Z_{tot} \times I_L = Z_{tot} \times (|I_L(mA)| \angle 0^\circ)$$
$$= (5.2 + j3.75) \times 40 = 256.4 \angle 35.80^\circ$$

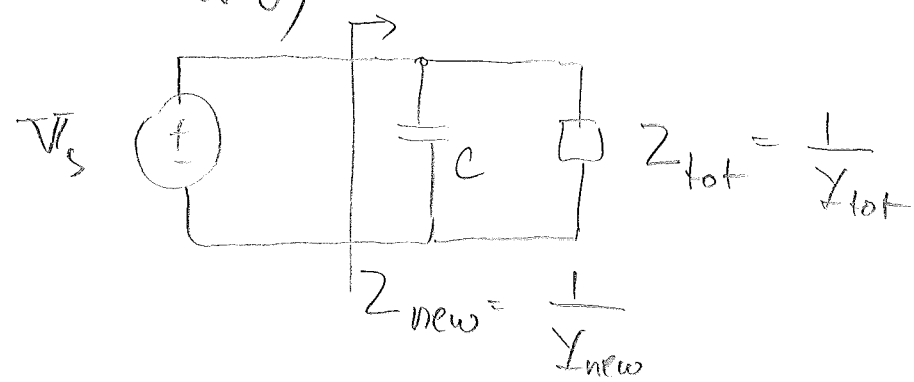- With C in place the source (recoll: whose pt now must become 0.9 lagging) sees:




$$Y_{new} = Y_{tot} + jB_p = (0.126 - j0.091) + j(2\pi f C)$$
$$= \underbrace{0.126}_{G_{new}} + j(\underbrace{120\pi C - 0.091}_{B_{new}})$$

60Hz

① → One way to do it:
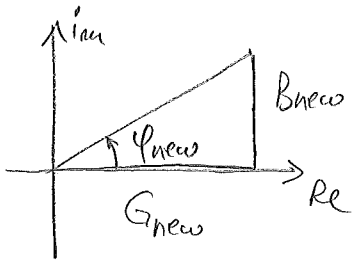
$$pf_{new} = \cos \varphi_{new} \Rightarrow \varphi_{new} = \cos^{-1} pf_{new} = \cos^{-1} 0.9 = 25.84^\circ$$



$$\tan \varphi_{new} = \frac{B_{new}}{G_{new}}$$

$$\tan 25.84^\circ = \frac{120\pi C - 0.091}{0.126} \Rightarrow \boxed{C = 79.48 \mu F}$$

② → Another way to do it:

use formula:

$$X_p = \frac{|\sqrt{I_s(rms)}|^2 / P_{tot}}{\tan(\cos^{-1} pf_{new}) - \tan(\cos^{-1} pf_{old})}$$

of the source!

$$X_p = \frac{256.4 / 8320}{\tan(\cos^{-1} 0.9) - \tan(\cos^{-1} 0.811)} = \frac{7.901}{-0.231} = -33.34$$

$$X_p = -\frac{1}{\omega C_p} \Rightarrow C_p = -\frac{1}{\omega X_p} = \frac{1}{2\pi f \times 33.34} = \frac{1}{120\pi \times 33.34} \approx 79.48 \mu F$$

//