

Chapter 15

Circuit analysis in the s-domain

1 Circuit element models


(a) Resistors

$v(t) = R \cdot i(t)$ take Laplace transform of both sides:


$$[\text{Volts} \times \text{sec}] \quad \boxed{V(s) = R \cdot I(s)} \quad (1)$$

$$\boxed{Z(s) = \frac{V(s)}{I(s)} = R}$$

[Amperes \times sec]

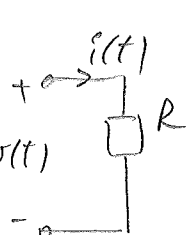

t-domain

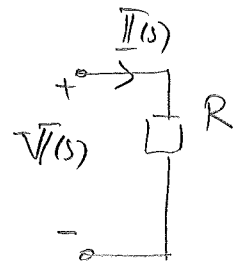

s-domain

(b) Inductors


$$v(t) = L \frac{di}{dt}$$

$$\boxed{V(s) = sL I(s) - Li(0^-)} \quad (2)$$


$$\boxed{Z(s) = sL}$$

initial condition is


the inductance current at time $t=0$!

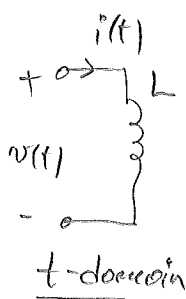

t-domain

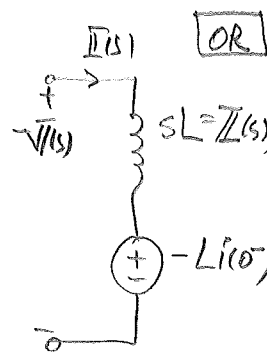




s-domain

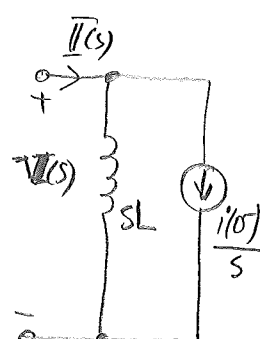

Note: if we had discussed first s-domain analysis without having introduced Laplace transform, we would have talked about "generalized impedance and admittance". \leftarrow These do not consider initial conditions. As a consequence, the unknown coefficients appearing in the transient component would have to be found on the basis of the initial conditions in the circuit. This could be a tedious and time-consuming process. In conclusion, using/studying directly Laplace transform is better!!!

(c) Capacitors

$$i(t) = C \frac{dv}{dt}$$

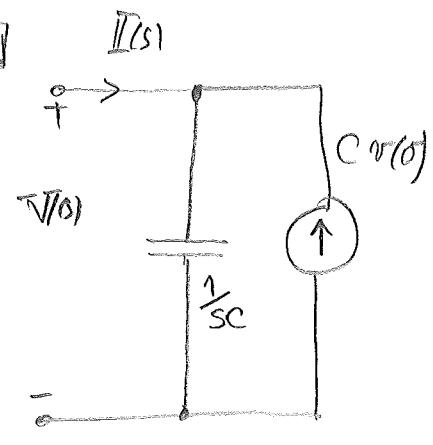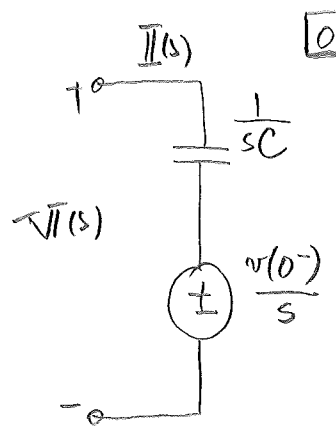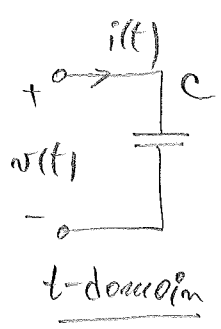

$$I(s) = sC V(s) - C v(0^-)$$



$$V(s) = \frac{1}{sC} \cdot I(s) + \frac{v(0^-)}{s} \quad (3)$$

$$Z(s) = \frac{1}{sC}$$

initial condition is the voltage across capacitance.

Example: Find voltage $v_o(t)$ given the initial current $i(0^-) = 1A$

$$v(t) = 3e^{-8t} \text{ [V]}$$

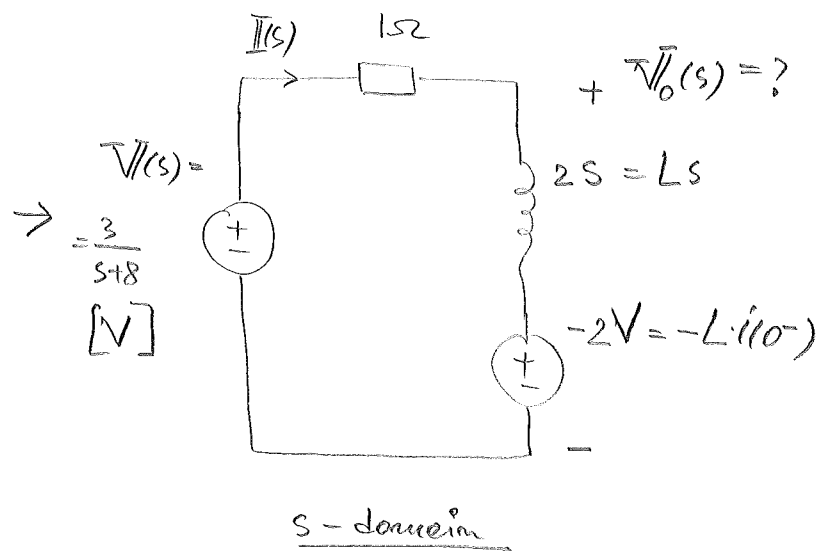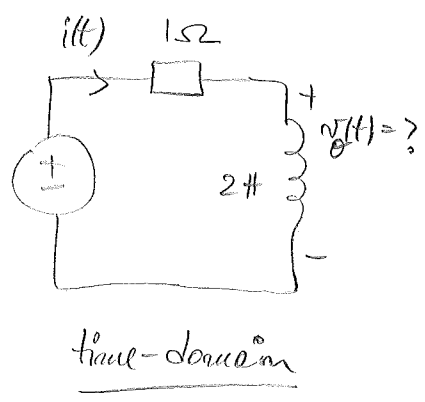

Solution: Transform whole thing to s-domain, find $V_o(s)$, then transform back to time-domain to find $v_o(t)$!

- KVL around loop:

$$V(s) = 1 \cdot I(s) + 2s \cdot I(s) + (-2)$$

$$\frac{3}{s+8} + 2 = (1+2s) \cdot I(s) \Rightarrow I(s) = \frac{\frac{3}{s+8} + 2}{1+2s} = \frac{s+9.5}{(s+8)(s+0.5)}$$

- Hence:

$$V_0(s) = 2s \cdot I(s) - 2 = \frac{2s(s+9.5)}{(s+8)(s+0.5)} - 2 = \frac{2s-8}{(s+8)(s+0.5)}$$

$$V_0(s) = \frac{A_1}{(s+8)} + \frac{A_2}{(s+0.5)}$$

$$A_1 = (s+8) \cdot V_0(s) \Big|_{s=-8} = \frac{2s-8}{s+0.5} \Big|_{s=-8} = 3.2$$

$$A_2 = (s+0.5) \cdot V_0(s) \Big|_{s=-0.5} = \frac{2s-8}{s+8} \Big|_{s=-0.5} = -1.2$$

$$\Rightarrow V_0(s) = \frac{3.2}{s+8} - \frac{1.2}{s+0.5}$$

- Finally:

$$v_0(t) = \mathcal{L}^{-1}\{V_0(s)\} = [3.2 \cdot e^{-8t} - 1.2 \cdot e^{-0.5t}] \cdot u(t)$$