

2. Nodal and mesh analysis in the s-domain

$$\text{KCL: } \sum_n I_{\text{in}}(s) = \sum_n I_{\text{out}}(s) \quad (1)$$

$$\text{KVL: } \sum_\ell V_{\text{rise}}(s) = \sum_\ell V_{\text{drop}}(s) \quad (2)$$

Circuit analysis via Laplace method involves steps: (formal statement)

- ① - Use t-domain form of circuit to find $i_L(0^-)$ thru each inductance, and $v_C(0^-)$ across each capacitor.
- ② - Redraw circuit in s-domain. Each voltage, current source replaced by its Laplace transform. Each element replaced by its s-domain equivalent.
- ③ - Analyze transformed circuit. The outcome is one or more algebraic equations relating the Laplace transform $Y(s)$ of the response to those of the applied sources!

- Once we know $Y(s)$ we find the time-domain:

$$y(t) = \mathcal{L}^{-1} \{ Y(s) \}$$

- Particular interest: a single applied source $X(s)$:

$$Y(s) = H(s) \cdot X(s) + Y_{\text{natural}}(s) \quad (3)$$

↑
network function


↑
function arising from
initial stored energies in
reactive elements.

Complete response:

$$y(t) = \mathcal{L}^{-1} \{ H(s) \cdot X(s) \} + \mathcal{L}^{-1} \{ Y_{\text{natural}}(s) \} \quad (4)$$

$\triangleq y_{\text{forced}}(t)$
 $\triangleq y_{\text{natural}}(t)$

Example 1: Find mesh currents $i_1(t)$, $i_2(t)$.
Zero initial conditions!

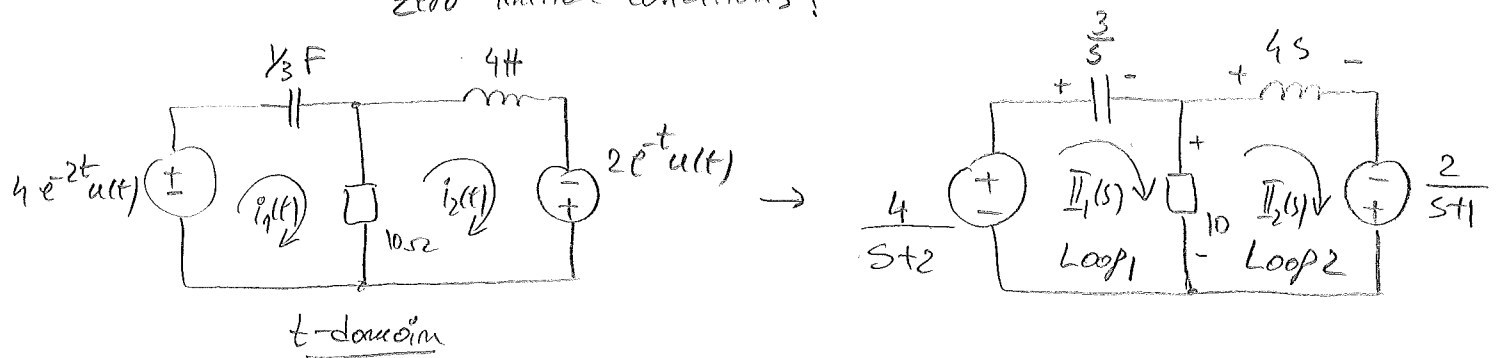

Loop 1: $\begin{cases} \frac{4}{s+2} = \frac{3}{s} \cdot I_1(s) + 10(I_1(s) - I_2(s)) \end{cases}$
 Loop 2: $\begin{cases} 10(I_1 - I_2) + \frac{2}{s+1} = 4s \cdot I_2 \end{cases}$

$\Rightarrow \begin{cases} (\frac{3}{s} + 10) I_1 - 10 I_2 = \frac{4}{s+2} \\ -10 I_1 + (4s + 10) I_2 = \frac{2}{s+1} \end{cases}$ 2 equations
2 unknowns. $AX=B$

where: $A = \begin{bmatrix} \frac{3}{s} + 10 & -10 \\ -10 & 4s + 10 \end{bmatrix}$ $B = \begin{bmatrix} \frac{4}{s+2} \\ \frac{2}{s+1} \end{bmatrix}$ $X = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$

- Solve to find:

$I_1 = \frac{2s(4s^2 + 19s + 20)}{20s^4 + 66s^3 + 73s^2 + 57s + 30} A$

$I_2 = \frac{30s^2 + 43s + 6}{(s+2)(20s^3 + 26s^2 + 21s + 15)} A$


- Take inverse Laplace transform:

$i_1(t) = -96.39 e^{-2t} - 344.8 e^{-t} + 841.2 e^{-0.15t} \cdot \cos(0.853t) + 1197.7 e^{-0.15t} \sin(0.853t)$ [mA]


$i_2(t) = -481.9 e^{-2t} - 241.4 e^{-t} + 723.3 e^{-0.15t} \cdot \cos(0.853t) + 472.8 e^{-0.15t} \sin(0.853t)$

Example 2: Find $v(t) = ?$

3

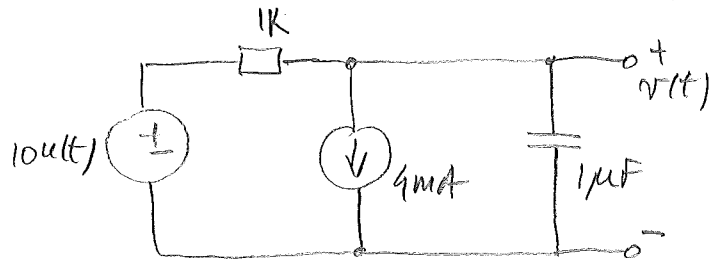

→
①

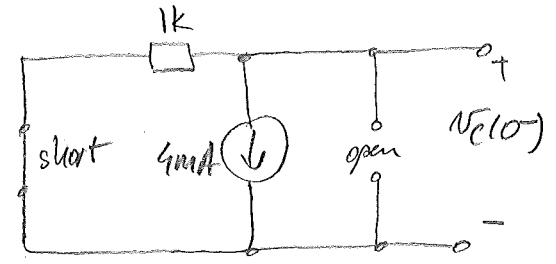


at time $t = 0^-$

$$v_C(0^-) = -1k \times 4mA = 4V$$

t-domain

②
↓ Convert to s-domain

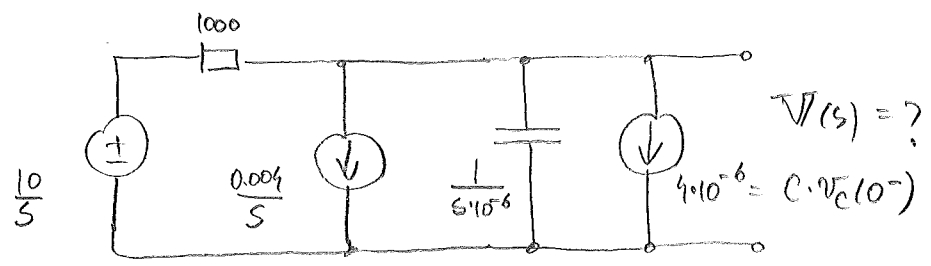

- Apply KCL:

$$\frac{10}{s} - \frac{V(s)}{100} = \frac{4 \cdot 10^{-3}}{s} + \frac{V(s)}{1/s \cdot 10^{-6}} + 4 \cdot 10^{-6}$$

$$\Rightarrow V(s) = \frac{6 \times 10^3 - 4s}{s(s + 10^3)} = \frac{6}{s} - \frac{10}{s + 10^3}$$

- Taking inverse Laplace:

$$v(t) = \mathcal{L}^{-1}\{V(s)\} = (6 - 10 \cdot e^{-10^3 t}) \cdot u(t)$$