
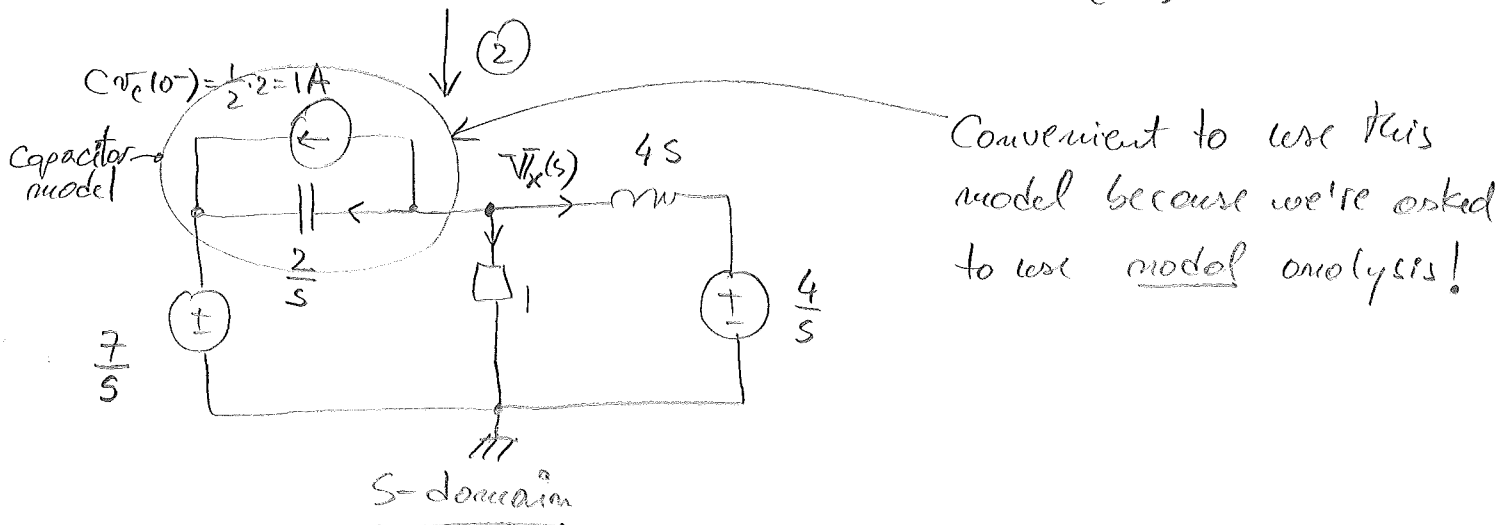


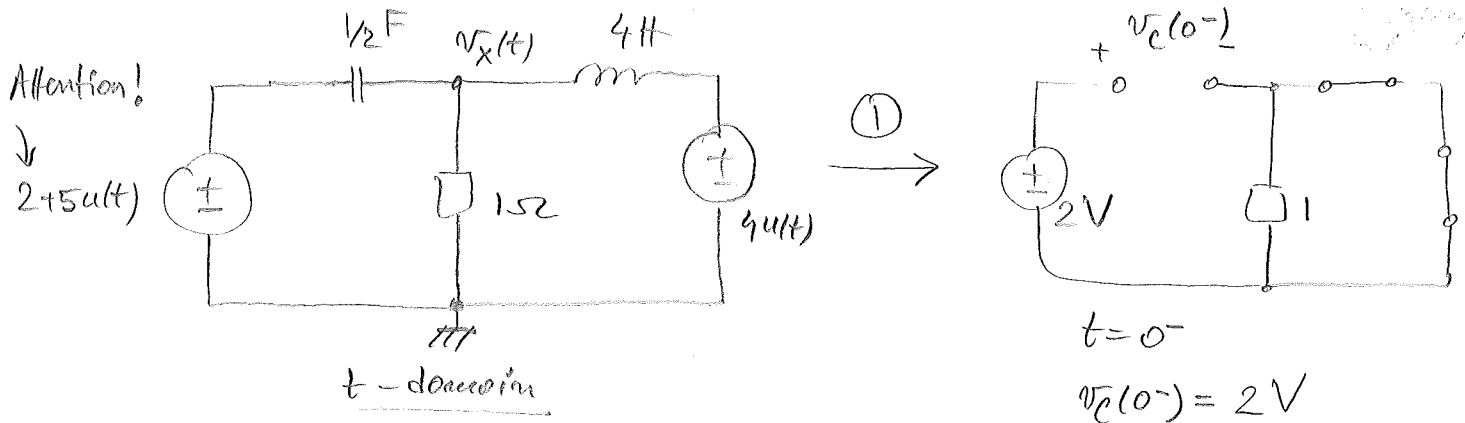Example 18 Find voltage $v_x(t)$. Use nodal analysis!



KCL for node $\bar{V}_x(s)$:

$$1 + \frac{\bar{V}_x - \frac{7}{s}}{\frac{2}{s}} + \frac{\bar{V}_x}{1} + \frac{\bar{V}_x - \frac{4}{s}}{4s} = 0$$

$$\overset{4s^2}{1} + \overset{2s^2}{s} \frac{\bar{V}_x - 7}{2} + \overset{4s^2}{\bar{V}_x} + \frac{s\bar{V}_x - 4}{4s^2} = 0$$

$$4s^2 + 2s^3 \bar{V}_x - 14s^2 + 4s^2 \bar{V}_x + s\bar{V}_x - 4 = 0$$

$$s(2s^2 + 4s + 1) \bar{V}_x = 10s^2 + 4$$

$$\bar{V}_x(s) = \frac{10s^2 + 4}{s(2s^2 + 4s + 1)} = \frac{5s^2 + 2}{s(s + 1 + \frac{\sqrt{2}}{2})(s + 1 - \frac{\sqrt{2}}{2})}$$

- See lecture notes of week #5, Mon:

(2)

$$\text{Poles: } \left\{ \begin{array}{l} P_1 = 0 \\ P_2 = -1 - \frac{\sqrt{2}}{2} \\ P_3 = -1 + \frac{\sqrt{2}}{2} \end{array} \right. \text{ all real and simple!}$$

Hence:

$$\mathcal{V}_x(s) = \frac{A_1}{s} + \frac{A_2}{s+1+\frac{\sqrt{2}}{2}} + \frac{A_3}{s+1-\frac{\sqrt{2}}{2}}$$

$$A_1 = s \cdot \mathcal{V}_x(s) \Big|_{s=0} = \frac{10s^2+4}{2s^2+4s+1} \Big|_{s=0} = 4$$

$$A_2 = (s+1+\frac{\sqrt{2}}{2}) \cdot \mathcal{V}_x(s) \Big|_{s=-1-\frac{\sqrt{2}}{2}} = \frac{5s^2+2}{s(s+1-\frac{\sqrt{2}}{2})} \Big|_{s=-1-\frac{\sqrt{2}}{2}} = 6.84$$

$$A_3 = (s+1-\frac{\sqrt{2}}{2}) \cdot \mathcal{V}_x(s) \Big|_{s=-1+\frac{\sqrt{2}}{2}} = \frac{5s^2+2}{s(s+1+\frac{\sqrt{2}}{2})} \Big|_{s=-1+\frac{\sqrt{2}}{2}} = -5.84$$


$$\mathcal{V}_x(s) = \frac{4}{s} + \frac{6.84}{s+1+\frac{\sqrt{2}}{2}} - \frac{5.84}{s+1-\frac{\sqrt{2}}{2}}$$

$\underbrace{\hspace{1.5cm}}_{1.707} \qquad \underbrace{\hspace{1.5cm}}_{0.293}$


- Finally:

$$\boxed{v_x(t) = \mathcal{L}^{-1} \{ \mathcal{V}_x(s) \} = [4 + 6.84 \cdot e^{-1.707t} - 5.84 \cdot e^{-0.293t}] \cdot u(t)}$$

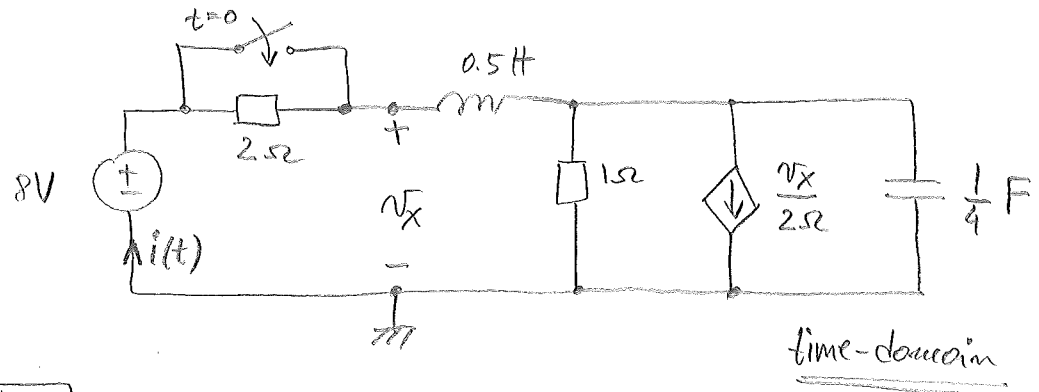
Example 2: Assume switch has been open for a long time. Find $i(t) = ?$ $t > 0$.



$t < 0$

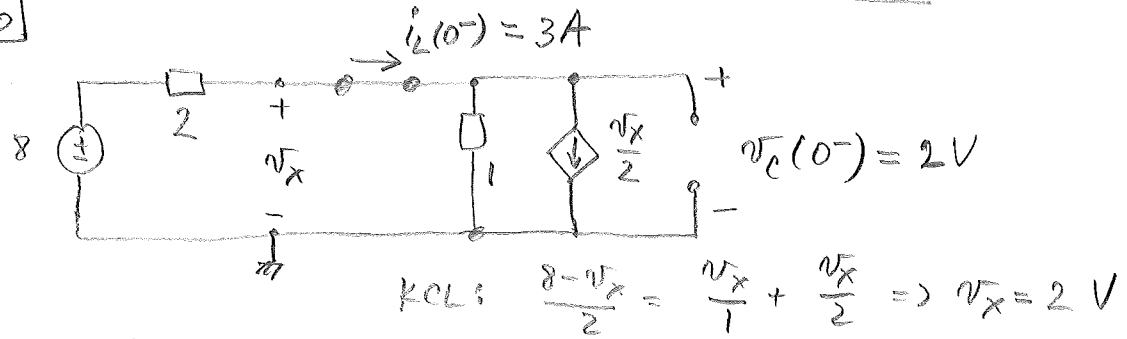

$t \geq 0$

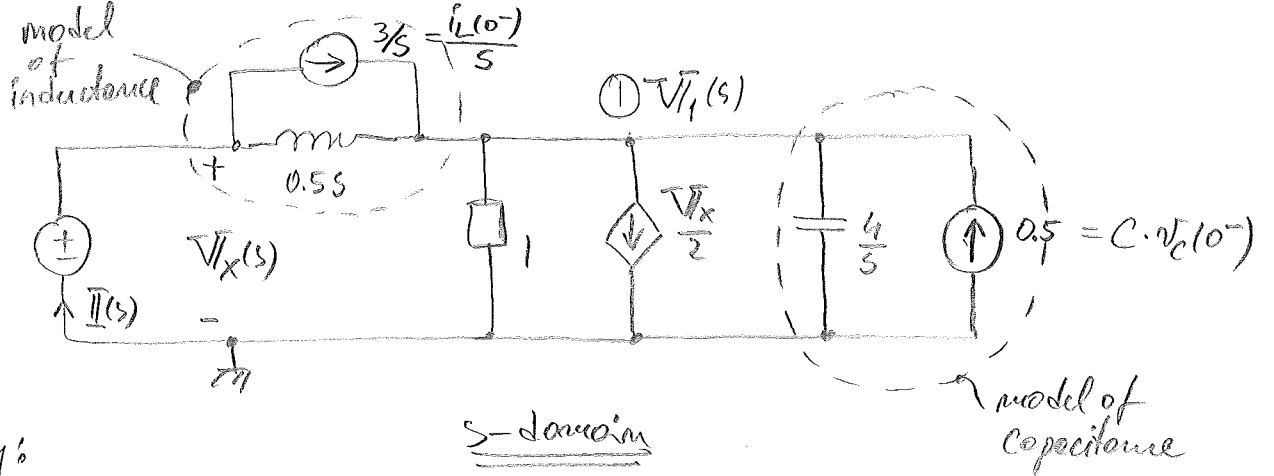

- Clearly:

$$v_x = \frac{8}{s}$$

- Use KCL: $\frac{3}{s} + \frac{\frac{8}{s} - v_1}{0.5s} + 0.5 = \frac{v_1}{1} + \frac{8/s}{2} + \frac{v_1}{4/s}$ } 2 eq. 2 unknowns.

- Ohm's law: $i = \frac{8/s - v_1}{0.5s} + \frac{3}{s}$

- Get v_1 and substitute to get:

$$i(s) = \frac{3s^2 + 24s + 96}{s(s^2 + 4s + 8)} = \frac{12}{s} + \frac{1.5\sqrt{10} \angle 161.56^\circ}{s + 2 - j2} + \frac{1.5\sqrt{10} \angle -161.56^\circ}{s + 2 + j2}$$

- See notes of week #5, Wednesday:

$$i(t) = \mathcal{L}^{-1}\{i(s)\} = 3 \cdot [4 + \sqrt{10} e^{-2t} \cos(2t + 161.56^\circ)] A$$