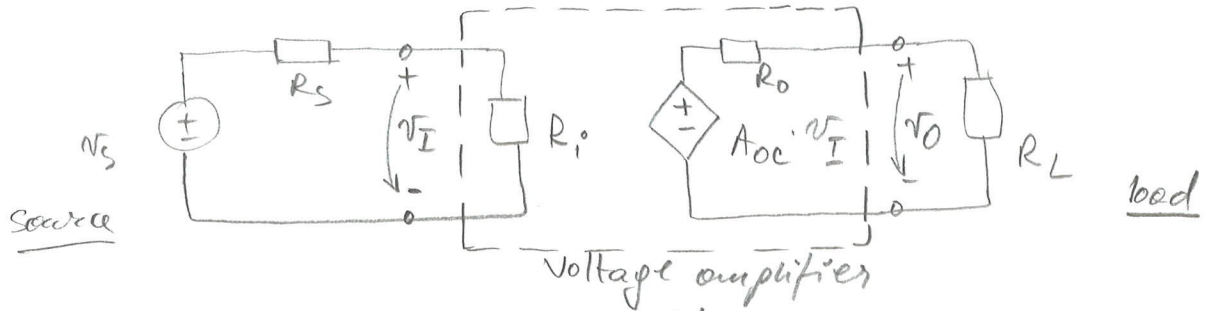


① - Voltage amplifier : amplification loading



A_{oc} def. voltage gain factor open-circuit unloaded.

$$A_{v_s} = \frac{v_o}{v_s} = \frac{R_i}{R_s + R_i} \cdot A_{oc} \cdot \frac{R_L}{R_o + R_L}$$

A_{v_s} def. source to load gain or amplification.

Attenuations referred to as loading


because of which $|A_{v_s}| \leq |A_{oc}|$ which is undesirable!

Minimize Loading by $R_s \downarrow \propto R_i \uparrow$ and $R_L \uparrow \propto R_o \downarrow$

- The Operational Amplifier (Op Amp) (OA)


A voltage amplifier with extremely high gain/amplification.

Symbol

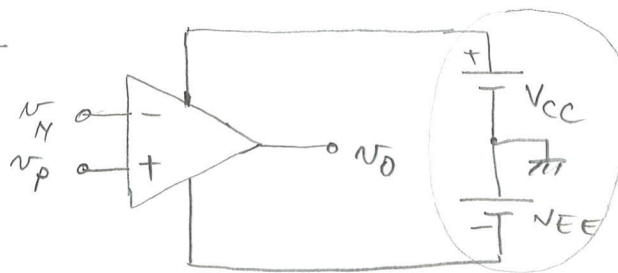

typically not drawn but present all the time!

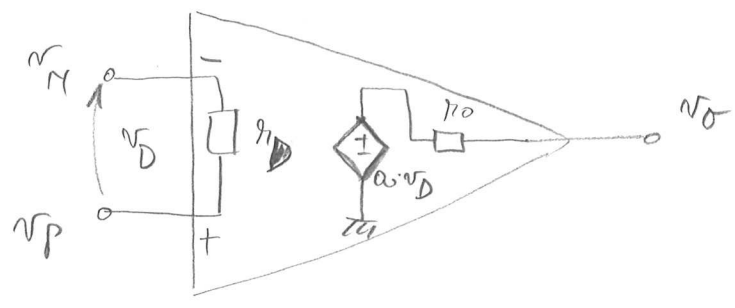"-" inverting input
" +" noninverting input.



$v_D = v_p - v_n$ $\stackrel{\text{def}}{=} \text{differential input voltage.}$

$$v_o = a v_D = a (v_p - v_n) \quad (\Rightarrow) \quad v_D = \frac{v_o}{a}$$


- $a \stackrel{\text{def}}{=} \text{unloaded gain, because when the loading is absent we have}$
- $r_O \triangleq \text{output resistance}$
- $r_D \triangleq \text{differential input resistance.}$

Example: $\mu\text{A}741$

$$\begin{cases} r_D = 2 \text{ M}\Omega \\ r_O = 75 \Omega \\ a = 200.000 \frac{\text{V}}{\text{V}} = 200 \frac{\text{V}}{\text{mV}} \end{cases}$$

② Ideal Op Amp

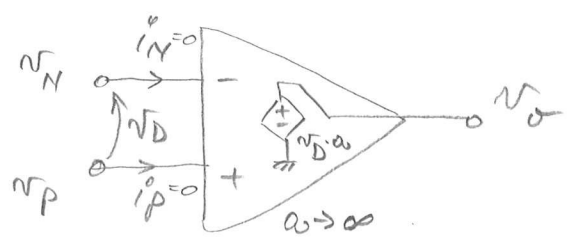Desired: $\begin{cases} r_D \rightarrow \infty \\ r_O \rightarrow 0 \\ a \rightarrow \infty \end{cases}$



Because we want to minimize loading! and have a gain as big as possible!



Desired also: $\begin{cases} i_n = 0 \\ i_p = 0 \end{cases}$

Very commonly use in a "first phase" analysis of a given circuit that uses Op Amp's!

Basic Op Amp configurations

(3)

③ The Noninverting Amplifier

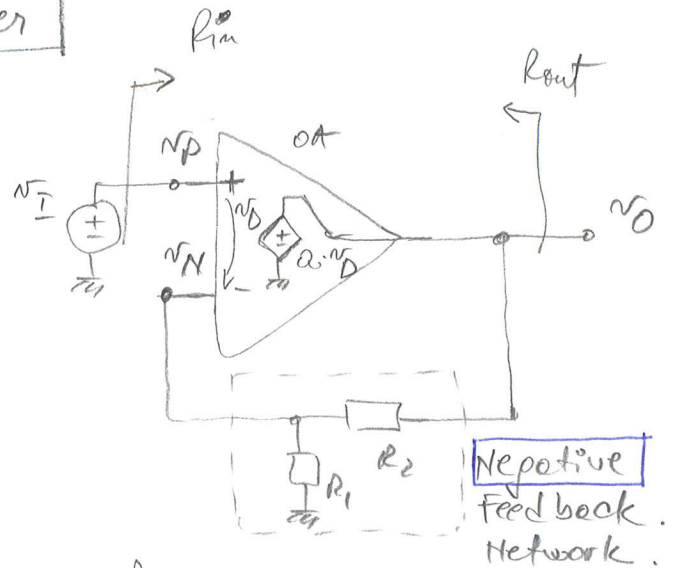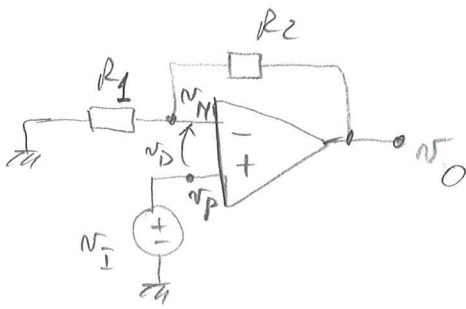

$$\left. \begin{aligned} v_D &= v_P - v_N \\ v_P &= v_I \\ v_N &= \frac{R_1}{R_1 + R_2} \cdot v_O \end{aligned} \right\} \Rightarrow v_D = v_I - \frac{R_1}{R_1 + R_2} v_O$$

$$\left. \begin{aligned} v_D \cdot a &= v_O = a(v_P - v_N) \end{aligned} \right\} \Rightarrow$$

$$\Rightarrow v_O = a \left[v_I - \frac{R_1}{R_1 + R_2} v_O \right] \Leftrightarrow v_O \left(1 + a \frac{R_1}{R_1 + R_2} \right) = a v_I$$

$$\Rightarrow A_v = \frac{v_O}{v_I} = \frac{a}{1 + a \frac{R_1}{R_1 + R_2}} = \frac{R_1 + R_2}{R_1} \cdot \frac{a}{a + \frac{R_1 + R_2}{R_1}}$$

(pull out)

$$A_v = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1} \right) \cdot \frac{1}{1 + \left(1 + \frac{R_2}{R_1} \right) \cdot \frac{1}{a}}$$

$\triangleq A_{ideal}$

It's an amplifier!
Noninverting.

because $A_{of} \xrightarrow{a \rightarrow \infty} A_{ideal} = 1 + \frac{R_2}{R_1}$

Terminology: $a \triangleq$ also known as the open-loop gain
 $A_v \triangleq$ closed-loop voltage gain.


A_{ideal} becomes independent of a . Depends only on external R_1, R_2
 \Rightarrow Controllability, Stability with temp. variations.

The price paid: gain a (eg. 200,000) is now $1 + \frac{R_2}{R_1}$ (eg. 10) !


Input and Output resistances:

$$\begin{cases} R_i = \infty \\ R_o = 0 \end{cases}$$

- Voltage follower

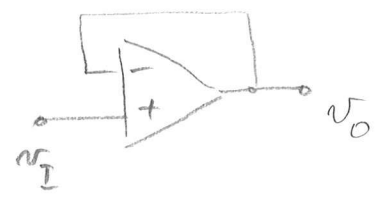

④ The inverting amplifier

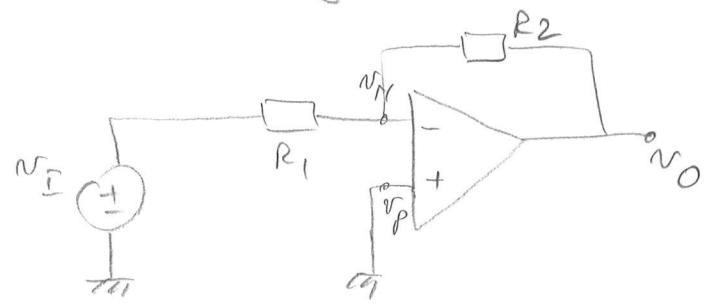

Homework: Derive $A_v = \frac{v_O}{v_I}$ similarly as we did for the non-inverting configuration.

$$A_v = \frac{v_O}{v_I} = \left(- \frac{R_2}{R_1} \right) \cdot \frac{1}{1 + \left(1 + \frac{R_2}{R_1} \right) a}$$