
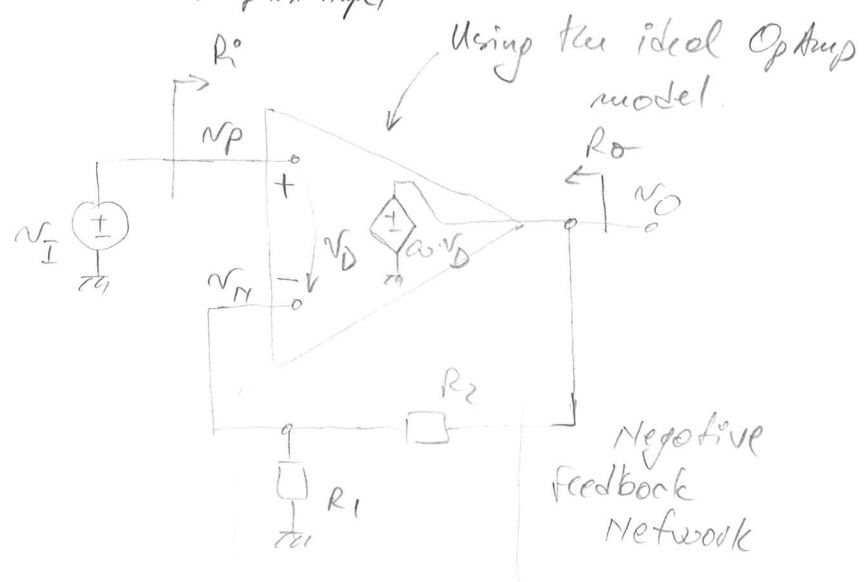


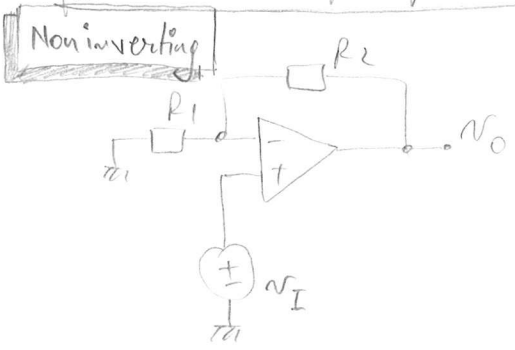1.3. Basic Op Amp Configurations (summary of last half)



$$A = \frac{v_O}{v_I} = \underbrace{\left(1 + \frac{R_2}{R_1}\right)}_{\triangleq A_{ideal}} \left(\frac{1}{1 + \underbrace{\left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1}{a}}_{\triangleq \frac{1}{\beta}}}} \right) \quad \text{closed loop gain.}$$


$$A = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1}{1 + \frac{1}{a\beta}} = \boxed{A_{ideal} \cdot \frac{1}{1 + \frac{1}{a\beta}} = A}$$

$$A_{ideal} = \lim_{a \rightarrow \infty} A = 1 + \frac{R_2}{R_1}$$

$$\begin{aligned} R_i &\approx \infty \\ R_o &\approx 0 \end{aligned}$$



Voltage Follower
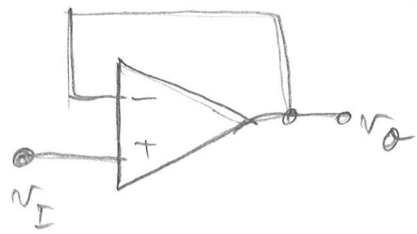
$$\begin{aligned} R_1 &\rightarrow \infty \\ R_2 &\rightarrow 0 \end{aligned}$$



It's a resistance transformer.

$$A = 1$$

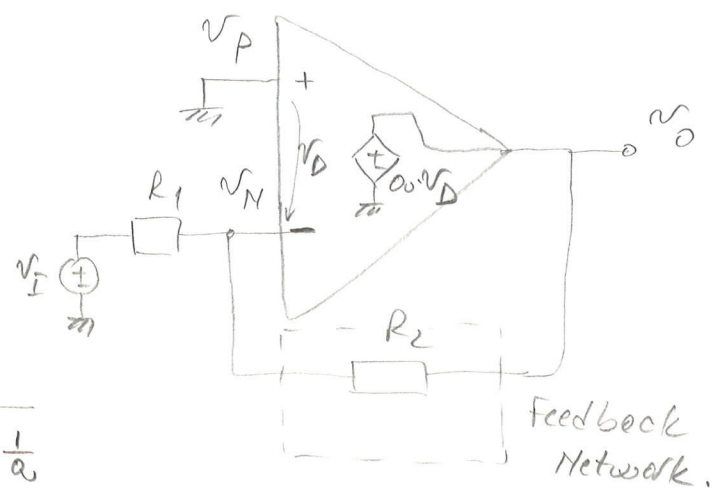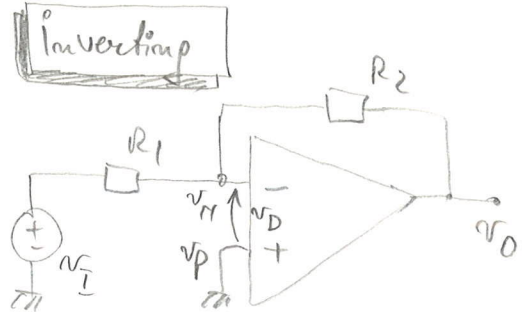

$$A = \frac{v_O}{v_I} = \left(-\frac{R_2}{R_1} \right) \cdot \frac{1}{1 + \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1}{a}}$$

lim_{ω→∞} A = A_{ideal} = - $\frac{R_2}{R_1}$

Phase φ(ω) = -π = -180°

In the limit, because $v_D = \frac{v_O}{a} \rightarrow 0$, v_N would follow v_P due to the Op Amp action via the negative feedback. Hence v_N appears to be a **virtual ground**.

This is true only because of the negative feedback.

So, we can approximate $R_i \cong R_1$
 $R_o \cong 0$

1.4 Ideal Op Amp Circuit Analysis

When Op Amp is operated with negative feedback:

$$v_D = \frac{v_O}{a} \rightarrow 0 \Rightarrow \lim_{a \rightarrow \infty} v_N = v_P : \text{"} v_N \text{ approaches } v_P \text{"}$$


- Concept:** - This property is called **input voltage constraint**. It makes the input terminals appear as if they were shorted together!
- Fact:** - Because $R_D \rightarrow \infty$ and no current is drawn, currents are zero and this property is called **input current constraint**. Inputs appear to be an open circuit!

⇒ designation of **virtual short** concept!

important: when operated with **negative feedback**, the OpAmp⁻³⁻ will provide the necessary current so that to drive v_N to 0. In other words to make v_N approach v_P but without drawing any current at the OpAmp inputs!

The virtual short concept is used to quickly analyze circuits.

Example: non-inverting:

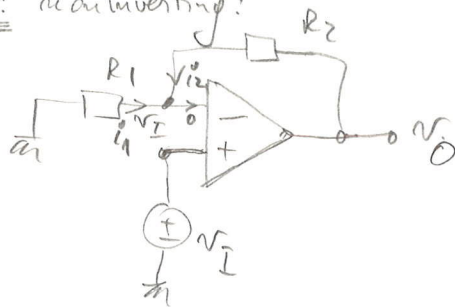

$$v_N = v_I \text{ due to virtual short}$$

$$i_1 = -i_2$$

$$i_1 = -\frac{v_I}{R_1}, \quad i_2 = \frac{v_O - v_I}{R_2} \quad \Rightarrow$$

$$\Rightarrow \frac{v_I}{R_1} = \frac{v_O - v_I}{R_2} \quad (\Rightarrow v_I (R_2 + R_1) = R_1 v_O \Rightarrow$$

$$\Rightarrow \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1} = A_{\text{ideal}}$$



important: Virtual-short-concept valid only for negative feedback, when v_N is tracking v_P !!!


Using the virtual short concept, one can easily analyze:

- summing amplifier
 - difference amplifier
 - Differentiator
 - integrator.
- : signal processing applications

because they are all negative feedback OpAmp configurations.

- Negative-resistance converter: impedance transformation.

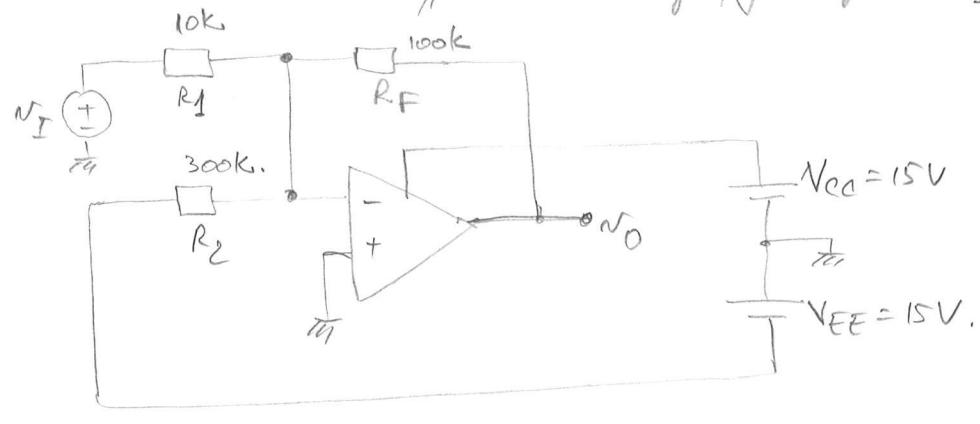Example: The use of summing amplifier to offset and amplify input V_I .




Offsetting amplifier

$$V_O = -\left(\frac{R_F}{R_1}\right)V_I - \frac{R_F}{R_2} \cdot (-V_{EE})$$

$$= -\frac{100k}{10k} V_I - \frac{100k}{300k} (-15V) = -10 \cdot V_I + 5V = V_O$$

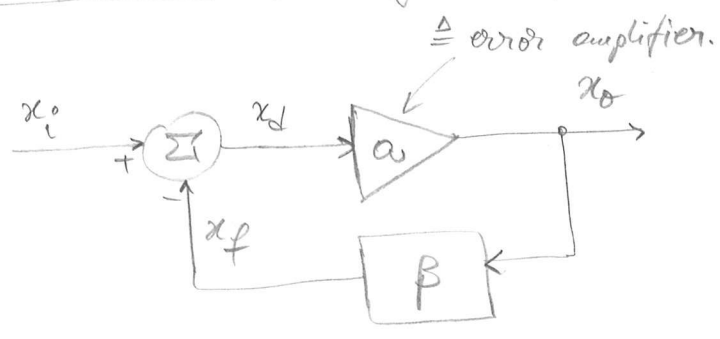1.5. Negative feedback

Basic structure of a negative-feedback circuit.



$a \triangleq$ open loop gain
 $\beta \triangleq$ feedback factor.

$$\left. \begin{aligned} x_o &= a \cdot x_d = a(x_i - x_f) \\ x_f &= \beta x_o \end{aligned} \right\} \Rightarrow x_o = a x_i - a \beta x_o$$

$$\Rightarrow x_o(1 + a\beta) = a x_i$$

$$\Rightarrow \boxed{\frac{x_o}{x_i} = \frac{a}{1 + a\beta}} = A \triangleq \text{Closed Loop Gain}$$

$$A = \frac{a}{1+a\beta} = \frac{1}{\beta} \cdot \frac{a\beta}{1+a\beta} = \frac{1}{\beta} \cdot \frac{T}{1+T}$$

$$T = a\beta \triangleq \text{loop gain.}$$

Letting $T \rightarrow \infty$ leads to the ideal situation:

$$\lim_{T \rightarrow \infty} A = A_{\text{ideal}} = \frac{1}{\beta}. \quad A \text{ becomes independent of } a.$$

Hence:

$$A = A_{\text{ideal}} \cdot \frac{T}{1+T} = A_{\text{ideal}} \cdot \frac{1}{1 + \frac{1}{T}}$$

Definition: Error function $\triangleq \frac{1}{1 + \frac{1}{T}} = 1 - \frac{1}{1+T} = 1 - \epsilon$

$$\epsilon = \frac{1}{1+T} \triangleq \text{fractional deviation.}$$

$$\Rightarrow A = A_{\text{ideal}} \cdot (1 - \epsilon)$$

$T \uparrow \Rightarrow \epsilon \downarrow$ and error function $\rightarrow 1$ while $A \rightarrow A_{\text{ideal}}$.

Definition: Gain error (%) = $100 \cdot \frac{A - A_{\text{ideal}}}{A_{\text{ideal}}} \approx -\frac{100}{T}$

Effect of negative feedback on signals x_d, x_f :

$$x_d = \frac{x_o}{a} = \frac{A \cdot x_i}{a} = \frac{\cancel{\infty}}{1+a\beta} \cdot \frac{1}{\cancel{\infty}} x_i = \frac{1}{1+T} \cdot x_i$$

$$x_f = \beta x_o = \beta A x_i = \frac{\beta a}{1+a\beta} x_i = \frac{T}{1+T} x_i = \frac{1}{1 + \frac{1}{T}} \cdot x_i$$

$$\Rightarrow \lim_{T \rightarrow \infty} x_d = 0$$

$$\lim_{T \rightarrow \infty} x_f = x_i$$

Negative feedback makes gain in closed loop

$A = \frac{a}{1+T}$ be $1+T$ times smaller.

Benefits of negative feedback:

a) - Gain desensitivity

$$\frac{dA}{A} = \frac{1}{1+T} \frac{da}{a}$$

The effect of a given percentage change in a upon A is reduced $(1+T)$ times!

$(1+T) \triangleq$ desensitivity factor.

b) - Nonlinear distortion reduction. (Linearization)

The transfer curve $v_O(v_I)$ is limited.

Applying negative feedback around an OpAmp - which may have a nonlinear transfer curve - but with a large T (which will make T large) - makes A stay linear even though a is not. \triangleq linearizing effect.

c) Some noise (depending where it occurs) is attenuated.

d) Input / Output resistances.