
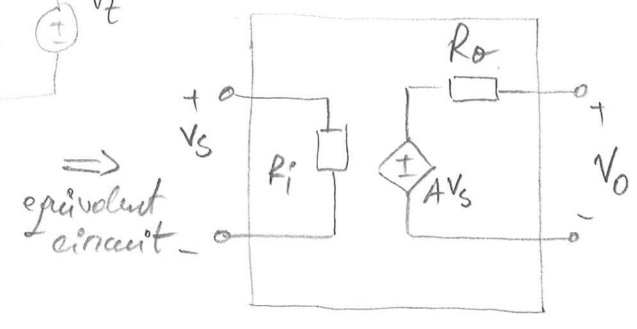


General detailed analysis of in/out resistances

1 Input/output resistances in closed-loop (negative-feedback) amplifiers → General case.

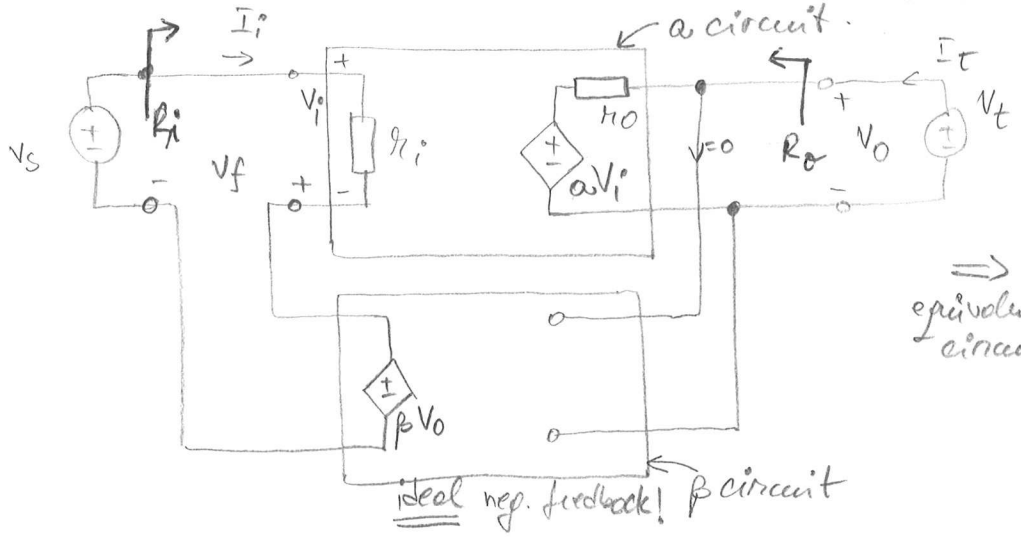Series-in, shunt-out feedback amplifier (compare voltage \square , sample voltage \square)



$$A = \frac{V_o}{V_s} = \frac{a}{1 + a\beta}$$

a, β have reciprocal units!

INPUT

$$R_i = \frac{V_s}{I_i} = \frac{V_s}{\frac{V_s}{r_i} + \frac{V_i + \beta a V_i}{r_i}}$$

$$(1) \quad R_i = r_i (1 + a\beta)$$

Because the feedback voltage V_f subtract from V_s , the voltage that appears across r_i becomes small \Rightarrow current I_i is small, which makes for R_i to "appear" large!

OUTPUT

$$I_t = \frac{V_t - aV_i}{r_o} \Rightarrow R_o = \frac{V_t}{I_t} = \frac{r_o}{1 + \beta a} = R_o \quad (2)$$

$$V_i = -V_f = -\beta V_t$$

$V_s = 0$

Note: (1) and (2) can be generalized to impedances: (1') $Z_i(jf) = z_i(jf) [1 + a(jf) \cdot \beta(jf)]$

$$(2') \quad Z_o(jf) = \frac{z_o(jf)}{1 + a(jf) \cdot \beta(jf)}$$



crucial observation :- when the negative feedback network is not ideal, it will load the open-loop amplifier lot of input and output!

- These loadings can be included into the base amplifier by incorporating the parameters with which we study the feedback network (example "h" parameters for series-in, shunt-out) into r_i and r_o . What's left from the feedback network is ideal!


very important!

→ Loading can be found by "looking" into feedback network with the other end shorted (or left open (for shunt (or series))

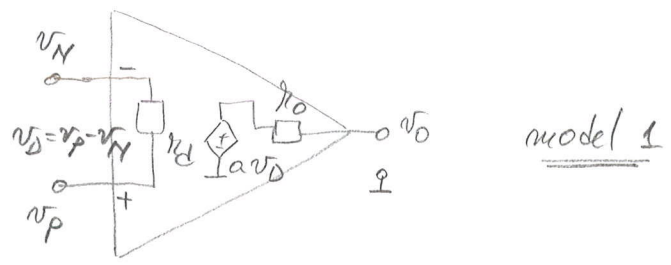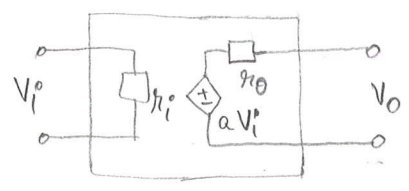
2 The particular case of the OpAmp as the base-amplifier (or the error amplifier)



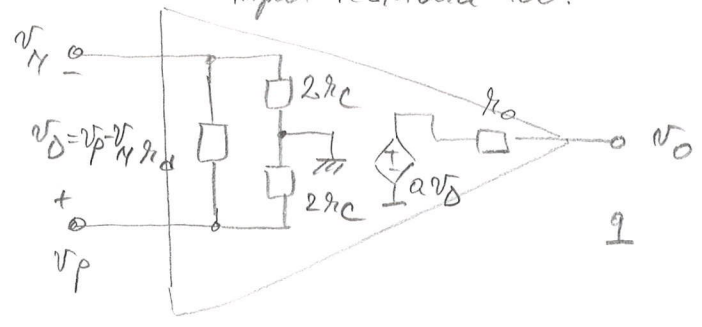or include also the common-mode input resistance too:



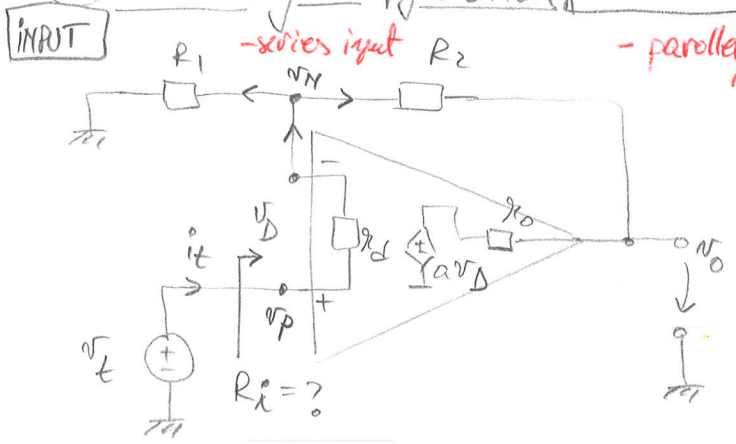2a Non-inverting configuration Method 1 "Brute-force" v_t/i_t



Because series at the input is the neg. feedback topology we know and expect:

$$R_i = r_i (1 + T)$$

where $r_i \approx r_d$

Verification: KCL at node v_N :

$$\frac{v_P - v_N}{r_d} = \frac{v_N}{R_1} + \frac{v_N - a v_D}{r_o + R_2}$$

$$\frac{v_t - v_N}{r_d} - \frac{v_N}{R_1} - \frac{v_N - a(r_d \cdot i_t)}{r_o + R_2} = 0 ; \quad v_N = v_t - r_d \cdot i_t$$

$$\Rightarrow v_t \left(-\frac{1}{R_1} - \frac{1}{r_o + R_2} \right) + i_t + \frac{r_d}{R_1} i_t + \frac{r_d}{r_o + R_2} i_t + \frac{a r_d}{r_o + R_2} i_t = 0$$

$$v_t \left(\underbrace{\frac{1}{R_1} + \frac{1}{r_o + R_2}}_{\triangleq \frac{1}{R_p}} \right) = i_t \left[1 + r_d \left(\underbrace{\frac{1}{R_1} + \frac{1}{r_o + R_2}}_{\triangleq \frac{1}{R_p}} + \frac{a}{r_o + R_2} \right) \right]$$

$$\frac{v_t}{i_t} = R_i = R_p + r_d R_p \left(\frac{1}{R_p} + \frac{a}{r_o + R_2} \right)$$

$$= \cancel{R_p \parallel (r_o + R_2)} + r_d \left(1 + \frac{a \cdot \frac{R_1 \cdot (r_o + R_2)}{R_1 + r_o + R_2}}{r_o + R_2} \right)$$


$\ll r_d$

$$\approx r_d \left(1 + \frac{a}{1 + \frac{r_o + R_2}{R_1}} \right) \approx r_d \left(1 + \frac{a}{1 + \frac{R_2}{R_1}} \right) = r_d (1 + a\beta)$$

$= \frac{1}{\beta}$

$R_i = r_d (1 + T)$ exactly what we expected!

OUTPUT

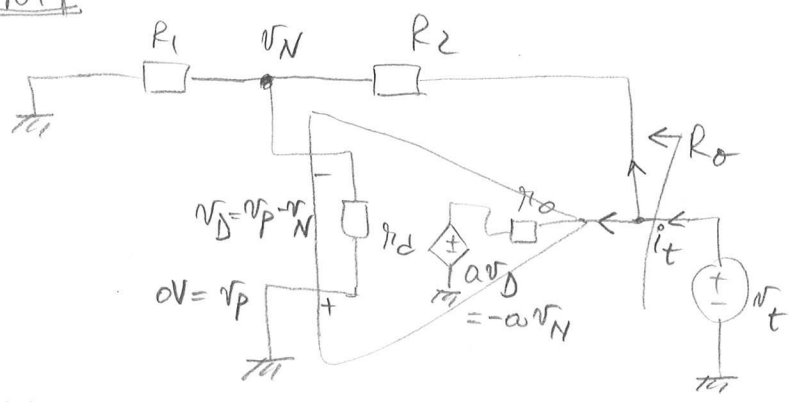

Because the neg. feedback is sum of output, we expect that:

$$R_o = \frac{r_o}{1 + T}$$

where $r_o \approx r_o$

Verification:

$$v_N = \frac{R_1 \parallel r_d}{R_1 \parallel r_d + R_2} \cdot v_t \quad ; \quad \text{Let } c \triangleq \frac{R_1 \parallel r_d}{R_1 \parallel r_d + R_2}$$

KCL at output node:
$$i_t = \frac{v_t - (-a v_N)}{r_o} + \frac{v_t - v_N}{R_2}$$

$$\Rightarrow i_t = \left(\frac{1 + ac}{r_o} + \frac{1 - c}{R_2} \right) v_t = \frac{(1 + ac) R_2 + (1 - c) r_o}{r_o R_2} v_t$$


$$\Rightarrow \frac{v_t}{i_t} = R_o = \frac{r_o R_2}{(1 + ac) R_2 + (1 - c) r_o} = \frac{r_o}{1 + ac + (1 - c) \frac{r_o}{R_2}} = \dots =$$

$$= \frac{r_o}{1 + (a + \frac{r_o}{R_1} + \frac{r_o}{r_d}) / (1 + \frac{R_2}{R_1} + \frac{R_2}{r_d})} \approx \frac{r_o}{1 + \frac{a}{1 + \frac{R_2}{R_1}}} = \frac{r_o}{1 + a\beta}$$

$1 + \frac{R_2}{R_1} = \frac{1}{\beta}$

$R_o = \frac{r_o}{1 + T}$ what we expected!

⑥ inverting configuration

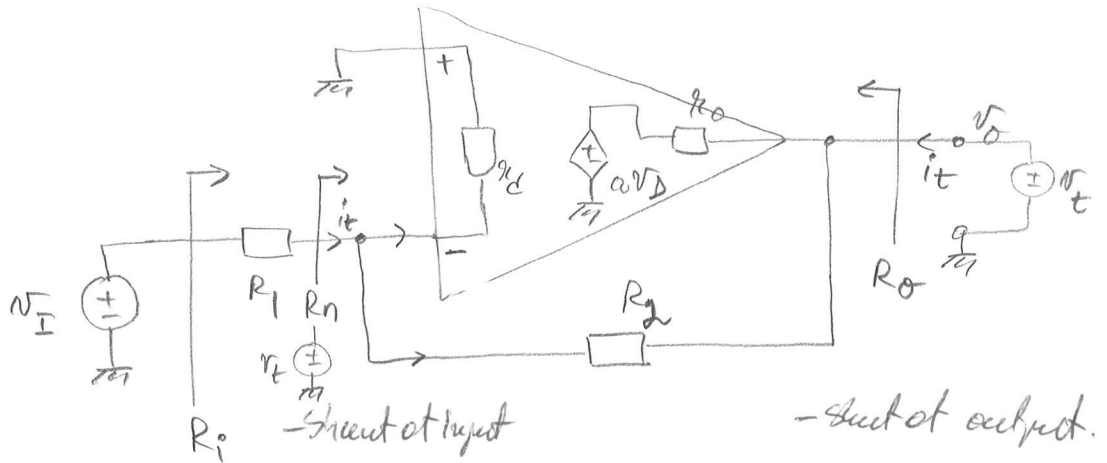

Because of neg. feedback, we expect:

$$R_i = R_1 + R_n \quad \text{and:} \quad \text{where } R_n = \frac{r_i}{1+A} \approx r_i \beta_g !!!$$

$$R_o = \frac{r_o}{1+A} \quad \text{where } r_o = r_o$$

INPUT

$$R_n = \frac{v_t}{i_t} = \frac{R_2 + r_o}{1+A + \frac{R_2 + r_o}{r_o}} \approx \frac{R_2}{1+A}$$



$$R_i = R_1 + R_n = R_1 + \frac{R_2}{1+A} \approx R_1$$

OUTPUT

The same derivation as in the case of the non-inverting config:

$$R_o \approx \frac{r_o}{1+A} \quad \checkmark$$

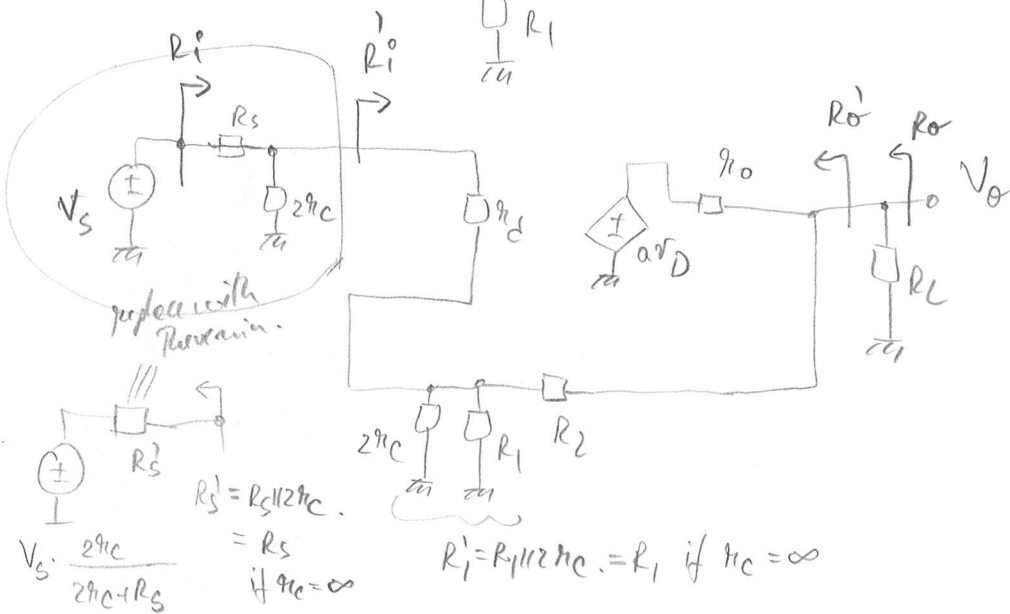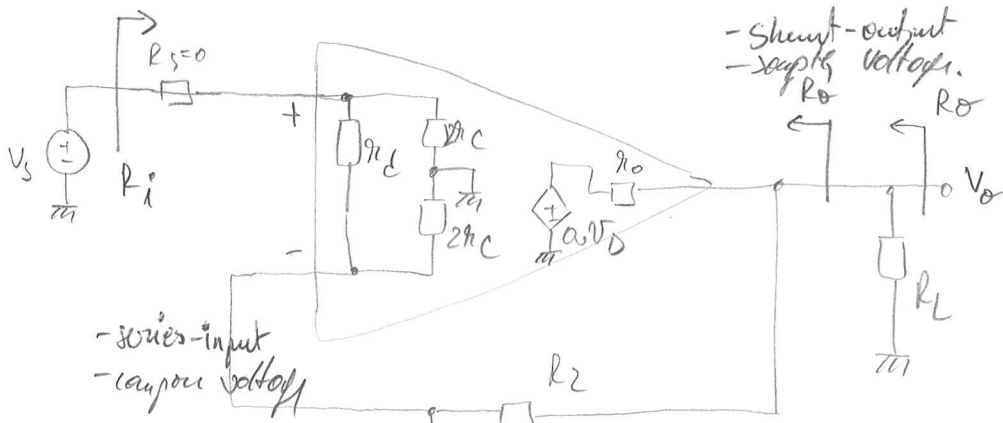
(a) Non-inverting configuration "loaded" → analysis as negative feedback amplifier. Method 2



input resistance is $R_i' = r_{i1}(1 + a v_D)$ with r_{i1} being the input into circuit as, which has loading due to neg. feedback network included!

$R_i = (2r_c) \parallel R_i'$, where:

circuit as:

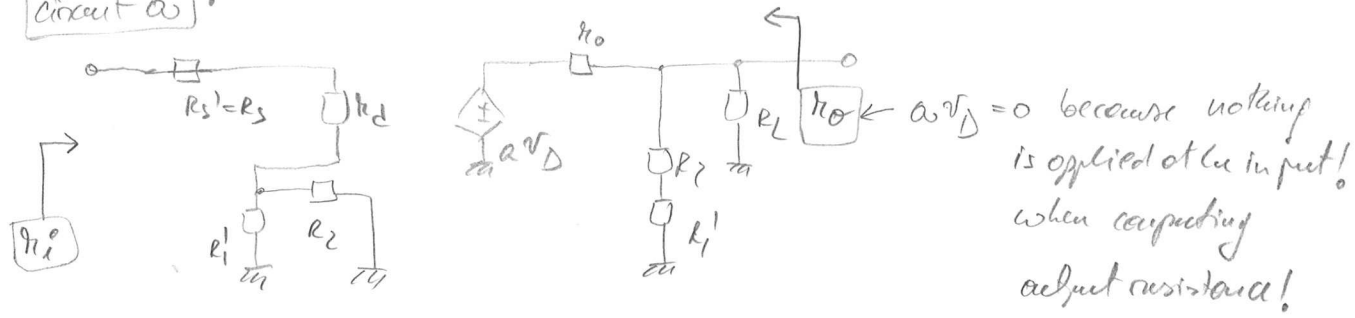

- $r_{i1} = R_s' + r_{i1} + R_1 \parallel R_2 \approx r_{i1} + (R_1 \parallel R_2) \approx r_{i1}$
 for ideal voltage source V_s , $R_s = 0$ and with $r_c = \infty$ loading.

$R_i = (2r_c) \parallel [r_{i1}(1 + a v_D)]$

- Output resistance:

$$R_o = \frac{r_{i0}}{1 + a\beta}$$


where r_{i0} being the output resistance of circuit a , with loading included!

Assume $R_L = \infty$ (no load); then $r_{i0} = R_L \parallel (R_2 + R_1') \parallel r_{i0} = (R_2 + R_1') \parallel r_{i0} \cong r_{i0}$

Here: $R_o = \frac{r_{i0}}{1 + a\beta}$

happens to be exactly $a\beta$, with a being the open-loop gain of the OpAmp!!! & $\beta = 1 + \frac{R_2}{R_1}$

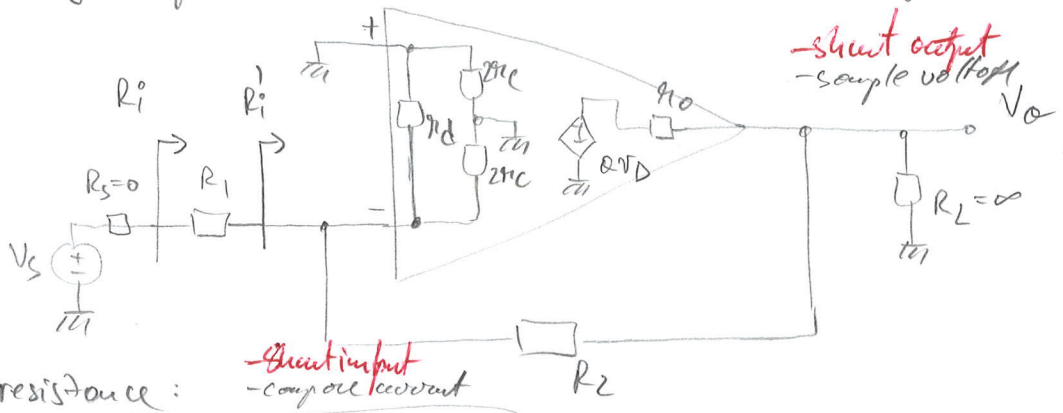(b) Inverting configuration \rightarrow Method 2 analysis as negative feedback.




input resistance:

$$R_i = R_1 + R_1'$$

$$R_1' = \frac{r_i}{1 + a\beta}$$

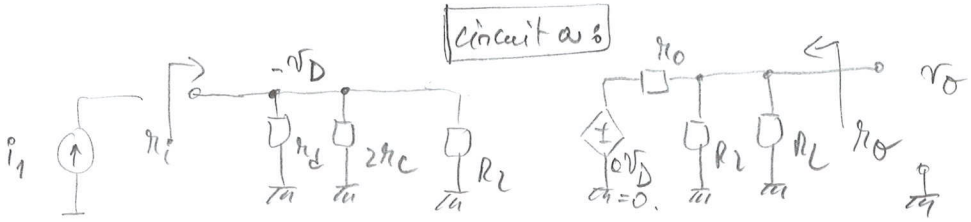with r_i being input resistance in circuit a .



$$r_{i0} = r_i \parallel (R_2 + R_L) \parallel r_o \cong R_2$$

$$R_i = R_1 + \frac{R_2}{1 + a\beta} \cong R_1 + \frac{R_2}{1 + a}$$

same as that by method 1 !!!

Output resistance:

$$R_o = \frac{r_{i0}}{1 + a\beta}$$

$$r_{i0} = R_L \parallel R_2 \parallel r_{i0} \cong r_{i0} \Rightarrow R_o \cong \frac{r_{i0}}{1 + a\beta}$$

$$R_o \cong \frac{r_{i0}}{1 + a\beta}$$

a_r is found with circuit "a": $a_r = \frac{v_o}{i_1} = \frac{R_2 \parallel R_L}{R_2 \parallel R_L + r_{i0}} \cdot a v_D \cdot \frac{1}{i_1} \cong \frac{R_2}{R_2 + r_{i0}} \cdot a \cdot \frac{(-i_1) \cdot (R_2 \parallel R_L)}{i_1}$

β_a can be found with circuit "b": $\beta_a = -\frac{v_2}{i_2} \Rightarrow \beta_a = -1$ $\Rightarrow a_r \beta_a = a$ of the OpAmp!