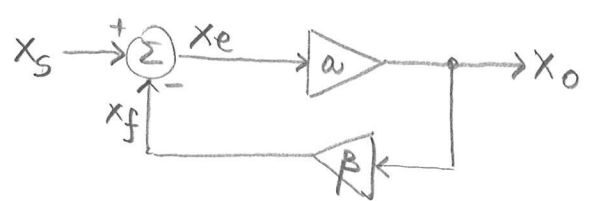


Negative feedback reference

→ General structure of a feedback amplifier:




→ Closed-loop gain is: $A \triangleq \frac{x_o}{x_s} = \frac{1}{\beta} \cdot \frac{a \cdot \beta}{1 + a \cdot \beta} \stackrel{(1)}{=} \frac{1}{\beta} \cdot \frac{T}{1 + T} \quad (1)$
 (2) $T = a \cdot \beta$: loop gain.


→ Based on the type of negative feedback topology (or configuration) the open-loop amplification a and the feedback factor β are "best" analyzed and computed as amplifications with meaning of transimpedance, transconductance, voltage-to-voltage, or current-to-current.

→ a and β can be easily computed using the so called "a" circuit and "beta" circuit.

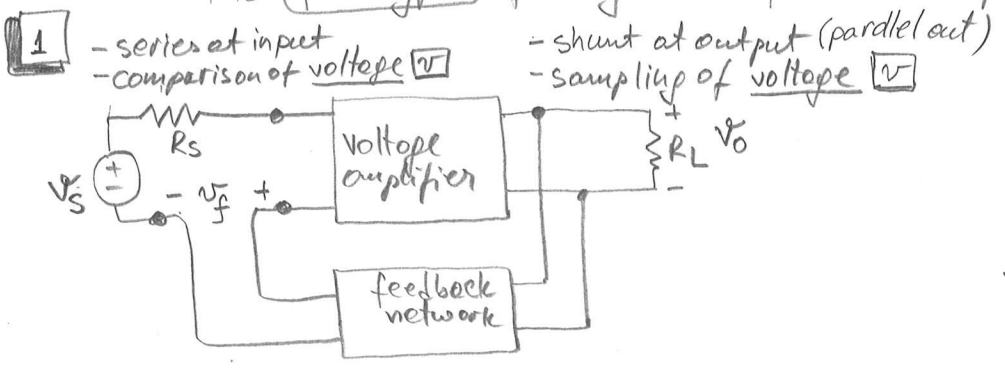→ The four types of negative feedback topology are:



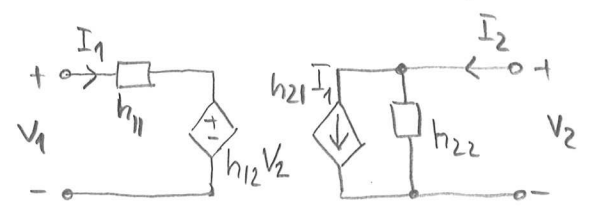→ Feedback network must be studied with h parameters:



Voltage to voltage (or simply voltage) amplification:

$$A_v = \frac{v_o}{v_s} = \frac{1}{\beta_v} \cdot \frac{a_v \cdot \beta_v}{1 + a_v \cdot \beta_v}$$


↑ voltage amplification ↑ voltage feedback factor

$$\begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 \\ V_2 = h_{21} I_1 + h_{22} V_2 \end{cases}$$


$$\beta_v = h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

open circuit.

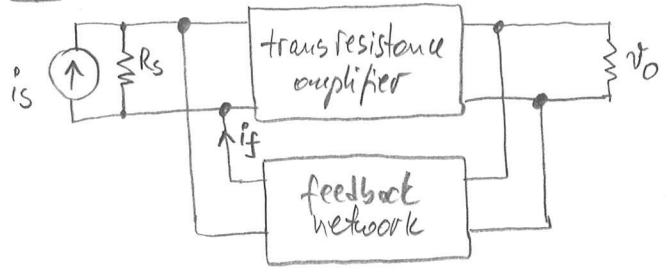2 - shunt at input
- comparison of i
- shunt at out
- sampling of v



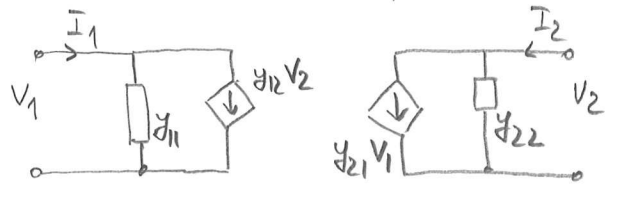→ Feedback network must be studied with y parameters:



Current to voltage ⇒ transresistance amplifier (or converter).

$$A_r = \frac{v_o}{i_s} = \frac{1}{\beta_g} \cdot \frac{a_r \beta_g}{1 + a_r \beta_g}$$


transresistance amplification
transconductance feedback factor

$$\begin{cases} I_1 = y_{11} V_1 + y_{12} V_2 \\ I_2 = y_{21} V_1 + y_{22} V_2 \end{cases}$$


$$\beta_g = y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

short circuit.

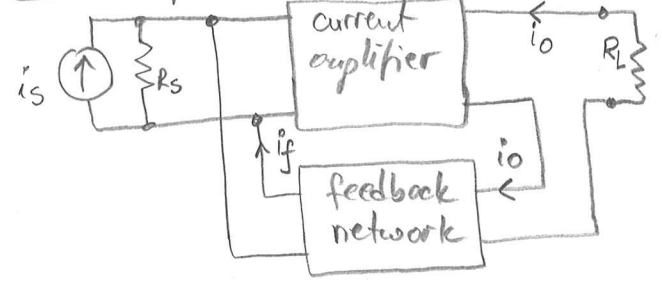3 - shunt/parallel at in
- comparison of i
- series at out
- sampling of i



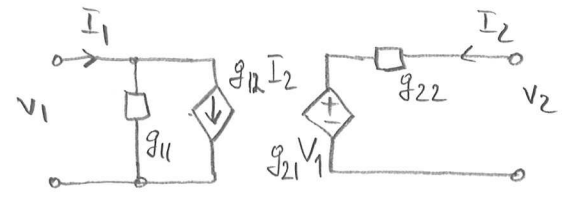→ feedback network must be studied with g parameters:



Current to current (or simply current) amplification:

$$A_i = \frac{i_o}{i_i} = \frac{1}{\beta_i} \cdot \frac{a_i \beta_i}{1 + a_i \beta_i}$$


current amplification
current feedback factor.

$$\begin{cases} I_1 = g_{11} V_1 + g_{12} I_2 \\ V_2 = g_{21} V_1 + g_{22} I_2 \end{cases}$$

$$\beta_i = g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0}$$

short circuit.

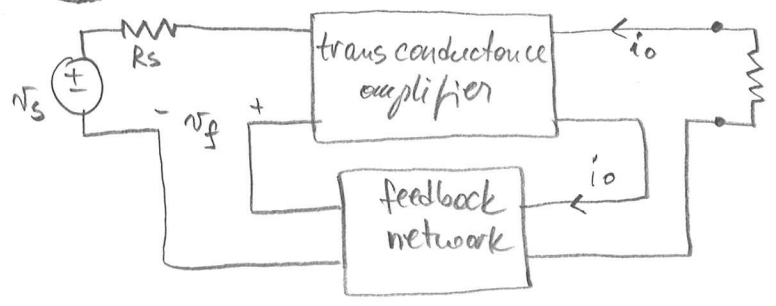- series at input
- compare voltage \checkmark
- series at output
- sampling current i




voltage to current (or transconductance) amplifier (or converter).

$$A_g = \frac{i_o}{v_s} = \frac{1}{R_n} \cdot \frac{a_g \cdot \beta_n}{1 + a_g \cdot \beta_n}$$

transconductance amplification \nearrow
 transresistance feedback factor \nearrow

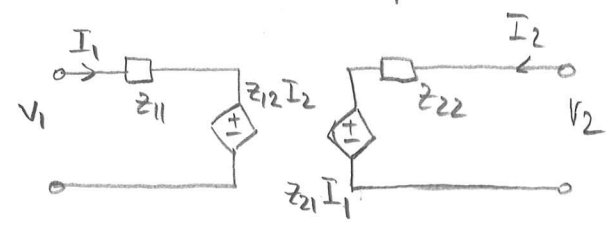→ feedback network must be studied with Z parameters:



$$\begin{cases} V_1 = z_{11} I_1 + z_{12} I_2 \\ V_2 = z_{21} I_1 + z_{22} I_2 \end{cases}$$

$$\beta = \frac{z_{12}}{R_n} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

↑
open circuit