


Negative  
Feedback in OpAmp circuits

1.6.

Basic topologies


Series at input

"comparison of voltage"  $v$

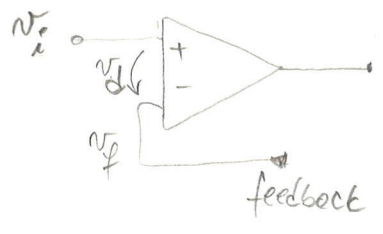

Series at Output


"sampling current"  $i$

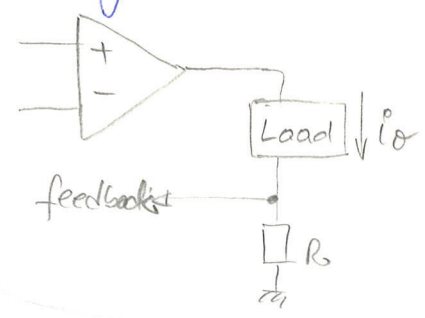

Shunt at input

(aka parallel at input)


"comparison of current"  $i$

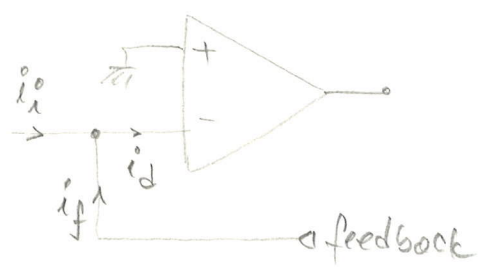

Shunt at output

parallel

"sampling voltage"  $v$


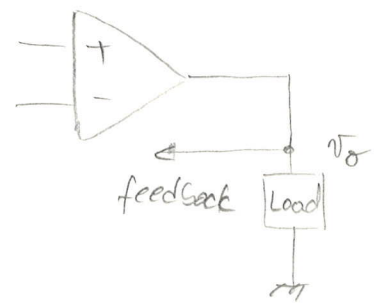


We can build amplifiers in four possible configurations:

	Input compon	Output sample	Type of amplifier
shunt - shunt	$i$	$v$	$A_v = \frac{v}{i}$ trans impedance
series - shunt	$v$	$v$	$A_v = \frac{v}{v}$ voltage
series - series	$v$	$i$	$A_p = \frac{i}{v}$ trans conductance
shunt - series	$i$	$i$	$A_i = \frac{i}{i}$ current

**Example 1: Non-inverting Configuration.**

Method 1 follows the textbook

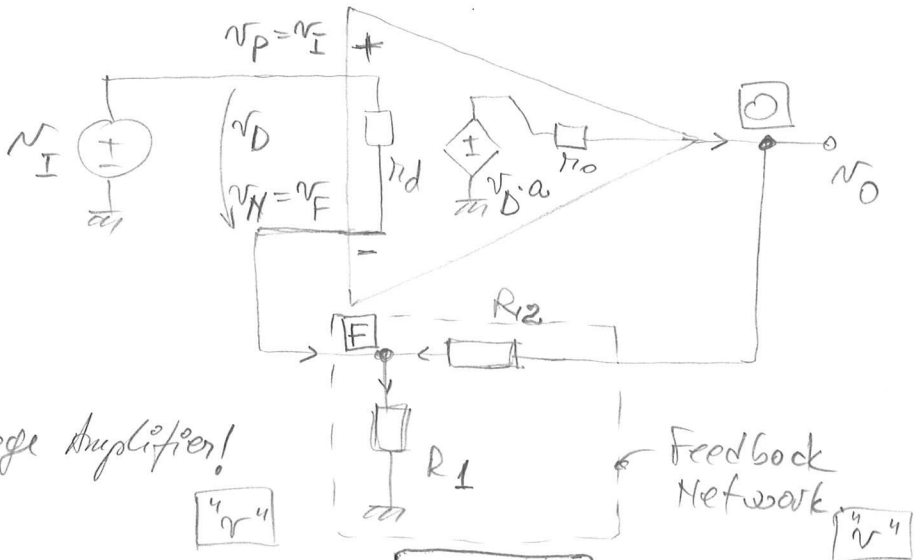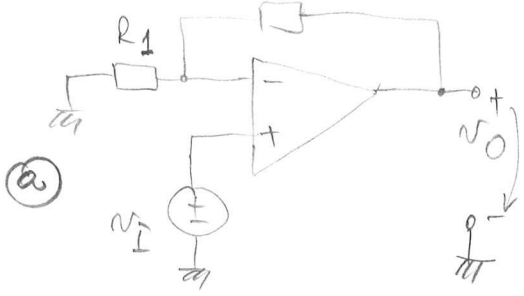

Feedback: series-shunt  
 { Sampling: voltage  
 { Compensing: voltage } => voltage amplifier!

$$\begin{cases} \frac{v_I - v_F}{r_I} - \frac{v_F}{R_1} + \frac{v_0 - v_F}{R_2} = 0 \\ \frac{v_0 - v_F}{R_2} = \frac{(v_I - v_F)\omega - v_0}{r_o} \end{cases}$$

$A = \frac{v_0}{v_I} = ?$

Eliminate  $v_F$  and derive (see page 2') the expression for: do it as an exercise

$$A_N = \frac{v_0}{v_I} = \frac{(1 + \frac{R_2}{R_1})\omega + \frac{r_o}{r_d}}{1 + \omega + \frac{R_2}{R_1} + \frac{(R_2 + r_o)}{r_d} + \frac{r_o}{R_1}}$$

$$(1) \quad A \approx \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{\omega}{(1 + \frac{R_2}{R_1}) + \omega} = \frac{1}{\beta} \cdot \frac{T}{1 + T}$$

where  $\beta = \frac{R_1}{R_1 + R_2}$

$\frac{1}{\beta} = 1 + \frac{R_2}{R_1} = A_{ideal}$

$$A \approx A_{ideal} \cdot \frac{T}{1 + T}$$

$T = \omega\beta \triangleq \text{loop gain}$

Derivation of  $A_r = \frac{v_0}{v_I} - (2)$

$$\left\{ \frac{v_I - v_F}{R_d} - \frac{v_F}{R_1} + \frac{v_0 - v_F}{R_2} = 0 \right.$$

$$\left. \frac{v_0 - v_F}{R_2} = \frac{v_D \cdot \omega - v_0}{R_0} = \frac{(v_I - v_F) \omega - v_0}{R_0} \right.$$

$$g_d (v_I - v_F) - g_1 v_F + g_2 (v_0 - v_F) = 0 \Leftrightarrow (g_d + g_1 + g_2) v_F = g_d v_I + g_2 v_0$$

$$g_2 v_0 - g_2 v_F = g_0 \omega (v_I - v_F) - g_0 v_0$$

$$\stackrel{\triangleq g}{=} g \cdot v_F = \frac{g_d v_I + g_2 v_0}{g}$$

$$g_2 v_0 + g_0 v_0 = g_0 \omega v_I + (g_2 - \omega g_0) v_F$$

$$(g_2 + g_0) v_0 = \omega g_0 v_I + (g_2 - \omega g_0) \frac{g_d}{g} v_I + (g_2 - \omega g_0) \frac{g_2}{g} v_0$$

$$\left[ (g_0 + g_2) - (g_2 - \omega g_0) \frac{g_2}{g} \right] v_0 = \left[ \omega g_0 + (g_2 - \omega g_0) \frac{g_d}{g} \right] v_I$$

$$\Rightarrow A_r = \frac{v_0}{v_I} = \frac{\omega g_0 + (g_2 - \omega g_0) \cdot \frac{g_d}{g}}{g_0 + g_2 - (g_2 - \omega g_0) \cdot \frac{g_2}{g}}$$

$$A_r = \frac{\omega g_0 g + g_2 g_d - \omega g_0 g_d}{g_0 g + g_2 g - g_2^2 + \omega g_0 g_d}$$

$$= \frac{\omega g_0 (g_1 + g_2 + g_d) + g_2 g_d - \omega g_0 g_d}{g_0 (g_1 + g_2 + g_d) + g_2 (g_1 + g_2 + g_d) - g_2^2 + \omega g_0 g_d}$$

$$= \frac{\omega g_0 (g_1 + g_2) + g_2 g_d}{g_0 g_2 (1 + \omega) + g_0 (g_1 + g_d) + g_2 (g_1 + g_d)}$$

$$A_r = \frac{\omega g_0 (g_1 + g_2) + g_2 g_d}{g_0 g_2 (1 + \omega) + (g_0 + g_d) (g_1 + g_d)}$$

The quantity:

$$\lim_{a \rightarrow 0} A = \frac{r_o/r_d}{1 + \frac{R_2}{R_1} + (R_2 + r_o)/r_d + \frac{r_o}{R_1}} \triangleq \text{feedthrough gain.}$$

- it refers to signal transmission from input  $\rightarrow$  output thru the feedback network! Negligible to keep things simple.

**b** Input resistance:

Apply  $\square$  test source  $\Rightarrow R_i = r_d \left( 1 + \frac{a}{1 + (R_2 + r_o)/R_1} \right) + R_1 \parallel (R_2 + r_o) \approx 0.$

$$R_i \approx r_d \cdot \left( 1 + \frac{a}{1 + \frac{R_2}{R_1} \beta} \right) = r_d (1 + a\beta) = \boxed{r_d (1 + T) = R_i} \quad (2)$$

**c** Output resistance


Apply  $\square$  test source  $\Rightarrow$

$$\Rightarrow R_o = \frac{r_o}{1 + \left( a + \frac{r_o}{R_1} + \frac{r_o}{r_d} \right) / \left( 1 + \frac{R_2}{R_1} + \frac{R_2}{r_d} \right)}$$

$$\boxed{R_o \approx \frac{r_o}{1 + T}} \quad (3)$$

Method 2: uses the technique based on circuit "a" and circuit "b"

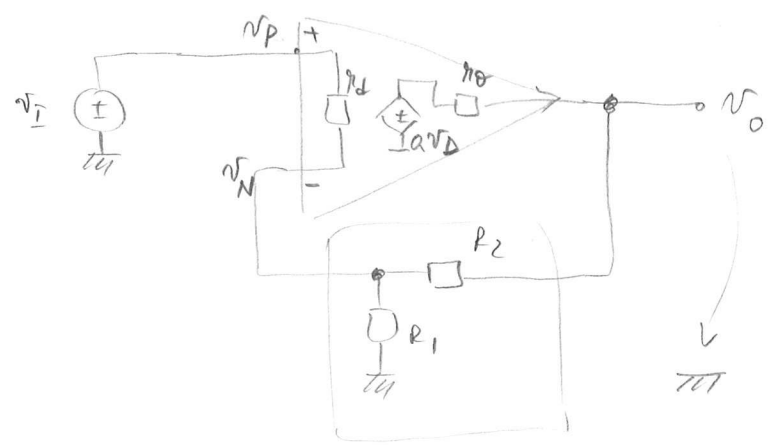- series input
- comparison of voltage  $v$




- parallel/shunt output
- coupling of voltage  $v$

Hence, this amplifier is best studied as a voltage amplifier!

$$A_{v_r} = \frac{a_{v_r}}{1 + a_{v_r} \beta_{v_r}} = \frac{1}{\beta_{v_r}} \cdot \frac{T}{1 + T}; \quad T = a_{v_r} \beta_{v_r}$$

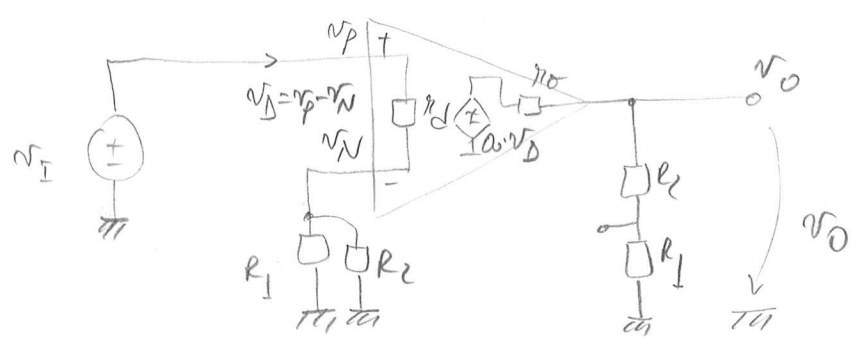(i) To find  $a_{v_r}$  we use circuit "a"



$$a_{v_r} = \frac{v_O}{v_I}$$


$$v_D = \frac{r_D}{r_D + R_1 + R_2} \cdot v_I \approx v_I$$

$$v_O = \frac{R_1 + R_2}{R_1 + R_2 + r_{O0}} \cdot (a v_D) \approx a v_D = a v_I \Rightarrow$$

$$a_{v_r} = \frac{v_O}{v_I} = a$$

The open loop gain of the Op Amp!

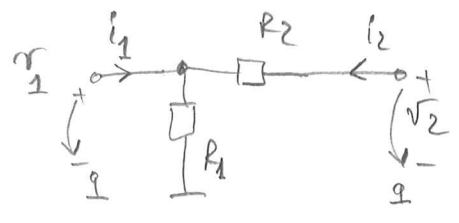(ii) To find  $\beta_{v_r}$  we use circuit "b"



$$\beta_{v_r} = \frac{v_1}{v_2} \Big|_{i_1=0} = \frac{R_1}{R_1 + R_2}$$

Analyzed with "h" parameters

Therefore the final closed loop amplification is:

$$A_{vR} = \frac{1}{\beta_r} \times \frac{a_v \beta_r}{1 + a_v \beta_r} = \frac{1}{\beta_r} \times \frac{T}{1+T} = \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{a_v \cdot \frac{R_1}{R_1 + R_2}}{1 + a_v \cdot \frac{R_1}{R_1 + R_2}} \quad (4)$$

$= A_{ideal}$

Note: → This is exactly the amplification we were interested in the first place!

→ Compare it to equation (1) from Method 1: here we found the result via a simpler and more general technique!

② Example 2 Inverting Configuration

Method 1: We could have worked directly with (textbook) voltage loops (like in the case of non-inverting) and arrived to:

②

$$A = \frac{v_o}{v_i} = - \frac{\omega R_2 - r_{10}}{(1+\omega)R_1 + (R_2+r_{10})(1+\frac{R_1}{r_d})} \quad (5)$$

Typically  $r_{10} \ll R_2, \frac{R_1}{r_d} \ll 1$

$\Rightarrow A \approx \left(-\frac{R_2}{R_1}\right) \cdot \frac{T}{1+T}$  with the loop gain  $T = \frac{\omega R_1}{R_1+R_2}$


Observation: Method 2 ← is better because fits the well established technique of studying circuits with feed back using the "a" and "p" (or "f") "circuits", and then just plug them into:  $A = A_{ideal} \cdot \frac{T}{1+T} = \frac{1}{\beta} \cdot \frac{op}{1+op}$ .

What we did here we used the OpAmp model with  $\{r_{10}, r_{11}, r_{12}, r_{13}\}$  and used Kinkoff's laws to derive  $\frac{v_o}{v_i}$  or  $\frac{v_o}{v_i}$ . After that we took the expression so that to identify  $A = A_{ideal} \cdot \frac{T}{1+T}$ . The other (more correct way) is to treat the amplifier as  $A_v, A_i, A_{r1}, A_{r2}$  and use the technique based on "e" and "f" circuit to derive  $A = \frac{1}{\beta} \cdot \frac{op}{1+op}$  directly!

The first term gain:

$$\lim_{\omega \rightarrow 0} A = \frac{r_{10}}{R_1 + (R_2 + r_{10}) \left(1 + \frac{R_1}{r_d}\right)}$$

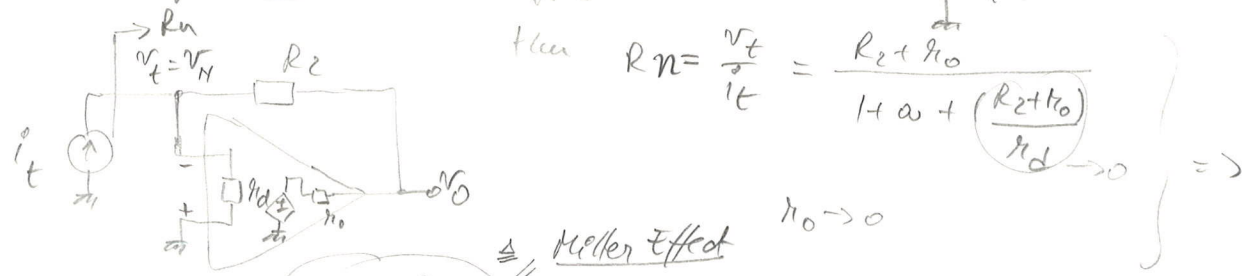⑥ Input resistance: Apply test current  $i_t$  and measure  $v_t$ ,



then  $R_N = \frac{v_t}{i_t} = \frac{R_2 + r_{10}}{1 + \omega + \left(\frac{R_2 + r_{10}}{r_d}\right)}$


$\Rightarrow R_N \approx \frac{R_2}{1 + \omega} \Rightarrow R_i = R_1 + R_N \approx R_1$  (6)

*Note: Moller Effect*

⑦ Output resistance (similar to noninverting config):


$$R_o \approx \frac{r_{10}}{1+T} \quad (7)$$

II Example 2 inverting configuration

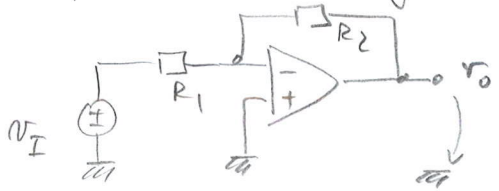

Method 2 ← present first method 1, 2 paper later.

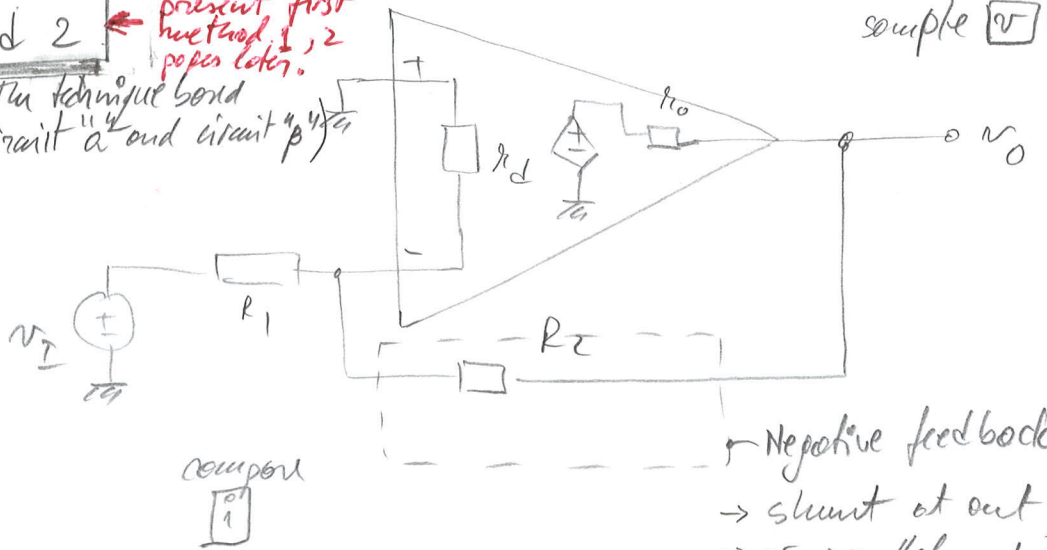using the technique bond our circuit "a" and circuit "b"




Negative feedback network  
 → shunt at out; shunt at input  
 → or parallel out; parallel input  
 → or sampling of voltage; comparison of current

Hence, this amplifier is best studied as a trans-impedance amplifier.

$$A_n = \frac{a_n r_o}{1 + a_n \beta_g} = \frac{1}{\beta_g} \cdot \frac{T}{1+T} \quad ; \quad \boxed{T = a_n \beta_g}$$

(i) To find  $a_n$  we use circuit "a"

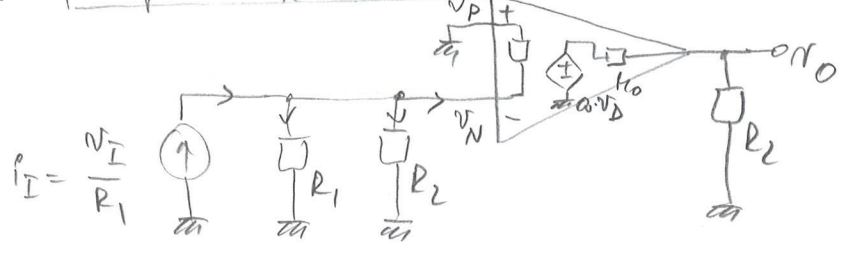

$$v_D = v_P - v_N = 0 - v_N = -v_N$$

$$i_I = \frac{v_N}{R_1} + \frac{v_N}{R_2} + \frac{v_N}{r_o} = v_N \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_o} \right) \approx v_N \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{1}{R_1 || R_2}$$


$$\Rightarrow v_D = -R_1 || R_2 \cdot i_I$$

$$v_O = \frac{R_2}{R_2 + r_o} (a \cdot v_D) \approx a \cdot v_D = -a R_1 || R_2 \cdot i_I$$


$$\Rightarrow a_n = \frac{v_O}{i_I} = -a R_1 || R_2 = \boxed{-a \frac{R_1 R_2}{R_1 + R_2} = a_n}$$



To find  $\beta_g$  we use circuit "p"

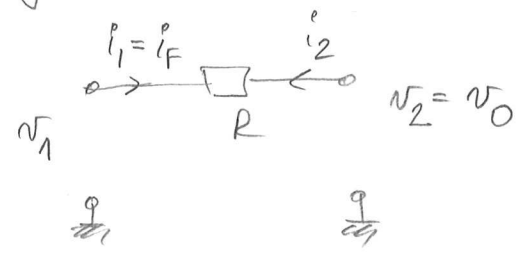

$$\beta_g = \left. \frac{i_1}{v_2} \right|_{v_1=0} = - \frac{i_2}{v_2} = - \frac{1}{R_2}$$

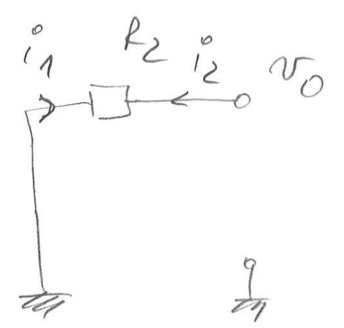

Analyzed with "y" parameters.

$$\beta_g = - \frac{1}{R_2}$$

Finally, the closed loop gain/amplification:

$$A_{ri} = \frac{v_0}{i_I} = \frac{a_{ri}}{1 + a_{ri} \beta_g} = \frac{1}{\beta_g} \cdot \frac{T}{1 + T} ; \quad T = a_{ri} \beta_g = -a_{ri} (R_1 || R_2) \cdot \left(-\frac{1}{R_2}\right) = a_{ri} \cdot \frac{R_1}{R_1 + R_2}$$

$$A_{ri} = \left(-R_2\right) \times \frac{a_{ri} \frac{R_1}{R_1 + R_2}}{1 + a_{ri} \frac{R_1}{R_1 + R_2}} \quad (8)$$

if we want the voltage amplification:

$$A = \frac{v_0}{v_I} = \underbrace{\left(\frac{v_0}{i_I}\right)}_{= A_{ri}} \cdot \underbrace{\left(\frac{i_I}{v_I}\right)}_{= \frac{1}{R_1}} = \underbrace{\left(-\frac{R_2}{R_1}\right)}_{= A_{ideal}} \times \frac{a_{ri} \frac{R_1}{R_1 + R_2}}{1 + a_{ri} \frac{R_1}{R_1 + R_2}} \quad (9)$$

NOTE: Compare this to equation (1.62) from textbook; whose derivation is done like of the noninverting amplifier (using KCL, KVL) ! Also, compare to eq. (5) from Method 1

Note: Compare this method 1 to page 36 from Book.

## 1.7 The Loop Gain

← Homework assignment or next time? <sup>-7-</sup>

Generally, for OpAmp circuits, the voltage gain is:

$$A = A_{ideal} \cdot \frac{T}{1+T}$$

found using the ideal opamp model (using the "virtual-short" technique)

$$R \approx r_o \times (1+T)^{\pm 1}$$

$r_o$  is the open-loop resistance calculated in the limit  $\omega \rightarrow 0$ .