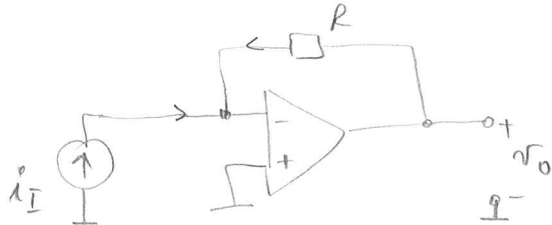


Chapter 2 Circuits with resistive feedback

- ① Opamp used to implement
 - IV converter (transresistance)
 - VI converter (trans conductance)
 - current amplifiers
- ② instrumentation concepts
 - difference amplifiers
 - instrumentation amplifiers (IA)
 - transducer bridge amplifiers

2.1 Current-to-voltage converter $i \rightarrow v$




- shunt in
- sample current i
- shunt out
- sample voltage v

ideal Opamp analysis:

$$\frac{v_O}{R} = -i_I \Rightarrow \boxed{\frac{v_O}{i_I} = -R = A_{IC}}$$

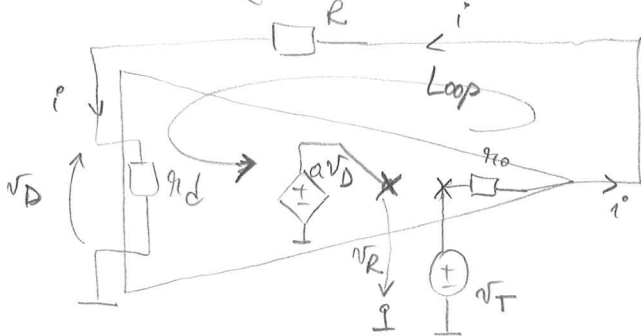② To find the loop gain T, use the technique from 1.7 (chapter 1)



$$T = - \frac{v_R}{v_T} \Big|_{X_T=0}$$


$$v_R = a v_D = a (-i_i R_D) = -a i_i R_D \cdot \frac{v_T}{R_D + R + R_o} \Rightarrow \boxed{T = \frac{R_D \cdot a}{R_D + R + R_o}}$$

→ Loop gain T is unit-less irrespective of the type of a_v, a_i, a_g, a_r and $\beta_v, \beta_r, \beta_n, \beta_g$!

→ So, this technique is ok for any type of neg. feedback configuration
 → Note we have T but we do not know a_v and β_g ! find them by "2" β circuits!

For example, finding β_g is always easier:

The "y" circuit is:

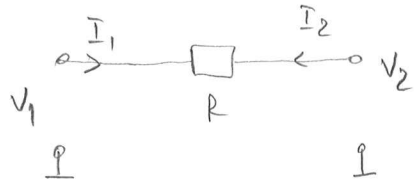


Using the reference-handout:

$$\beta_g = \frac{I_1}{V_2} \Big|_{V_1=0} = (y_{12}) = -\frac{1}{R}$$

Therefore the closed loop amplification of this IV converter is:

$$A_{\beta} = \frac{1}{\beta_g} \cdot \frac{T}{1+T} = -R \cdot \frac{T}{1+T}; \text{ where } T = \frac{\mu_d \omega}{\mu_d + R + h_o}$$

input resistance \rightarrow Method 1

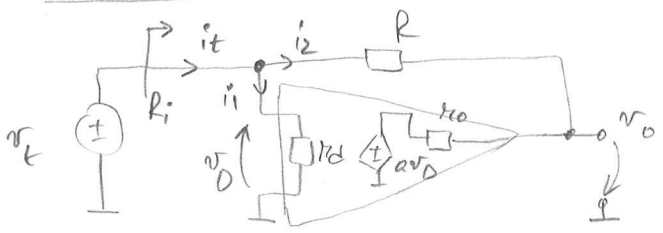

$$v_t = -v_D = i_1 \mu_d \Rightarrow i_1 = \frac{v_t}{\mu_d}$$

$$i_2 = \frac{v_t - v_o}{R} = \frac{v_t - \mu_d i_2 - a v_D}{R}$$

$$(R + h_o) i_2 = v_t - a v_D = (1+a) v_t = -v_t$$

$$\Rightarrow i_t = i_1 + i_2 = \frac{v_t}{\mu_d} + \frac{1+a}{R+h_o} v_t = \left(\frac{1}{\mu_d} + \frac{1+a}{R+h_o} \right) v_t$$


$$R_i = \frac{v_t}{i_t} = \frac{\mu_d (R+h_o)}{R+h_o + \mu_d (1+a)} = \frac{\mu_d (R+h_o)}{\mu_d + (R+h_o)} \cdot \frac{\mu_d + (R+h_o)}{(R+h_o) + \mu_d (1+a)} = \frac{\mu_d \parallel (R+h_o)}{1+T} = \frac{1}{1 + \frac{\mu_d \omega}{\mu_d + R + h_o}} = \frac{1}{1+T}$$

Method 2 (read page 37)

We know that one of the benefits of the neg. feedback is:

$$R_i = \begin{cases} R(1+T), & \text{for series topology at in} \\ \frac{R}{1+T}, & \text{for shunt/parallel topology at in} \end{cases}$$

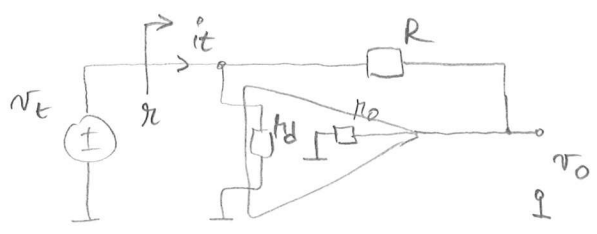R_i is the input resistance into amplifier with $\omega=0$




$$R_i = \frac{v_t}{i_t} \Big|_{\omega=0} = \mu_d \parallel (R+h_o)$$

$$\text{Therefore: } T = \frac{R}{1+T} = \frac{\mu_d \parallel (R+h_o)}{1+T}$$

Same as before!

Output resistance → Method 1

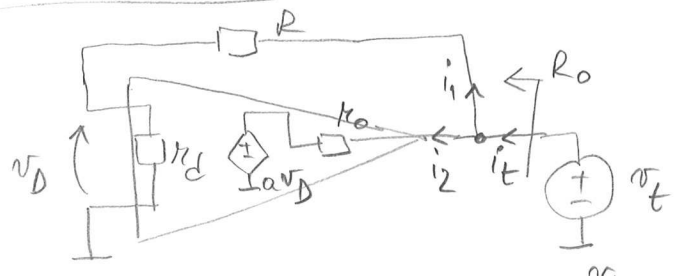

$$i_1 = \frac{v_t}{R+r_D}$$

$$i_2 = \frac{v_t - a v_D}{r_o} = \frac{v_t + a r_D i_1}{r_o}$$

$$v_D = -r_D i_1$$

$$i_t = i_1 + i_2 = \frac{v_t}{R+r_D} + \frac{v_t + a r_D \cdot \frac{v_t}{R+r_D}}{r_o}$$


$$= v_t \left(\frac{1}{R+r_D} + \frac{R+r_D + a r_D}{r_o(R+r_D)} \right) = v_t \left(\frac{r_o + R + (1+a)r_D}{r_o(R+r_D)} \right)$$

$$\Rightarrow R_o = \frac{v_t}{i_t} = \frac{r_o(R+r_D)}{r_o + R + (1+a)r_D} = r_o \cdot \frac{1}{1 + \frac{r_o + a r_D}{R+r_D}} \approx \frac{r_o}{1+T}$$

Recall $T = \frac{r_D \cdot a}{r_D + R + r_o} \approx \frac{r_D \cdot a}{r_D - R}$

Method 2: (read page 37)

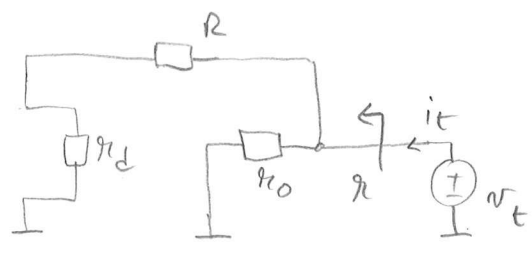$R_o \approx \frac{r_o}{1+T}$; r_o is the output resistance from amplifier with $a=0$.



$$r_o = \frac{v_t}{i_t} = r_o \parallel (R+r_D) \approx r_o$$


Therefore $R_o \approx \frac{r_o}{1+T}$
Sources before!

use those techniques to calculate $\beta = -\frac{v_D}{v_T} / \alpha_I = 0$ because here $\alpha_I = 0$ (4)
 the feedback network brings for comparison a current!

► insert here the Notes on the theory of negative-feedback and the universal relation: $A = A_{ideal} \cdot \frac{\alpha\beta}{1 + \alpha\beta}$.

2.2. **Voltage-to-current Converters** $v \rightarrow i$
 (trans-conductance "g" amplifiers)

Floating-load Converter

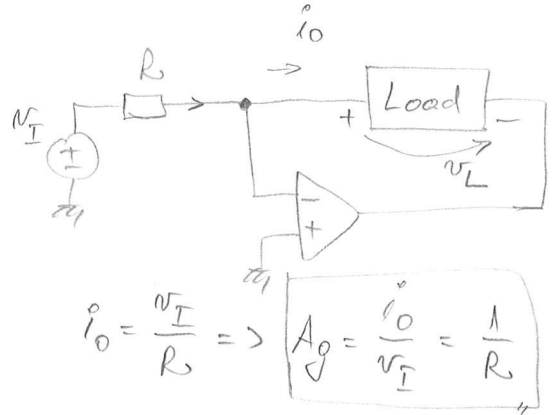


$$i_o = \frac{v_I}{R} \Rightarrow A_g = \frac{i_o}{v_I} = \frac{1}{R}$$

Feedback: shunt-series
 (compare voltage - sample current)
 \Rightarrow "g" amplifier.
 See Fig. 1.26.


Grounded-load Converter

HOWLAND current pump: Negative feedback topology:

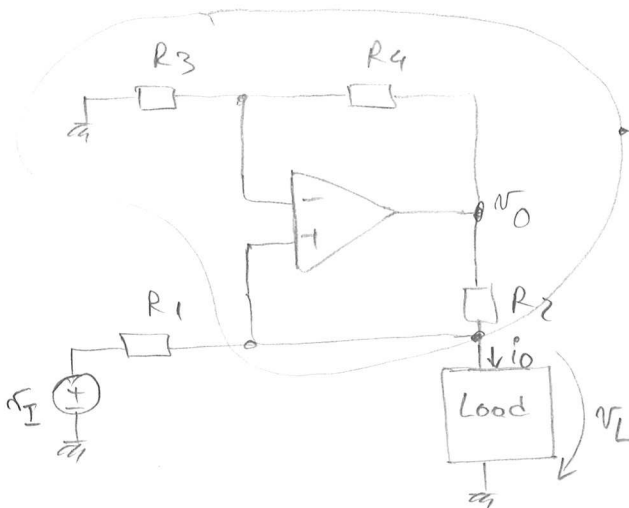"series-series": more appropriate for "g" amplifier!



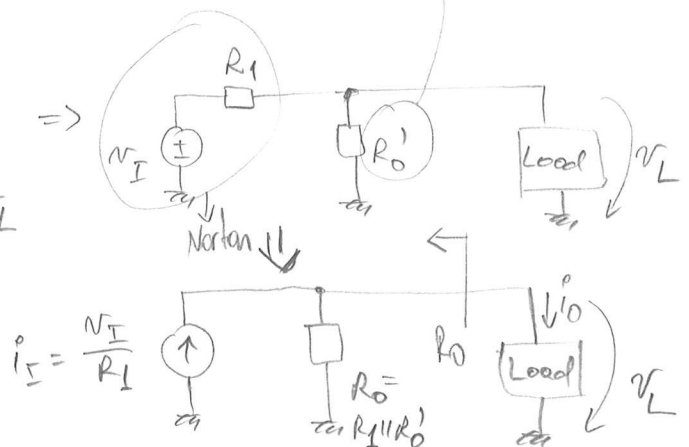Negative resistor $= -\frac{R_2 R_3}{R_4}$



$$R_0 = R_1 \parallel \left(- \frac{R_2 R_3}{R_4} \right) = \frac{R_1 \cdot \left(- \frac{R_2 R_3}{R_4} \right)}{R_1 + \left(- \frac{R_2 R_3}{R_4} \right)} =$$

$$= \frac{- \frac{R_1 R_2 R_3}{R_4}}{R_1 R_4 - R_2 R_3} = \frac{R_1 R_2 R_3}{R_2 R_3 - R_1 R_4} = \boxed{\frac{R_2}{\frac{R_2}{R_1} - \frac{R_4}{R_3}} = R_0}$$

Observe: $\lim_{\frac{R_2}{R_1} \rightarrow \frac{R_4}{R_3}} R_0 = \infty$

This is a "g" amplifier \Rightarrow at the output it has to be seen as a current source \Rightarrow ideally $R_0 \rightarrow \infty$. That is the case for

$$\boxed{\frac{R_2}{R_1} = \frac{R_4}{R_3}}$$

The gain: $A_g = \frac{i_o}{v_I} = ?$

$$i_o = \frac{R_0}{R_0 + R_L} \cdot i_I = \frac{R_0}{R_0 + R_L} \cdot \frac{v_I}{R_1} \Rightarrow \boxed{A_g = \frac{i_o}{v_I} = \frac{1}{R_1} \cdot \frac{R_0}{R_0 + R_L}}$$

Ideally: $\lim_{R_0 \rightarrow \infty} A_g = \boxed{\frac{1}{R_1} = A_{ideal}}$

Important

Howland circuit has both negative and positive feedbacks:

$$\beta_N = \frac{R_3}{R_3 + R_4} = \frac{1}{1 + R_2/R_1}$$

$$\beta_P = \frac{R_1 R_L}{R_1 R_L + R_2} = \frac{1}{1 + R_2/R_1 + R_2/R_L}$$

$\Rightarrow \beta_P < \beta_N \Rightarrow$ Negative feedback prevails!

\Rightarrow We can still apply the "virtual short" concept.

Also the circuit will be stable!

② Effect of resistance mismatch

⑥

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} (1 - \epsilon) \quad \epsilon \triangleq \text{imbalance factor.}$$

$$\Rightarrow \boxed{R_0 = \frac{R_1}{\epsilon}}$$

the smaller the imbalance the higher R_0 .

③ Effect of finite open-loop gain

$$i_o = \frac{v_I - v_L}{R_1} + \frac{v_O - v_L}{R_2}$$

$$v_O = v_L \cdot \frac{\omega}{1 + \omega \frac{R_3}{R_3 + R_4}}$$


: I look at it as a non-inverting amplifier
 $v_L \rightarrow v_O$

Assume perfect $\frac{R_4}{R_3} = \frac{R_1}{R_2}$

$$\Rightarrow i_o = \frac{1}{R_1} v_I - \frac{1}{R_0} v_L$$

$$\text{where } R_0 = (R_1 || R_2) \left(1 + \frac{\omega}{1 + \frac{R_2}{R_1}} \right)$$

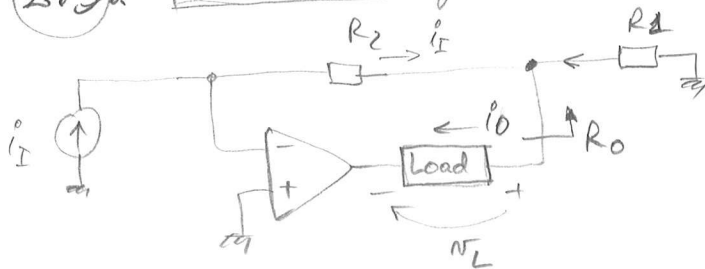2.3. Current amplifiers $i_i \rightarrow i_o$



$$A_i = \frac{i_o}{i_i}$$

$$\text{Typically: } \boxed{i_o = A i_i - \frac{1}{R_0} v_L}$$

R_0 = output resistance as seen by the load.


$$i_o = i_i + \frac{R_2 i_i}{R_1} \Rightarrow \boxed{A_i = \frac{i_o}{i_i} = 1 + \frac{R_2}{R_1}}$$

Holds regardless of v_L
 \Rightarrow circuit provides $R_0 \rightarrow \infty$

If ω is finite, it can be proven:

$$A = 1 + \frac{R_2/R_1}{1 + \frac{1}{\omega}} \quad \boxed{R_0 = R_1(1 + \omega)}$$

Proof: Method 1

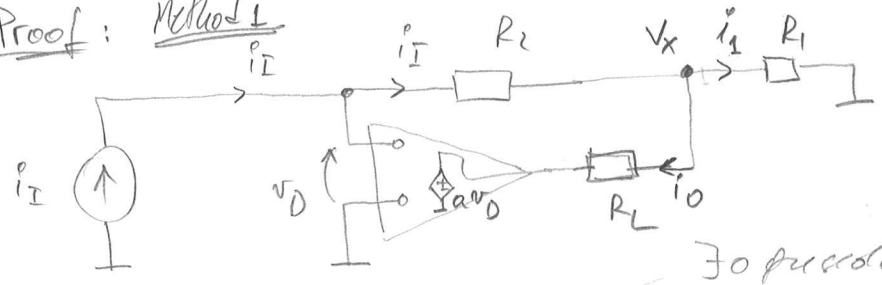

to proceed.

$$\left\{ \begin{aligned} v_x &= R_L i_o + a v_D = -R_2 i_I - v_D \\ v_D &= -R_2 i_I - R_1 i_1 = -R_2 i_I - R_1 (i_I - i_o) \end{aligned} \right. \Rightarrow R_L i_o + a [-R_2 i_I - R_1 (i_I - i_o)] = -R_2 i_I$$


$i_1 = i_I - i_o$

$$\Rightarrow (R_L + a R_1) i_o = (a R_2 + a R_1 - R_2) i_I$$

$$A_i = \frac{i_o}{i_I} = \frac{a(R_1 + R_2) - R_2}{a R_1 + R_L} = 1 + \frac{(a-1) R_2}{a R_1} = 1 + \frac{R_2}{R_1} \left(1 - \frac{1}{a}\right) \approx 1 + \frac{R_2}{R_1} \frac{1}{1 + 1/a}$$

$\approx \frac{1}{1 + 1/a}$ because $\frac{1}{a} \ll 1$
see verso for $R_o = ?$

Method 2: (So Franco's solution)

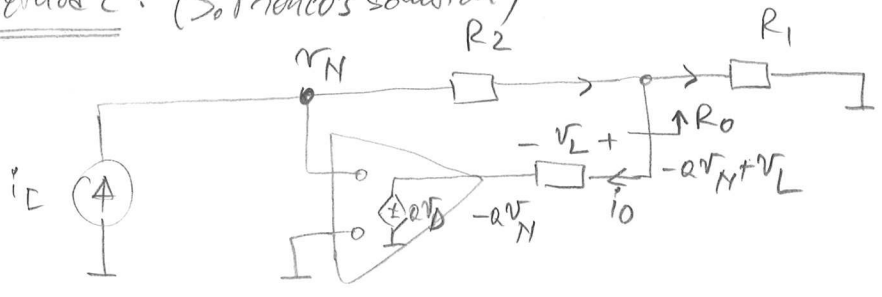

$$v_N - (-a v_N + v_L) = R_2 i_I$$

$$\Rightarrow v_N = (R_2 i_I + v_L) / (1+a)$$

$$i_o = i_I + \frac{a v_N - v_L}{R_1} = i_I + \frac{a \frac{R_2 i_I + v_L}{1+a} - v_L}{R_1} - \frac{v_L}{R_1}$$


$$= i_I \left(1 + \frac{R_2/R_1}{1 + 1/a}\right) - \frac{v_L}{R_1} \left(1 - \frac{a}{1+a}\right) = A_i i_I - \frac{v_L}{R_o}$$

$= \frac{1}{R_1(1+a)} = \frac{1}{R_o}$

$$A_i = 1 + \frac{R_2}{R_1} \frac{1}{1 + 1/a}$$


$$R_o = R_1(1+a)$$

2.4. Difference amplifiers

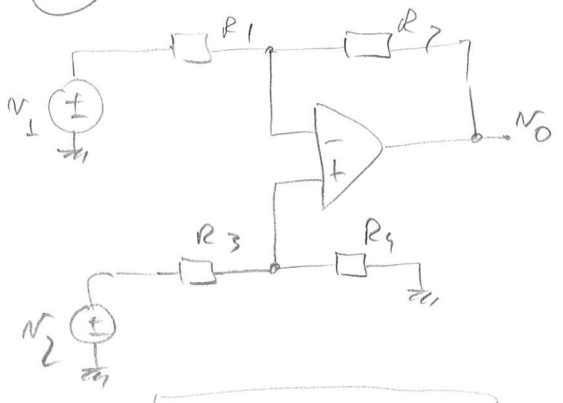

$$v_0 = \frac{R_2}{R_1} (v_2 - v_1)$$

if $\frac{R_4}{R_3} = \frac{R_2}{R_1}$

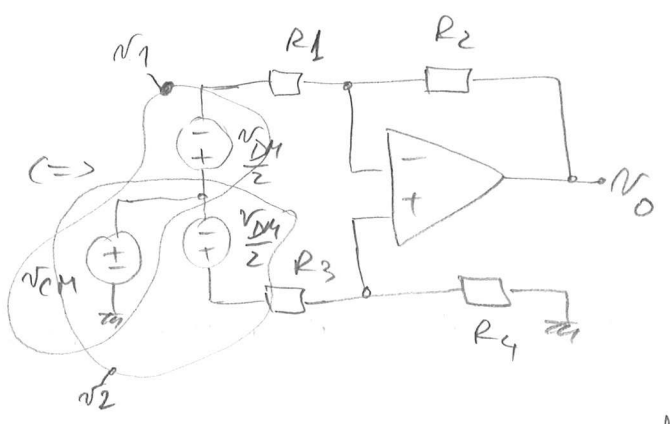


$$\begin{cases} v_{DM} = v_2 - v_1 \\ v_{CM} = \frac{v_1 + v_2}{2} \end{cases} \Rightarrow \begin{cases} v_1 = v_{CM} - \frac{v_{DM}}{2} \\ v_2 = v_{CM} + \frac{v_{DM}}{2} \end{cases}$$

Using this arrangement it's easier to study it, more insightful!


=> A true difference amplifier responds only to v_{DM} ! and completely ignores v_{CM}

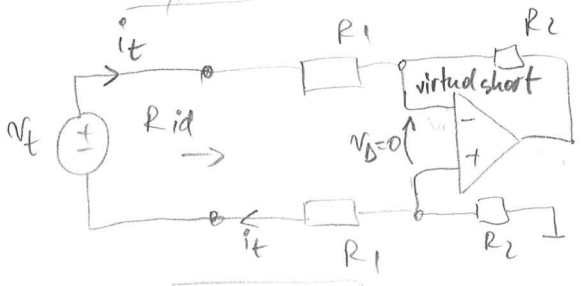Differential-mode, common-mode input resistances



$$R_{id} = 2R_1$$
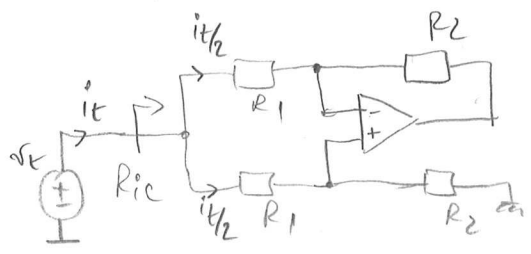
$$v_t = R_1 i_t - v_D + R_1 i_t \Rightarrow \frac{v_t}{i_t} = 2R_1 = R_{id}$$




$$R_{ic} = \frac{R_1 + R_2}{2}$$

$$v_t = \frac{i_t}{2} (R_1 + R_2) \Rightarrow \frac{v_t}{i_t} = \left(\frac{R_1 + R_2}{2} \right) = R_{ic}$$

Effect of resistance mismatches
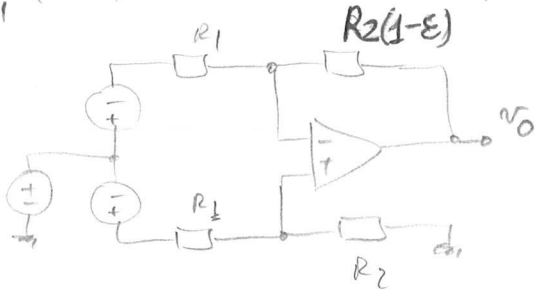
$$\frac{R_4}{R_3} = \frac{R_2}{R_1} (1 - \epsilon) \quad \epsilon \triangleq \text{imbalance factor.}$$



Use superposition:

$$V_0 = -\frac{R_2(1-\epsilon)}{R_1} \left(v_{CM} - \frac{v_{DM}}{2} \right) + \frac{R_1+R_2(1-\epsilon)}{R_1} \times \frac{R_2}{R_1+R_2} \left(v_{CM} + \frac{v_{DM}}{2} \right)$$

$$\Rightarrow \boxed{V_0 = A_{DM} \cdot v_{DM} + A_{CM} \cdot v_{CM}}$$

$$A_{DM} = \frac{R_2}{R_1} \left(1 - \frac{R_1+2R_2}{R_1+R_2} \cdot \frac{\epsilon}{2} \right) \xrightarrow{\epsilon \rightarrow 0} \frac{R_2}{R_1}$$

$$A_{CM} = \frac{R_2}{R_1+R_2} \cdot \epsilon \xrightarrow{\epsilon \rightarrow 0} 0$$

$\frac{A_{DM}}{A_{CM}} \triangleq CMRR$ Common mode rejection ratio, expressed in dB:

$$CMRR_{dB} = 20 \cdot \log \left| \frac{A_{DM}}{A_{CM}} \right|$$

True difference amplifier $\Rightarrow CMRR_{dB} \rightarrow \infty$

$$CMRR_{dB} \approx 20 \cdot \log \left| \frac{1 + \frac{R_2}{R_1}}{\epsilon} \right|$$

- Variable gain

- Ground-loop interference elimination

home
exercise for
students!