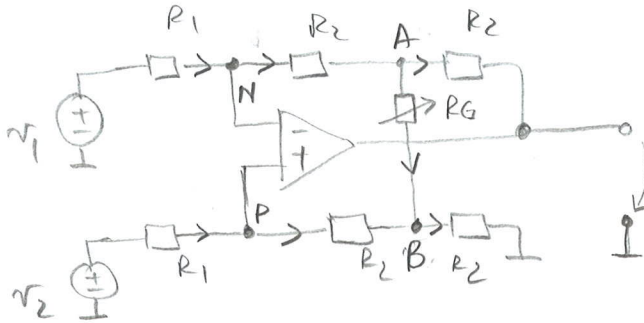


Variable gain difference amplifier



$$v_o = \frac{2R_2}{R_1} \left( 1 + \frac{R_2}{R_G} \right) (v_2 - v_1)$$

Method 1

$$\begin{cases} \text{KCL at node N:} \\ \text{KCL at node P:} \end{cases} \begin{cases} \frac{v_1 - v_N}{R_1} = \frac{v_N - v_A}{R_2} \\ \frac{v_2 - v_P}{R_1} = \frac{v_P - v_B}{R_2} \end{cases}$$

Subtract with  $v_N = v_P$

$$\frac{v_2 - v_1}{R_1} = \frac{v_A - v_B}{R_2} \Rightarrow v_A - v_B = \frac{R_2}{R_1} (v_2 - v_1)$$

key trick.

$$\begin{cases} \text{KCL node A:} \\ \text{KCL node B:} \end{cases} \begin{cases} \frac{v_N - v_A}{R_2} = \frac{v_A - v_o}{R_2} + \frac{v_A - v_B}{R_G} \\ \frac{v_P - v_B}{R_2} = \frac{v_B}{R_2} - \frac{v_A - v_B}{R_G} \end{cases}$$

Subtract with  $v_N = v_P$

$$\frac{v_A - v_B}{R_2} = -\frac{v_A - v_B}{R_2} + \frac{v_o}{R_2} - \frac{2}{R_G} (v_A - v_B) \Rightarrow$$


$$\left( \frac{2}{R_2} + \frac{2}{R_G} \right) (v_A - v_B) = \frac{v_o}{R_2}$$

$$\Rightarrow \frac{v_o}{R_2} = \left( \frac{2}{R_2} + \frac{2}{R_G} \right) \cdot \frac{R_2}{R_1} (v_2 - v_1)$$

$$\frac{v_o}{R_2} = \frac{2(R_G + R_2)}{R_1 R_G} \cdot \frac{R_2}{R_1} (v_2 - v_1) \Rightarrow v_o = 2 \cdot \frac{R_2}{R_1} \left( 1 + \frac{R_2}{R_G} \right) (v_2 - v_1)$$

# Method 2 Superposition

Case 1:  $v_1 = 0, v_2 \neq 0$

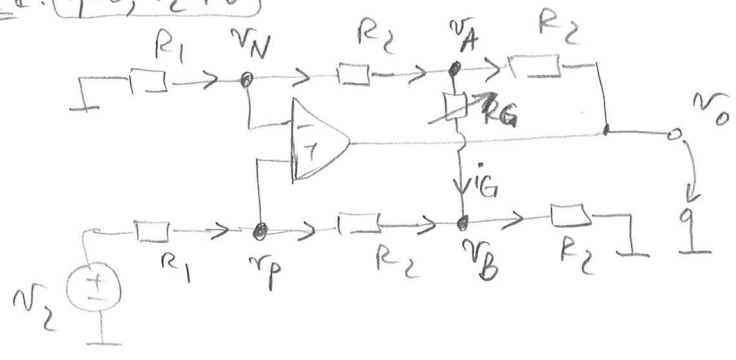

$$\begin{cases} v_P = \frac{R_2}{R_1 + R_2} v_2 + \frac{R_1}{R_1 + R_2} v_B \\ v_N = \frac{R_1}{R_1 + R_2} v_A \end{cases} \Rightarrow$$

$$\Rightarrow v_P = v_N \Leftrightarrow R_2 v_2 = R_1 (v_A - v_B) \Rightarrow v_2 = \frac{R_1}{R_2} (v_A - v_B)$$


KCL node A:  $\frac{v_N - v_A}{R_2} = \frac{v_A - v_B}{R_G} + \frac{v_A - v_0}{R_2}$

KCL node B:  $\frac{v_P - v_B}{R_2} = -\frac{v_A - v_B}{R_G} + \frac{v_B}{R_2}$  subtract  $v_N = v_P$

$$\frac{v_A - v_B}{R_2} = -2 \frac{v_A - v_B}{R_G} - \frac{v_A - v_B}{R_2} + \frac{v_0}{R_2} \Rightarrow \frac{v_0}{R_2} = \left( \frac{2}{R_2} + \frac{2}{R_G} \right) (v_A - v_B)$$

$$\Rightarrow \frac{v_0}{R_2} = \left( \frac{2}{R_2} + \frac{2}{R_G} \right) \cdot \frac{R_2}{R_1} v_2 \Rightarrow v_0 = 2 \frac{R_2}{R_1} \left( 1 + \frac{R_2}{R_G} \right) v_2$$

Case 2:  $v_1 \neq 0, v_2 = 0$

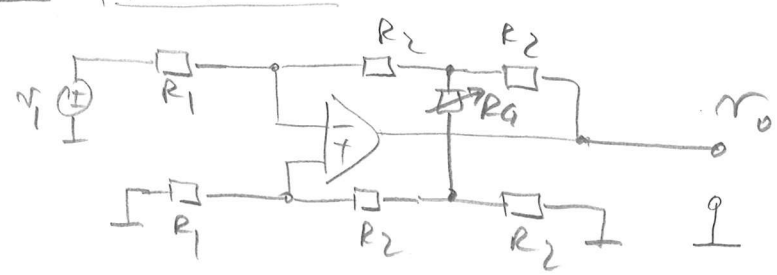


Similarly:  $v_0 = -2 \frac{R_2}{R_1} \left( 1 + \frac{R_2}{R_G} \right) v_1$

finally by  $\Rightarrow$  superposition

$$v_0 = 2 \frac{R_2}{R_1} \left( 1 + \frac{R_2}{R_G} \right) (v_2 - v_1)$$

Example 2.12 improved Howland circuit.

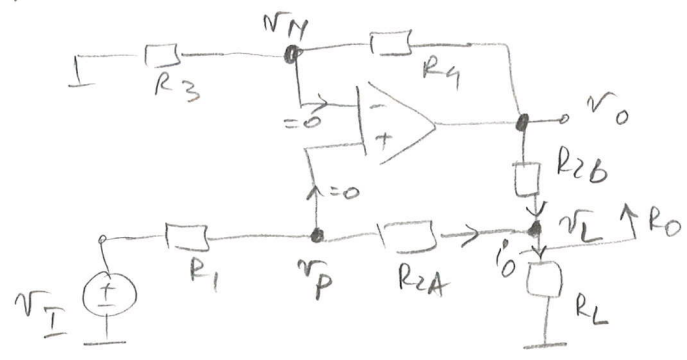

Prove that when:  $\frac{R_4}{R_3} = \frac{R_{2A} + R_{2B}}{R_1}$

- (a)  $R_o = \infty$
- (b)  $i_o = \frac{R_2}{R_1 \cdot R_{2B}} v_I$

(a) 
$$v_o = \left(1 + \frac{R_4}{R_3}\right) v_p = \left(1 + \frac{R_4}{R_3}\right) \cdot \frac{R_{2A} v_I + R_1 v_L}{R_1 + R_{2A}}$$

$$v_p = \frac{R_{2A}}{R_1 + R_{2A}} v_I + \frac{R_1}{R_1 + R_{2A}} v_L$$
 by superposition.

KCL at  $v_L$ : 
$$i_o = \frac{v_I - v_L}{R_1 + R_{2A}} + \frac{v_o - v_L}{R_{2B}} = v_I \left(\frac{1}{R_1 + R_{2A}}\right) - v_L \left(\frac{1}{R_1 + R_{2A}} + \frac{1}{R_{2B}}\right) + \frac{v_o}{R_{2B}} =$$

$$= v_I \left[ \frac{1}{R_1 + R_{2A}} + \frac{1}{R_{2B}} \left(1 + \frac{R_4}{R_3}\right) \cdot \frac{R_{2A}}{R_1 + R_{2A}} \right] - v_L \left[ \frac{1}{R_1 + R_{2A}} + \frac{1}{R_{2B}} - \frac{1}{R_{2B}} \cdot \left(1 + \frac{R_4}{R_3}\right) \cdot \frac{R_1}{R_1 + R_{2A}} \right]$$

$\Delta \frac{1}{R}$  because for  $v_I = 0$  we get:  $i_o = -\frac{v_o}{R_o}$

$\Delta \frac{1}{R_o} = \frac{v_I}{R} - \frac{v_L}{R_o}$  This is key trick!

related because  $R_o = \frac{v_L}{-i_o}$  !

$$\frac{1}{R} = \frac{R_3 R_{2B} + R_{2A} (R_3 + R_4)}{R_{2B} R_3 (R_1 + R_{2A})} = \frac{R_{2A} R_4 + R_3 (R_{2A} + R_{2B})}{R_{2B} R_3 (R_1 + R_{2A})}$$

$$\frac{1}{R_o} = \frac{R_{2B} + \cancel{R_1} - R_{2A} - \left(1 + \frac{R_4}{R_3}\right) R_1}{R_{2B} (R_1 + R_{2A})} = \frac{R_{2A} + R_{2B} - \frac{R_4}{R_3} R_1}{R_{2B} (R_1 + R_{2A})} = \frac{\frac{R_{2A} + R_{2B}}{R_1} - \frac{R_4}{R_3}}{R_{2B} \left(1 + \frac{R_{2A}}{R_1}\right)}$$



we can see that  $R_o \rightarrow \infty$  if  $\frac{R_{2A} + R_{2B}}{R_1} - \frac{R_4}{R_3} = 0$  !  $\Rightarrow \frac{R_2}{R_1} = \frac{R_4}{R_3}$  where

(b)  $\left[ R_{2A} + R_{2B} \triangleq R_2 \right] \Rightarrow R_o = \frac{R_3 R_{2B} (R_1 + R_{2A})}{R_3 R_2 + R_{2A} R_4} = \frac{R_3 R_{2B} (R_1 + R_{2A})}{\left(\frac{R_4 R_1}{R_2} + R_{2A} R_4\right)} = \frac{R_3 R_{2B} (R_1 + R_{2A})}{R_4 (R_1 + R_{2A})} = \frac{R_3 R_{2B}}{R_4}$

Finally: 
$$i_o = \frac{v_I}{R_o} = \frac{R_4}{R_3} \cdot \frac{1}{R_{2B}} \cdot v_I$$
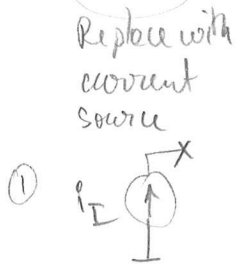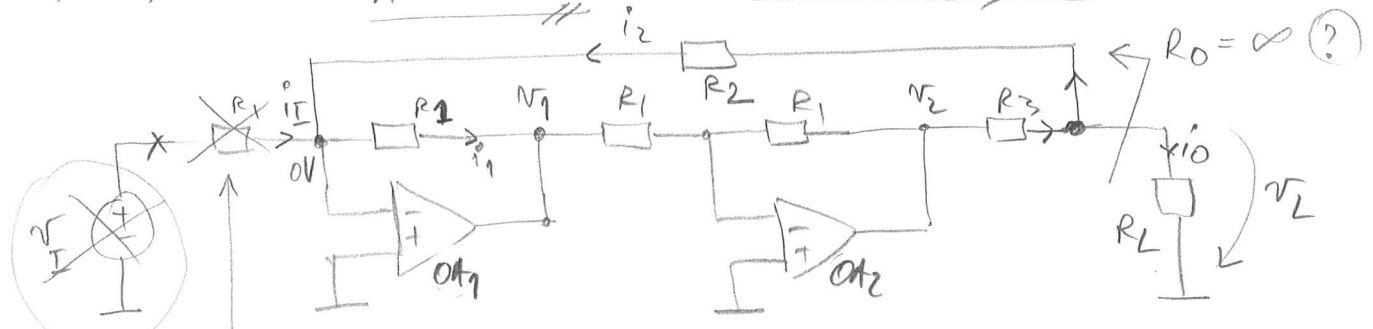
### Example 2.24

Modify given circuit so that it becomes a current amplifier with  $R_i = 0$ ,  $A = 10 \text{ A/A}$ ,  $R_o = \infty$ . Assume ideal Opamps.



this will make  $R_i = 0$ .

3) By superposition:

$$v_1 = -R_1 i_I - R_1 \left( \frac{v_L}{R_2} \right) = i_2$$

4)

$$v_2 = -v_1 = R_1 i_I + \frac{R_1}{R_2} v_L$$

$$i_o = \frac{v_2 - v_L}{R_3} - \frac{v_L}{R_2} = \frac{1}{R_3} \left( R_1 i_I + \frac{R_1}{R_2} v_L \right) - \left( \frac{1}{R_3} + \frac{1}{R_2} \right) v_L$$

needed this  $\frac{1}{R_2}$  to introduce  $R_o$ !

$$i_o = \frac{R_1}{R_3} i_I + \left[ \frac{R_1}{R_2 R_3} - \frac{R_2 + R_3}{R_2 R_3} \right] v_L = \frac{R_1}{R_3} i_I - \left[ \frac{R_2 + R_3}{R_2 R_3} - \frac{R_1}{R_2 R_3} \right] v_L$$

$\triangleq \frac{1}{R_o}$  that is some key trick!


because:  $i_o = \frac{-v_L}{R_o} \Big|_{i_I=0}$

$\Rightarrow$  To get  $R_o = \infty$  we need:  $R_1 = R_2 + R_3$

Also, To get a gain of  $A = 10 \frac{\text{A}}{\text{A}}$  we need:  $\frac{R_1}{R_3} = 10$

Use  $R_1 = 10k$ ,  $R_3 = 1k$  and  $R_2 = 9.09k$

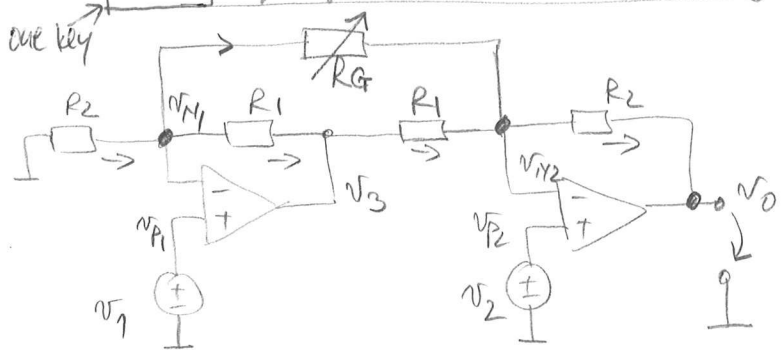Example 2.38 (Figure 2.24, pp. 83)  
 Dual Op Amp IA with variable gain



$$v_0 = A(v_2 - v_1)$$

$$A = 1 + \frac{R_2}{R_1} + \frac{2R_2}{R_G}$$

(a)

$$v_{N1} = v_{P1} = v_1$$

$$v_{N2} = v_{P2} = v_2$$

KCL:  $\frac{v_0 - v_1}{R_2} = \frac{v_1 - v_2}{R_G} + \frac{v_1 - v_3}{R_1}$  want to get rid of!

KCL:  $\frac{v_2 - v_0}{R_2} = \frac{v_1 - v_2}{R_G} + \frac{v_3 - v_2}{R_1}$  add. equations.

$$\frac{v_2 - v_1}{R_2} - \frac{v_0}{R_2} = 2 \frac{v_1 - v_2}{R_G} + \frac{v_1 - v_2}{R_1}$$

$$(v_2 - v_1) \left( \frac{1}{R_2} + \frac{1}{R_1} + \frac{2}{R_G} \right) = \frac{1}{R_2} v_0$$

$$v_0 = \left( 1 + \frac{R_2}{R_1} + 2 \frac{R_2}{R_G} \right) (v_2 - v_1)$$

however gain does not vary linearly with  $R_G$ .

(b) specify components to get:  $10 \text{ V/V} \leq A \leq 100 \text{ V/V}$  by means of  $10 \text{ k}\Omega$ .


Let  $R_G = R_{GA} + R_{GB} = 10 \text{ k}\Omega$

Let arbitrarily  $\frac{R_2}{R_1} = 1 \Rightarrow A = 2 \left( 1 + \frac{R_2}{R_G} \right)$ .

$$5 \leq \left( 1 + \frac{R_2}{R_G} \right) \leq 50 \Rightarrow 4 \leq \frac{R_2}{R_G} \leq 49$$


$$\left. \begin{array}{l} \text{case: } R_G = 0 + R_{GB} \Rightarrow \frac{R_2}{R_{GB}} = 49 \\ \text{case: } R_G = 10 + R_{GB} \Rightarrow \frac{R_2}{10 + R_{GB}} = 4 \end{array} \right\} \Rightarrow \left\{ \begin{array}{l} R_{GB} = 889 \Omega \text{ (use } 887 \Omega, 1\%) \\ R_2 = 49 R_{GB} = 43.5 \text{ k}\Omega = R_1 \\ \text{(use } R_1 = R_2 = 43.2 \text{ k}\Omega, 1\%) \end{array} \right.$$

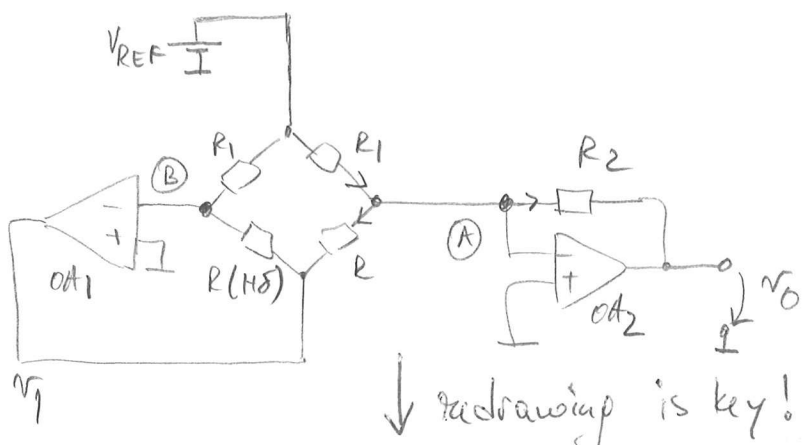Example Problem 2.49 Simple transducer circuit with linear response



$$v_0 = \frac{R_2}{R_1} \delta \cdot V_{REF}$$

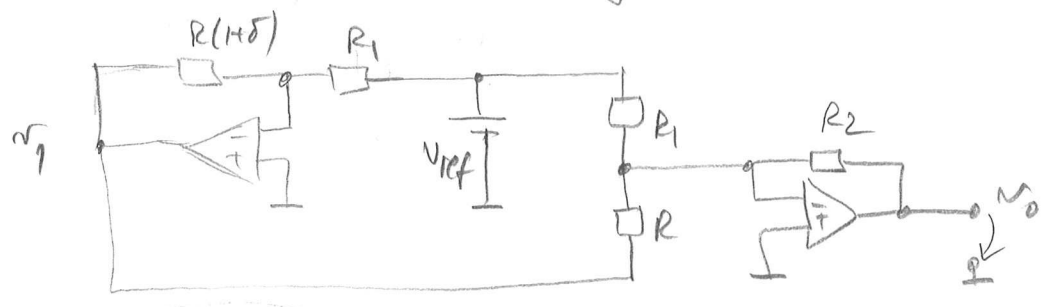redrawing is key! to notice configuration.



$$v_1 = - \frac{R(1+\delta)}{R_1} V_{ref}$$

By superposition:

$$v_0 = - \frac{R_2}{R_1} V_{ref} - \frac{R_2}{R} v_1 = - \frac{R_2}{R_1} V_{ref} + \frac{R_2}{R} \cdot \frac{R}{R_1} (1+\delta) V_{ref}$$

$$v_0 = V_{ref} \left( - \frac{R_2}{R_1} + \frac{R_2}{R_1} (1+\delta) \right) = \frac{R_2}{R_1} \delta \cdot V_{ref}$$

$$v_0 = \frac{R_2}{R_1} \delta \cdot V_{ref}$$