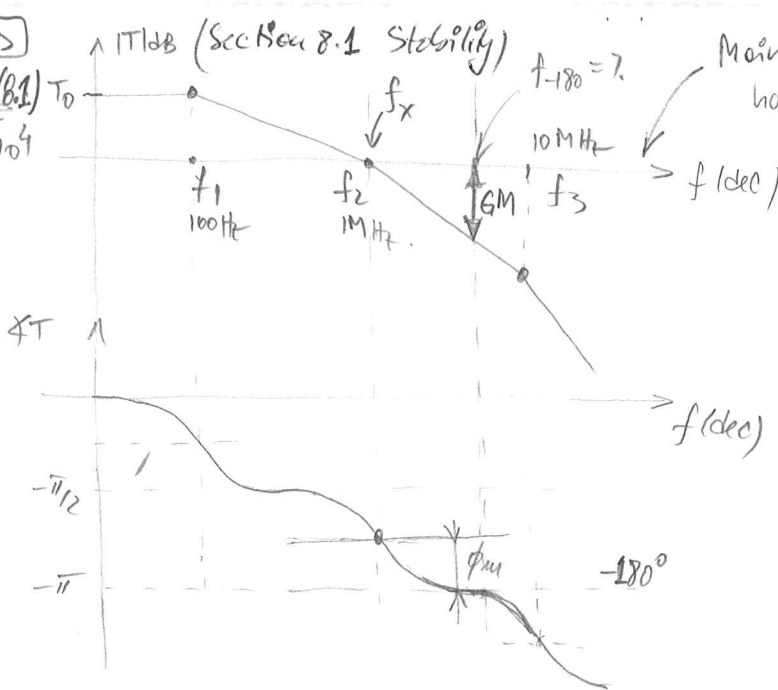


Ch8 Examples

Example (B.1)

$T_0 = 10^4$



Main idea for $|T|$ here to have 2nd, 3rd, ... poles below zero dB line!
 $f_1 = 100 \text{ Hz}$
 $f_2 = 1 \text{ MHz}$
 $f_3 = 10 \text{ MHz}$
 $T_0 = 10^4$

- (a) $GM = ?$
- (b) $\phi_m = ?$
- (c) $T_0 = ?$ for $\phi_m = 60^\circ$

(a) to find GM we need $f_{-180} = ?$ to plug into: $GM = 20 \log \frac{1}{|T(jf_{-180})|}$

where $|T(jf)| = \frac{T_0}{\sqrt{1 + (\frac{f}{f_1})^2} \cdot \sqrt{1 + (\frac{f}{f_2})^2} \cdot \sqrt{1 + (\frac{f}{f_3})^2}}$ (1)

1) Clearly: $f_2 < f_{-180} < f_3$

2) Start with a guess $f_{-180}^1 = 5 \text{ MHz}$
 & use (2) to compute

$\phi_T(jf_{-180}^1) = -195.3^\circ$ too low

b) Update guess $f_{-180}^2 = 3 \text{ MHz}$, & use (2) to compute

$\phi_T(jf_{-180}^2) = -178.3^\circ$ too small

c) Update guess $f_{-180}^3 = 4 \text{ MHz} \dots$

$f_{-180} = 3.16 \text{ MHz} \Rightarrow GM = 20 \log \frac{1}{|T(jf_{-180})|} = 20 \log \frac{1}{1.04 \cdot 10^{-3}}$

$GM = 20.82 \text{ dB}$

(b) Need to find $f_x = ?$

We see that a) $f_x^1 = f_2 = 1 \text{ MHz} \Rightarrow$ Use (1) to get: $|T(jf_x^1)| = 0.7036$ too small

b) $f_x^2 = 700 \text{ kHz} \Rightarrow |T(jf_x^2)| = 1.167$ too large

$f_x = 784 \text{ kHz} \Rightarrow \phi_m = 47.5^\circ$

(c) $\phi_{m} = 60^\circ$ we want $|T(jf_{-120})| = 1$

We can find by trial and error: $f_{-120} = 572 \text{ kHz} \Rightarrow T_0 = 5760$ down from $T_0 = 10^4$.

Comments: HW #7: 8.6 8.16 8.26 8.36
 HW #8: 8.4 8.30 8.37

Example 2: (Prob. 8.11) (Section 8.2 Stability of constant-GM op amp circuits)

An OpAmp with $a(jf) = \frac{10^5}{1+jf/10}$ placed in a negative feedback with

$$\beta(jf) = \frac{\beta_0}{(1+jf/10^5)^2}$$

Find β_0 (a) corresponding to the onset of oscillatory behaviour.

(b) $\phi_m = 45^\circ$


(c) GM = 20 dB

$$|T(jf)| = \frac{10^5 \beta_0}{\sqrt{1+(f/10)^2} \cdot [1+(f/10^5)^2]} \quad (3)$$

$$T(jf) = a(jf) \cdot \beta(jf) = \frac{10^5 \beta_0}{(1+jf/10)(1+jf/10^5)^2}$$

↑ double pole!
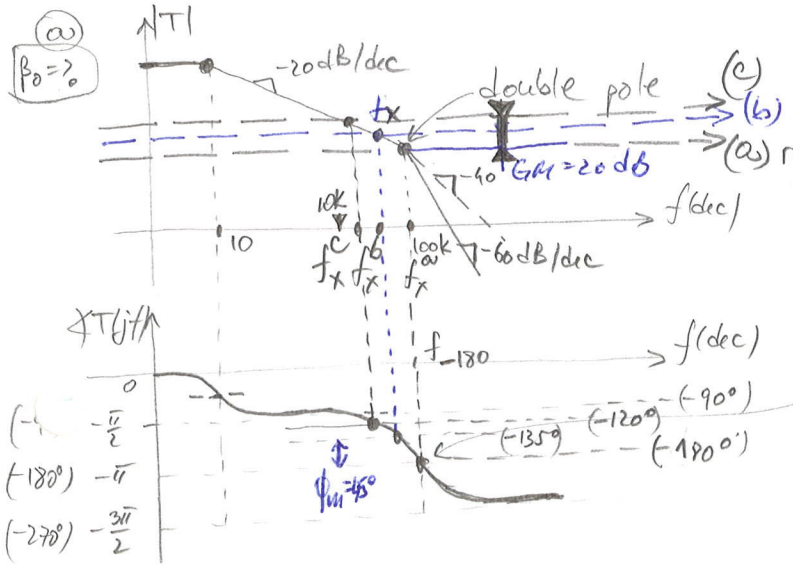
$$\angle T(jf) = -[\tan^{-1}(f/10) + \tan^{-1}(f/10^5) + \tan^{-1}(f/10^5)] = -[\tan^{-1}(f/10) + 2 \tan^{-1}(f/10^5)] \quad (2)$$



(a) $\beta_0 = ?$
 (b) required 0 dB axis for $\phi_m = 45^\circ$
 (c) required to be on the onset of oscillations!

phase $\angle T(jf)$ crosses -180° exactly at $f_{-180} \approx 100 \text{ kHz}$, the double pole freq.
 where $|T| \approx \frac{10^5 \beta_0}{10^4 \cdot (1+1^2)} = 5\beta_0$
 The onset of oscillations occurs for $|T|=1 \Rightarrow \beta_0 = \frac{1}{5} = 0.2 \text{ V/V}$

b) $\beta_0 = ?$

$\phi_{m} = 45^\circ \Rightarrow f_x = f_{-135^\circ} = 41.4 \text{ kHz}$

found by trial and error as in example 1 (Example 8.1 page 350)

$\Rightarrow |T(jf)| \Big|_{f_x = 41.4 \text{ kHz}} = 20.6 \beta_0 \Rightarrow \beta_0 = \frac{1}{20.6} \text{ V/V}$


c) $\beta_0 = ?$

$GM = 20 \text{ dB} \Rightarrow f_x = f_{-120^\circ} = 26.8 \text{ kHz}$

$\Rightarrow |T(jf)| \Big|_{f_x = 26.8 \text{ kHz}} = 34.8 \beta_0 \Rightarrow \beta_0 = \frac{1}{34.8} \text{ V/V}$

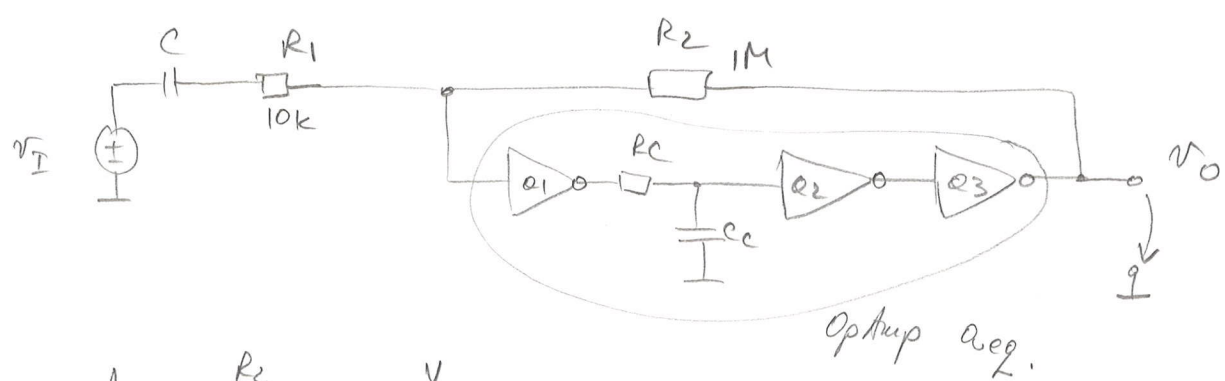Example 3 (8.29) (Section 8.3 internal freq. compensation)

- 3 CMOS inverters cascaded to create an OpAmp.
- inverting configuration: $A_v = -100 \text{ V/V}$



$A_v = -\frac{R_2}{R_1} = -100 \text{ V/V}$


$\omega_1 = \omega_2 = \omega_3 = -\frac{10^2}{1 - j \cdot f/10^5}$

a) if $R_c = C_c = 0 \Rightarrow$ circuit is unstable

b) $R_c = ?$ $C_c = ?$ such that $\phi_m = 45^\circ$

(a) $R_C = C_C = 0 \Rightarrow a_{ef} = 0, a_2 a_3 = -\frac{10^6}{(1+jf/10^5)^3}$

(4)

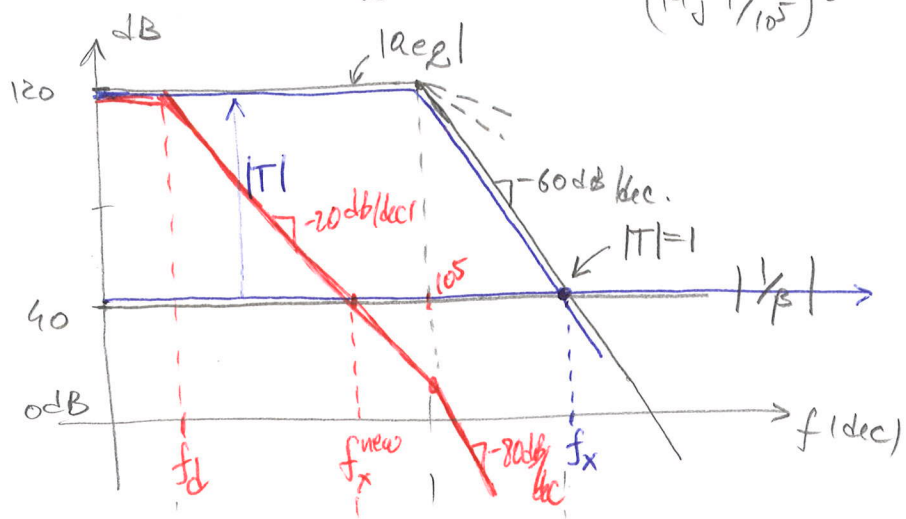


$\frac{1}{\beta} = 1 + \frac{R_2}{R_1} = 101 \approx 40 \text{ dB}$

Using the rate of closure (ROC) technique, we get (page 353)

$ROC = |\text{Slope}(|a_{ef}|) - \text{Slope}(|1/\beta|)| \Big|_{f=f_x} = |-60 \text{ dB/dec} - 0| = 60 \text{ dB/dec}$

(Eq. 8.9) $\Rightarrow \phi_m \approx -90^\circ, \Rightarrow \text{unstable!}$

Alternatively: draw $\angle T(jf)$

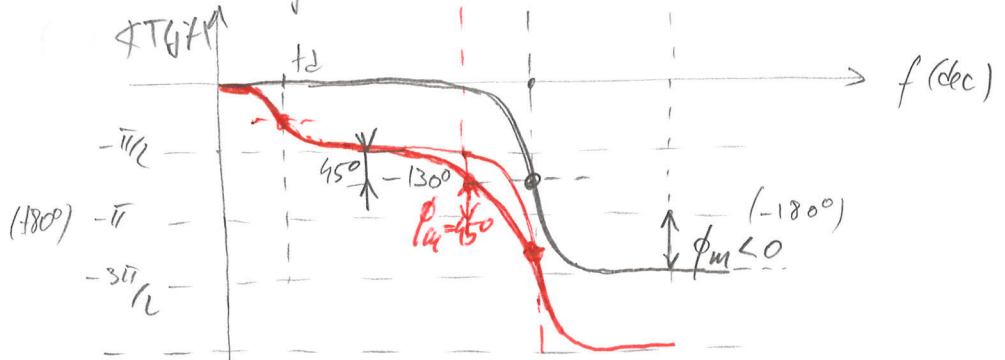

(b) We introduce a dominant pole at f_d and want a phase margin $\phi_m = 45^\circ$

- f_d introduces (or contributes) -90° at $f = f_x^{\text{new}}$
 - we want $\phi_m = 45^\circ$
- \Rightarrow the phase contribution


of $a_{ef}(jf) \Big|_{f=f_x^{\text{new}}}$ should be -45° . Since a_{ef} has 3 identical poles, the contribution of each pole at f_x^{new} must be $-\frac{45^\circ}{3} = -15^\circ$

\Rightarrow impose $-15^\circ = \tan^{-1} \frac{f_x^{\text{new}}}{10^5} \Rightarrow \boxed{f_{x\text{new}} = 26.8 \text{ kHz}}$

Finally, $f_d = \frac{f_x^{new}}{\beta \cdot a_{00}} = \frac{26.8 \times 10^3}{\left(\frac{10^6}{101}\right)} = 2.7 \text{ Hz}$

\Rightarrow Use $C_c = 100 \text{ nF}$ & $R_0 = 620 \text{ k}\Omega$

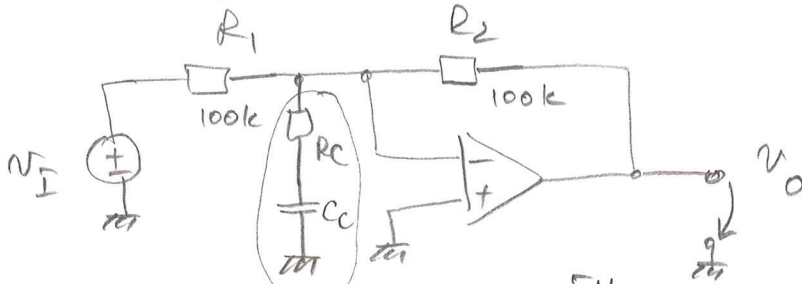
Example 4: (8.35) (Section 8.4 External freq. compensation)



input-lag compensation!
 $\omega_0 = 10^5 \text{ rad/s}$
 $f_1 = 10 \text{ kHz}$
 $f_2 = 3 \text{ MHz}$
 $f_3 = 30 \text{ MHz}$

$$\rightarrow a(jf) = \frac{10^5}{(1+jf/10^4)(1+jf/3 \cdot 10^6)(1+jf/30 \cdot 10^6)}$$

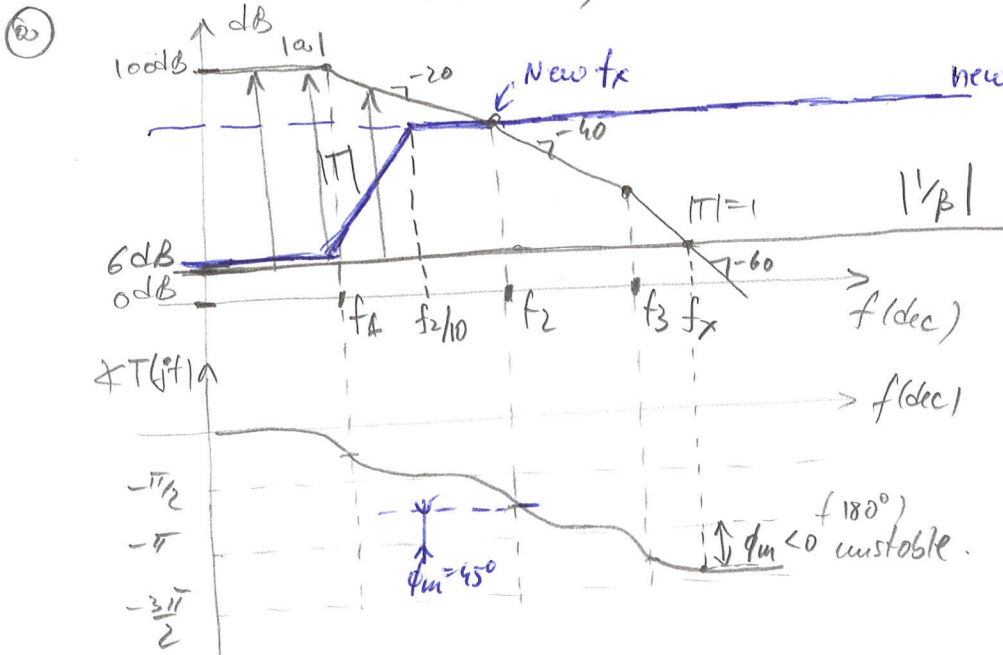(2) Use input-lag compensation to stabilize for $\phi_{min} = 45^\circ$ (Find $A(jf)$) (see page 375)



(See Fig. 8.25) (page 376)

$$\frac{1}{\beta} = 1 + \frac{R_2}{R_1} = 2 \approx 6 \text{ dB}$$

Use eq. (8.30) to get:

$$R_c = \frac{R_2}{|a(jf_2)| - (1 + \frac{R_2}{R_1})} = \frac{100 \text{ k}\Omega}{234.5 - (1 + \frac{100}{100})} \approx \boxed{430 \Omega}$$

Use eq. (8.31) to get:

$$C_c = \frac{5}{\pi R_c f_2} = \frac{5}{\pi \cdot 430 \cdot 3 \cdot 10^6} \approx \boxed{1.2 \text{ nF}}$$

6) $A(jf) = ?$

Refer to fig. 8.25b and note that for $f < f_2/10$, $|T|$ is fairly large, indicating that $A(jf) \cong A_{ideal} = -1 \frac{V}{V}$.

for $f > f_2/10$ we can write $\left\{ \begin{array}{l} 1/\beta \cong |a(jf_2)| \\ a(jf) \cong \frac{a_0}{(j\frac{f}{f_1})(1+j\frac{f}{f_2})(1+j\frac{f}{f_3})} \end{array} \right. \Rightarrow$

$\rightarrow \frac{1}{T} = \frac{1}{a\beta} \cong \frac{|a(jf_2)|}{a_0} \cdot (j\frac{f}{f_1})(1+j\frac{f}{f_2})(1+j\frac{f}{f_3})$

$\Rightarrow A(jf) = A_{ideal} \times \frac{1}{1 - \frac{1}{T}} = (-1) \times \frac{1}{1 + (j\frac{f}{f_2})(1+j\frac{f}{f_2})(1+j\frac{f}{f_3})}$

use fact:
 $|a(jf_2)| \cdot f_2 = a_0 \cdot f_1$


or: $A(jf) = - \frac{1}{1 + j\frac{f}{f_2} - (\frac{f}{f_2})^2 + (j\frac{f}{f_3}) [j\frac{f}{f_2} - (\frac{f}{f_2})^2]}$

in the neighborhood of f_2 ($f_2 \ll f_3$) we can approximate:

$A(jf) \cong \frac{-1}{1 + j\frac{f}{f_2} - (\frac{f}{f_2})^2} = -H_{LP} \quad f_0 = f_2, Q = 1$

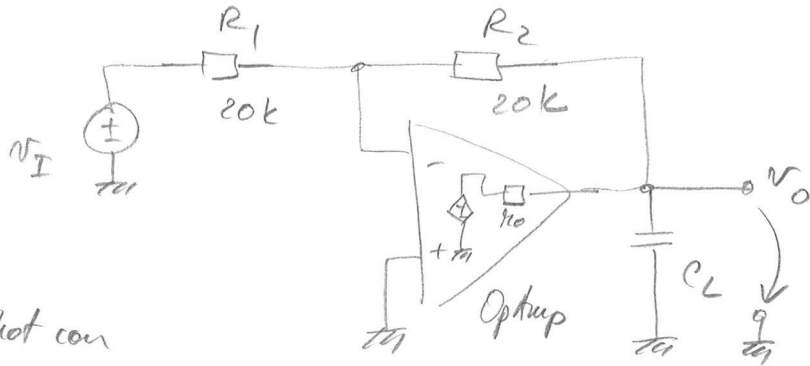Example 5

$f_t = 10 \text{ MHz}$
 $f_b = 1 \text{ Hz}$
 $\eta_0 = 100 \mu\text{s}$



Find maximum C_L that can be connected at the output and still allow a phase margin of $\phi_m \geq 45^\circ$


$$a(jf) \approx \frac{a_0}{j + f/f_b}$$

$$a_0 \cdot f_b = 1 \cdot f_t \Rightarrow a_0 = 10^7$$

C_L introduces a pole f_p ignoring the loading of the feedback network, the loaded gain is:

$$a_{\text{loaded}} \approx a \cdot \frac{1}{1 + jf/f_p} = \frac{a_0}{j + f/f_b} \cdot \frac{1}{1 + jf/f_p}$$

where $f_p = \frac{1}{2\pi \eta_0 C_L}$

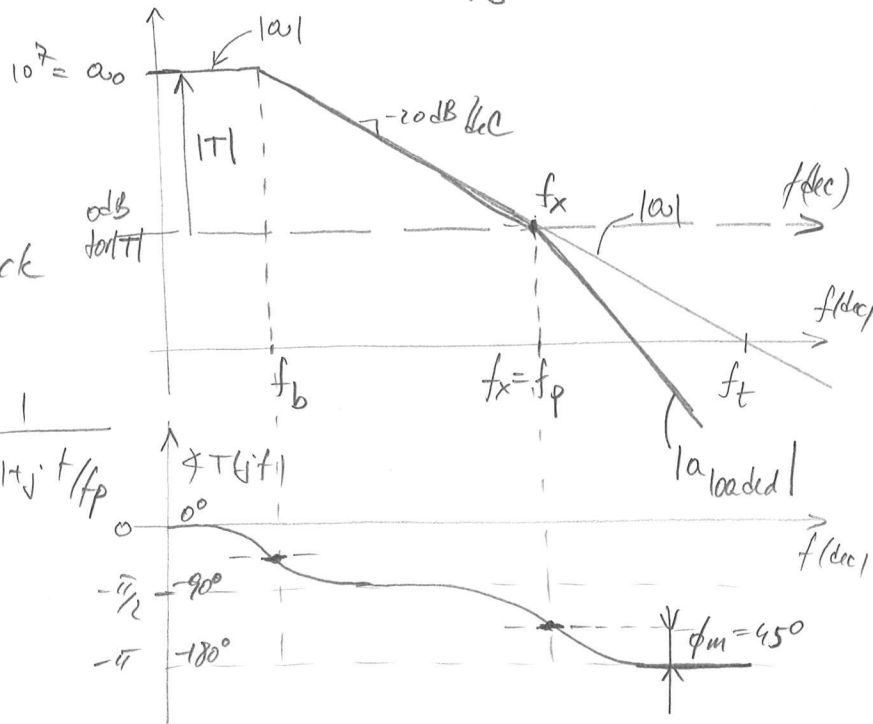

$$T(jf) = a(jf) \cdot \beta = \frac{a_0}{j + f/f_b} \cdot \frac{R_1}{R_1 + R_2}$$

From Bode diagram, impose crossover frequency $f_x \leq f_p$ at which $|T(jf_x)| = 1$ for equality.

$$|T(jf_x)| = 1 \Leftrightarrow \frac{a_0}{\left(\frac{f_x}{f_b}\right) \cdot \sqrt{1+1}} \cdot \frac{R_1}{R_1 + R_2} = 1 \Rightarrow f_x = \frac{a_0 f_b}{\sqrt{2}} \cdot \frac{R_1}{R_1 + R_2}$$

$$f_p = \frac{1}{2\pi \eta_0 C_L}$$

$$\Rightarrow \frac{a_0 f_b}{\sqrt{2}} \cdot \frac{R_1}{R_1 + R_2} \leq \frac{1}{2\pi \eta_0 C_L} \Rightarrow C_L \leq 318 \text{ pF}$$