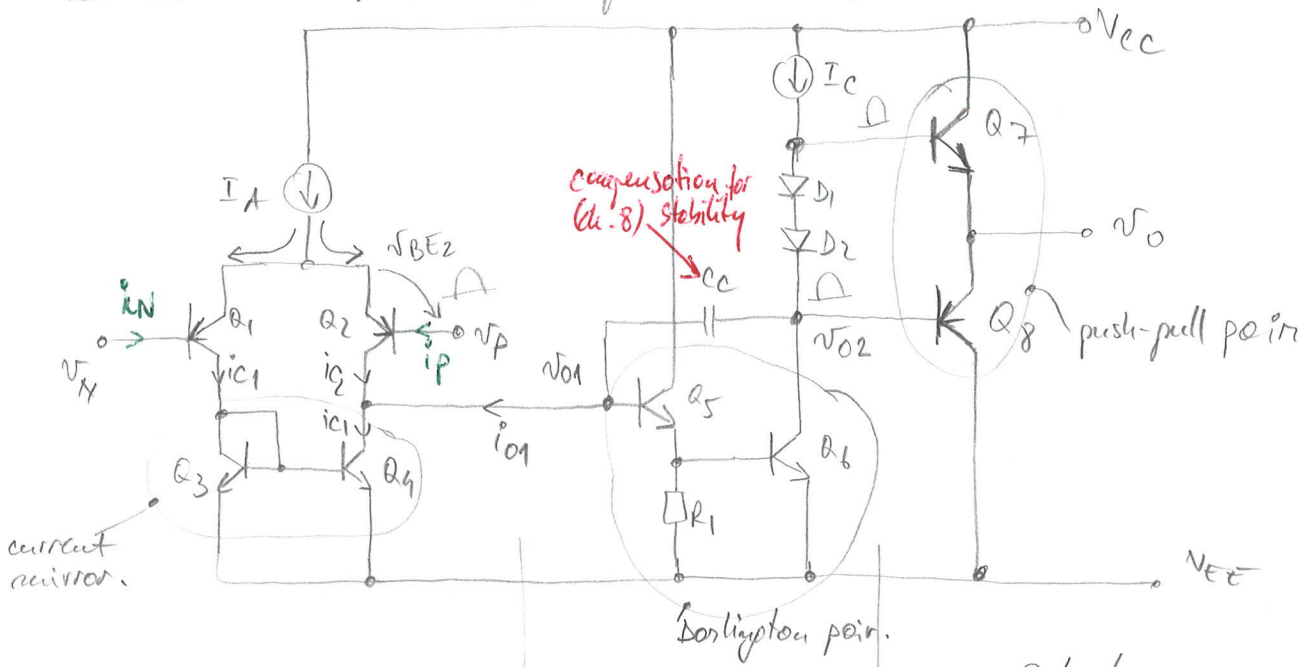
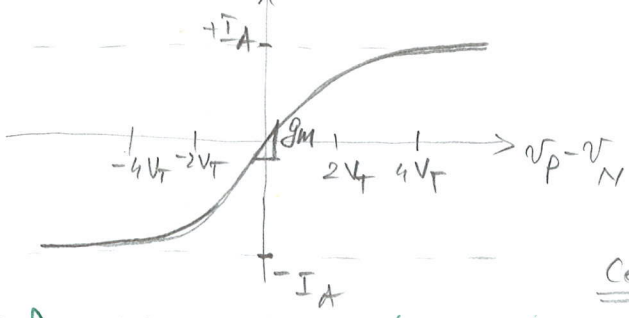


Ch. 5. 5.1 Simplified Op amp Circuit diagram



← Input stage → Provide high input impedance and small i_P/i_N
 ← Second stage → provide more gain and signal swing!
 ← Output stage → Provide low output impedance!



$$i_{O1} = g_{m1} (v_P - v_N) \quad (1)$$

↑
input stage transconductance.

Assume $v_N = \text{const}$ stays &

Case 1:

$$v_P \uparrow \Rightarrow v_{BE2} \downarrow \Rightarrow \begin{cases} i_{C1} \uparrow \\ i_{C2} \downarrow \end{cases}$$

$$i_{O1} = i_{C1} - i_{C2}$$

$\Rightarrow i_{O1} \uparrow \Rightarrow Q_5$ moves into off state
 $\Rightarrow v_{O2} \uparrow \Rightarrow \begin{cases} Q_8 \rightarrow \text{off} \\ Q_7 \rightarrow \text{sat.} \end{cases}$
 $\Rightarrow v_{CEQ7} \rightarrow 0.1 \Rightarrow v_O \uparrow$

Case 2: $v_P \downarrow \Rightarrow \dots \Rightarrow v_O \downarrow$

② Pay attention to the small range of $v_P - v_N$ for which we have linear gain!

It can be shown:

$$i_{O1} = I_A \tanh \frac{v_P - v_N}{2V_T} \quad (2)$$

Thermal voltage $V_T \approx 26\text{mV}$ at room temperature.

From (1) & (2) $\Rightarrow \left[g_{m1} \triangleq \frac{di_{O1}}{d(v_P - v_N)} \right]_{v_P = v_N} = \frac{I_A}{2V_T} \quad (3)$

Note: See book by P. Gray for nice analysis & discussion of this!

① "Key take-home" - The input currents i_P, i_N are different from 0. They are needed as the base current for forward biasing of Q_1, Q_2 !

- For the detailed analysis of this pt 741
see P.Gray's book { section 6.8. (both dc and small signal analysis)
 { Ch. 10 (Sedra & Smith)
- More on differential pairs (→ section 3.5 (P. Gray book)
 ↔ section 6.1 (Sedra & Smith)
- More on the Darlington pair (→ section 3.4 (P. Gray book)
 ↔ popl (675) (Sedra & Smith)
 ↔ popl (544)
- More on the push-pull output stage (→ section 5.4 (P. Gray book)
 ↔ section (9.595) Sedra & Smith)