

Examples from ch. 5 & 6. (also see examples to st. notations of ch. 6.)

Example 5.6

Reminder: input offset voltage V_{OS} can be written as in the general expression, in terms of different operating changes affecting it:

$$V_{OS} = V_{OS\phi} + TC(V_{OS}) \cdot \Delta T + \frac{\Delta v_{CM} \approx v_P}{CMRR} + \frac{\Delta V_S}{PSRR} + \frac{\Delta v_O}{a}$$

initial input offset voltage (due to mismatches in the input stage)

because V_{OS} varies w/ temperature. All characteristics of transistors vary with T !

models the variation of v_O as a consequence of the change in v_{CM} (which alters the mismatches)

similar to the prev. one but due to changes in power supply voltage.

related to changes in $v_P - v_N = v_D$ due to changes in v_O because a of the $OpAmp$ is finite.

The $OpAmp$ has the ratings:

$$\left\{ \begin{array}{l} a = 10^5 \text{ V/V} \quad a_{min} = 10^4 \text{ V/V} \\ TC(V_{OS})_{avg} = 3 \mu\text{V}/^\circ\text{C} \\ CMRR = PSRR = \begin{cases} 100 \text{ dB} & \text{typical} \\ 80 \text{ dB} & \text{minimum} \end{cases} \end{array} \right.$$

Find worst case and most probable change of V_{OS} over the following

$$\text{operating ranges: } \left\{ \begin{array}{l} 0^\circ\text{C} \leq T \leq 70^\circ\text{C} \\ V_S = \pm 15\text{V} \pm 5\% \\ -1 \leq v_P \leq 1 \text{ V} \\ -5 \leq v_O \leq 5 \text{ V} \end{array} \right.$$

Thermal change from room temperature:

(1) $\Delta V_{OS1} = 3 \mu\text{V}/^\circ\text{C} \cdot (70 - 25)^\circ\text{C} = 135 \mu\text{V}$

$$\frac{1}{CMRR} = \frac{1}{PSRR} = \left\{ \begin{array}{l} 10^{-100/20} = 10 \mu\text{V/V} \text{ typical} \\ 10^{-80/20} = 100 \mu\text{V/V} \text{ maximum} \end{array} \right. \Rightarrow$$

Note: here we used definition of decibels:

$$CMRR_{dB} = 20 \log CMRR \Rightarrow \Rightarrow CMRR = 10^{\frac{CMRR_{dB}}{20}} = \frac{1}{CMRR} = 10^{-\frac{CMRR_{dB}}{20}}$$

(2) $\Rightarrow \left\{ \begin{array}{l} \Delta V_{OS2} = \frac{\Delta v_P}{CMRR} = \frac{\pm 1\text{V}}{CMRR} = \begin{cases} \pm 10 \mu\text{V} \text{ typical} \\ \pm 100 \mu\text{V} \text{ maximum} \end{cases} \end{array} \right.$

(3) $\Delta V_{OS3} = \frac{\Delta V_S}{PSRR} = \frac{2 \times (\pm 0.75)}{PSRR} = \begin{cases} \pm 15 \mu\text{V} \text{ typical} \\ \pm 150 \mu\text{V} \text{ maximum} \end{cases}$

(4) $\Delta V_{OS4} = \frac{\pm 5\text{V}}{a} = \begin{cases} \pm 5 \mu\text{V} \text{ typical} \\ \pm 500 \mu\text{V} \text{ maximum} \end{cases}$

Hence:

(a) worst case Vos change is:

$$\Delta V_{os} = \pm (135 + 100 + 150 + 500) \mu V = \pm 885 \mu V = \pm 0.885 mV$$

(b) Most probable Vos change is given by the root-mean-square (RMS):

$$\Delta V_{os} = \pm (135^2 + 100^2 + 150^2 + 500^2)^{\frac{1}{2}} = \pm 145 \mu V = \pm 0.145 mV$$

Example 6.2 page 265

- (a) Design an audio amplifier using $\mu A741$ opamps with a gain of 60 dB.
- (b) sketch its magnitude plot
- (c) Find actual bandwidth.

(a) $A_o^{dB} = 60 dB = 20 \log_{10} A_o \Rightarrow A_o = 10^{\frac{60}{20}} = 10^3 = 10^3 V/V$ required!

Bandwidth is $f_B \geq 20 kHz$ (audio) required!


By equation (6.14), page 265,

the gain-bandwidth product of the non-inverting OpAmp based amplifier is:

$$GBP = A_o f_B = f_t = 1 MHz \text{ for } \mu A741 \text{ OpAmp.}$$

$$\Rightarrow f_B = \frac{f_t}{A_o} = \frac{10^6}{10^3} = 10^3 Hz = 1 kHz < 20 kHz \text{ that is required!}$$

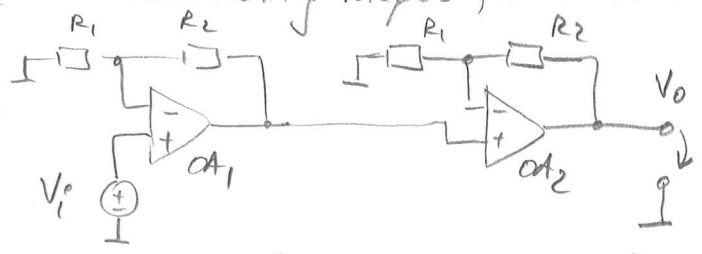\Rightarrow Cascade two noninverting stages, each with smaller gain but wider bandwidth!




Gain $A_1 = 1 + \frac{R_2}{R_1}$ Gain $A_2 = 1 + \frac{R_2}{R_1}$: make them equal for maximum bandwidth!!!

Total gain $A = A_1 \cdot A_2 = A_1^2 = 10^3 V/V$ required!
 $A_1 = A_2$

$$\Rightarrow A_1 = A_2 = \sqrt{1000} = 31.62 V/V \text{ or } 30 dB.$$

$$\text{Therefore: } f_{B1} = f_{B2} = \frac{10^6}{31.62} = 31.62 kHz > 20 kHz ! \text{ which is good!}$$

(b) $A = A_1^2 \Rightarrow |A|_{dB} = 2 \cdot |A_1|_{dB} \Rightarrow$ magnitude plot of A can be obtained by $\times 2$ that of A_1 !

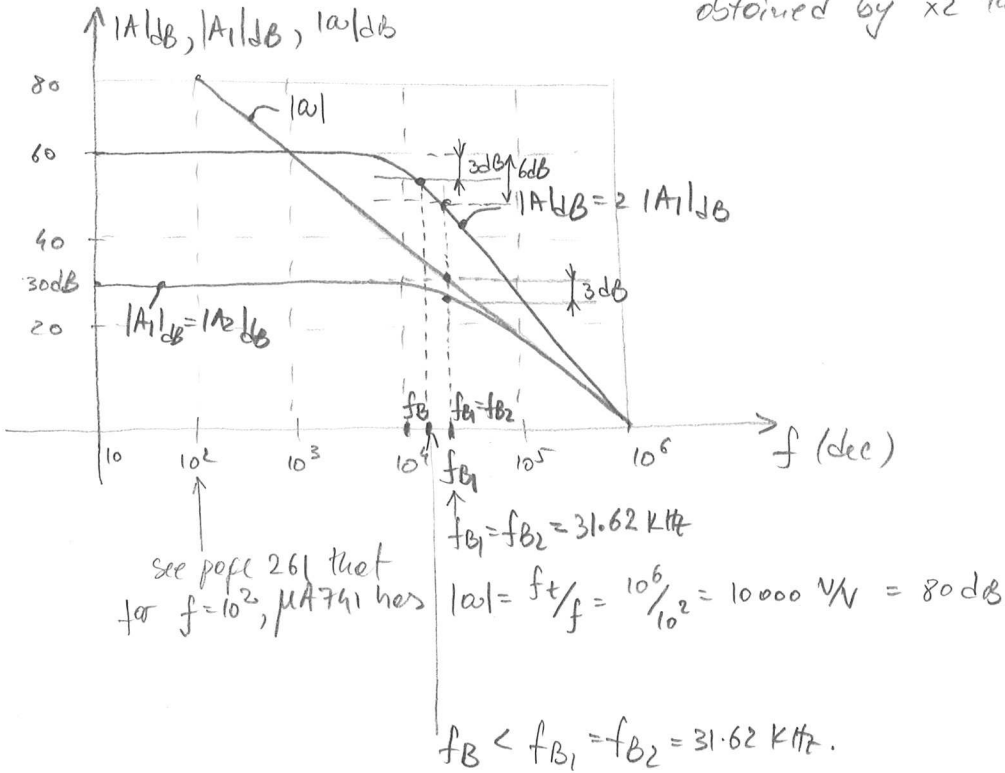

(c) but by definition, bandwidth is f_B for which gain decreases with 3dB!

$|A(f_B)| = \frac{10^3}{\sqrt{2}}$ must be equal to:

$$|A_1(f)| \Big|_{f=f_B} = \frac{31.62^2}{1 + \left(\frac{f_B}{f_{B1}}\right)^2} = \frac{31.62^2}{1 + \frac{f_B^2}{(31.62 \times 10^3)^2}} = \frac{10^3}{\sqrt{2}} \Rightarrow f_B = 31.62 \sqrt{\sqrt{2}-1} = 20.35 \text{ kHz}$$

$f_B = 20.35 \text{ kHz} > 20 \text{ kHz}$ that we needed! nice!

Example 6.3

→ Veri simulation with LTSpice!