


# Ch. 6. Dynamic OpAmp Limitations

## Part 2

Last time:

- Open loop opamp gain
- Unity gain  $f_t = \omega_0 \cdot f_b$
- Gain Bandwidth Product:
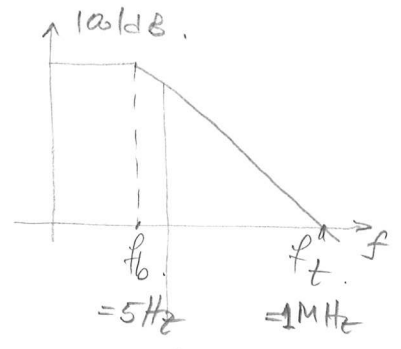
$$a(jf) = \frac{\omega_0}{1 + j \frac{f}{f_b}}$$



$$GBP = |a(jf)|_f \times f = f_t = \text{const.}$$

for  $f \gg f_b$  where opamp behaves as integrator



Today: First: (See previous notes)

- Questions: How does (1) affect the closed loop gains of
  - noninverting
  - inverting
- How does (1) affect the input/output impedances for configurations of the negative feedback:
  - series
  - shunt

Today: Second: { - Slew Rate (transient response)  
 - Current-feedback amplifiers.

6.4 Transient Response

Rise time

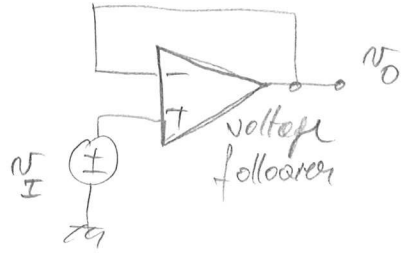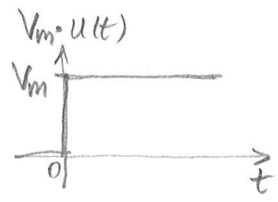

$A(jf) = \frac{1}{1 + j \frac{f}{f_t}}$  : transfer function.

Pole at  $s = -2\pi f_t$   
 $A(s) = \frac{\omega_t}{s + \omega_t}$  (remainder)

$v_I(t) = V_m \cdot u(t)$   
 $V_I(s) = \frac{V_m}{s}$


$\Rightarrow V_O(s) = V_m \cdot \frac{\omega_t}{s(s + \omega_t)} \Rightarrow$

$\Rightarrow V_O(s) = V_m \left[ \frac{1}{s} - \frac{1}{s + \omega_t} \right]$

$\Rightarrow v_O(t) = V_m \cdot [1 - e^{-\omega_t \cdot t}] \cdot u(t)$

$v_O(t) = V_{mi} \cdot [1 - e^{-2\pi f_t \cdot t}] \cdot u(t)$

$\omega_t = 2\pi f_t$

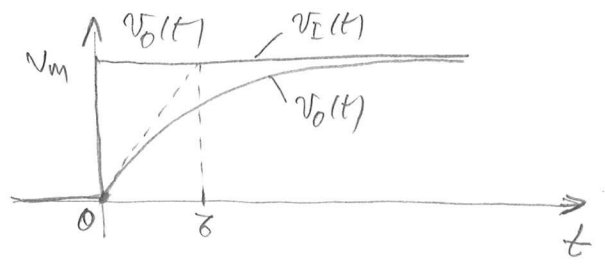

$\delta = \frac{1}{\omega_t} = \frac{1}{2\pi f_t}$

$t_R \triangleq$  Rise time  $\triangleq$  time for  $v_O$  to swing from 10% to 90% of  $V_{mi}$ .


$t_R = \delta [\ln(0.9) - \ln(0.1)] = \frac{0.35}{f_t} = t_R$  [sec]

The higher  $f_t$ , the lower  $t_R$ !

Example:  $\mu A741$   $t_R \approx 350$  ns.

Slew rate

"a measure of how fast the output can change"  
 $\frac{dv_O(t)}{dt} \Big|_{t=0} = \frac{V_{mi}}{\delta} \Rightarrow$  slope is proportional to  $V_{mi}$ .

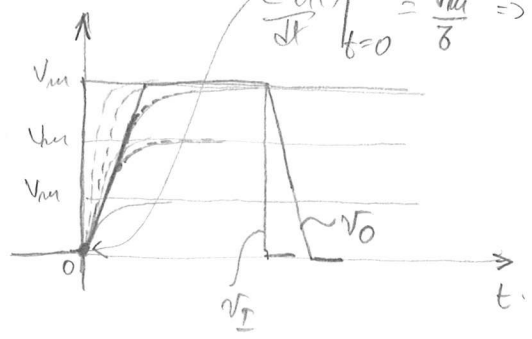

The rate at which  $v_O$  slew saturates to a constant value for increasing values of  $V_{mi}$ ! That value is called **slew rate**  $\triangleq$  **SR** [ $V/\mu\text{sec}$ ].

Ex:  $\mu A741$   $SR = 0.5 \frac{V}{\mu s}$

- SR is due to the limited current capabilities of charging/discharging  $C_c$  mainly.   
 *↑ gives a tradeoff between fast response and dominant-pole model/stability*
- Critical  $V_{om}$  output-step magnitude corresponding to the onset of slew-rate limiting is such that:

$$\frac{V_{om}(crit)}{s} = SR \Rightarrow V_{om}(crit) = \frac{SR}{2\pi f_t}$$

Example:  $V_{om}(crit) = 80mV$  for  $\mu A741$

② Full-power bandwidth

SR-limiting  $\Rightarrow$  output signal is distorted.

For a sin signal at input  $\Rightarrow v_0 = V_{om} \sin 2\pi f t$

$$\frac{dv_0}{dt} = 2\pi f \cdot V_{om} \cdot \cos 2\pi f t \Big|_{max} = 2\pi f V_{om}$$

We need:  $\left(\frac{dv_0}{dt}\right)_{max} \leq SR \Leftrightarrow 2\pi f V_{om} \leq SR$

$$f V_{om} \leq \frac{SR}{2\pi}$$

in order not to have distortions!

*trade-off between amplitude and frequency!*

Definition: FPB (full-power bandwidth) = maximum frequency at which the opamp will yield undistorted signal at the largest possible amplitude!

$$FPB = \frac{SR}{2\pi V_{set}}$$


Ex:  $\mu A741$

$$\begin{aligned} V_{set} &= 13V \\ SR &= 0.5 \frac{V}{\mu s} \end{aligned} \Rightarrow FPB = 6.1 kHz$$

① The settling time  $t_s$

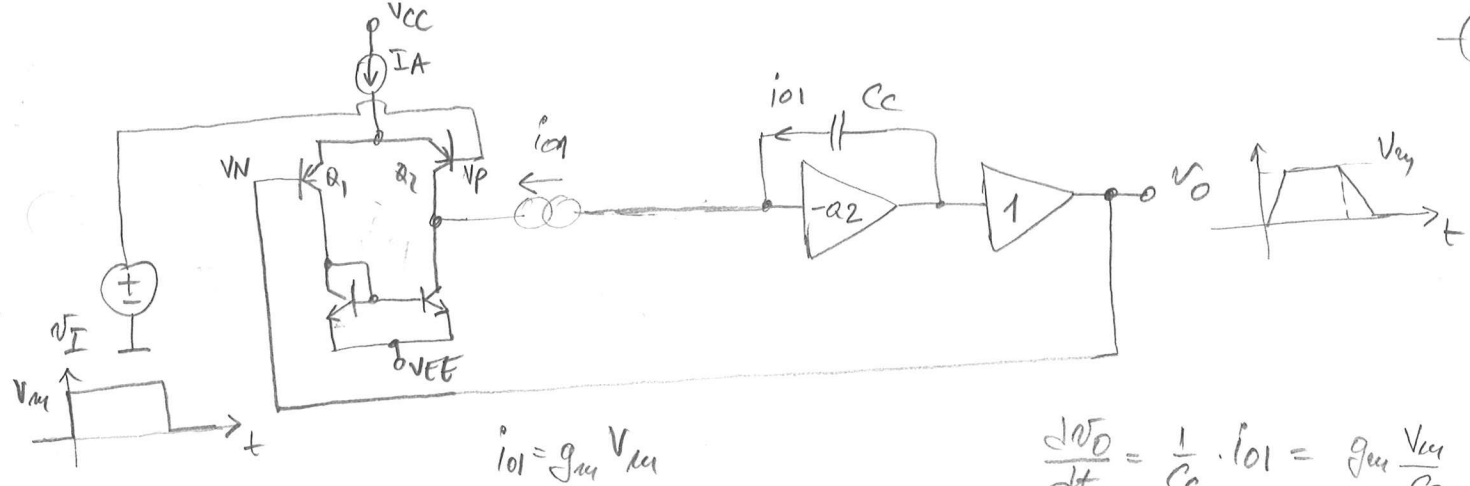Exercise!

③ SR-limiting: Races & Curves  $\rightarrow$  see next page!



$$i_{o1} = g_{m1} v_{in}$$

$$\frac{dv_o}{dt} = \frac{1}{C_c} \cdot i_{o1} = g_{m1} \frac{v_{in}}{C_c}$$

(1) - Low \$v\_{in} \Rightarrow \frac{dv\_o}{dt} = \frac{1}{C\_c} i\_{o1} = g\_{m1} \frac{v\_{in}}{C\_c}\$

(2) - If we overdrive input \$\Rightarrow Q\_1\$ or \$Q\_2\$ will saturate and conduct \$I\_A\$  
 \$\Rightarrow\$ Capacitor \$C\_c\$ will become current starved and

$$\left(\frac{dv_o}{dt}\right)_{max} = \frac{I_A}{C_c} = SR!$$

In previous lecture we had found (see eq. 6.8) \$f\_{cut}\$:

$$f_t = \frac{g_{m1}}{2\pi C_c} = \frac{I_A}{8qV_T C_c} \Rightarrow C_c = \frac{I_A}{8qV_T f_t} = \frac{g_{m1}}{2\pi f_t}$$

$$\Rightarrow SR = \frac{2\pi I_A f_t}{g_{m1}}$$

tells us how to improve SR!

- (a) increase \$f\_t\$
- (b) decrease \$g\_{m1}\$
- (c) increase \$I\_A\$.