

(1)

Examples

6.3. (problem 6.3 from textbook, page 303)

Constant GBP setup has
of fig. less than f_b .


Example 1:

(detektion in 2011)

$$a) f_x = ? \text{ at which } \angle \alpha = -60^\circ = \angle \alpha(jf_x) \quad |f_1|$$

$$b) f_x = ? \text{ at which } |\alpha| = 2 \text{ V/V}$$

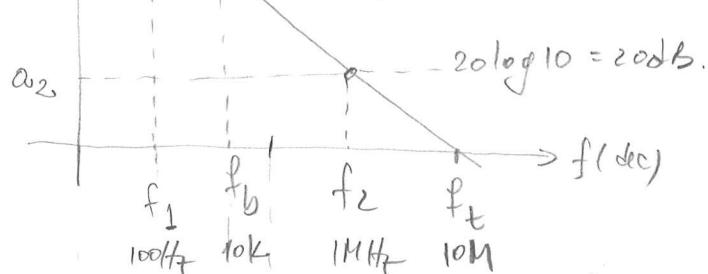Solution: ω_0 $\uparrow \omega_1 \text{ dB}$ $\dots 20 \log 10^3 = 60 \text{ dB}$




$$\text{GBP} = f_t = \alpha_f \cdot f = \omega_2 \cdot f_2 = 10 \cdot 1 \text{ MHz} = \boxed{10 \text{ MHz} = f_t}$$

$$\text{Also: } f_b = \frac{f_t}{\omega_0} = \frac{10 \text{ MHz}}{10^3} = \boxed{10 \text{ kHz} = f_b}$$

$$(a) \alpha(jf) = \frac{\omega_0}{1 + jf/f_b} \Rightarrow \angle \alpha = \angle \arg(f) = -\arctan\left(\frac{f}{f_b}\right) = -\tan^{-1}\left(\frac{f}{f_b}\right)$$

$$-60 = -\tan^{-1}\left(\frac{f_x}{f_b}\right)$$
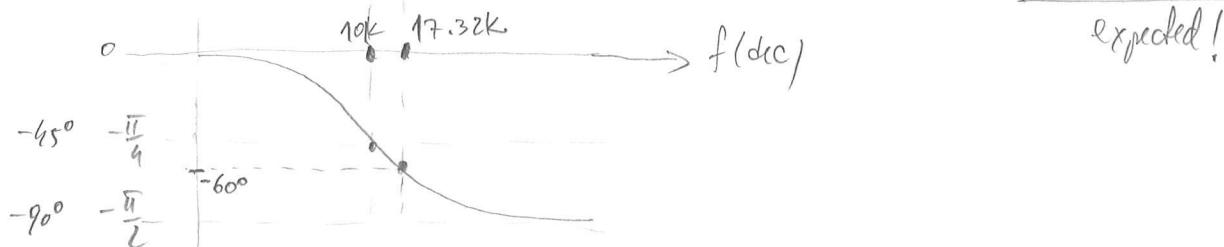
$$60 = \tan^{-1}\left(\frac{f_x}{10^4}\right) \Rightarrow \boxed{f_x = 17.32 \text{ kHz}}$$




$$(b) |\alpha(jf)| = \frac{\omega_0}{\sqrt{1 + \left(\frac{f}{f_b}\right)^2}} \Bigg|_{f=f_x} = 2 \frac{\text{V}}{\text{V}} \Rightarrow \left(\frac{\omega_0}{2}\right)^2 = 1 + \left(\frac{f_x}{f_b}\right)^2$$

$$\frac{10^6}{4} = 1 + \frac{f_x^2}{(10^4)^2} \Rightarrow \boxed{f_x = 5 \text{ MHz}}$$

6.8 Example 2

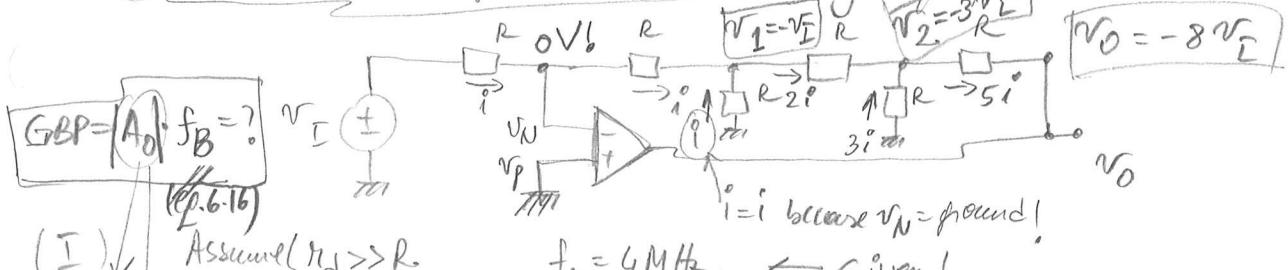(a) Find the closed-loop GBP of the inverting amplifier.



$$(I) \quad \text{Assume} \begin{cases} r_d > R \\ h_0 \ll r_s \end{cases}$$

$$f_t = 4 \text{ MHz.} \quad \leftarrow \text{Given!}$$

$$i^o = \frac{V_L}{R}$$

$$V_1 = -V_E, \quad V_2 = V_1 - R \cdot 21^\circ = -3V_E, \quad V_0 = V_2 - R \cdot 51^\circ = -8V_E$$

$$\Rightarrow A_{ideal}^o = -8 \frac{V}{N} = A_0$$

$$(II) f_B = \beta \cdot f_t \quad (\text{see q. 6.15(b)}).$$

$$f_B = 5 \Rightarrow = 4 MHz.$$

Negative feedback taken separately
 to study $\boxed{\beta} \stackrel{\Delta}{=} \frac{v_N}{v_0}$

Circuit diagram for question 1:

- A series circuit consisting of three resistors (R_1 , R_2 , R_3) and a voltage source (V_0).
- An additional branch with a resistor (R) and a capacitor (C) is connected between the first and second resistors.
- The angle β is indicated at the junction before the first resistor.
- The angle α_1 is indicated at the junction after the first resistor.
- The angle α_2 is indicated at the junction after the second resistor.
- The angle α_3 is indicated at the junction after the third resistor.
- A box labeled N contains a resistor R and a capacitor C .

~~neg. feedback network.~~


$$i = \frac{v_N}{R}, \quad v_1 = 2v_N; \quad v_2 = v_1 + R \times 3i = 5v_N; \quad v_0 = v_2 + 8P \times R = 13v_N$$

$$\Rightarrow \beta = \frac{v_N}{T_0} = \frac{v_N}{13v_N} = \frac{1}{13} \frac{V}{V}$$

$$\Rightarrow f_B = \frac{4 \text{ MHz}}{13} \cdot \frac{V}{U} \Rightarrow \boxed{GBP = A_0 \cdot f_B = 18 \cdot \frac{4 \text{ MHz}}{13} = \frac{32}{13} \text{ MHz.}}$$

(b)

Repeat for non-inverting configuration:

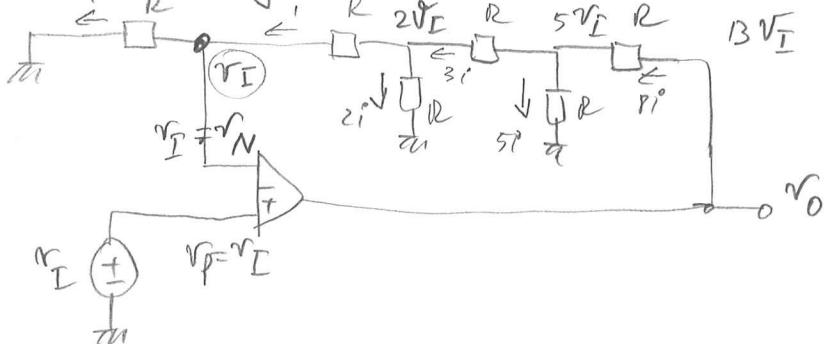

(3)


some current ratios or
in port \bar{a} from a).

Left for exercise!

$$\Rightarrow A_0 = 13 \text{ V/V} \quad \beta = \frac{1}{13} \text{ V/V} \Rightarrow G_{BP} = A_0 \cdot \beta f_t = 13 \cdot \frac{1}{13} \cdot 4 \text{ MHz} = 4 \text{ MHz.}$$

$$= f_B$$

(c)

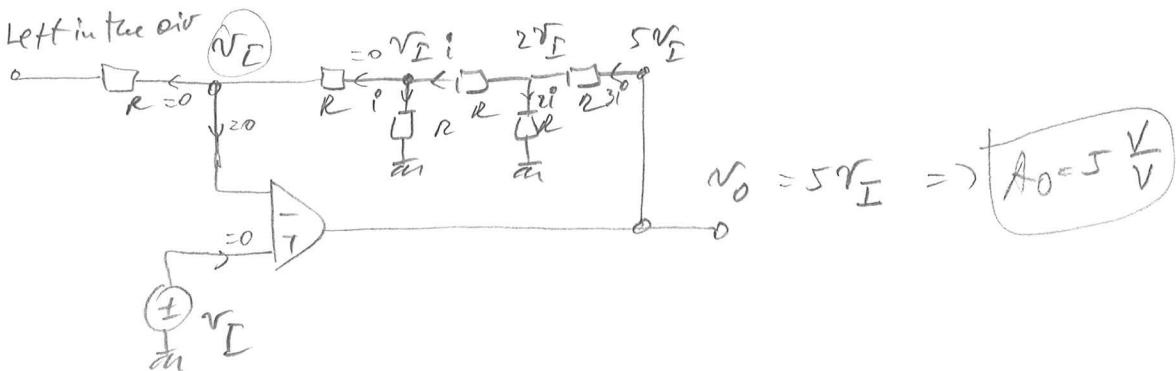

$$A_0 = 5 \text{ V/V} \quad \beta = \frac{1}{5} \Rightarrow G_{BP} = 4 \text{ MHz.}$$

(Exam 1; Spring '11)

PROBLEM 5


The open-loop frequency characteristic of an OpAmp, using the dominant pole model, is shown in the figure below. The OpAmp has $r_d = 1M\Omega$ and $r_0 = 100\Omega$.

- Find the value of f_b for the OpAmp. *Important!*
- If the OpAmp is used to build a non-inverting amplifier with a gain of 10, calculate the bandwidth of the amplifier. Calculate the input impedance for an input frequency of 500kHz.

$$\textcircled{a} \quad \omega_0 = 10^{\frac{100}{20}} = 10^5$$

$$f_t = 2 \text{ MHz} = f_b \cdot \omega_0 \Rightarrow$$
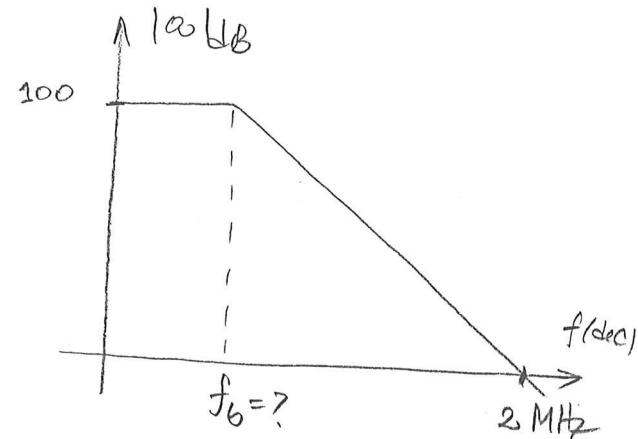
$$\Rightarrow f_b = \frac{f_t}{\omega_0} = 20 \text{ Hz}$$




$$\textcircled{b} \quad A_o = 10 \quad , \quad f_t = A_o \cdot f_B \quad \Rightarrow \quad f_B = \frac{f_t}{A_o} = 200 \text{ kHz.}$$

Bandwidth!

The input impedance of a "series input" negative feedback configuration is:

$$Z_i = R_{id} \frac{1 + j \frac{f/f_B}{f/f_b}}{1 + j \frac{f/f_B}{f/f_b}}, \text{ where: } R_{id} = r_d (1 + A_o \beta) \quad \text{and} \quad \beta = \frac{R_1}{R_1 + R_2} = \frac{1}{10}$$
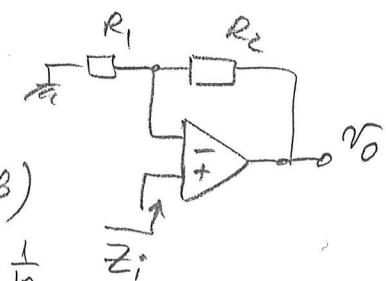
$$\Rightarrow R_{id} = 1M \left(1 + 10^5 \cdot \frac{1}{10}\right) \approx 10^9 \text{ M}\Omega = 10 \text{ G}\Omega$$



$$f = 500 \text{ kHz} \Rightarrow |Z_i| = R_{id} \cdot \left| \frac{1 + j \frac{f/f_B}{f/f_b}}{1 + j \frac{f/f_B}{f/f_b}} \right|$$

$$= 10 \text{ G}\Omega \cdot \frac{\sqrt{1 + \left(\frac{500k}{200k}\right)^2}}{\sqrt{1 + \left(\frac{500k}{20}\right)^2}}$$

(5)

EXAM 2- ECE 723 - SPRING 2009
Open Book, Closed Notes, 50 minutes

PROBLEM 1


The open-loop frequency characteristic of an OpAmp, using the dominant pole model, is shown in the figure below. The OpAmp has $r_d = 1M\Omega$ and $r_o = 100\Omega$, $C_c = 30pF$.

- Find the value of f_t for the OpAmp.
- If the OpAmp is used to build an **inverting** amplifier with $R_1=10k$ and $R_2=40k$, sketch its frequency response and calculate:
 - the 3dB bandwidth (that is f_B)
 - the unity gain bandwidth of the amplifier (that is f'_t)
- If the OpAmp is used to build an **inverting** amplifier with a gain of 10, derive the formula calculate the frequency f_x at which the input impedance is $1.2R_1$. Assume that such frequency $f_b \ll f_x \ll f_t$.

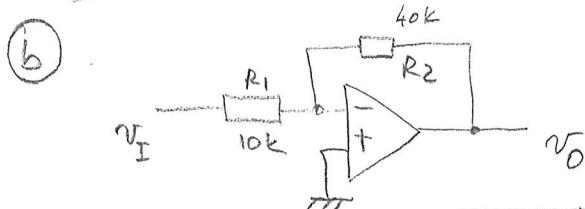(a) $10\omega_0 dB = 120 \Rightarrow 120 = 20 \cdot \log \omega_0$

$$\Rightarrow \omega_0 = 10^6$$

$f_t = \omega_0 \cdot f_b = 10^6 \cdot 10 \text{ Hz} = 10 \text{ MHz}$




$$A(jf) = A_0 \cdot \frac{1}{1 + j \frac{f}{f_B}} \quad | \quad \text{Eq. 6.15.a}$$

$$|A_0| = \left| 1 - \frac{R_2}{R_1} \right| = 4 \quad f_B \approx \beta \cdot f_t = \frac{R_1}{R_1 + R_2} \cdot f_t = \frac{1}{5} \cdot 10 \text{ MHz} = 2 \text{ MHz.}$$

$$f_B = 2 \text{ MHz}$$

Use Eq. 6.16 $\Rightarrow f'_t = (1 - \beta) f_t = \frac{4}{5} \cdot 10 \text{ MHz} = 8 \text{ MHz}$

$$f'_t = 8 \text{ MHz}$$

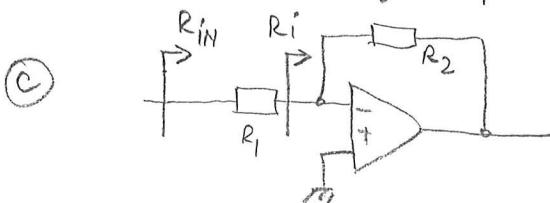


Use Eq. 6.23 $\Rightarrow R_{IN} = R_1 + R_i = R_1 + \frac{R_2}{1 + \omega_0} \cdot \frac{1 + j \frac{f}{f_B}}{1 + j \frac{f}{f_t}} \Rightarrow$

$$\Rightarrow 1.2 \cdot R_1 = \left| R_1 + \frac{R_2}{1 + \omega_0} \cdot \frac{1 + j \frac{f_x}{f_B}}{1 + j \frac{f_x}{f_t}} \right| \cong \left| R_1 + \frac{R_2}{1 + \omega_0} \cdot \left(j \cdot \frac{f_x}{f_B} \right) \right| \Rightarrow$$

$$\Rightarrow 1.2^2 = \left| 1 + \left(\frac{R_2}{R_1} \cdot \frac{1}{1 + \omega_0} \right)^2 \cdot \left(\frac{f_x}{f_B} \right)^2 \right|^2 \Rightarrow f_x = \dots$$

(This is similar to last problem of Exam #1)

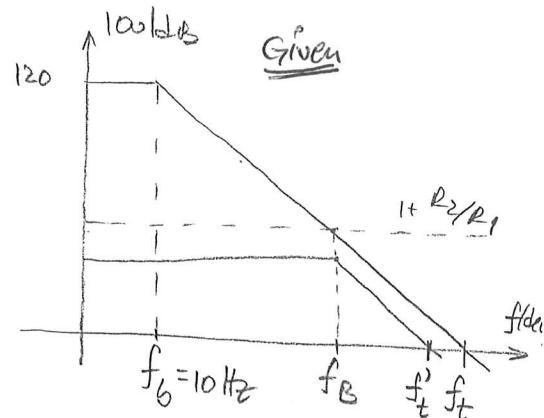

PROBLEM 2

(Exam 2; Spring 11)


P. 6.24.?

In the given circuit, all resistances are equal to $5k\Omega$. The Op Amp has $a_0 = 10^5 \text{ V/V}$, $f_t = 10 \text{ MHz}$, $r_d = \infty$, $r_o = 0$. Sketch the magnitude plot of the impedance Z_0 seen by the load.

$$V_{\text{test}} = V_P$$

$$\left\{ \begin{array}{l} V_O = a \cdot (V_P - V_N) = a \cdot (V_{\text{test}} - V_N) \\ V_O = 2 \cdot V_N \end{array} \right\} \Rightarrow$$
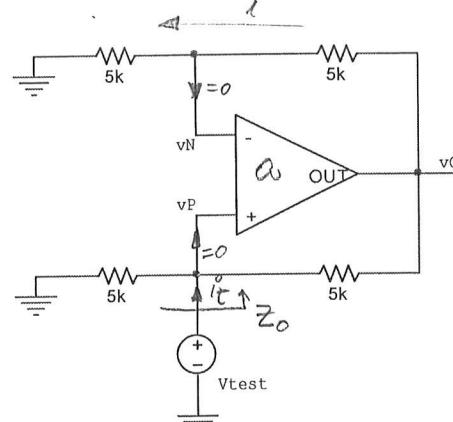
$$\Rightarrow V_N = \frac{a}{2+a} \cdot V_{\text{test}}$$



$$i_t = \frac{V_{\text{test}}}{R} + \frac{V_{\text{test}} - V_O}{R} = \frac{V_{\text{test}} + V_{\text{test}} - 2V_N}{R} = \frac{2}{(1 + \frac{a}{2})R} \cdot V_{\text{test}} \Rightarrow$$


$$\Rightarrow Z_0 = \frac{V_{\text{test}}}{i_t} = \frac{R}{2} \left(1 + \frac{a}{2} \right)$$

$$\text{We know: } a_0 = \frac{a_0}{1 + j \frac{f}{f_b}}$$

$$\text{where } f_b = f_t / a_0 = 100 \text{ Hz}$$

$$\Rightarrow Z_0 = (2.5 \text{ k}\Omega) \cdot \left(1 + \frac{10^5 / 2}{1 + j \frac{f}{100 \text{ Hz}}} \right)$$
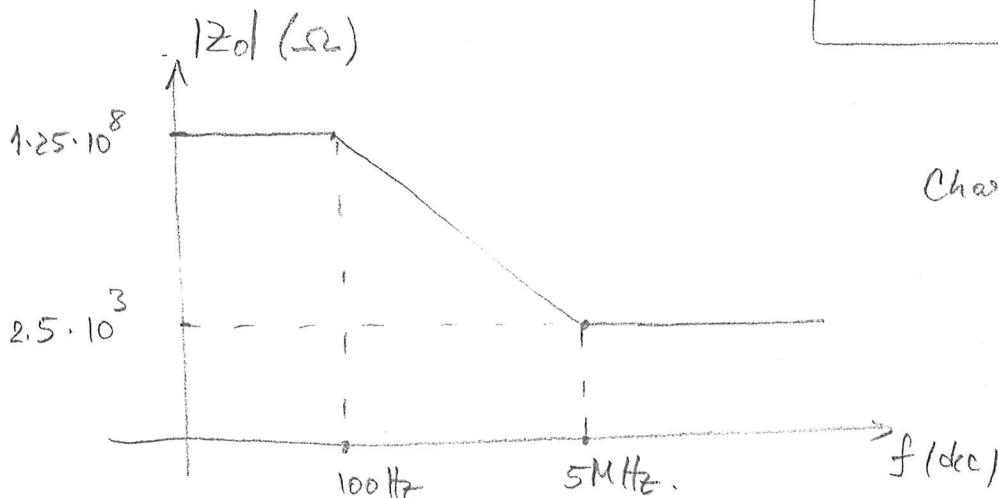
$$\approx 1.25 \cdot 10^8 \cdot \frac{1 + j \frac{f}{5 \text{ MHz}}}{1 + j \frac{f}{100 \text{ Hz}}} = Z_0$$



Character capacitive!

(This is similar to a problem from HW #5!)