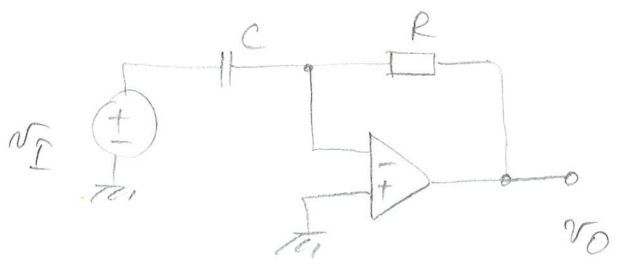


Ch 8. Part 2

- Do the example started last time.
- Discuss the role of closure (ROC)
- 8.2 Stability in constant GBP OpAmp circuits
See page 5 of last notes...

The idea is that we do not want two poles of T to the left of f_x :
but only one!
because in this case f_{-180} will be far $T < 1$.

Example of feedback pole: The Differentiator Circuit



$\omega \rightarrow \infty \Rightarrow H_{ideal} = -j\omega / f_0$

$\beta = \frac{Z_c}{Z_c + R_o}, \quad Z_c = \frac{1}{j\omega C}$



$\beta(j\omega) = \frac{1}{1 + j\omega / f_0}$

Using ROC:

$ROC = |slope | \omega |_{f=f_x} - slope | 1/\beta |_{f=f_x}|$
 $= |-20 - (+20)| = 40 \text{ dB/dec} \Rightarrow$
 $\Rightarrow \phi_{min} \cong 0^\circ \text{ unstable!}$

\Rightarrow large ω so $f_0 \ll f_t$ (or $f_0 \cong \frac{f_t}{10}$).

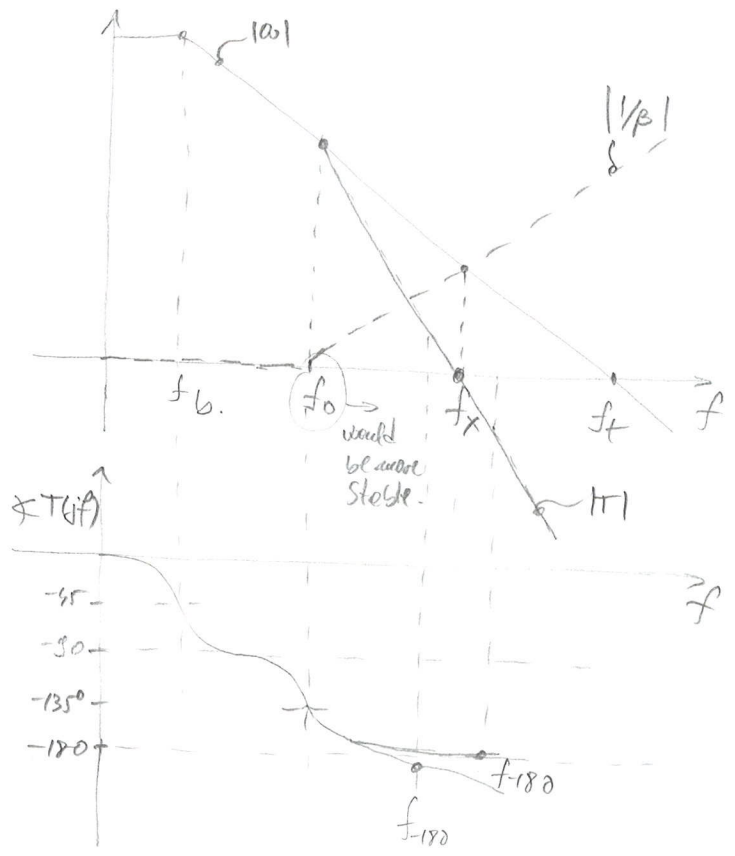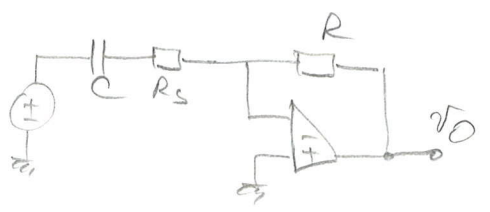
- To stabilize it \Rightarrow add R_s in series with C :




Depending on how small f_0 is compared to f_t the phase margin approaches $0^\circ \Rightarrow$ instability.

At LF $\Rightarrow R_c$ no effect because C is open anyway.

At HF $\Rightarrow C$ short, but $|1/\beta_\infty| = 1 + \frac{R}{R_s} \Rightarrow |1/\beta|$ has a pole (or zero for $|\beta|$)

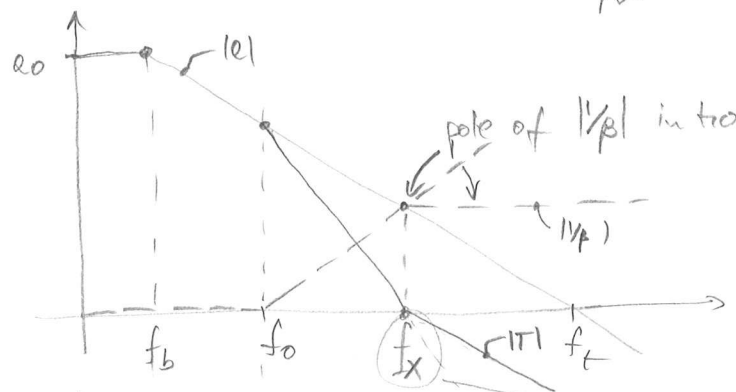

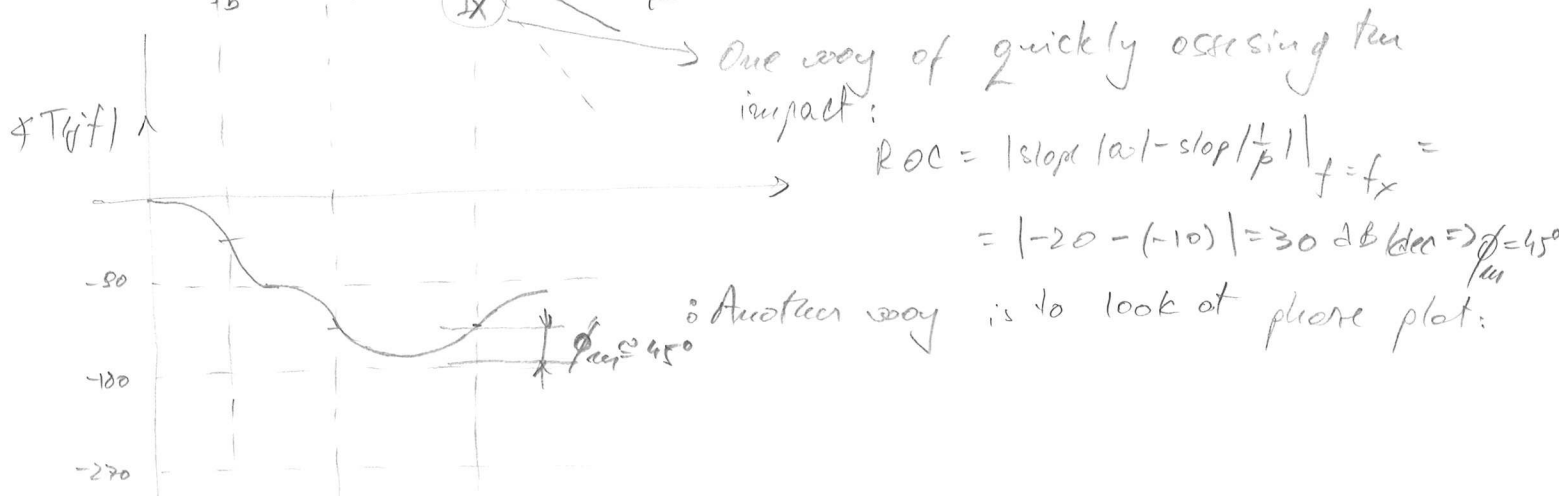pole of $1/\beta$ introduced by R_s , which is located intentionally at f_x



One way of quickly assessing the impact:



$$ROC = |\text{slope } |a| - \text{slope } |1/\beta| |_{f=f_x} = |-20 - (-10)| = 30 \text{ dB/dec} \Rightarrow \phi = 45^\circ$$

Another way is to look at phase plot:

- Stray input capacitance compensation
- Capacitive Load isolation

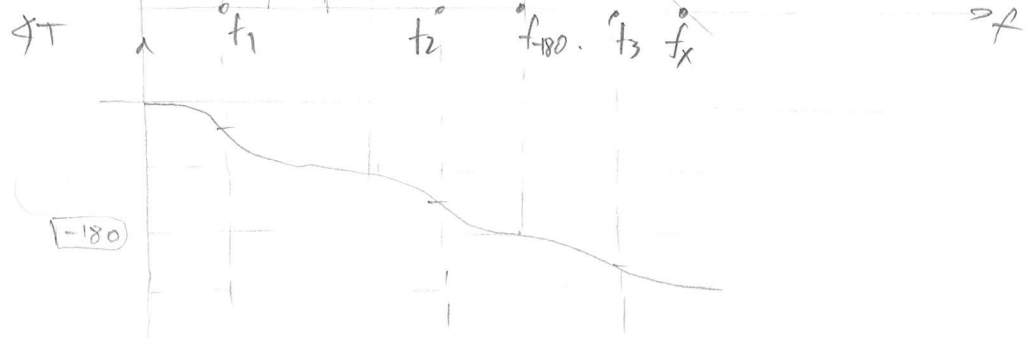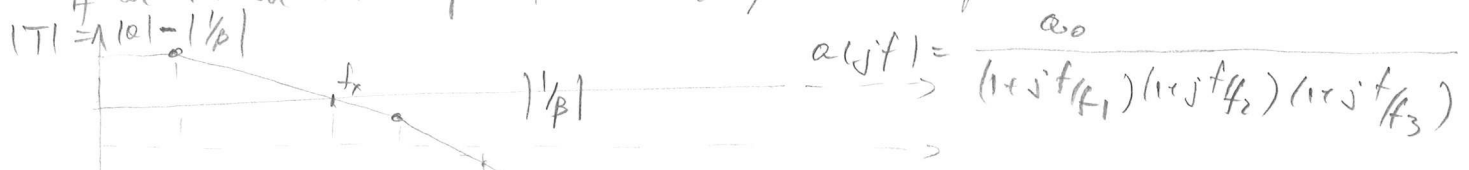8.3 internal frequency compensation



if we summat for 30pF internal compensation capacitor \Rightarrow



This could be made stable only for $|1/\beta| = (A_0)$ high enough so that odd line of $|T|$ is less than f_2 .

- Dominant-pole compensation (new f_2 pole is introduced)
- Shunt-capacitance compensation (f_1 is made more dominant)
- Miller compensation (pole splitting)
- Feed-forward compensation
- Pole-zero compensation

Exercise!

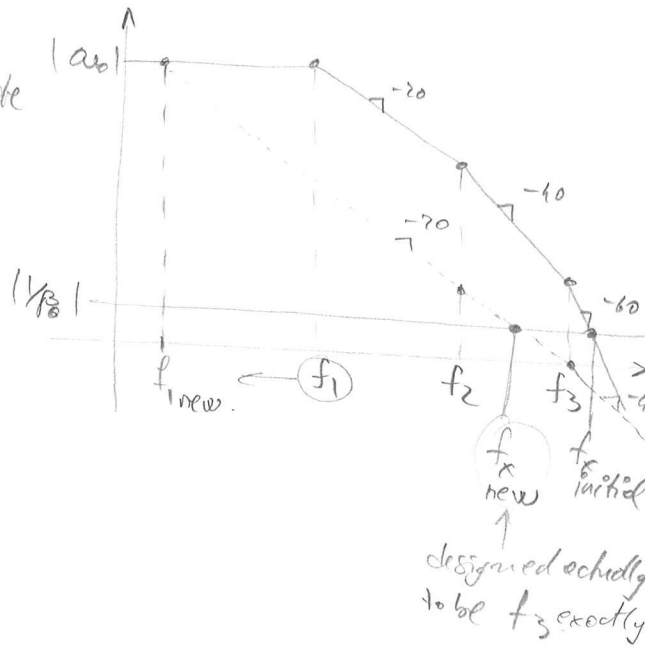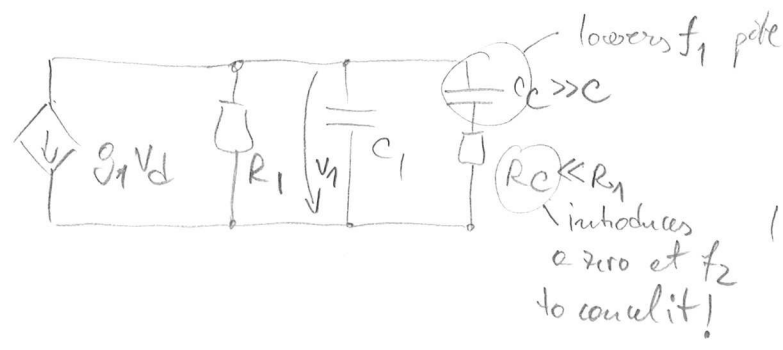

This has an effect that:

$$\frac{v_1}{v_d} \approx (-g_m R_1) \cdot \frac{(1 + j\omega/f_2)}{(1 + j\omega/f_{1new})(1 + j\omega/f_4)}$$

$$f_{1new} \approx \frac{1}{2\pi R_1 C_c} \quad f_2 \approx \frac{1}{2\pi R_c C_c} \quad f_4 \approx \frac{1}{2\pi R_c C_1} > f_3$$

If we make $f_2 = f_4 \Rightarrow$ zero-pole cancellation:

$$\text{and } |G(f)| = \frac{A_0}{(1 + j\omega/f_{1new})(1 + j\omega/f_3)(1 + j\omega/f_4)}$$

Also let $f_2 = f_3 \Rightarrow \phi_{max} = 45^\circ$

8.4 External frequency compensation

idea: modify the feedback factor $\beta \rightarrow \beta(f)$

- Reducing the loop-gain \Rightarrow shift $|1/\beta|$ upward! Exercise!
- input-loop compensation \Rightarrow shift $|1/\beta|$ upward only at HF! (sawtooth!)
- Feedback-loop compensation \Rightarrow introduce a zero for $|1/\beta| \Rightarrow$ phase of T will go upward away from -180° !
- Decompensated Opamps