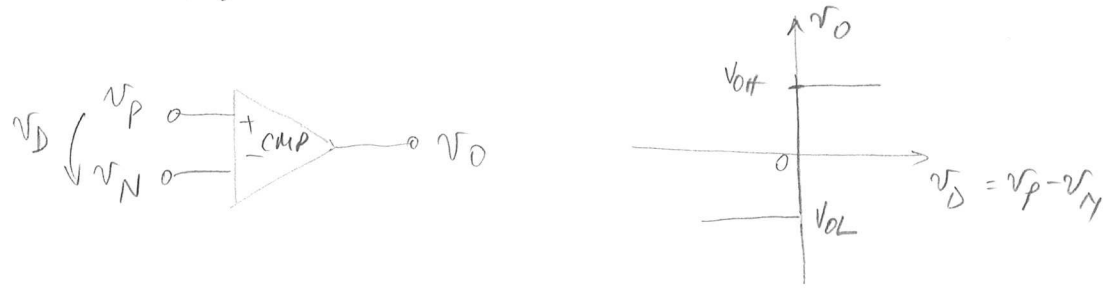


Ch 9 Part 1





Nonlinear circuits

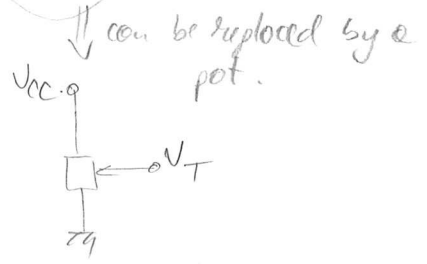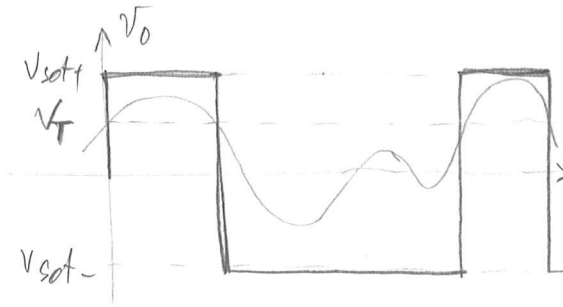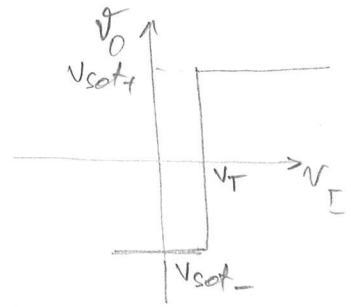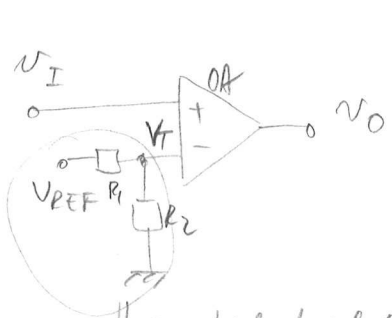Q.1. Voltage comparators ← key 1

- Same symbol as an OpAmp!



The simplest comparator is an OpAmp! Limitation: works for low freq's only.





≡ Threshold detector!

- OpAmps are intended to work in neg. feedback circuits.
- Their output cannot be interfaced directly with digital circuits.

⇒ Voltage Comparators were designed specifically!
They are manufactured as dedicated IC!

Simplified implementation details

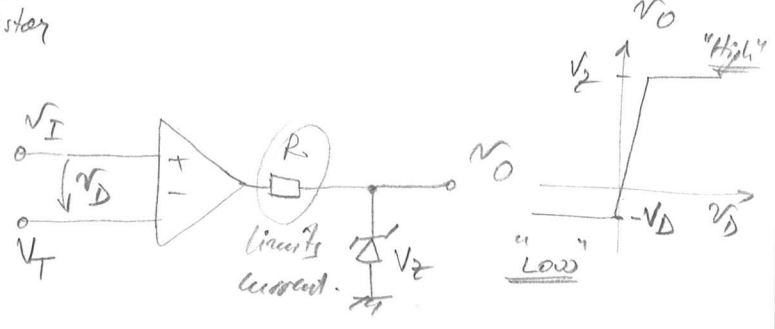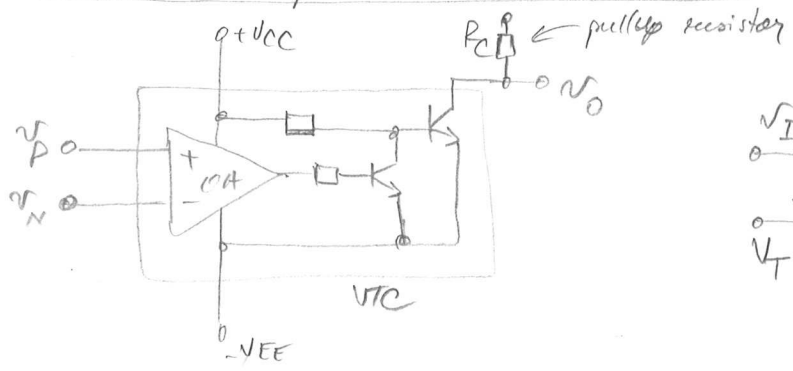


Q.2 VTC Applications

- AD converters
- waveform generators
- High voltage digital logic gates.

Level Detector (Threshold detector)

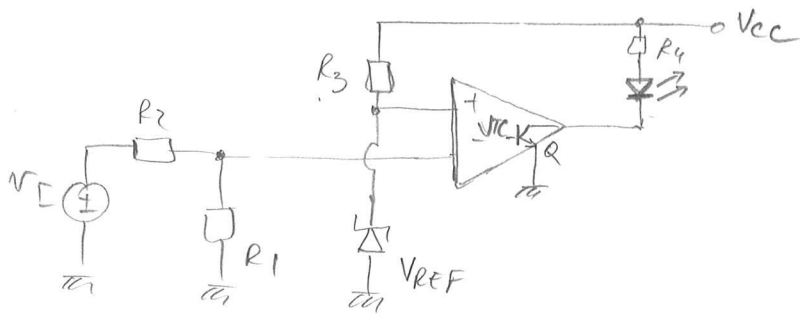
Monitor a physical variable that can be expressed as a voltage signal!



$\frac{R_1}{R_1 + R_2} V_I \geq V_{REF}$. The threshold voltage is $V_T = (1 + \frac{R_2}{R_1}) V_{REF}$.

$\left\{ \begin{array}{l} V_I < V_T \Rightarrow Q \text{ is off} \Rightarrow \text{LED is off.} \\ V_I > V_T \Rightarrow Q \text{ is saturated} \Rightarrow \text{LED will glow!} \end{array} \right.$



Example: photocell circuit.

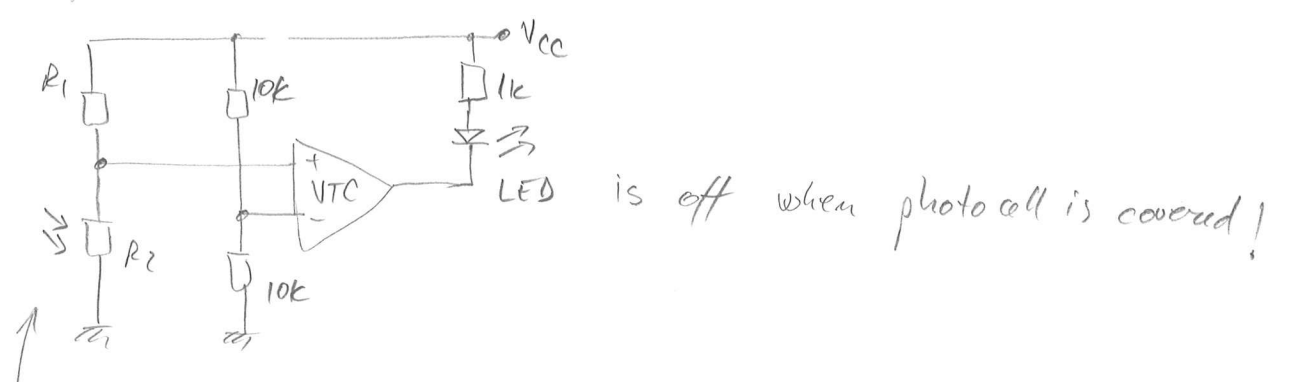

LED is off when photocell is covered!

Sensor can be for temperature, pressure, strain, fluidic level, light and sound intensity!

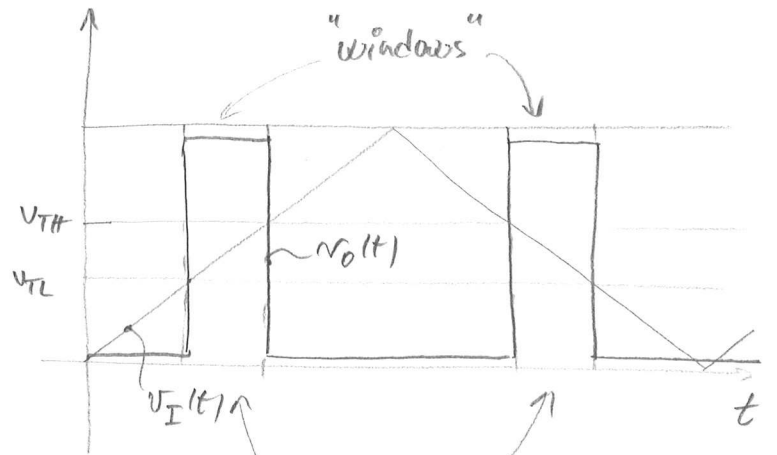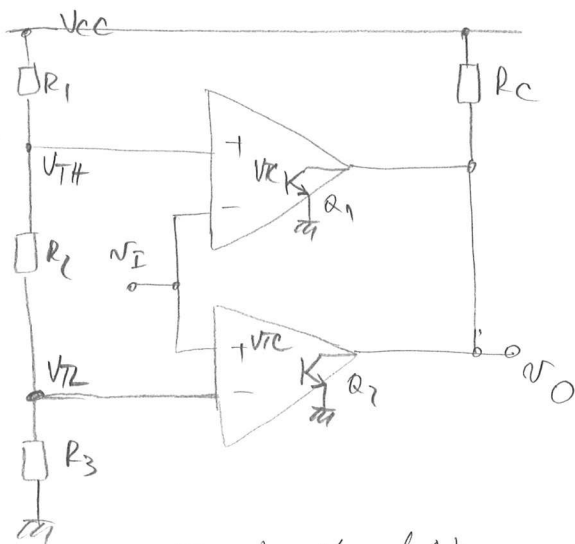Voltage window detector (window comparator)




Transfer characteristic:



Q_1, Q_2 are both off and R_c pulls up v_o to V_{cc} .



Bus-prog meters (exists actually as dedicated chips: LM3914)

Example: 4 level-voltage detector.

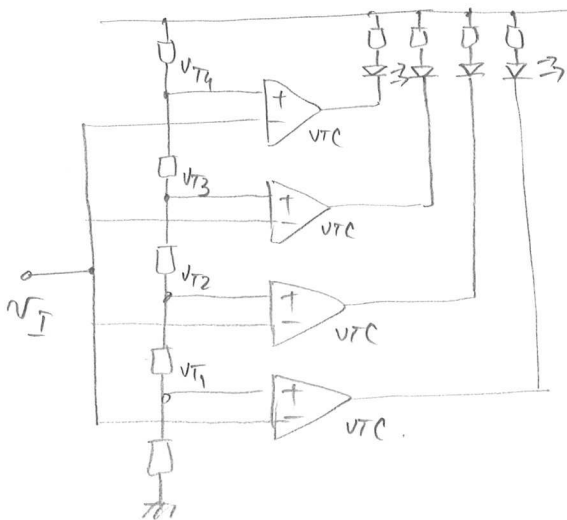

Signal Generators

② Square-wave generator ← Skip This

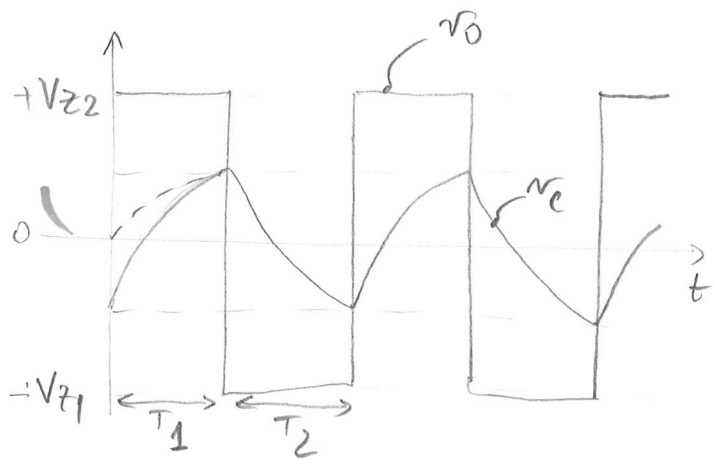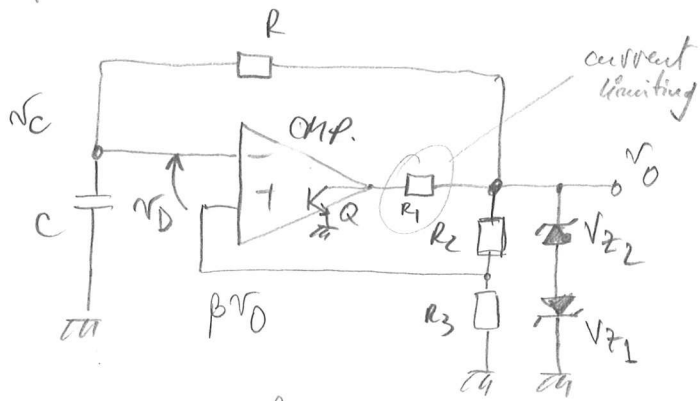

$$\beta = \frac{R_3}{R_2 + R_3}$$

$$v_D = \beta v_O - v_C$$

$$V_{z1} = V_{z2} = V_z$$

$$v_C(t) = V_z \left[1 - (1 + \beta) e^{-\frac{t}{RC}} \right]$$

$$T_1 = T_2 = T/2 \Rightarrow T = 2RC \ln \frac{1 + \beta}{1 - \beta}$$



independent of $V_z!$

- Frequency range: 10 Hz ÷ 10 kHz; after that slew-rate becomes important.

- Circuit can be generated without the Zener diodes => swing between $V_{sat-} \div V_{sat+}$ (key 2)

See ④ page for triangular wave generator!

9.3 Schmitt trigger - Positive feedback

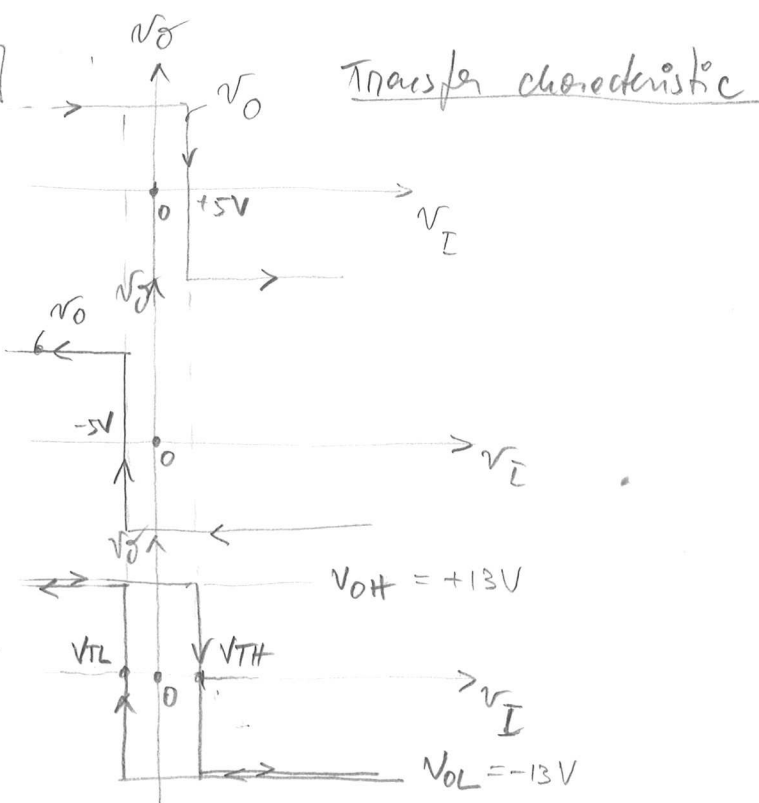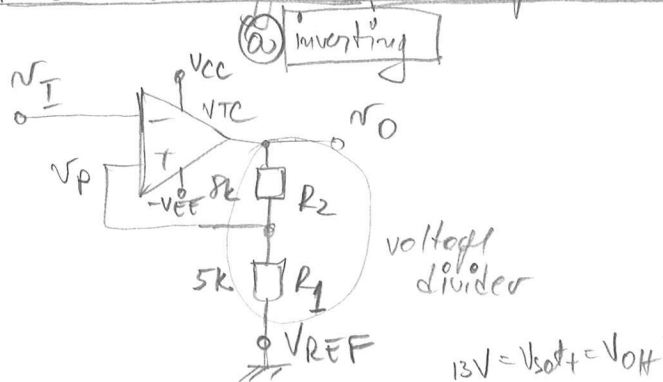


$$v_{TH} = \frac{R_2}{R_1 + R_2} v_{REF} + \frac{R_1}{R_1 + R_2} v_{OH}$$


$$v_{TL} = \frac{R_2}{R_1 + R_2} v_{REF} + \frac{R_1}{R_1 + R_2} v_{OL}$$

Hysteresis voltage $V_H \triangleq v_{TH} - v_{TL}$

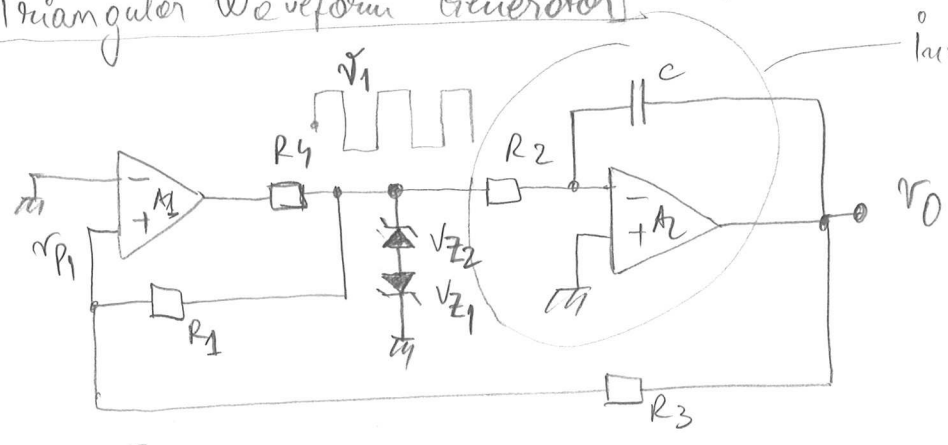⑥ Triangular Waveform Generator ← skip this




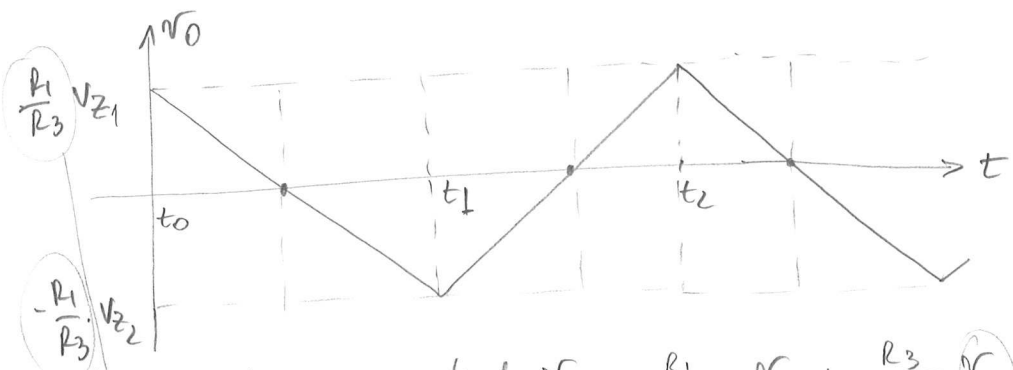integrator has inversion => feedback to "+" terminal of OA2.





Obtained by observing that $v_{P1} = \frac{R_1}{R_3 + R_1} v_O + \frac{R_3}{R_1 + R_3} v_1$
 $= v_{Z1}$ or v_{Z2}

crosses zero in up or down directions

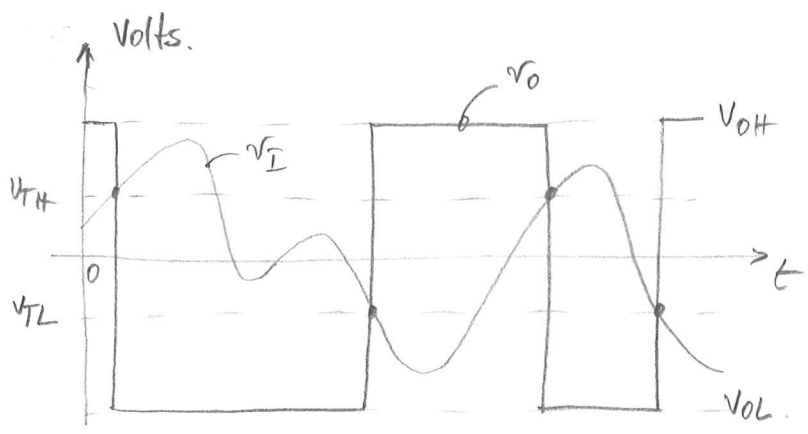

If $V_{REF} = 0 \Rightarrow V_H = V_{TH} - V_{TL} = \frac{R_1}{R_1 + R_2} (V_{OH} - V_{OL}) = \Delta V_T$

⑥ Noninverting Schmitt Trigger

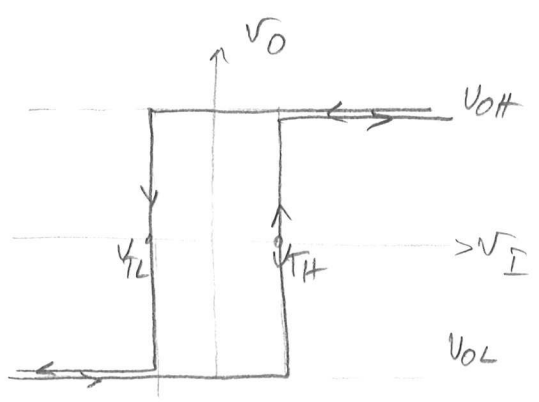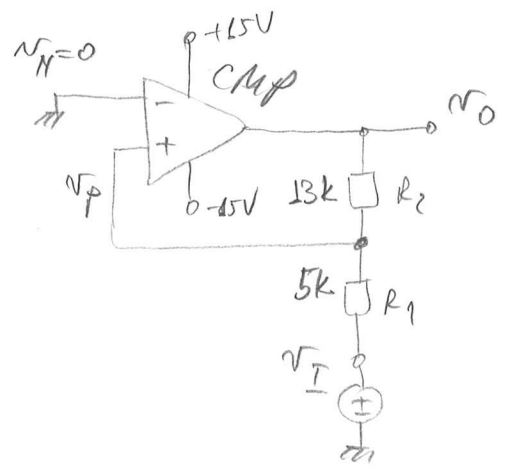

- $v_I \ll 0 \Rightarrow v_O = V_{OL} (-15V)$

To switch v_O to V_{OH} we have to raise v_I so that v_P approaches and crosses $v_N = 0. \Rightarrow$


$$v_P = \frac{R_2}{R_1 + R_2} v_I + \frac{R_1}{R_1 + R_2} v_O$$

$$0 = \frac{R_2}{R_1 + R_2} v_{TH} + \frac{R_1}{R_1 + R_2} V_{OL}$$

$$\Rightarrow v_{TH} = - \frac{R_1}{R_2} V_{OL}$$

- Similarly: $v_{TL} = - \frac{R_1}{R_2} V_{OH}$

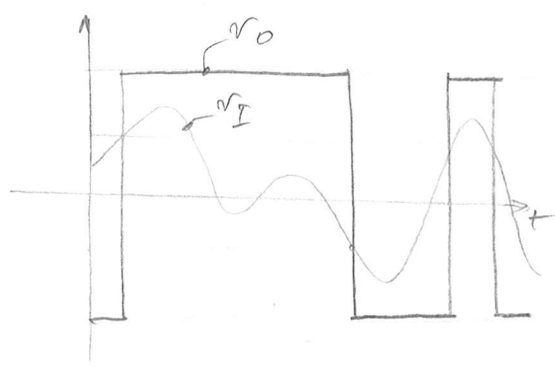
Hysteresis: $V_H = \Delta V_T = \frac{R_1}{R_2} (V_{OH} - V_{OL})$



Half Wave Precision Rectifier

← Skip this (go to next notes, part 2)

Most suitable in audio circuits

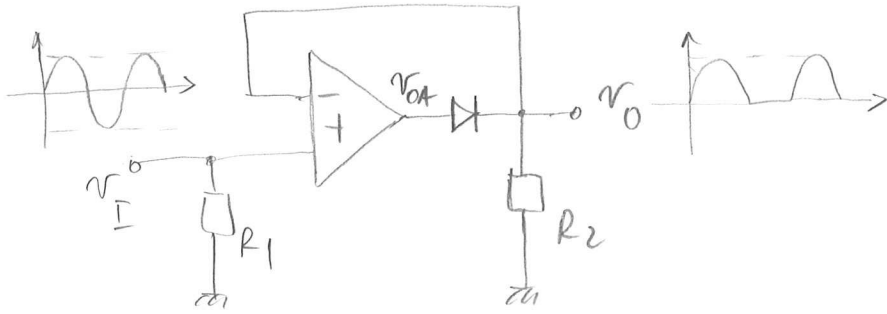


- Low frequency, on positive values => voltage follower!
- input signal negative => op-amp has no feedback

$v_{OA} \rightarrow -V_{EE}$ (actually V_{set-})
 $v_O \rightarrow 0$ as R_2 cannot draw current from anywhere.

Main limitation: works well for low frequencies $< 10\text{kHz}$

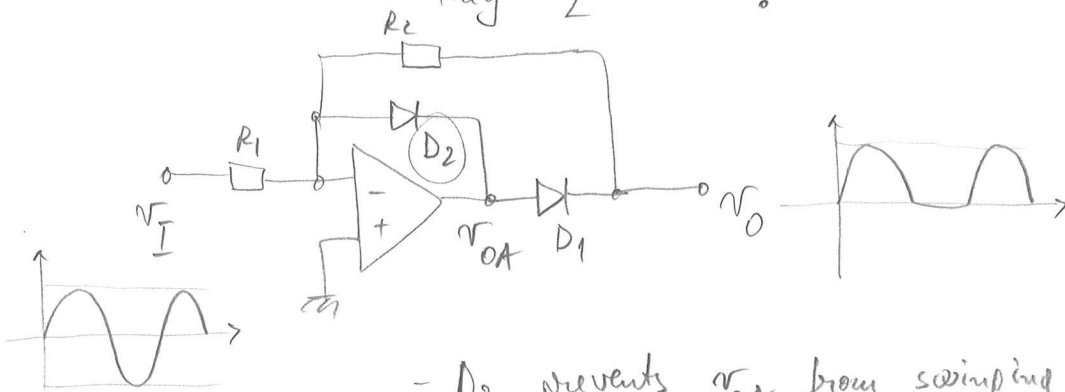Improved version - idea is to eliminate large swings for v_{OA} , because they require time!




- D_2 prevents v_{OA} from swinging to the negative rail $-V_{EE}$

Limitations

- input resistance low (depends on R_1)

Full Wave Rectifier

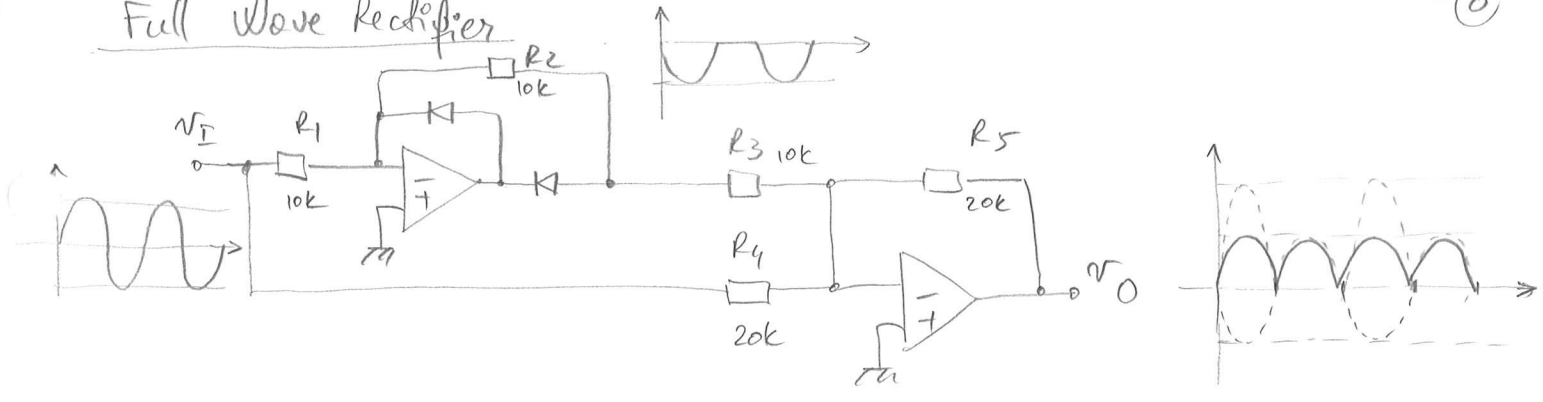

Limitation :- input loading
 - limited frequency response

Simplified alternative

