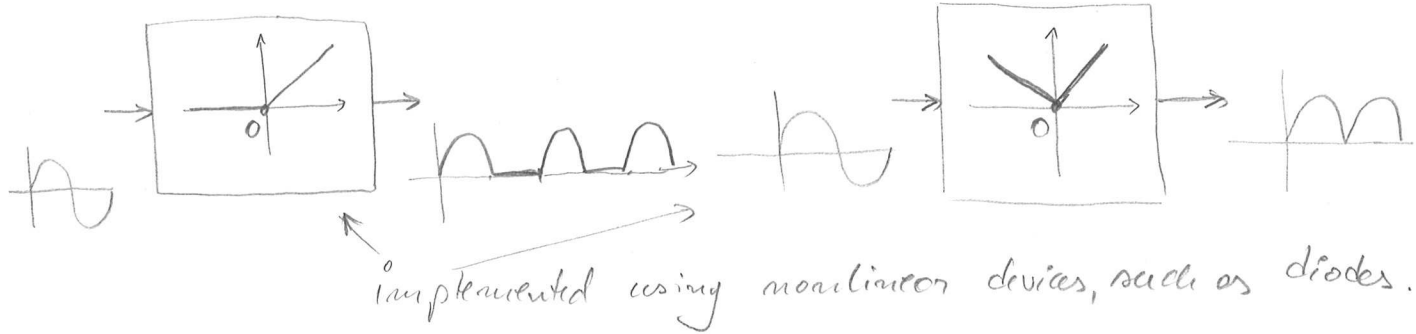


- Finish talking about Schmitt triggers



9.4 Precision Rectifiers

Half-wave rectifier (HWR)


Full-wave Rectifier (FWR)



Half-wave rectifiers: Superdiode

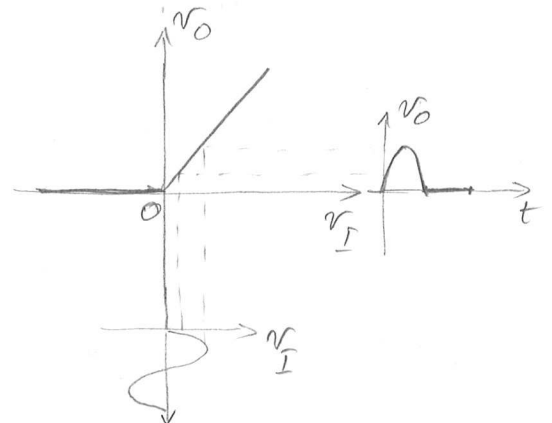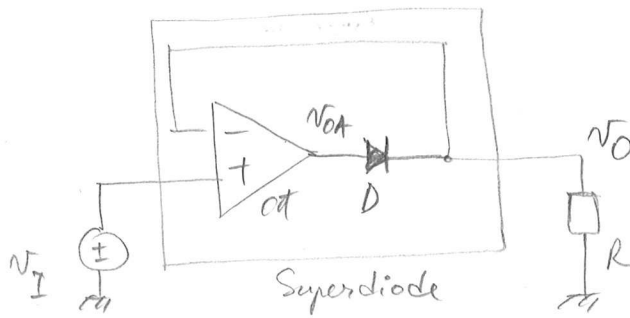


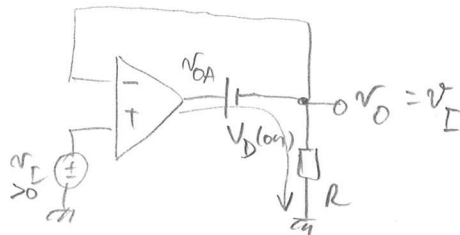Case: $v_I > 0 \Rightarrow v_{OA}$ will swing toward $V_{OH} \Rightarrow D = ON \Rightarrow$ Negative feedback (\exists)





$$v_{OA} = v_O + V_D \approx v_O + 0.7V$$

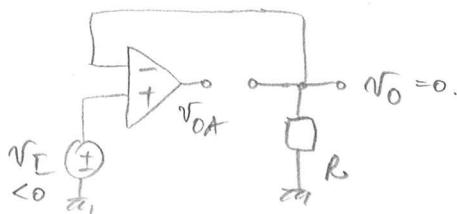Case: $v_I < 0 \Rightarrow v_{OA}$ will swing toward $V_{OL} \Rightarrow D = OFF$



$$v_{OA} = V_{OL}$$

Improved HWR



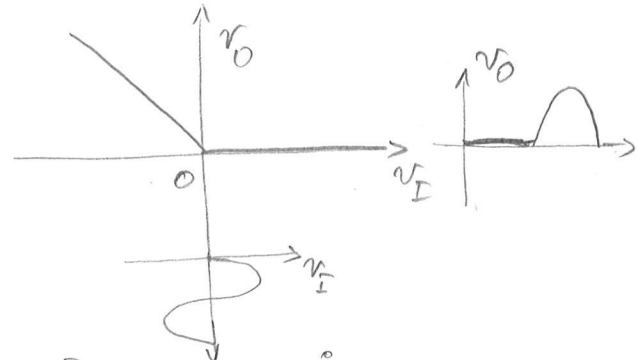
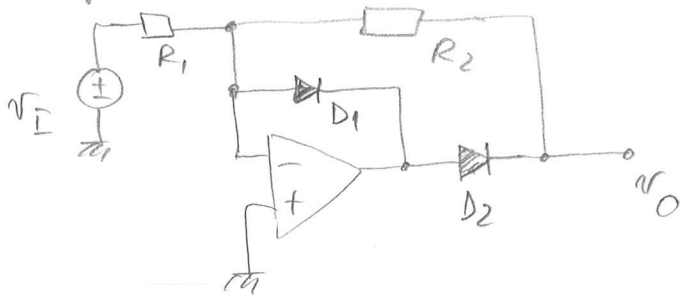


Case 1: $v_I > 0 \Rightarrow D_1 = ON, D_2 = OFF \Rightarrow v_O = 0$ or $i_{R2} = 0$.


Case 2: $v_I < 0 \Rightarrow D_1 = OFF, D_2 = ON \Rightarrow (\exists) i_{R2} : \frac{v_O - 0}{R_2} = \frac{0 - v_I}{R_1}$

$$v_O = -\frac{R_2}{R_1} v_I$$

Full-Wave Rectifier (FWR)

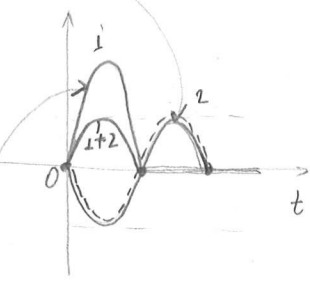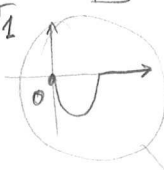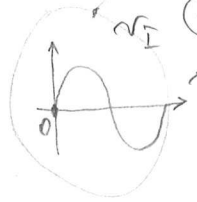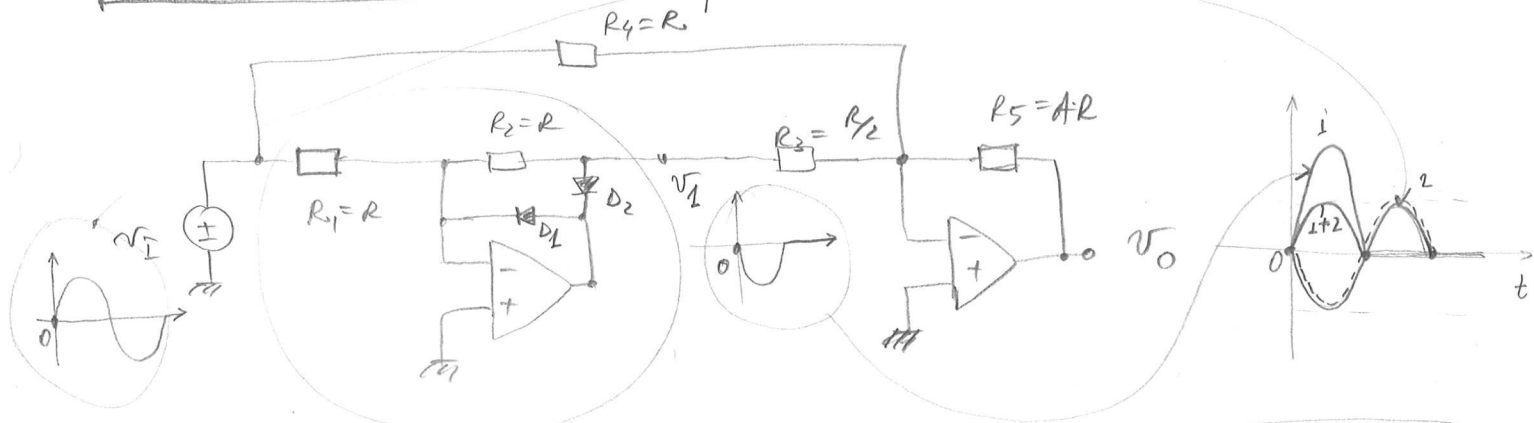

Improved HWR

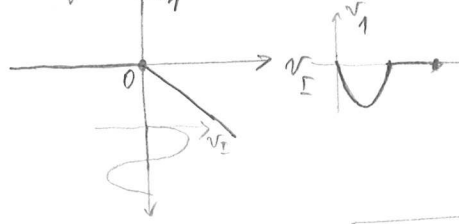

$$v_O = -\frac{R_5}{R_4} v_I - \frac{R_5}{R_3} v_1$$

$$\begin{cases} v_O = A_p \cdot v_I, & v_I > 0 \text{ V} \\ v_O = -A_n v_I, & v_I < 0 \text{ V} \end{cases}$$


$$A_p = \frac{R_2 R_5}{R_1 R_3} - A_n$$

$$A_n = \frac{R_5}{R_4}$$


We want $|A_n| = |A_p|$, and we take the values shown in the figure we achieve an amplification of A.
 Note: application is ac-dc converters.

9.6. Peak detectors

(test and measurement instrumentation)

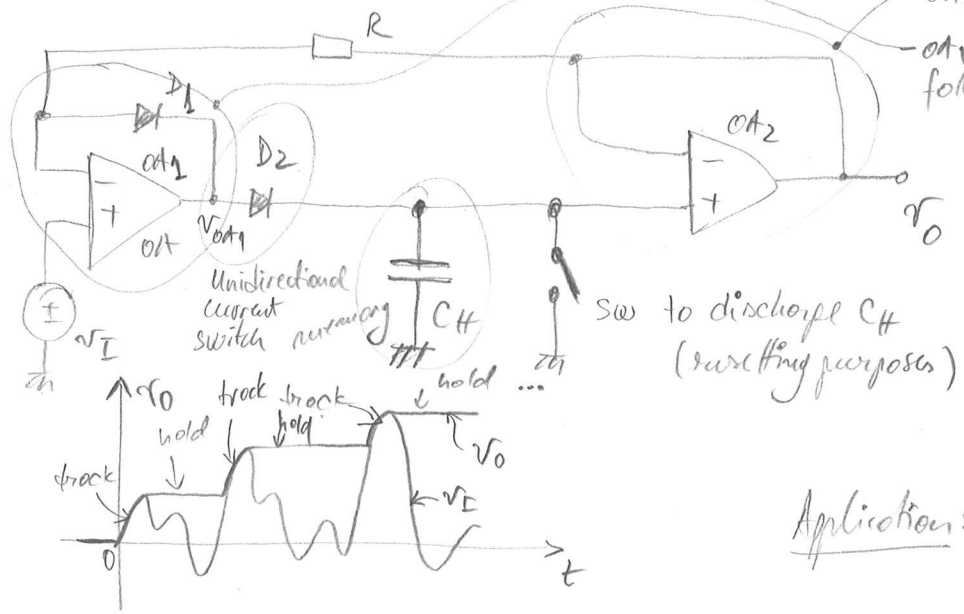

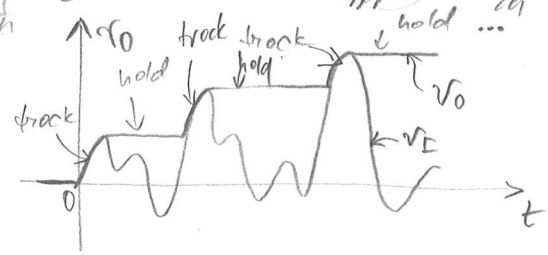
OA2 recharges/ out load to prevent discharge of C_H
 OA1 follower to track the input v_I when it goes higher than the currently stored.



Applications: test and measurement instrumentation.

Track mode:

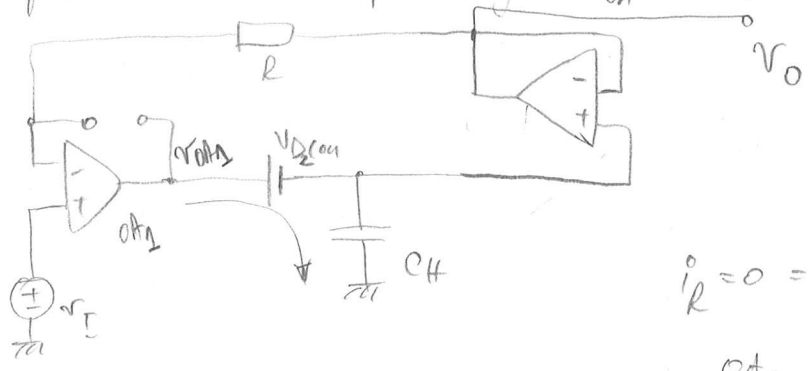
A new peak arrives \Rightarrow OA1 swings v_{OA1} toward $V_{OH} \Rightarrow D_1 = OFF, D_2 = ON$



$i_R = 0 \Rightarrow v_O$ follows v_I via OA1 with negative feedback $v_{D2} = v_{OA2} - R$.

Hold mode

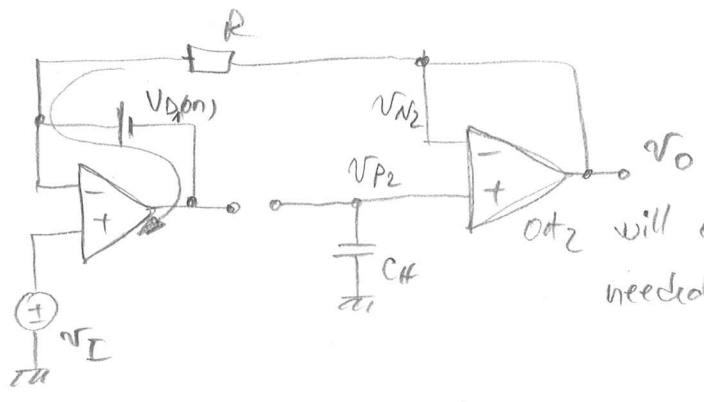After peaking $v_I \downarrow \Rightarrow v_{OA1} \downarrow \Rightarrow D_1 = ON, D_2 = OFF \Rightarrow$ OA1 has an alternative feedback via D_1



OA2 will output whatever current is needed to keep v_O equal to v_{P2} .

Problem 9.4. Using

- 2 comparators of type 339

- thermistor: $R(T) = R(T_0) \cdot e^{B(\frac{1}{T} - \frac{1}{T_0})}$

, T_0 some reference temp.

$B = 4000 \text{ K}$

$R_s(25^\circ\text{C}) = 10 \text{ k}\Omega$



$\uparrow T_0$

Design a circuit that yields:

$v_o = 5 \text{ V}, 0^\circ\text{C} < T < 5^\circ\text{C}$

0, otherwise

This how NTC should look like!

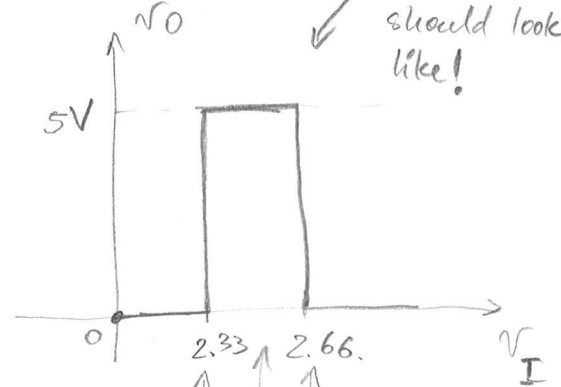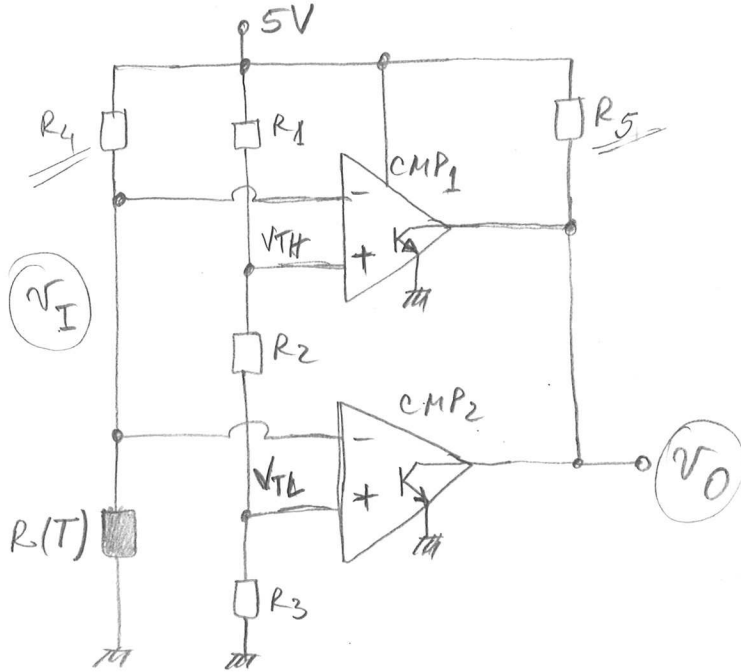

$R(10^\circ) = 10 \text{ k}\Omega \times e^{4000(\frac{1}{273} - \frac{1}{298})} \approx 34.12 \text{ k}\Omega$

$R(5^\circ) = 26.23 \text{ k}\Omega$

Let $R_4 = 30 \text{ k}\Omega \Rightarrow \begin{cases} v_{TL} = 5 \text{ V} \cdot \frac{26.23}{26.23 + 30} = 2.33 \text{ V} \\ v_{TH} = 5 \text{ V} \cdot \frac{34.12}{34.12 + 30} = 2.66 \text{ V} \end{cases}$

Use $\begin{cases} R_3 = 23.2 \text{ k}\Omega \\ R_2 = 3.32 \text{ k}\Omega \\ R_1 = 23.4 \text{ k}\Omega \end{cases}$ to implement v_{TL}, v_{TH} !

Problem 9.12

(a) Sketch the VTC of this new modified Schmitt trigger.

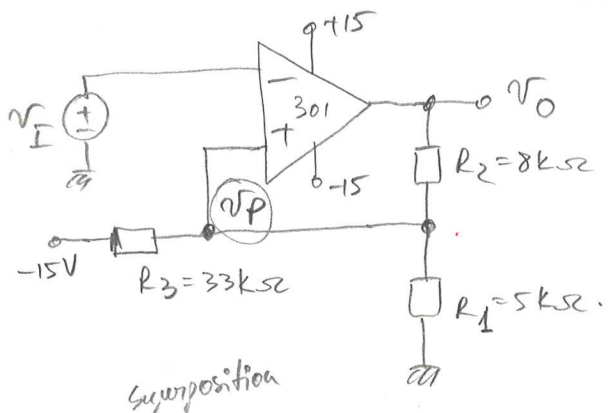



Fig. 9.20. Inverting Schmitt trigger modified with R3

Exercise: what if R1 is pulled out connected to VREF?

superposition

$$v_p = \frac{33||15}{33||15+8} \cdot v_0 + \frac{8||15}{8||15+33} \cdot (-15) \approx 0.352 v_0 - 1.279V$$


$$\left\{ \begin{aligned} V_{TH} = v_p \Big|_{v_0=13V} &= \underline{3.29V} \\ V_{TL} = v_p \Big|_{v_0=-13V} &= \underline{-5.85V} \end{aligned} \right.$$

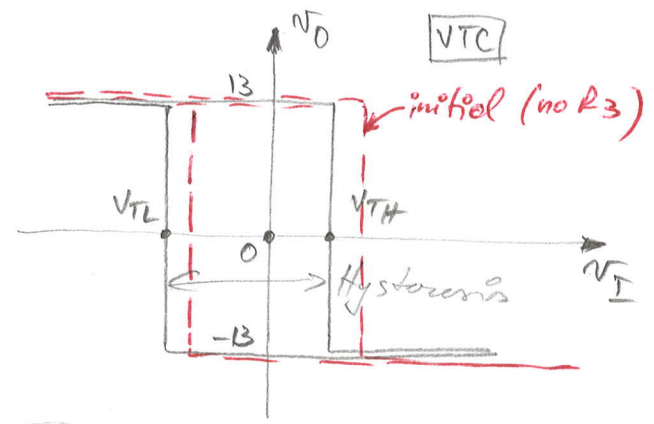

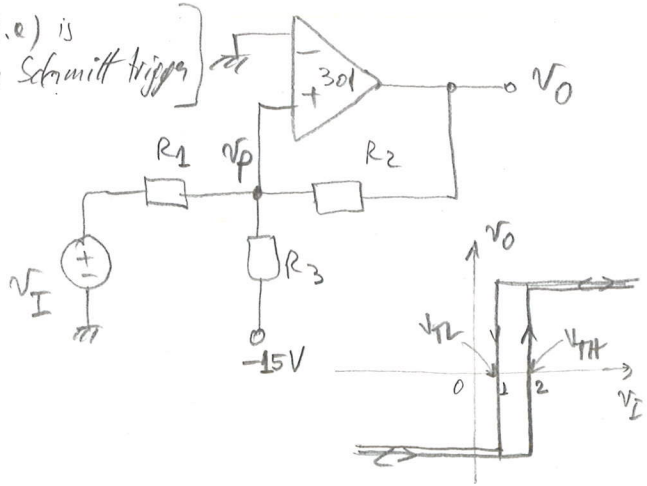(b) Modify the circuit of Fig. 9.21(a) so that it gives $V_{TL}=1V$, $V_{TH}=2V$: wanted!

Observation: we have to add -15V via a resistor to v_p .

[Fig. 9.21(a) is non-inverting Schmitt trigger]



$v_p = 0$ in two cases:

Case 1: $v_0 = v_{OL} \text{ \& \ } v_I = V_{TH}$

$$\frac{2-0}{R_1} = \frac{0-(-15)}{R_3} + \frac{0-(-13)}{R_2}$$

Case 2: $v_0 = v_{OH} \text{ \& \ } v_I = V_{TL}$

$$\frac{13-0}{R_2} + \frac{1-0}{R_1} = \frac{0-(-15)}{R_3} \Rightarrow$$

\Rightarrow these are 2 equations, 3 unknowns.
 \Rightarrow fix $R_1 = 10k\Omega$, then $R_3 = 100k\Omega$, $R_2 = 260k\Omega$ use $261k\Omega$.