


Signal Generators

- Has the function to generate a waveform of prescribed characteristic such as frequency, amplitude, shape and duty cycle.
- Generally can be seen as a f_{up} converter $DC \rightarrow f$. (similar to $f_1 \rightarrow f_2$, with $f_1 = 0$)

Sinusoidal oscillators

Type 1

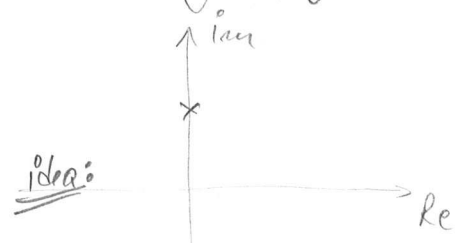- pair of conjugate poles on the imaginary axis of the complex plane




"Sinusoidal purity" is expressed via THD = total harmonic distortion.

$$THD (\%) = 100 \cdot \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots}$$

$$D_k = \frac{\text{amplitude of the } k\text{-th harmonic}}{\text{amplitude of the fundamental}}, \quad k = 2, 3, 4, \dots$$

idea: Ask in class if they master s-plane and complex plane!

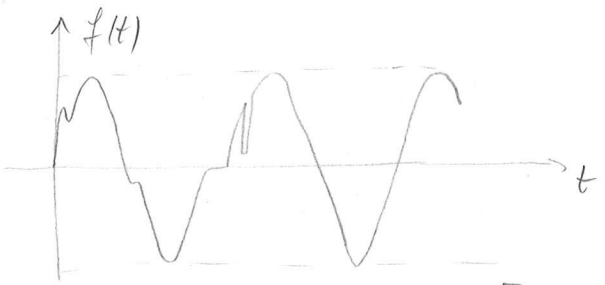A sine wave has THD = 0%, a triangle wave THD \approx 12%.



where: $a_0 = \frac{1}{T} \int_{-T}^T f(t) dt$

The Fourier series of $f(t)$ is:

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(nt) + b_n \sin(nt)]$$

where a_n, b_n are the Fourier coefficients.

$$\begin{cases} a_n = \frac{1}{T} \int_{-T}^T f(t) \cos(nt) dt \\ b_n = \frac{1}{T} \int_{-T}^T f(t) \sin(nt) dt \end{cases}$$

$f(t)$ is periodic of period $2\pi = T$

[Exponential Fourier series

$$f(t) = \sum_{n=-\infty}^{\infty} F[n] \cdot e^{jnt}$$

$$F[n] = \frac{1}{T} \int_{-T}^T f(t) \cdot e^{-jnt} dt$$

if $f(t)$ is periodic with period T:

$$f(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\omega t) + b_n \sin(n\omega t)]$$

$$\omega = \frac{2\pi}{T}$$

$$a_n = \frac{2}{T} \int_{-T/2}^{T/2} f(t) \cos(n\omega t) dt$$

The n th term of the Fourier series:

$a_n \cos(n\omega t) + b_n \sin(n\omega t)$ is called the " n th harmonic" of it.

Its amplitude is:

$A_n = \sqrt{a_n^2 + b_n^2}$, $A_n^2 = a_n^2 + b_n^2$ is called energy of the n th harmonic.]

Relaxation Oscillators


- employ bistable devices; repeatedly charge/discharge a capacitor (usually).

Typ(2)

- typical waveforms - triangular, sawtooth, square, exponential

- Charging/discharging of a capacitor can be - linear - exponential

$\Delta t = \frac{C}{I} \Delta V$ (1)

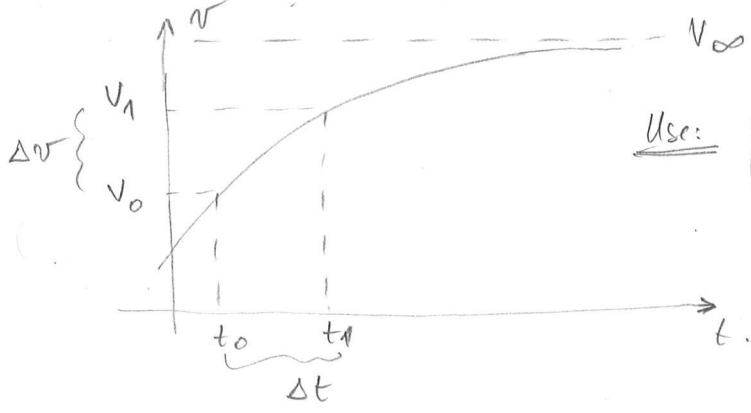

Use: $v(t) = V_{\infty} + [V_0 - V_{\infty}] \cdot e^{-\frac{t-t_0}{\tau}}$ Exercise! (its derivation)


to obtain: $\Delta t = \tau \cdot \ln \frac{V_{\infty} - V_0}{V_{\infty} - V_1}$ (2) very useful to compute T

10.1 Sine-wave generators

- 1) { Wien-bridge oscillator
quadrature oscillator
- 2) { triangular → sine conversion

Wien-bridge Oscillator

fascinating circuit!

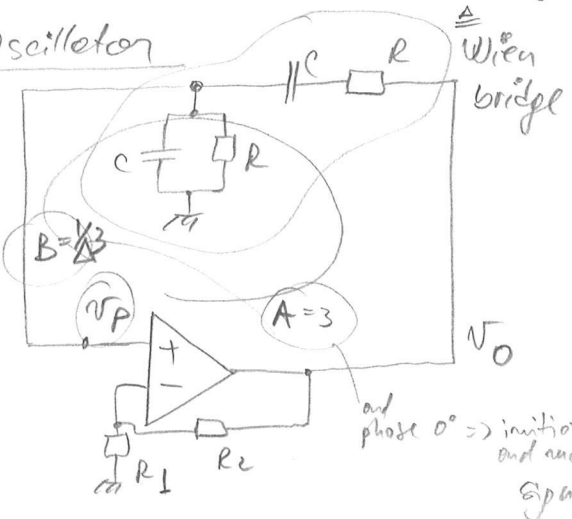

Wien bridge as positive feedback!

Can be seen as a noninverted amplifier:

$A = \frac{v_O}{v_P} = 1 + \frac{R_2}{R_1}$

and phase $0^\circ \Rightarrow$ initiated and maintained to signal!

The positive feedback:

$$v_p = \frac{z_p}{z_p + z_s} v_0 = B(jf)$$

$$\begin{cases} z_p = R \parallel \frac{1}{j2\pi f C} \\ z_s = R + \frac{1}{j2\pi f C} \end{cases}$$


$$\Rightarrow B(jf) = \frac{v_p}{v_0} = \frac{1}{3 + j\left(\frac{f}{f_0} - \frac{f_0}{f}\right)}$$

$$f_0 = \frac{1}{2\pi RC}$$

Therefore the loop gain (around the positive feedback loop):

$$T(jf) = A \cdot B = \frac{1 + R_2/R_1}{3 + j\left(\frac{f}{f_0} - \frac{f_0}{f}\right)} = \left(1 + \frac{R_2}{R_1}\right)$$

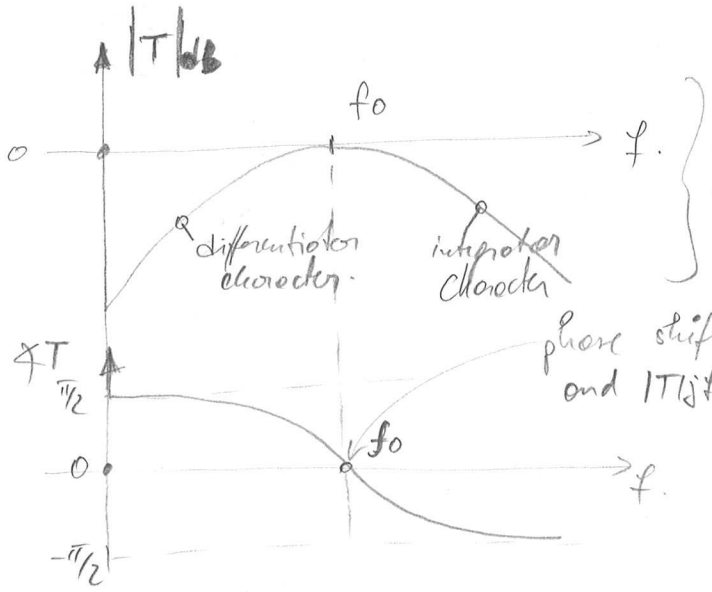Band-pass function!
 The peak value occurs at $f = f_0$.
 when $T(jf_0) = \frac{1}{3} \left(1 + \frac{R_2}{R_1}\right)$.




sort of let's go thru only the f_0 component and STOP the rest!
imagine the f_0 started and then maintained thru the positive loop!

Cases: ① $T(jf_0) < 1$ ($\Rightarrow A < 3$) \Rightarrow loop gain less than unity, & oscillations are degenerative.

- Negative feedback prevails over the positive one!

② $T(jf_0) > 1$ ($\Rightarrow A > 3$) \Rightarrow a disturbance will be amplified regeneratively.

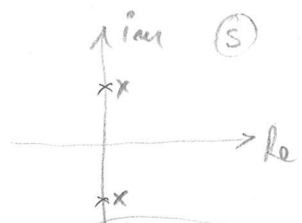- Oscillations build up.
- System is unstable
- Poles are in the right plane
- Positive feedback prevails




③ $T(jf_0) = 1$ ($\Rightarrow A = 3$) \Rightarrow oscillations ($\Rightarrow \frac{R_2}{R_1} = 2$)
 $\nabla T(jf_0) = 0^\circ, |T(jf_0)| = 1 \triangleq$ Barkhausen Criterion.

Issue: $A=3 \Leftrightarrow \frac{R_2}{R_1} = 2$ exactly is difficult to maintain due to component tolerances

Solution: **automatic amplitude control**: all practical oscillators must have it. (controls the amplitude too)

$\frac{R_2}{R_1}$ is made dependent on amplitude such that:

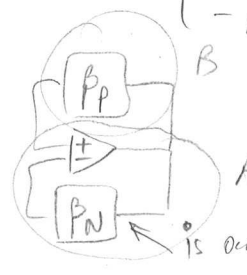- low signal levels $\Rightarrow \frac{R_2}{R_1} > 2$
 - high signal levels $\Rightarrow \frac{R_2}{R_1} < 2$
- \equiv poles in right half to ensure start-up!
 Δ amplitude stabilization!
 (Typically using nonlinear elements such as diodes)




is amplitude dependent / feedbacked negative feedback :-)

Observations-

- R_2/R_1 controls the amplitude stabilization in all practical oscillators!
- RC (the Wien bridge) controls the frequency of oscillations
- components have to be of good quality.
- How is V_{rms} (amplitude) determined? By what?




Oscillator generalization

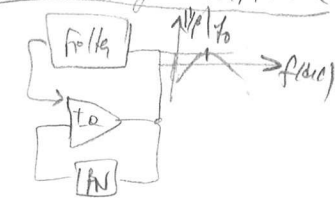

10.2. Multi-vibrators

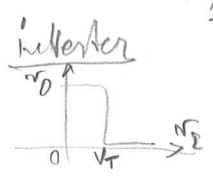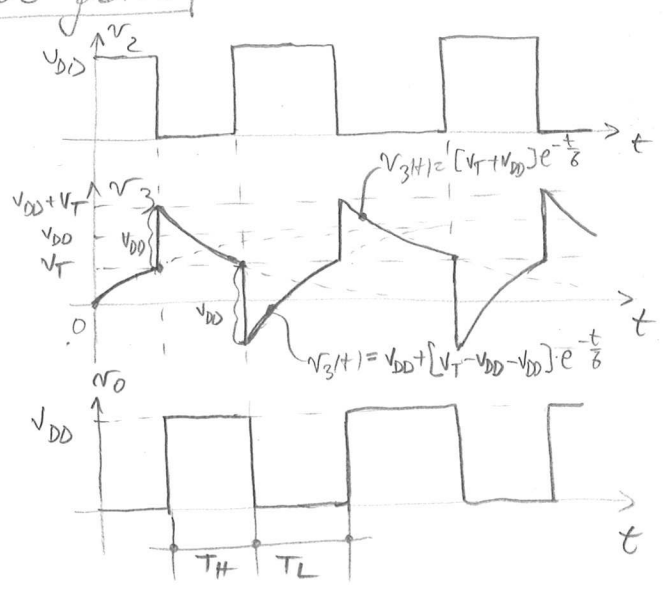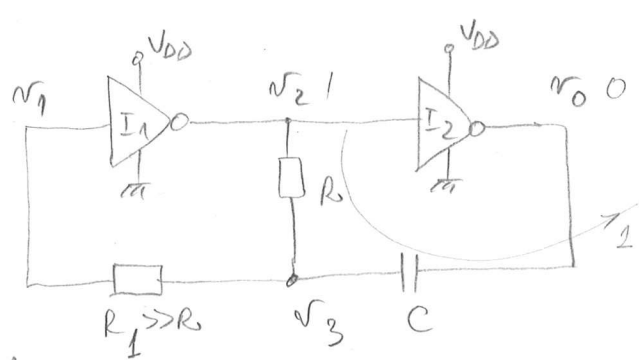- Exercise!
- Schmitt based (basic free-running)
 - square wave generator with selectable decodes.
 - single supply free-running.
 - CMOS Crystal Oscillator.
 - Monostable vibrator.

Free-running multivibrator using CMOS gates



$$f_0 = \frac{1}{T_H + T_L} = ?$$

$$v_C(t) = V_\infty - [V_\infty - V_0] e^{-\frac{t}{\tau}} = V_\infty + [V_0 - V_\infty] e^{-\frac{t}{\tau}} \quad (5)$$

Exercise: derive it!

case 1:

$$\Delta t = T_H, \quad \begin{cases} V_\infty = 0 \\ V_0 = V_T + V_{DD} \end{cases}, \quad V_1 = V_T \quad \left| \begin{array}{l} (10.3) \\ \Rightarrow T_H = \tau \cdot \ln \frac{0 - (V_T + V_{DD})}{0 - V_T} \end{array} \right.$$

$$\Rightarrow T_H = \tau \cdot \ln \frac{V_T + V_{DD}}{V_T}$$

$$\text{case 2: } \Delta t = T_L, \quad \begin{cases} V_\infty = V_{DD} \\ V_0 = V_T - V_{DD} \end{cases}, \quad V_1 = V_T \quad \left| \begin{array}{l} (10.3) \\ \Rightarrow T_L = \tau \cdot \ln \frac{V_{DD} - (V_T - V_{DD})}{V_{DD} - V_T} \end{array} \right. \Rightarrow$$

$$\Rightarrow T_L = \tau \cdot \ln \frac{2V_{DD} - V_T}{V_{DD} - V_T}$$

$$\Rightarrow T_H + T_L = T = \tau \cdot \ln \frac{V_T + V_{DD}}{V_T} \cdot \frac{2V_{DD} - V_T}{V_{DD} - V_T}, \quad \tau = RC$$

$$\Rightarrow f_0 = \frac{1}{T} = \frac{1}{RC \cdot \ln \frac{(V_T + V_{DD}) \cdot (2V_{DD} - V_T)}{(V_T - V_{DD}) \cdot (V_T)}}$$

$$\text{if } V_{DD}/2 = V_T \Rightarrow f_0 = \frac{1}{RC \cdot \ln 9} = \frac{1}{2.2 \cdot RC}$$

and $D(\%) = 50\%$