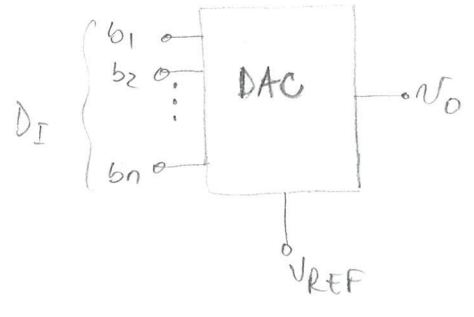


Ch. 12 Part 1  
 DA and AD converters  
 huge topic!



DA converters (DAC)

ideal transfer characteristic




$$V_o = k \cdot V_{REF} \cdot D_I$$

$$= k \cdot V_{REF} \left( b_1 \cdot \frac{1}{2} + b_2 \cdot \frac{1}{2^2} + \dots + b_n \cdot \frac{1}{2^n} \right)$$

$$= k \cdot V_{REF} \sum_{i=1}^n \frac{b_i}{2^i}$$

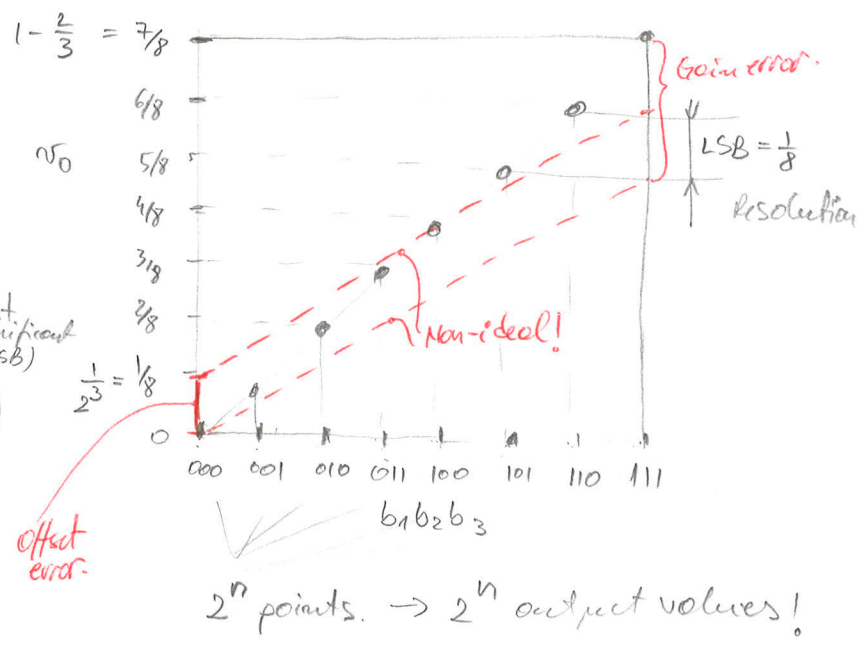Most significant (MSB)      Least significant (LSB)




This is called a multiplying DAC because  $V_o$  is obtained by multiplying  $V_{REF} \times D_I$


$$D_I = b_1 \cdot 2^{-1} + b_2 \cdot 2^{-2} + \dots + b_n \cdot 2^{-n}$$

- Definitions:
- full scale range (FSR):  $V_{FSR} = k \cdot V_{REF}$
  - full scale value (FSV):  $V_{FSV} = (1 - 2^{-n}) V_{FSR}$
  - Resolution: LSB is  $\frac{V_{FSR}}{2^n}$
  - integral nonlinearity
  - differential nonlinearity

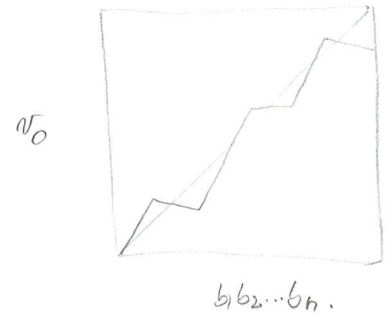
The most important characteristic is **monotonicity**


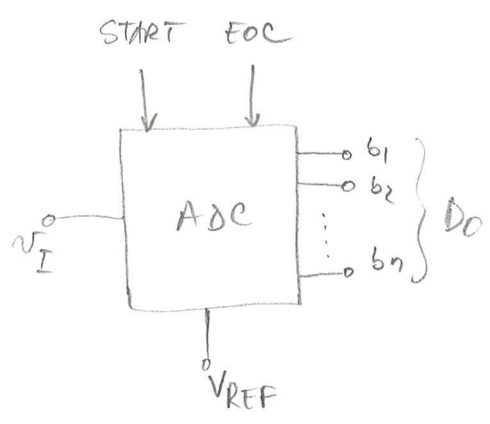
# AD converters (ADC) - provides the inverse function of DAC!




$$D_0 = b_1 b_2 b_3 \dots b_n$$

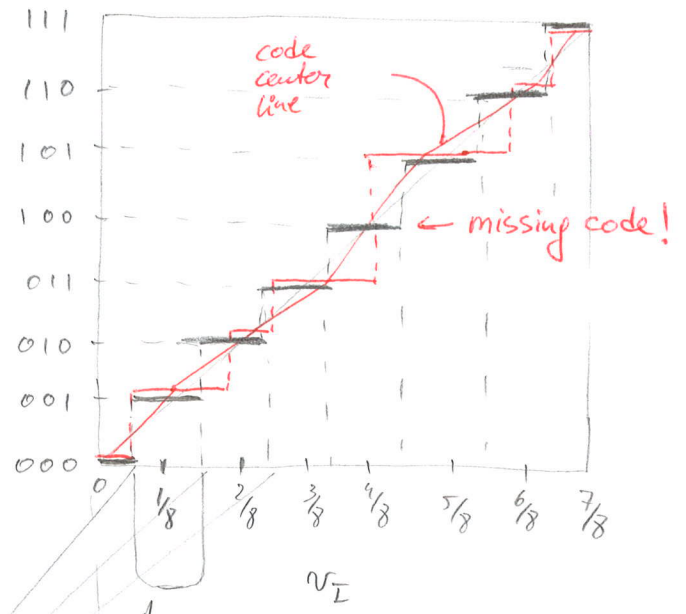

$$D_0 = b_1 \cdot \frac{1}{2} + b_2 \cdot \frac{1}{2^2} + \dots + b_n \cdot \frac{1}{2^n}$$

$$= \frac{V_I}{K \cdot V_{REF}} = \frac{V_I}{V_{FSR}}$$

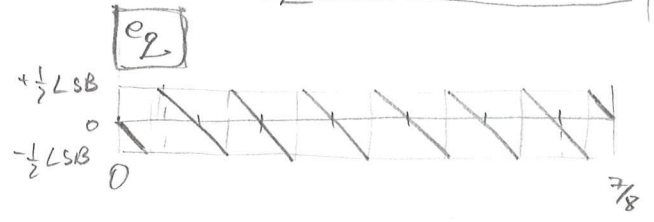Any input value in this range will be coded as 001! We have an error.  $\hat{=}$  quantization error. [eq]




ideally these transitions take place at odd numbers of  $\frac{1}{2}$  LSB! if not we have nonlinearity/error.

Conversion time  $\hat{=}$  time for ADC to complete the transition!

Examples

1) Weighted Resistor DAC

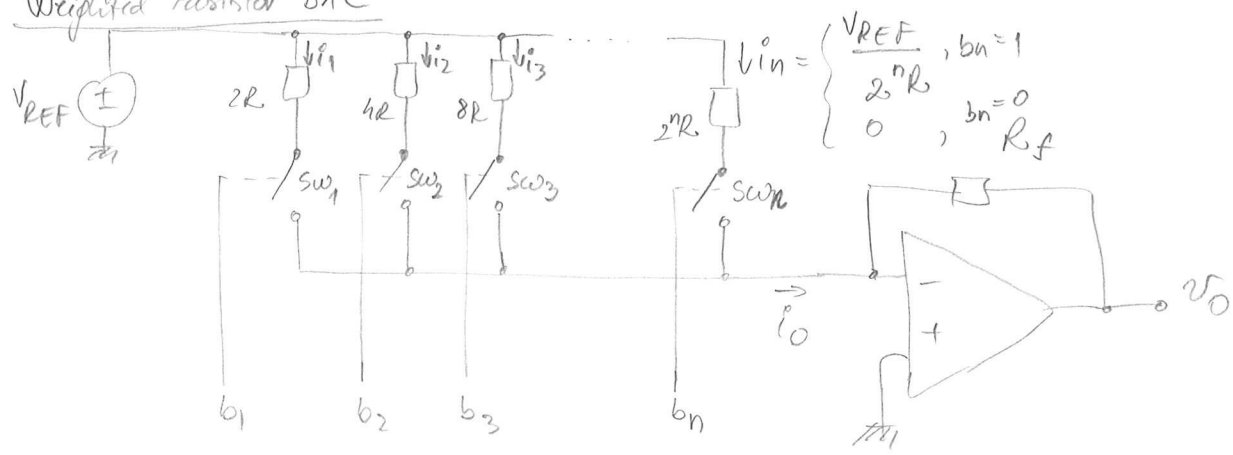

$$v_{in} = \begin{cases} \frac{V_{REF}}{2^n R}, & b_n = 1 \\ 0, & b_n = 0 \end{cases} R_f$$

$$\frac{v_O}{R_f} = -i_O$$


$$v_O = -\frac{R_f}{R} \cdot V_{REF} \cdot \left( b_1 \frac{1}{2} + b_2 \frac{1}{4} + b_3 \frac{1}{8} + \dots + b_n \frac{1}{2^n} \right)$$

Drawbacks: - non zero switch resistances!

- a wide spread of resistance values: exponential increase!

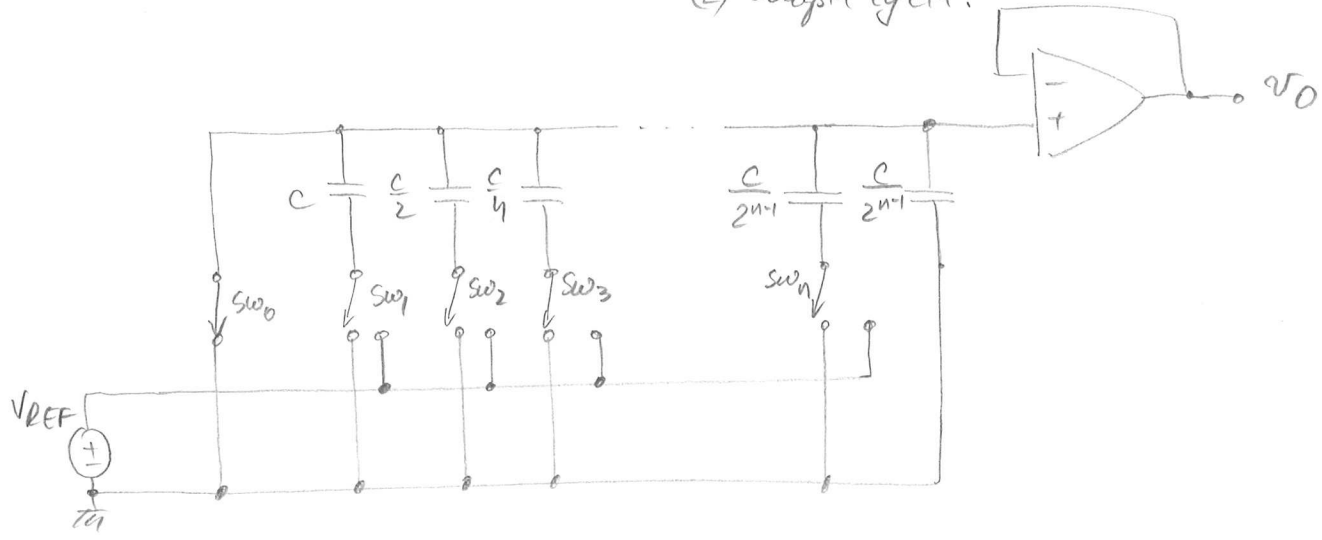2) Weighted-capacitor DAC

Operation alternates between (1) reset cycle: for resetting.  
(2) sample cycle.




$$v_O = V_{REF} \cdot \frac{C_r}{C_t} = 2C$$

$C_r = \sum$  of capacitances connected to  $V_{REF}$   
 $C_t = \sum$  of all capacitors!

$$v_O = V_{REF} (b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n})$$



5) Current-mode R-2R ladder

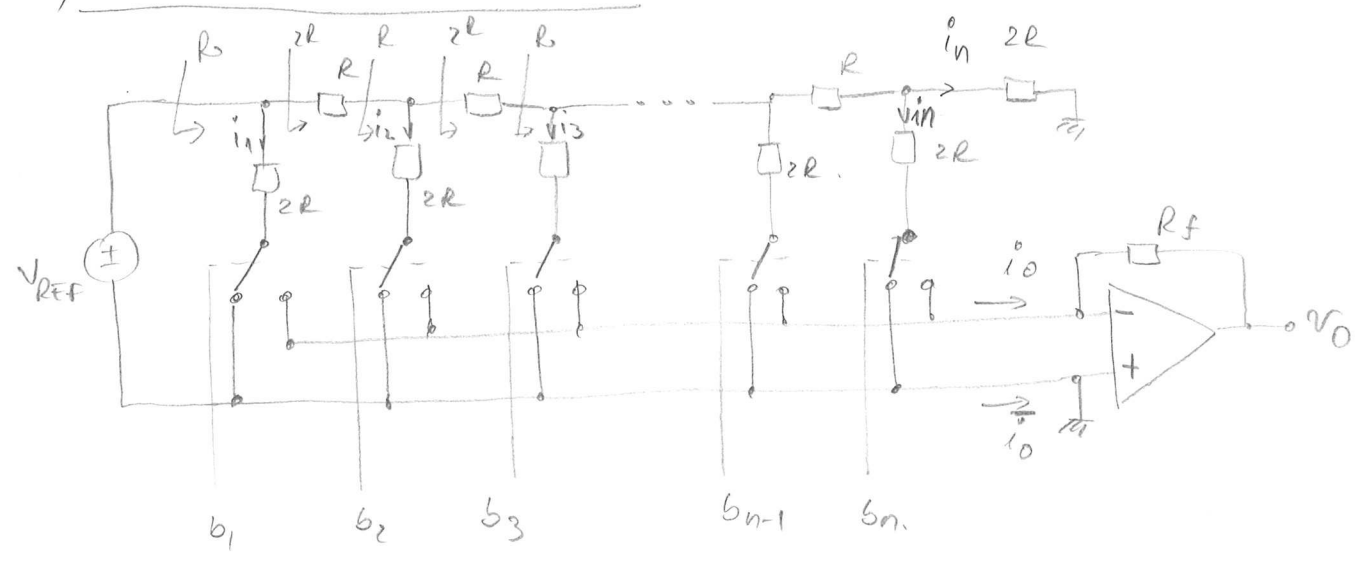

$$\begin{cases}
 i_1 = \frac{V_{REF}}{2R} = \frac{V_{REF}}{R} \cdot \frac{1}{2} \\
 i_2 = \frac{V_{REF}}{4R} = \frac{V_{REF}}{R} \cdot \frac{1}{2^2} \\
 \dots \\
 i_n = \frac{V_{REF}}{R} \cdot \frac{1}{2^n}
 \end{cases}$$

$$v_o = -i_o \frac{R_f}{R_f}$$

$$v_o = -R_f \cdot i_o$$


$$v_o = -\left(\frac{R_f}{R}\right) V_{REF} \left( b_1 \cdot \frac{1}{2} + b_2 \cdot \frac{1}{2^2} + \dots + b_n \cdot \frac{1}{2^n} \right)$$

$$\triangleq K = -\frac{R_f}{R}$$

Note that  $i_o + \bar{i}_o = (1 - 2^{-n}) \frac{V_{REF}}{R}$  regardless of  $D_I = b_1 b_2 \dots b_n$  !

$\bar{i}_o \triangleq$  is said to be complementary to  $i_o$ .

6) Voltage-mode R-2R ladder

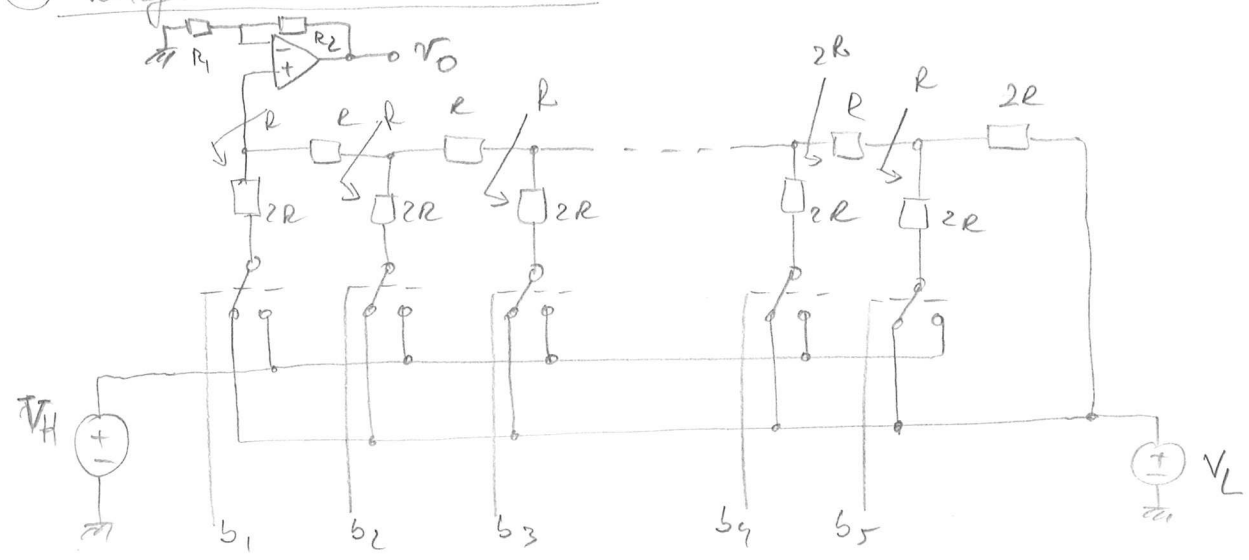

$$LSB = \frac{V_H - V_L}{2^n}$$

from  $V_L \div \left(1 - \frac{1}{2^n}\right) (V_H - V_L)$

$$K = 1 + \frac{R_2}{R_1}$$


Advantage: we can interpolate between any  $V_L, V_H$

# Segmentation

High resolution DAC are obtained (for  $n > 12$ ) using a hybrid approach.


The idea:

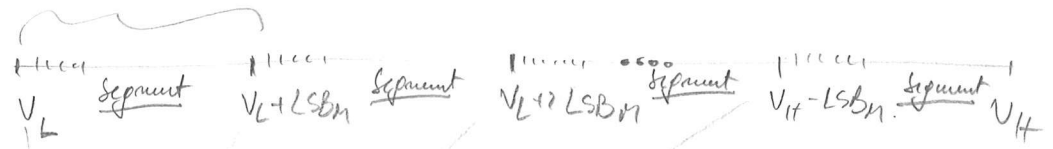Master  $LSB_M = \frac{1}{2^4} (V_H - V_L)$     16 segments in this case!



16 bit DAC

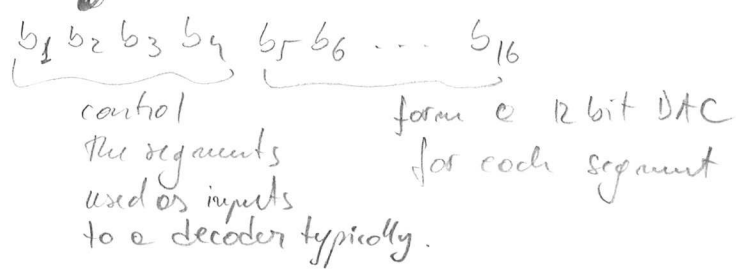- 1) Divide it into 16 equal segments, sum of segments acts as bits.
- 2) Every segment, there is interpolated by the same 12 bit DAC.



⊕ In this way monotonicity is easier to achieve!