
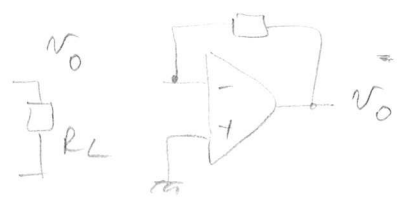
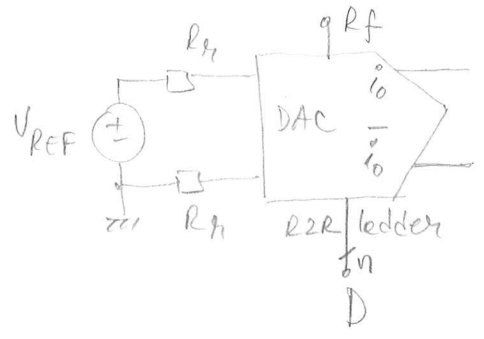



Ch. 12 Part 2

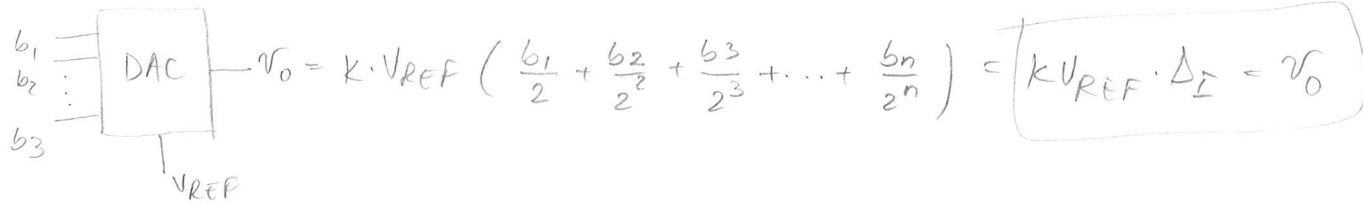• We talked about digital to analog converters DAC




$i_0 = \frac{V_{REF}}{R_n} \left(\frac{b_1}{2} + \frac{b_2}{2^2} + \dots + \frac{b_n}{2^n} \right)$

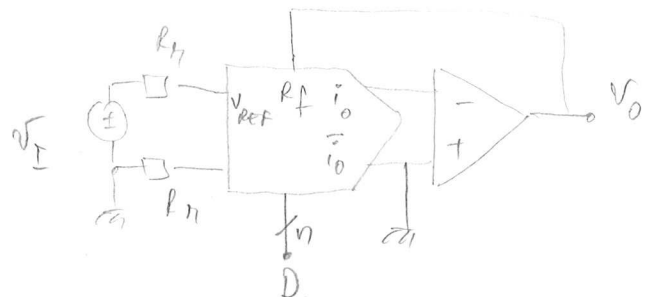• Digitally programmable attenuators and amplifiers.




$V_0 = -D \cdot V_I$, $D = \frac{b_1}{2} + \frac{b_2}{2^2} + \dots + \frac{b_n}{2^n}$.

Analog to digital converters

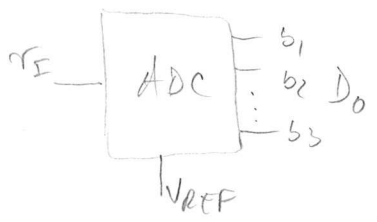


$V_I = K V_{REF} \cdot D_0$
 $D_0 = \frac{V_I}{K V_{REF}}$


(a) Successive Approximation ADC

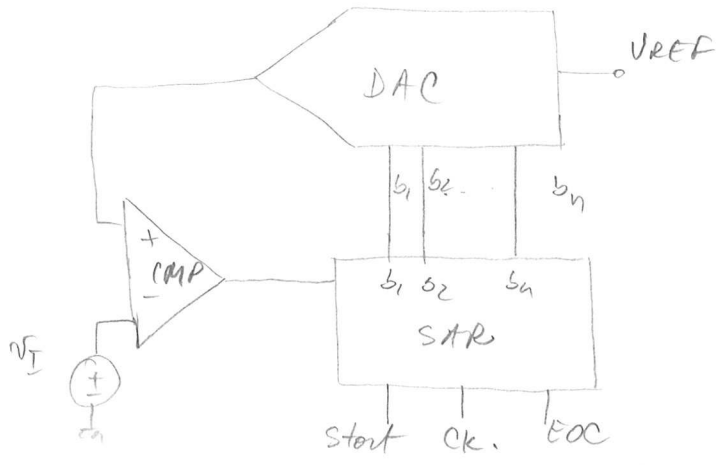

⑥ integrating converters **ADC**

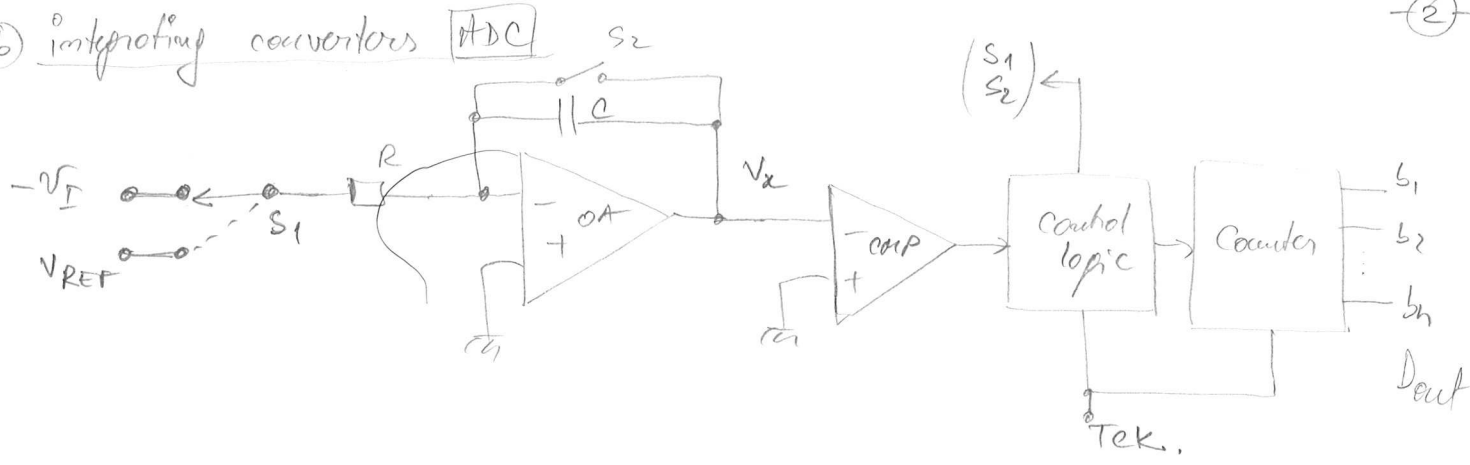

Phase 1: $S_1 = -V_I$
 C charges through the integrator, till $\frac{V_I \cdot T_1}{RC}$
 for 2^n clock cycles: $T_1 = 2^n T_{ck}$

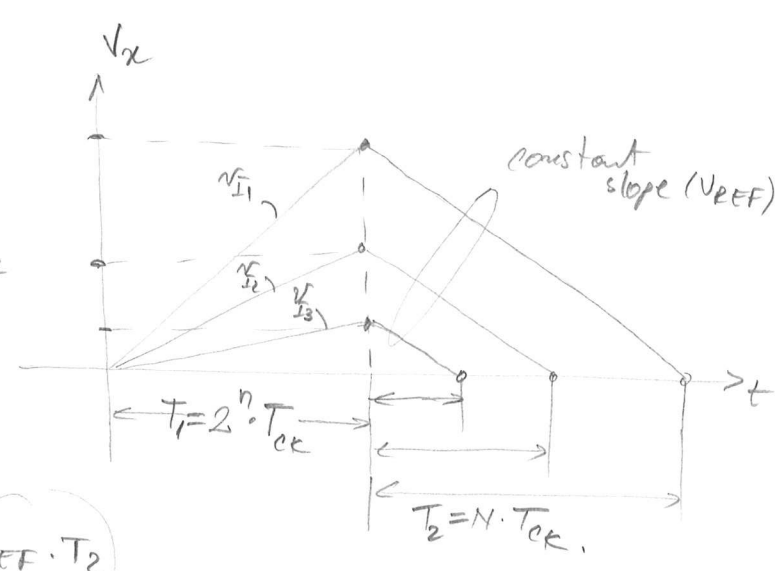

Phase 2: $S_2 = V_{REF}$
 C discharges and
 $T_2 = N T_{ck}$ so that: $\frac{V_{REF} \cdot T_2}{RC}$

$$\frac{V_I T_1}{RC} = \frac{V_{REF} T_2}{RC} \Rightarrow T_2 = T_1 \frac{V_I}{V_{REF}}$$

$$N = 2^n \frac{V_I}{V_{REF}}$$

OSs: - The idea is that N is proportional to V_I
 = useful in slow speed applications!
 - for faster operation use flash-converters!