


Ch.3 Part 2

Finish stability discussion of last time.

3.2 First-order active filters ← mention only this

- Derivators → Exercise!
- integrators

s
 $-\frac{1}{s}$

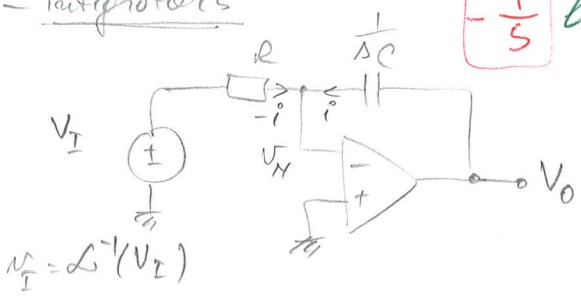


$\frac{V_O}{\frac{1}{sC}} = -\frac{V_I}{R} \Rightarrow H(s) = \frac{V_O}{V_I} = \left(-\frac{1}{sRC}\right) \Rightarrow$
 $\Rightarrow H(j\omega) = -\frac{1}{j\frac{\omega}{\omega_0}}, \omega_0 = \frac{1}{RC}$

inverting integrator


$V_I = \mathcal{L}^{-1}(V_I)$

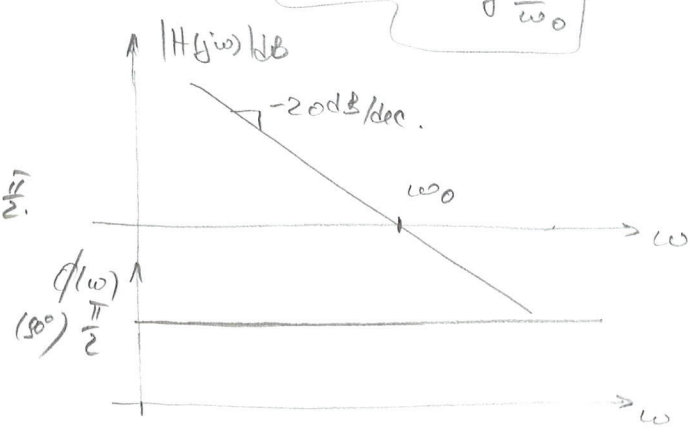$\phi(\omega) = \pi - \arctan \frac{\omega/\omega_0}{0} = \pi - \frac{\pi}{2} = \frac{\pi}{2}$



- Deboo integrator

Nic

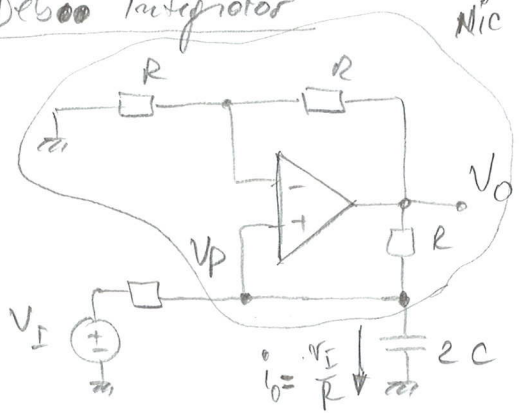

$\frac{1}{s}$

$H(s) = \frac{1}{sRC}$
non inverting!

- Low-pass filter with gain → Exercise!


$\frac{1}{s\tau_1}$

High-pass filter with gain

HP

Question: how do you expect the transfer function to be?

$$\frac{s}{s+p_1}$$

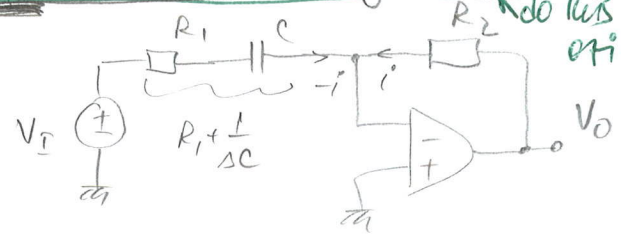

$$\frac{V_O}{R_2} = -\frac{V_I}{R_1 + \frac{1}{sC}} \Rightarrow H(s) = \frac{V_O}{V_I} = -\frac{R_2}{R_1 + \frac{1}{sC}} = -\frac{R_2}{1 + \frac{1}{sRC}} = -\frac{R_2}{R_1} \cdot \frac{R_1 \cdot s}{1 + R_1 C s}$$

$$H(j\omega) = H_0 \cdot \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}$$


← zero in the origin
pole at $s = -\frac{1}{R_1 C}$

$$\omega_0 = \frac{1}{R_1 C}$$

$$H_0 = -\frac{R_2}{R_1}$$

$$H(j\omega) = -\frac{R_2}{R_1} \cdot \frac{j\frac{\omega}{\omega_0}}{1 + j\frac{\omega}{\omega_0}}$$

$$|H(j\omega)| = \frac{\left|\frac{R_2}{R_1}\right| \cdot \sqrt{\left(\frac{\omega}{\omega_0}\right)^2}}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

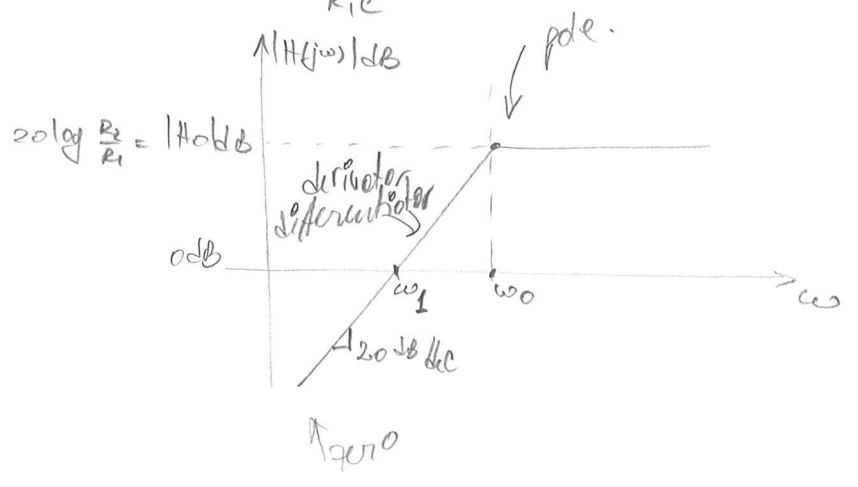


Gain: $G(\omega) = |H(j\omega)|_{dB}$

$$= 20 \log \frac{R_2}{R_1} + 20 \log \frac{\omega}{\omega_0} - 20 \log \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2} = \begin{cases} 20 \log \frac{R_2}{R_1} + 20 \log \frac{\omega}{\omega_0} & , \omega \rightarrow 0 \\ 20 \log \frac{R_2}{R_1} & , \omega \rightarrow \infty \end{cases}$$

Phase: $\phi(\omega) = \arg\left(-\frac{R_2}{R_1}\right) + \arg\left(j\frac{\omega}{\omega_0}\right) - \arg\left(1 + j\frac{\omega}{\omega_0}\right) = \arg\left(\frac{R_2}{R_1} j\frac{\omega}{\omega_0}\right) - \arg\left(1 + j\frac{\omega}{\omega_0}\right)$

$$= -\pi + \arg\left(\frac{\omega/\omega_0}{0}\right) - \arg\left(\frac{\omega/\omega_0}{1}\right) = -\pi + \frac{\pi}{2} - \frac{\pi}{2} = -\pi$$
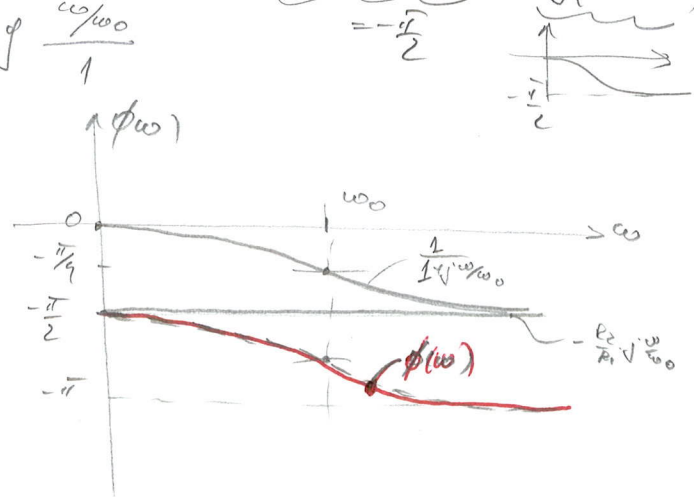
$$= -\frac{\pi}{2} = \arg\left(\frac{\omega}{\omega_0}\right)$$




- Wideband pass filter - Exercise.

- Phase shifters

$$\frac{s}{(s+p_1)(s+p_2)}$$

obtained from HP and adding one more pole at higher frequencies.

(3)

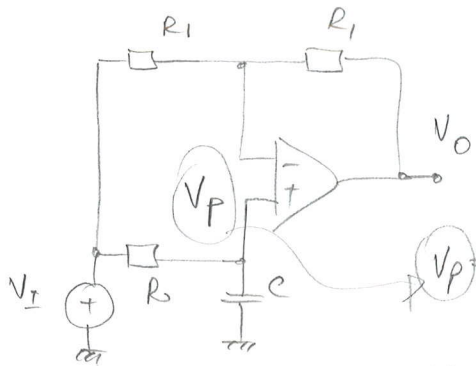


$$\frac{1}{R + \frac{1}{sC}} V_I = \frac{1}{1 + sRC} V_I$$

$$V_O = \left(1 + \frac{R_1}{R_1}\right) \cdot V_P - \frac{R_1}{R_1} V_I =$$

$$= 2 \cdot \frac{1}{1 + sRC} V_I - V_I = \frac{1 - sRC}{1 + sRC} V_I$$

$$H(s) = \frac{V_O}{V_I} = \frac{1 - sRC}{1 + sRC}$$
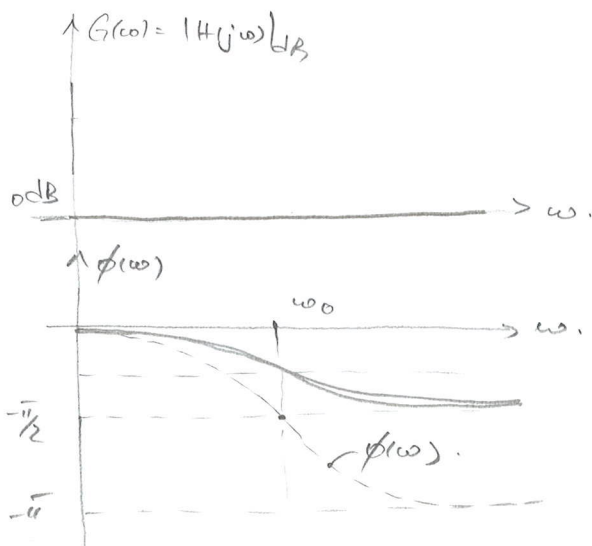
$$H(j\omega) = \frac{1 - j\frac{\omega}{\omega_0}}{1 + j\frac{\omega}{\omega_0}}, \quad \omega_0 = \frac{1}{RC}$$



$$\phi(\omega) = -20 \text{ deg} \frac{\omega}{\omega_0} - 20 \text{ deg} \frac{\omega}{\omega_0}$$

3.3 Audio filter applications

- Phono preamplifier
- Tone preamplifier
- Active tone control
- Graphic Equalizer

3.4 Standard Second-order Responses

Standard form: $H(s) = \frac{N(s)}{\left(\frac{s}{\omega_0}\right)^2 + 2\zeta\left(\frac{s}{\omega_0}\right) + 1}$

Lost time: $H(s) = s^2 + 2\zeta s + \omega_0^2$
 $\omega_0 = \zeta \omega_0$

Poles: $P_{1,2} = \omega_0 \left(-\zeta \pm \sqrt{\zeta^2 - 1} \right)$

$\zeta \triangleq$ damping ratio

$\zeta > 1 \Rightarrow$ poles are real \Rightarrow Natural response are two decaying exponentials.
 is overdamped




$0 < \zeta < 1 \Rightarrow$ poles are complex and conjugate in the LHP of the complex plane.

$P_{1,2} = -\zeta \omega_0 \pm j \omega_0 \sqrt{1 - \zeta^2}$


Natural response is underdamped

$x_0(t) = 2|A|e^{-\zeta \omega_0 t} \cos(\omega_0 \sqrt{1 - \zeta^2} t + \phi)$

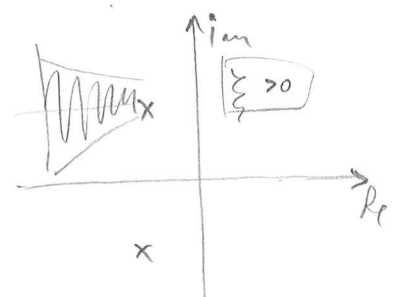

$\zeta = 0 \Rightarrow$ poles on an imaginary axis

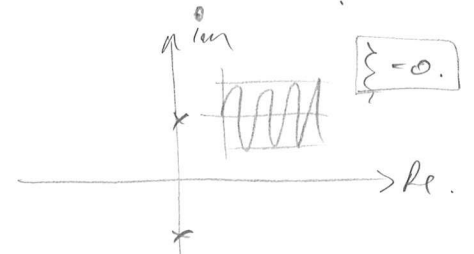Natural response is undamped \Rightarrow oscillations occur.




$\zeta < 0 \Rightarrow$ poles are complex and conjugate in the RHP

Natural response is diverging.

$x_0(t) = 2|A|e^{-\zeta \omega_0 t} \cos(\omega_0 \sqrt{1 - \zeta^2} t + \phi)$

$\zeta < 0 \Rightarrow e^{-\zeta \omega_0 t} \Rightarrow e^{|\zeta| \omega_0 t}$

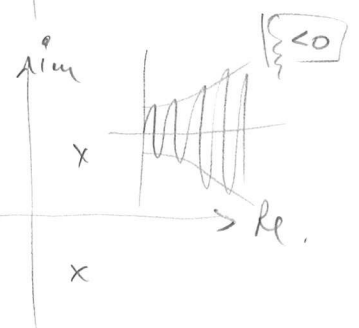

$s \rightarrow j\omega$

$$H(j\omega) = \frac{N(j\omega)}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{1}{Q}\left(\frac{\omega}{\omega_0}\right)}$$

with new notation:

$$Q = \frac{1}{2\xi}$$

$$Q = \frac{\omega_0}{2\alpha} = \frac{1}{2\xi}$$

My notation

$$\alpha = \xi\omega_0$$

Use this to obtain the discussion in the textbook!

- The Low-pass (LP) Response H_{LP}


$$H_{LP}(j\omega) = H_{OLP} \cdot H_{LP}(j\omega)$$

$H_{OLP} \triangleq$ dc gain.

$$H_{LP}(j\omega) = \frac{1}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{\omega}{\omega_0} \cdot \frac{1}{Q}}$$

Using last time notation
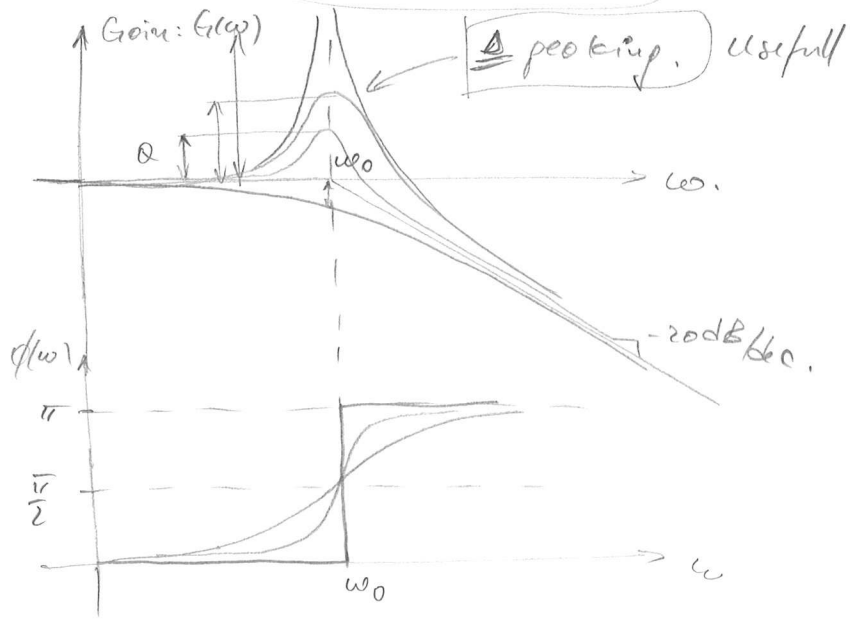
$$H(s) = \frac{1}{s^2 + 2\xi s + \omega_0^2}$$




- The High-Pass (HP) Response H_{HP}

$$H(s) = \frac{s^2}{s^2 + 2\xi s + \omega_0^2}$$

$$H_{HP}(j\omega) = \frac{-\left(\frac{\omega}{\omega_0}\right)^2}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{1}{Q}\frac{\omega}{\omega_0}}$$

- The Band-Pass (BP) Response H_{BP}

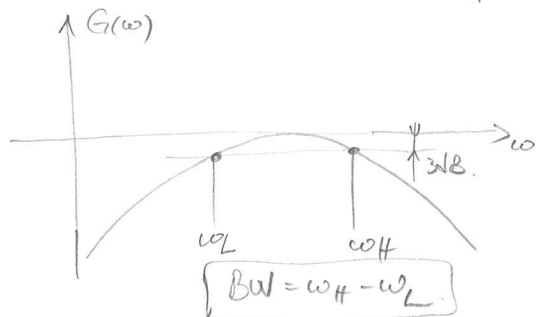

$$H_{BP}(j\omega) = \frac{j\frac{\omega}{\omega_0} \cdot \frac{1}{Q}}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{1}{Q}\frac{\omega}{\omega_0}}$$

- The Notch Response H_N

$$H_N(j\omega) = \frac{1 - \left(\frac{\omega}{\omega_0}\right)^2}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{1}{Q} \cdot \frac{\omega}{\omega_0}}$$

$$= H_{LP} + H_{HP} = 1 - H_{BP} = H_N$$

- The all-pass response H_{AP}

$$H_{AP}(j\omega) = \frac{1 - \left(\frac{\omega}{\omega_0}\right)^2 - j\frac{\omega}{\omega_0} \cdot \frac{1}{Q}}{1 - \left(\frac{\omega}{\omega_0}\right)^2 + j\frac{\omega}{\omega_0} \cdot \frac{1}{Q}}$$