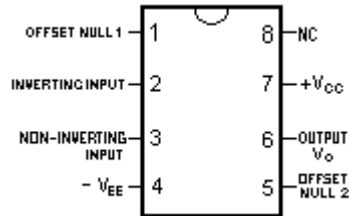


Lab 4: *Basic Operational Amplifier Circuits*

Objective: To verify the operation of two common operational amplifier (op amp) circuits.

Equipment Needed: Lab kit, CADET, multimeter (DMM), power supply.

Note: the pin definitions for the LM741 op amp are shown to the right.



Part I. Summing Amplifier

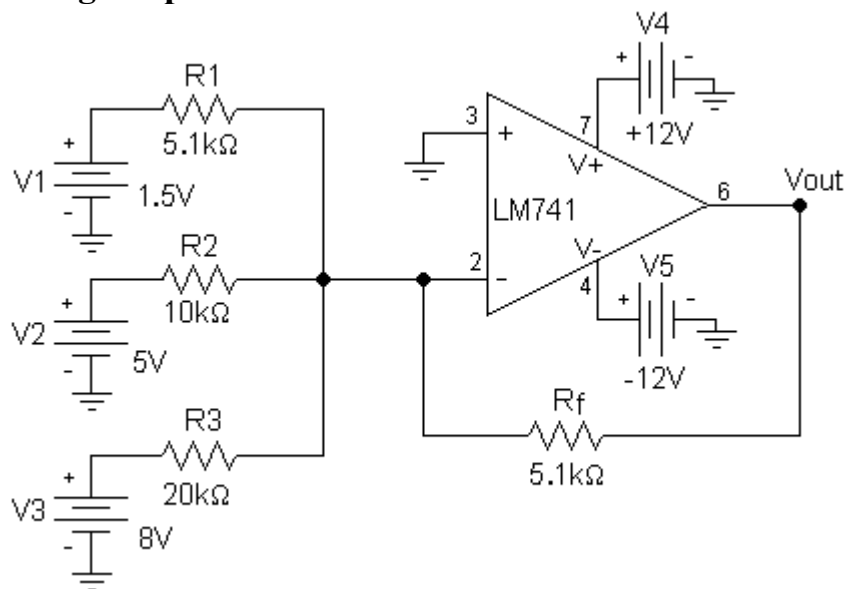


Figure 1. Summing Amplifier

- Construct the circuit shown in Fig. 1 using parts from your lab kit. Set $V^+ = 12\text{ V}$ and $V^- = -12\text{ V}$ (V^+ and V^- can be obtained from the CADET power supplies).
- In addition to the values shown, apply at least two different sets of values of V_1 and V_3 (from the separate power supply), where V_1 and V_3 are smaller and different from 1.5 V and 8 V , respectively. Use the DMM to measure the input voltages V_1 , V_2 , and V_3 and output voltage V_{out} . Show that the following relationship holds for each measurement:

$$V_{out} = -\left(\frac{R_f}{R_1}\right) \times V_1 - \left(\frac{R_f}{R_2}\right) \times V_2 - \left(\frac{R_f}{R_3}\right) \times V_3$$

Part II. Differential Amplifier

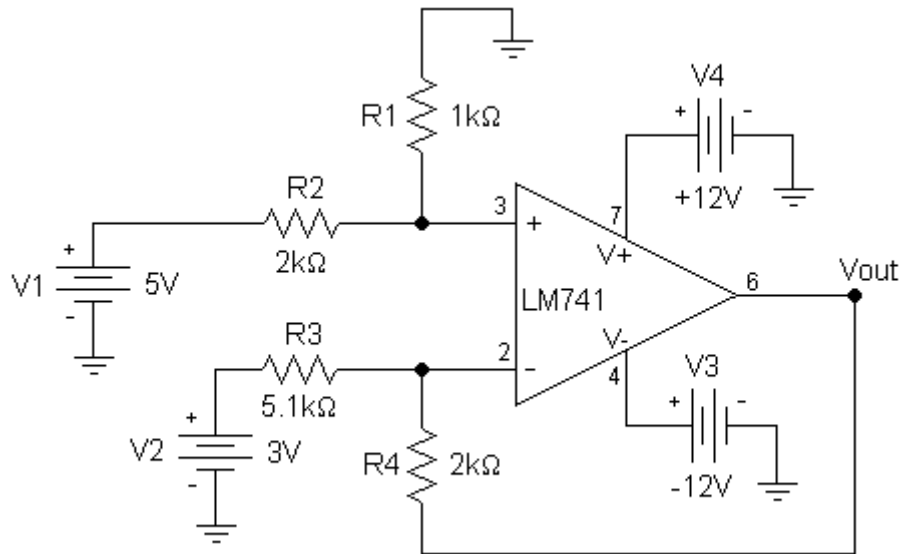


Figure 2. Differential Amplifier

- Construct the circuit shown in Fig. 2. Again set $V^+ = 12\text{ V}$ and $V^- = -12\text{ V}$.
- Apply 5.0 V dc to $V1$ and 3.0 V dc to $V2$, and then measure V_{out} . Exchange the resistance value of $R4$ for the value of $R1$, and the value of $R1$ for $R4$, and measure V_{out} . Then exchange the values of $R2$ and $R3$ in the same manner and measure V_{out} . Show that the following relationship holds for each measurement:

$$V_{out} = V1 \times \left(\frac{(R3 + R4) \times R1}{(R1 + R2) \times R3} \right) - V2 \times \left(\frac{R4}{R3} \right)$$

- Analytically solve the circuit in Fig. 2 for V_{out} , assuming the ideal op amp model.

Report:

Your lab report should include all recorded data, calculations, and discussion. Your report is due at the next simulation period.