
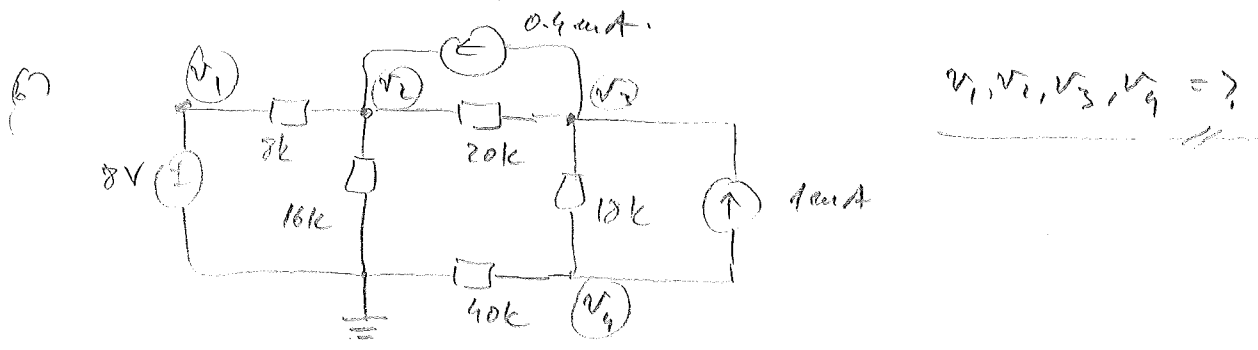




- ①- Nodal analysis
- ②- Mesh analysis
- ③- Thevenin/Norton equivalent } also super-node, super-mesh?
- ④- General N/A & L/A or Superposition
- A surprise - counting trick you can solve as you like.

① Nodal analysis


(pp. 109, Franco)

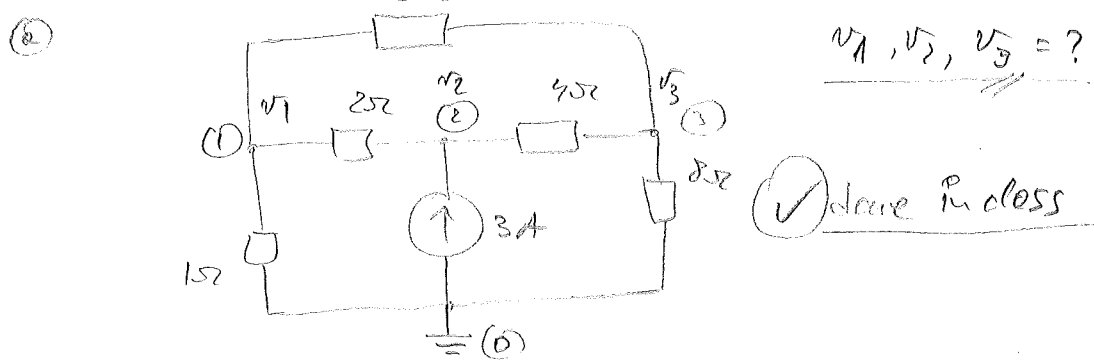

③ Superposition

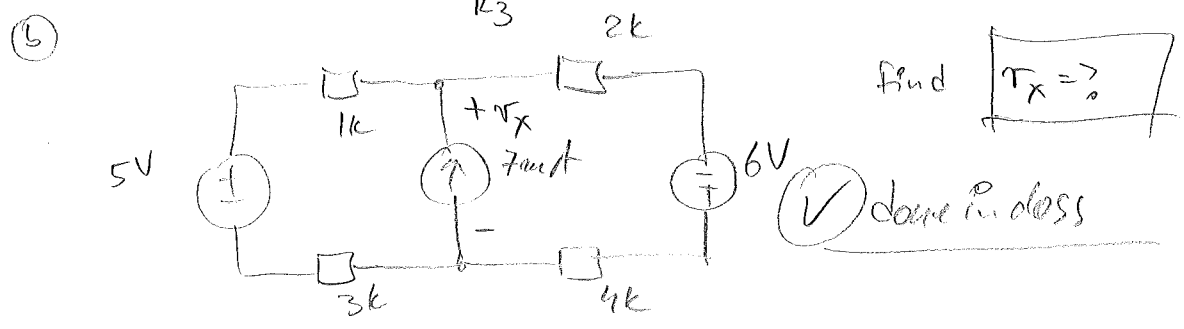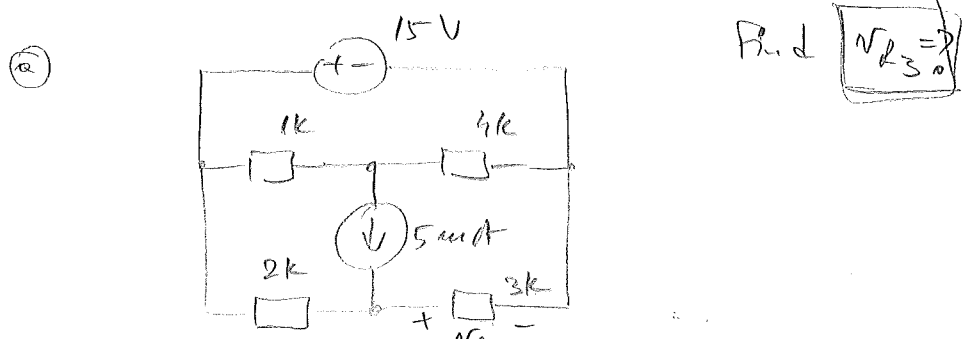


2 Mesh/loop analysis

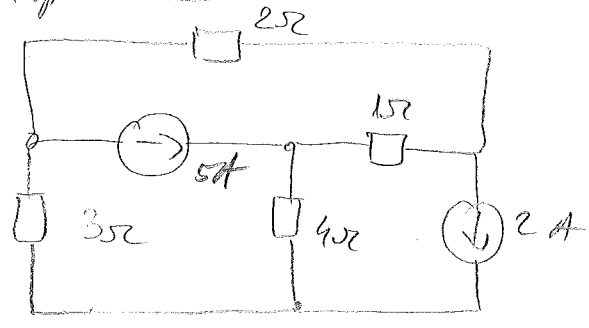

Apply loop analysis to find the power dissipated by R_4 .

4 Thevenin's theorem

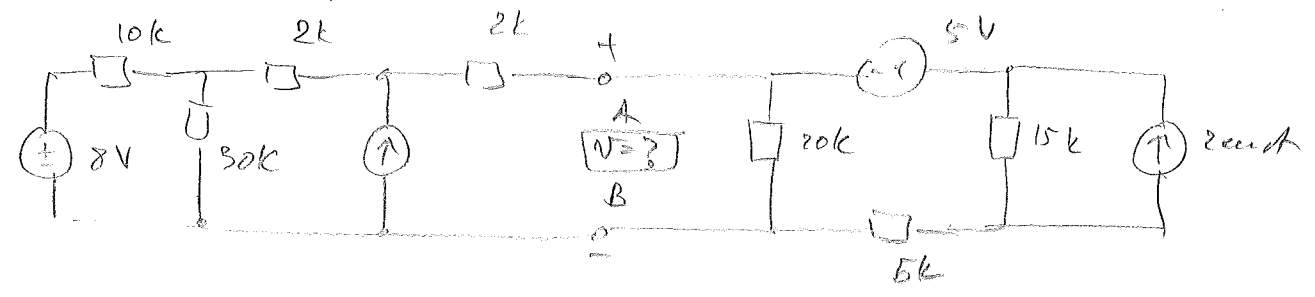

5 General loop analysis

see work # 8 Friday (blue sign)