
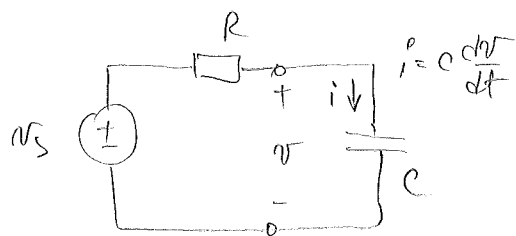


Natural response of RL and RC circuits

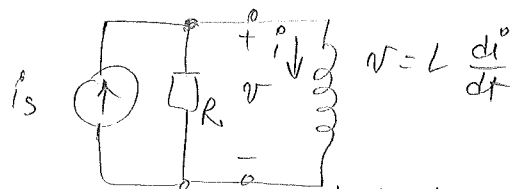- Analysis of RLC circuits still done using KCL & KVL
- However C, L have i-v characteristics that depend on time, equations are not anymore algebraic, they involve time derivatives, or integrals or both!
- When we have only one Capacitor or Inductor the circuit could be reduced using Thevenin or Norton equivalents to:



(a) "capacitive" case



(b) "inductive" case.

Basic first-order circuits! whose functioning is governed by first-order differential equations

(a)

$$i = C \frac{dv}{dt}$$

$$\text{KVL: } v_s = R \cdot i + v = RC \frac{dv}{dt} + v$$

$$\boxed{RC \frac{dv}{dt} + v = v_s} \quad (1)$$

(b)

$$v = L \frac{di}{dt}$$

$$\text{KCL: } i_s = \frac{v}{R} + i = \frac{L}{R} \frac{di}{dt} + i$$

$$\boxed{\frac{L}{R} \frac{di}{dt} + i = i_s} \quad (2)$$

Note that both equations are of the type:

$$\tau \frac{dy(t)}{dt} + y(t) = x(t) \quad (3)$$

has the dimension of time [s]

the unknown variable

the "forcing" or the input.

$$\boxed{\tau = RC} \quad (4)$$


$$\boxed{\tau = \frac{L}{R}} \quad (5)$$

This is a differential equation of the first order.

∴ first-order circuits!

we'll solve first (3) for the simple case when $x(t) = 0$!

The source-free or natural response

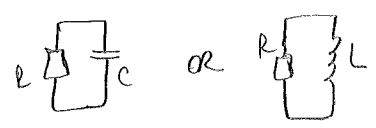

- Let: $x(t) = 0$ (could be $v_s = 0$ or $i_s = 0$!)

(3) $\Rightarrow \tau \frac{dy(t)}{dt} + y(t) = 0$ (6)

- This is homogeneous differential equation.
- its solution is the homogeneous solution, or the source-free solution for the RC and RL circuits!



$y = -\tau \frac{dy}{dt}$ (the unknown and its derivative must be the same!)

- Recall from calculus, that only the exponential function enjoys the unique property that its derivative is still exponential!
- So, we assume or guess (see pp. 258 of textbook) a solution of the type:

$y(t) = A \cdot e^{st}$ (7)

($e = 2.718$ the base of natural logarithms)

Still, we need to find $A, s = ?$

(i) Substitute (7) in (6):

$s = ?$

$\tau s \cdot A \cdot e^{st} + A e^{st} = 0$

$(\tau s + 1) \cdot A e^{st} = 0$

- we seek a solution $A e^{st} \neq 0$. Therefore: $\tau s + 1 = 0$ (8) $\Rightarrow s = -\frac{1}{\tau}$ (9)

Δ the characteristic equation!

- $s = -\frac{1}{\tau}$ has the dimensions of the reciprocal of time. $\Rightarrow s$ is called the natural frequency, the characteristic freq $\left[\frac{Np}{s}\right]$ or the critical frequency.

Np is dimensionless.

(ii) Use the initial condition $y(0)$ in the circuit =

$A = ?$

= { initial voltage across the capacitor in the circuit } which are related to the initial stored energy: $\begin{cases} w(t) = \frac{Cv^2(t)}{2} \\ w(t) = L \frac{i^2(t)}{2} \end{cases}$

- So, let $t \rightarrow 0$ in (7) $\Rightarrow y(0) = A$

- So, finally the solution is $y(t) = y(0) \cdot e^{-\frac{t}{\tau}}$ (10)

Extremely important!

$y(0) = V_0$ for circuit (a) RC


$y(0) = I_0$ for circuit (b) RL

- $y(t)$ is an exponentially decaying function, from initial value $y(0)$ to final value $y(\infty) = 0$.

- This decay depends only on $y(0)$ and τ ! which are peculiar characteristics of the circuit irrespective of any particular forcing function, this solution is called the **natural response**.


or. **source-free response**

or. **homogeneous solution**!

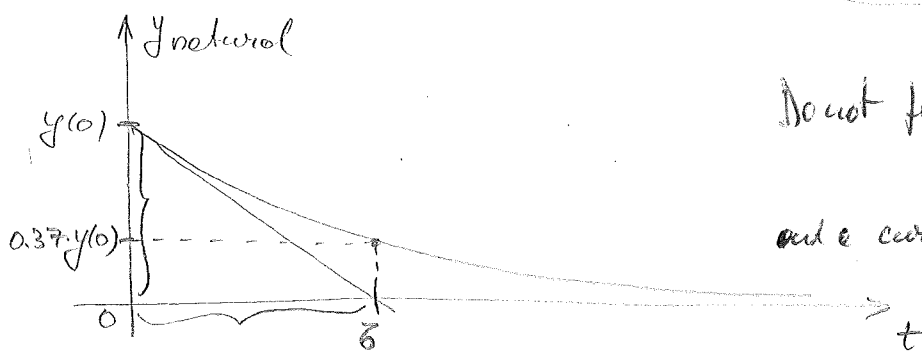

Don't forget y is a voltage for $\tau = RC$



and a current for $\tau = \frac{L}{R}$

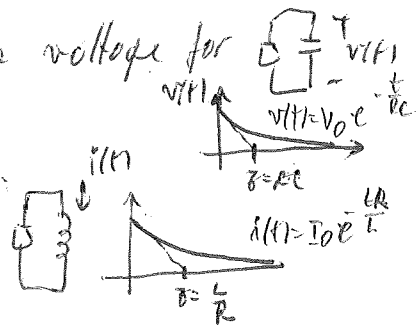

$\tau = RC$

$\tau = \frac{L}{R}$

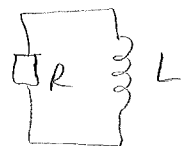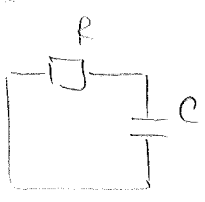is a measure of how rapidly the exponential decay takes place!



(1) τ represents the time it takes for the natural response to decay to $\frac{1}{e} \approx 37\%$ of its initial value

(2) τ represents the time at which the tangent to the natural response in the origin intercepts t axis.

