

Response to DC and AC forcing functions

$$x(t) \neq 0$$

General solution to the differential equation

$$\tau \frac{dy(t)}{dt} + y(t) = x(t) \quad \left| \times \frac{1}{\tau} e^{\frac{t}{\tau}} \right.$$

$$\frac{dy(t)}{dt} \cdot e^{\frac{t}{\tau}} + \frac{1}{\tau} y(t) \cdot e^{\frac{t}{\tau}} = \frac{1}{\tau} x(t) \cdot e^{\frac{t}{\tau}}$$

$$\frac{d}{dt} \left[y(t) \cdot e^{\frac{t}{\tau}} \right] = \frac{1}{\tau} x(t) \cdot e^{\frac{t}{\tau}}$$

Replace t with dummy variable ξ and integrate both sides from 0 to t .

$$\int_0^t \frac{d}{d\xi} \left[y(\xi) \cdot e^{\frac{\xi}{\tau}} \right] d\xi = \int_0^t \frac{1}{\tau} x(\xi) \cdot e^{\frac{\xi}{\tau}} d\xi$$

$$y(t) \cdot e^{\frac{t}{\tau}} - y(0) \cdot e^0 = \frac{1}{\tau} \int_0^t x(\xi) \cdot e^{\frac{\xi}{\tau}} d\xi$$

initial value of $y(t)$

$$y(t) = y(0) e^{-\frac{t}{\tau}} + \frac{1}{\tau} e^{-\frac{t}{\tau}} \int_0^t x(\xi) \cdot e^{\frac{\xi}{\tau}} d\xi \quad (1)$$

crucial!

Response contains 2 components!

(I) independent of the forcing function! is the function natural response.

(II) depends on the particular forcing function $x(t)$ is called the forced response.

Their sum is called the complete response

$$y(t) = y_{\text{natural}} + y_{\text{forced}} \quad (2)$$


$$y_{\text{natural}} = y(0) \cdot e^{-\frac{t}{\tau}} \quad (3)$$

$$y_{\text{forced}} = \frac{1}{\tau} e^{-\frac{t}{\tau}} \int_0^t x(\xi) \cdot e^{\frac{\xi}{\tau}} d\xi \quad (4)$$

Response to a DC forcing function

$$x(t) = X_S \text{ constant.}$$

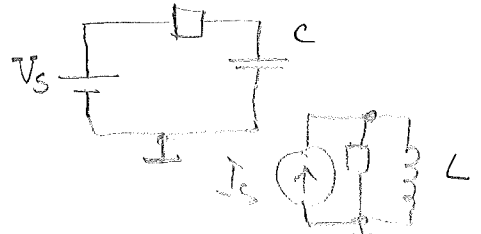Example: $\begin{cases} \text{RC circuit we have } v_S = V_S \\ \text{RL circuit we have } i_S = I_S \end{cases}$



$$y_{\text{forced}} = \frac{1}{\tau} e^{-\frac{t}{\tau}} \int_0^t X_S \cdot e^{\frac{\xi}{\tau}} d\xi = \frac{X_S}{\tau} e^{-\frac{t}{\tau}} \cdot \tau \left(e^{\frac{\xi}{\tau}} \Big|_0^t \right) = X_S (1 - e^{-\frac{t}{\tau}})$$

$= (e^{\frac{t}{\tau}} - 1)$

$$y_{\text{forced}} = X_S (1 - e^{-\frac{t}{\tau}}) \quad (5)$$

Hence, the complete response:

$$y(t) = \underbrace{y(0) e^{-\frac{t}{\tau}}}_{= y_{\text{natural}}} + \underbrace{X_S (1 - e^{-\frac{t}{\tau}})}_{= y_{\text{forced}}} \quad (6)$$


Note that in the limit $t \rightarrow \infty$: $y(t) \rightarrow X_S = y(\infty)$ we can rewrite

(6) as:

$$y(t) = [y(0) - y(\infty)] e^{-\frac{t}{\tau}} + y(\infty) \quad (6')$$

The complete response is an exponential transition from the initial value $y(0)$ to the final value $y(\infty)$! This transition is governed by the time constant τ .

Example: when $y(\infty) > y(0)$:

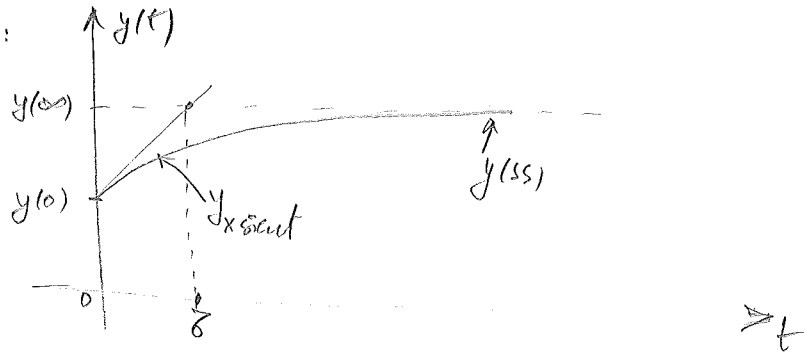

Seen like this:

$$y(t) = \underbrace{[y(0) - y(\infty)] \cdot e^{-\frac{t}{\tau}}}_{y_{\text{transient}}} + \underbrace{y(\infty)}_{y_{\text{SS}}} \quad (6')$$

transient component

steady-state component

$$y_{\text{transient}} = [y(0) - y(\infty)] \cdot e^{-\frac{t}{\tau}} \quad (7)$$

$$y_{\text{SS}} = y(\infty) \quad (8)$$

Observation: it is common to refer to the complete response to a DC forcing function as simply the transient response!

(b) Response to an AC forcing function

$$x(t) = X_{\text{ac}} \cos \omega t$$

↑
amplitude

↑
angular frequency of the ac signal. [radians/s] [rad/s]

$$\text{Example: } \begin{cases} v_s = V_m \cos \omega t & \text{for RC circuit} \\ i_s = I_m \cos \omega t & \text{for RL circuit} \end{cases}$$

$$y_{\text{forced}} = \frac{X_{\text{ac}}}{\tau} \cdot e^{-\frac{t}{\tau}} \cdot \int_0^t e^{\frac{t}{\tau}} (\cos \omega \xi) d\xi$$

$$\text{Use formula: } \int e^{a\xi} (\cos b\xi) d\xi = \frac{e^{a\xi}}{a^2 + b^2} (a \cos b\xi + b \sin b\xi)$$

$$\text{In our case } a = \frac{1}{\tau}, b = \omega$$

$$y_{\text{forced}} = \frac{X_{\text{ac}}}{\tau} e^{-\frac{t}{\tau}} \times \frac{e^{\frac{t}{\tau}}}{\frac{1}{\tau^2} + \omega^2} \left(\frac{1}{\tau} \cos \omega \xi + \omega \sin \omega \xi \right) \Big|_0^t$$

$$y_{\text{forced}} = \frac{X_{\text{ac}}}{1 + (\omega\tau)^2} (\cos \omega t + \omega\tau \sin \omega t - e^{-\frac{t}{\tau}}) \quad (9)$$

Use trigonometric identity:

(4)

$$A \cos \alpha + B \sin \alpha = \sqrt{A^2 + B^2} \cdot \cos \left[\alpha - \tan^{-1} \frac{B}{A} \right]$$

with $A=1$, $B=\omega\delta$

$$y_{\text{forced}} = - \frac{X_{ac}}{1 + (\omega\delta)^2} \cdot e^{-\frac{t}{\delta}} + \frac{X_{ac}}{\sqrt{1 + (\omega\delta)^2}} \cos(\omega t - \tan^{-1} \omega\delta) \quad (10)$$

Finally the complete response:

$$y(t) = \left[y(0) - \frac{X_{ac}}{1 + (\omega\delta)^2} \right] \cdot e^{-\frac{t}{\delta}} + \frac{X_{ac}}{\sqrt{1 + (\omega\delta)^2}} \cdot \cos(\omega t - \tan^{-1} \omega\delta) \quad (11)$$

$$= y_{\text{transient}}$$

$$= y_{\text{SS}} = Y_m \cdot \cos(\omega t + \phi)$$

where we introduced notation:

$$Y_m = \frac{X_{ac}}{\sqrt{1 + (\omega\delta)^2}} ; \quad \phi = -\tan^{-1} \omega\delta$$

\triangleq amplitude \triangleq phase angle.

So, again:

$$y(t) = y_{\text{transient}} + y_{\text{SS}}$$

of the steady-state response.

Observations

It is common practice to refer to the steady-state response to an ac forcing function as simply the ac response!

frequency dependent!

