
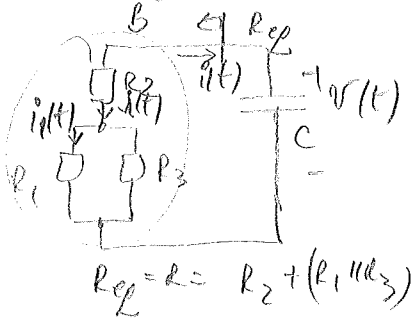


Seminar Nov. 8.

Group 8.5 (PP 273)

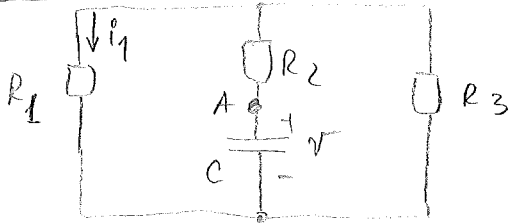

$$i_1(t) = ? , t \geq 0$$

By current division:

$$i_1(t) = \frac{R_3}{R_1 + R_3} (-i(t))$$

$$i_1(t) = \frac{R_3 V_0}{R_1 R_3 R_{eq}} e^{-\frac{t}{R_{eq} C}} = \frac{R_3}{R_1 + R_3} \cdot \frac{1}{R_2 + R_1 || R_3} \cdot V_0 \cdot e^{-\frac{t}{R_{eq} C}} = i_1(t)$$

$$t=0^+ \Rightarrow i_1(0^+) = \frac{R_3}{R_1 + R_3} \cdot \frac{V_0}{R_2 + \frac{R_1 R_3}{R_1 + R_3}}$$

$$= \frac{R_3 V_0}{R_1 R_3 + R_1 R_2 + R_2 R_3} = i_1(0^+)$$


week #12

Nov. 8. Mon. (1)  
Nov. 10. Wed. (11)

$$v(0^-) = V_0$$

Find  $v(0^+)$   $i_1(0^+)$

( $\Rightarrow$ )

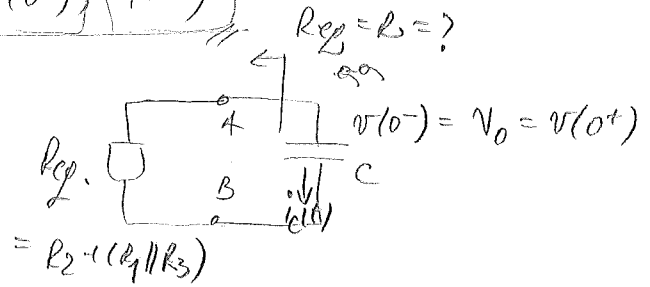

This is the natural-response case with initial condition  $v(0^-) = V_0$

So: the voltage  $v_c(t)$ :


$$v_c(t) = v(0^+) \cdot e^{-\frac{t}{\tau}}$$

$$v_c(t) = V_0 \cdot e^{-\frac{t}{R_{eq} C}} ; t \geq 0$$


$$i(t) = C \frac{dv_c(t)}{dt} = -\frac{V_0}{R_{eq}} e^{-\frac{t}{R_{eq} C}} = i_c(t) ; t \geq 0$$

$$i_1(t) = \frac{R_3}{R_1 + R_3} \cdot \frac{1}{R_2 + R_1 || R_3} \cdot V_0 \cdot e^{-\frac{t}{R_{eq} C}} = i_1(t)$$

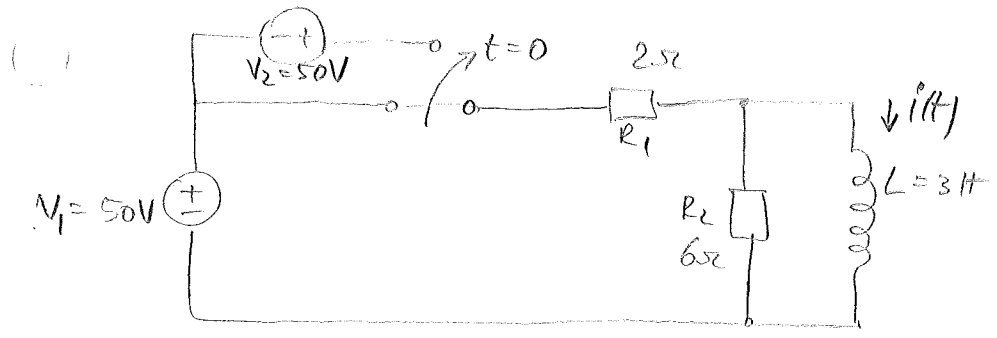Example 8.8 { pp. 286 } ← Do it in class too; to illustrate  $i(t)$  step function!



(i)  $t < 0$




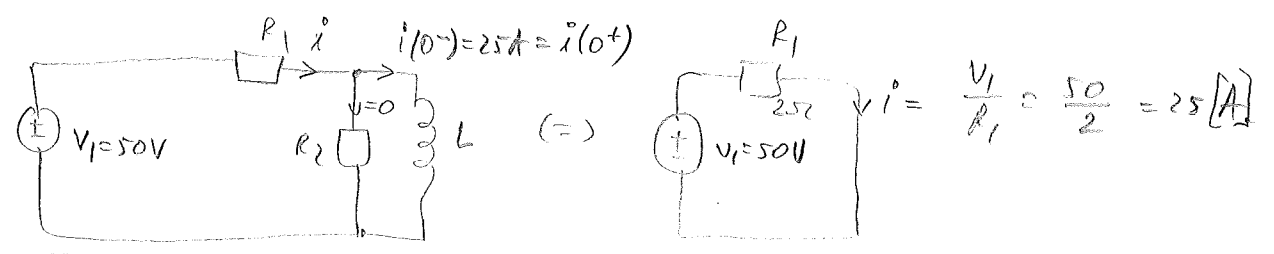


dc circuit; in dc, L is a short-circuit.

For  $t < 0$ ;  $i(t) = 25$

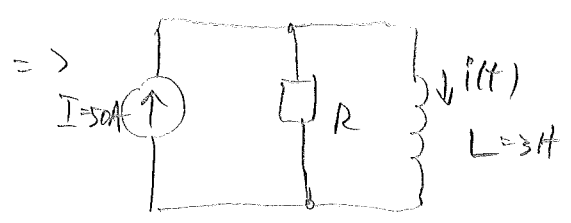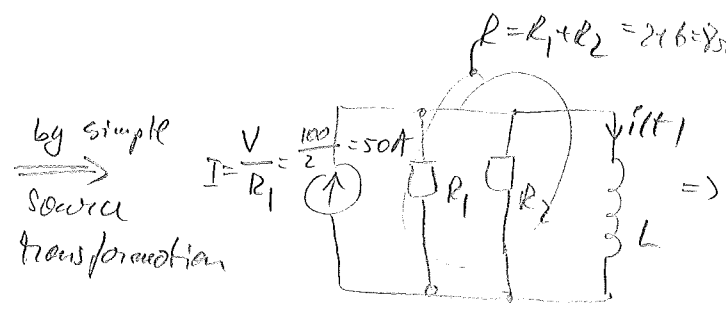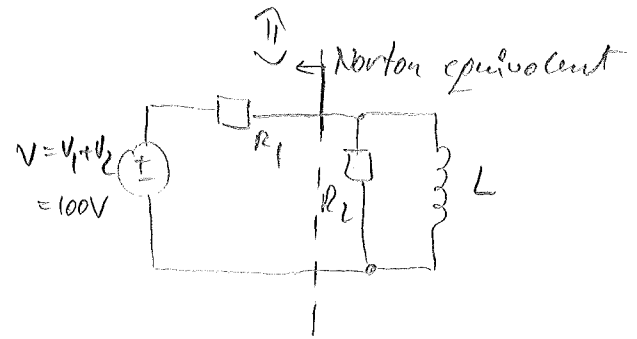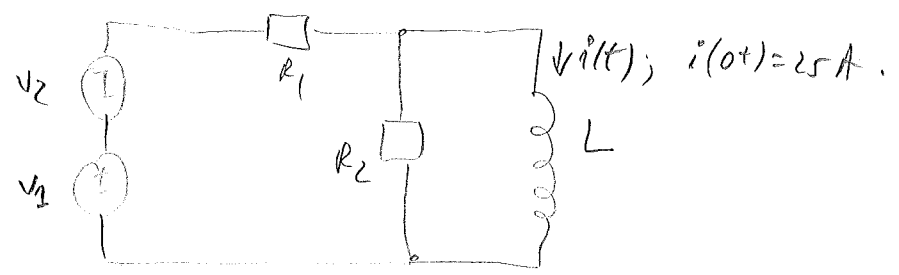(ii)  $t \geq 0$

$i(0^-) = 25A = i(0^+)$  by continuity rule ('crucial obs #2')



Recall: Summary  $y(t) = y(0) \cdot e^{-\frac{t}{\tau}} + X_S (1 - e^{-\frac{t}{\tau}})$   
 $i(t) \quad i(0) = 25A \quad I = 50A = y(\infty) \quad \tau = \frac{L}{R} = \frac{3}{8}$   
 or:  $y(t) = [y(0) - y(\infty)] e^{-\frac{t}{\tau}} + y(\infty)$



Therefore:  $i(t) = [25 - 50] e^{-\frac{t}{\tau}} + 50$

$i(t) = \underbrace{50}_{i(t)_{\infty}} - \underbrace{25}_{i(t)_{\text{start}}} e^{-\frac{t}{\tau}}$   $= 50 - 25 \cdot e^{-\frac{8}{3}t} = i(t)$ ;  $t \geq 0$


One can use  $u(t)$  the step-function to write the complete solution:

$i(t) = \begin{cases} 25A, & t \leq 0 \\ 50 - 25 \cdot e^{-\frac{8}{3}t}, & t \geq 0 \end{cases}$  OR:  $i(t) = (50 - 25e^{-\frac{8}{3}t}) \cdot u(t)$


where:

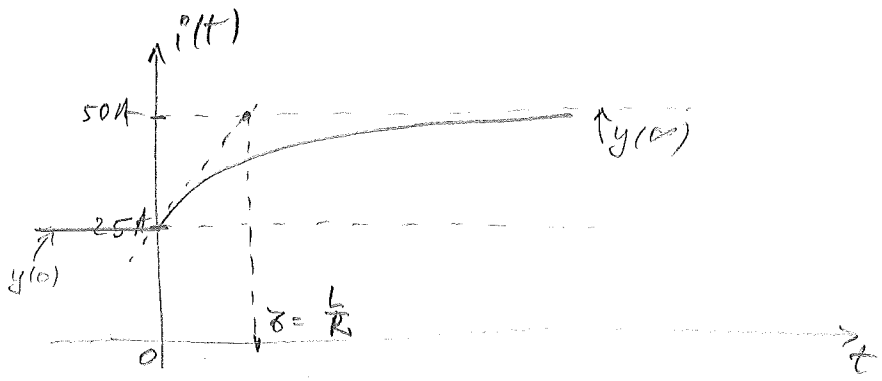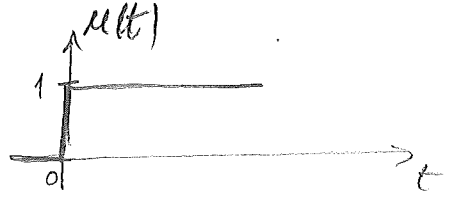



Example 8.10. pp. 290

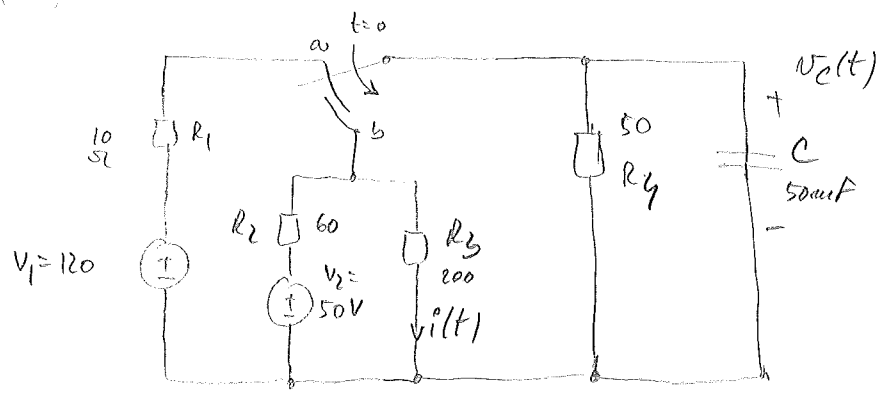


i)  $t \leq 0$

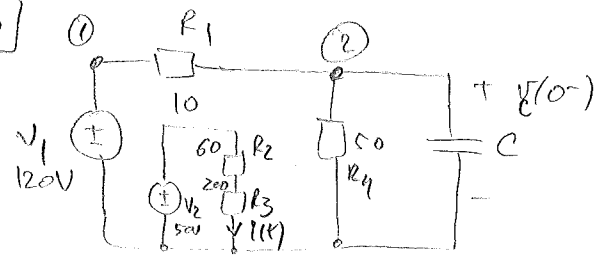

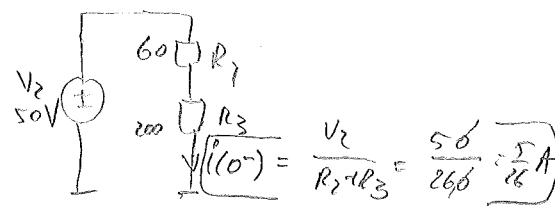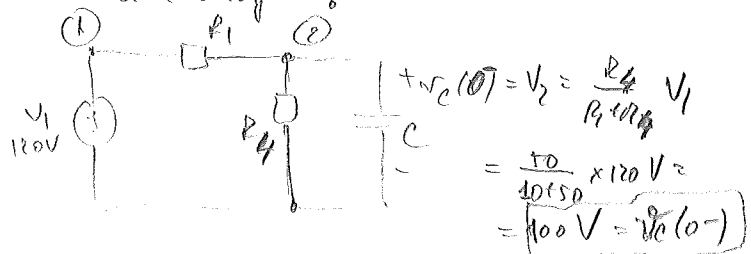dc circuit, C is an open after it has been charged!




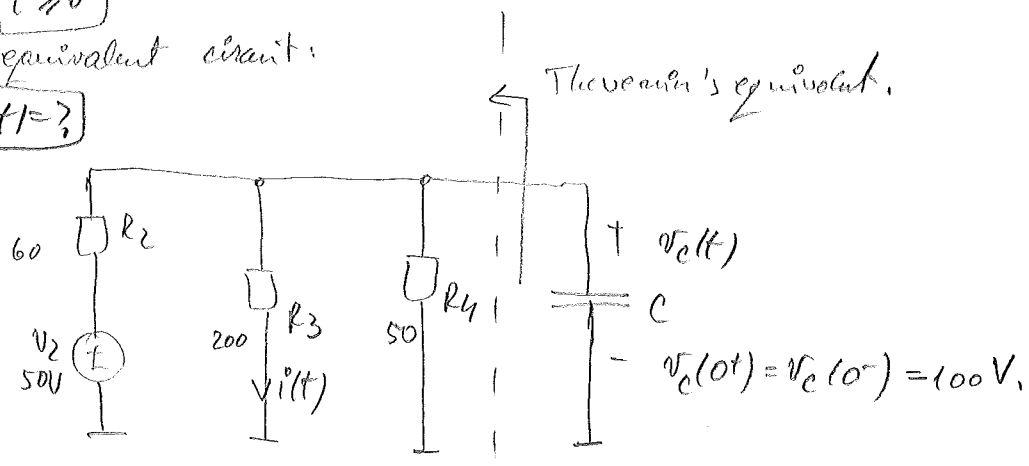(ii)  $t \geq 0$   
 equivalent circuit:  
 $v_c(t) = ?$



("Circuit obs # 1")  
 continuity rule.


(a)  $R_{eq} = ? = R_{TH}$

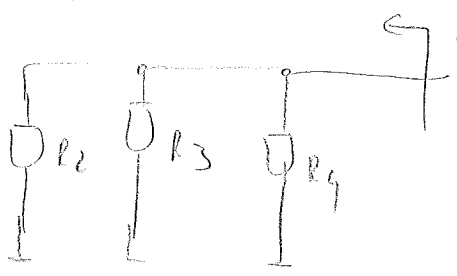


$R_{eq} = R_2 || R_3 || R_4 = 24.52 = R_{TH}$

$60 || 200 || 50$   
 $\frac{200 \times 50}{250} = \frac{1000}{250} = 40$   
 $60 || 40 = \frac{60 \times 40}{100} = \frac{2400}{100} = 24$

(b)  $V_{TH} = ?$

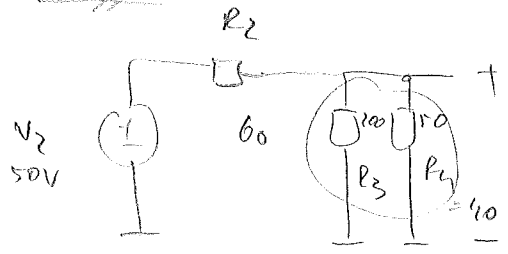

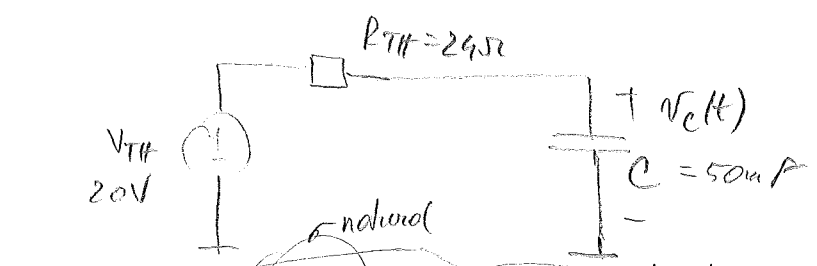$V_{OC} = V_{TH} = \frac{40}{40+60} \times 50V = 20V.$



Recall:  $y(t) = y(0) \cdot e^{-\frac{t}{\tau}} + X_S (1 - e^{-\frac{t}{\tau}})$

$\tau = R_{TH} \cdot C = 24 \times 50 \times 10^{-6} \text{ sec.}$

OR:  $y(t) = [y(0) - y(\infty)] e^{-\frac{t}{\tau}} + y(\infty)$


$v_c(t) = [100 - 20] e^{-\frac{t}{\tau}} + 20 = 80 e^{-\frac{t}{\tau}} + 20$

transient                      steady-state.

see verso !!!


$$v_c(t) = 20 + 80e^{-\frac{t}{\tau}}; t \geq 0$$
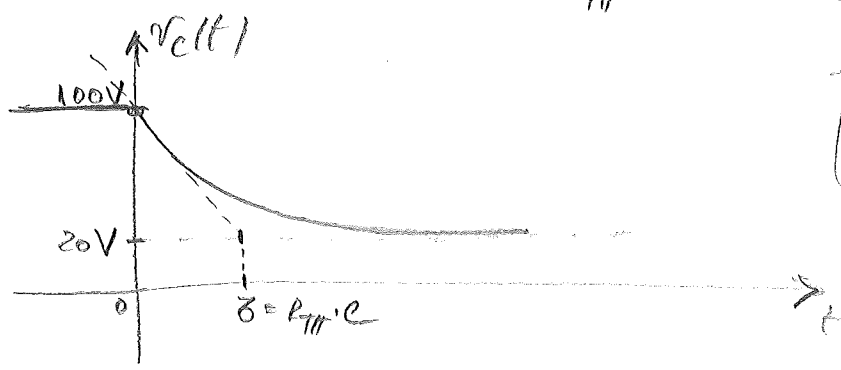
$$\tau = R_{TH} \cdot C = 1.2 \text{ sec.}$$



$$v_c(t) = \begin{cases} 20 + 80 \cdot e^{-\frac{t}{\tau}} & ; t \geq 0 \\ 100V & ; t < 0 \end{cases}$$

$$i(t) = ?$$

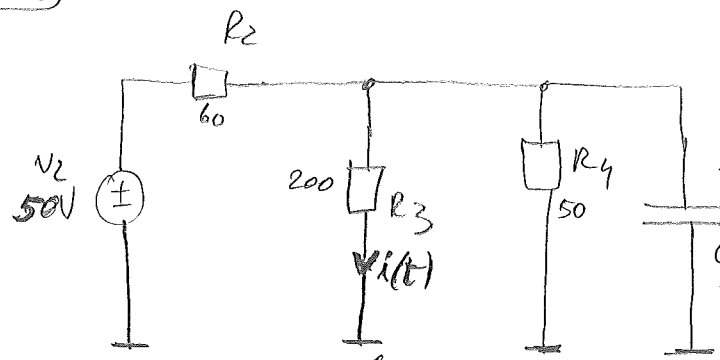


$$v_c(t) = 20 + 80e^{-\frac{t}{\tau}}$$

acts as an open for DC

$$i(0^-) = \frac{5}{26} \text{ A}$$

Think of superposition!

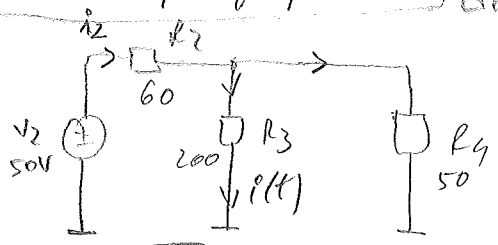

Textbook Method

Forced response:

$$i_p(t) = \frac{R_4}{R_3 + R_4} \cdot i_2 = \frac{R_4}{R_3 + R_4} \cdot \frac{V_2}{R_2 + R_3 \parallel R_4} = \frac{50}{50 + 200} \cdot \frac{50V}{60 + \frac{50 \cdot 200}{50 + 200}} = 0.1 \text{ A} = 100 \text{ mA}$$

$$i_2 = \frac{V_2}{R_2 + R_3 \parallel R_4}$$

The natural response: has form:  $i_n(t) = A \cdot e^{-\frac{t}{\tau}}$

$$i(t) = i_p(t) + i_n(t) = 0.1 + A \cdot e^{-\frac{t}{\tau}}$$

- to find A we need  $i_t(0^+)$


$v_C(0^-) = 100V = v_C(0^+)$  needs to be used here!

$$i(0^+) = \frac{100V}{R_3} = \frac{100}{200} = 0.5A$$

$$\Rightarrow i(t=0^+) = 0.1 + A \cdot e^0 = 0.5 \Rightarrow A = 0.4A$$

Therefore:
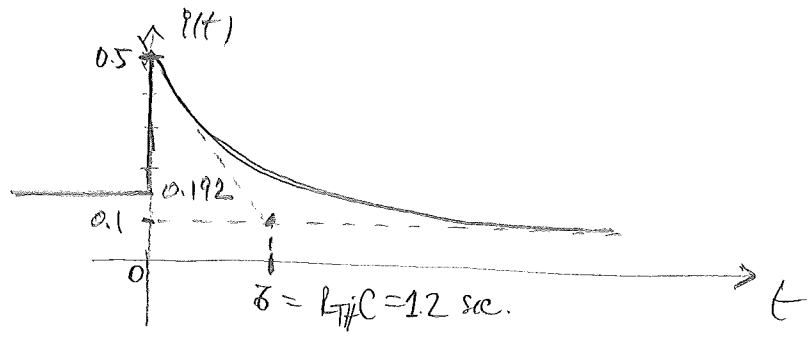
$$i(t) = 0.1 + 0.4e^{-\frac{t}{12}}; t \geq 0$$
$$i(t) = \frac{5}{20} A; t < 0$$



Method | Lecturer's way

do this


Think of the solution as: (this is key idea!)

$$y(t) = [y(0) - y(\infty)] \cdot e^{-\frac{t}{\delta}} + y(\infty)$$

$$i(t) = [i(0^+) - i(\infty)] \cdot e^{-\frac{t}{\delta}} + i(\infty)$$

(1)  $i(0^+)$  must be obtained from  $v_C(0^-) = 100V = v_C(0^+)$   
 $i(0^+) = \frac{v_C(0^+)}{R_3} = \frac{100V}{200\Omega} = 0.5A$

(2)  $i(\infty) = ?$

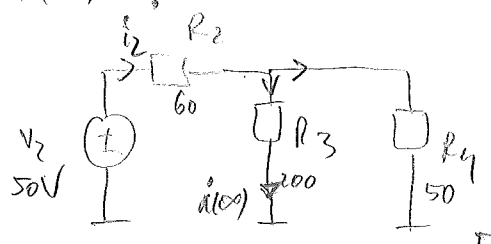

$$i(\infty) = \frac{R_4}{R_3 + R_4} \cdot i_2 = \frac{R_4}{R_3 + R_4} \cdot \frac{V_2}{R_2 + R_3 || R_4} = 0.1A$$

Therefore:

$$i(t) = [0.5 - 0.1] \cdot e^{-\frac{t}{12}} + 0.1 = 0.1 + 0.4e^{-\frac{t}{12}}; t \geq 0$$

$$i(t) = \frac{5}{20} A, t < 0$$

Plot is the next!