

Sinusoids and Phasors


$$x(t) = X_m \sin \frac{2\pi}{T} \cdot t = X_m \sin 2\pi f \cdot t = X_m \sin \omega t$$

↑ period $T = \frac{1}{f}$ ↑ frequency (cyclical, ordinary) ↑ amplitude ↑ angular frequency

1) General form:

$$x(t) = X_m \cdot \cos(\omega t + \phi)$$

↑ phase angle (rad or degrees)

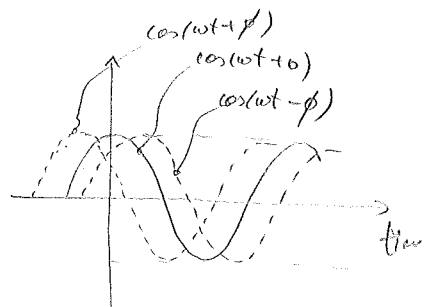

2) For conversion we know

$$2\pi \text{ rad} = 360^\circ$$

$$\begin{cases} \cos \omega t = \sin(\omega t + \frac{\pi}{2}) \\ \sin \omega t = \cos(\omega t - \frac{\pi}{2}) \end{cases}$$

$$\begin{cases} \cos(u \pm v) = \cos u \cdot \cos v \mp \sin u \cdot \sin v \\ \sin(u \pm v) = \sin u \cdot \cos v \pm \cos u \cdot \sin v \end{cases}$$

3) Phase difference:

$$\begin{cases} x(t) = X_m \cos(\omega t + \phi_x) \\ y(t) = Y_m \cos(\omega t + \phi_y) \end{cases}$$

$$\phi = \phi_y - \phi_x$$

4) Phasors:

- if we apply a sinusoidal signal to a circuit R, L, C and possibly dependent sources, all resulting voltages and currents will oscillate with the same frequency ω , differing only in amplitude and phase angle!

- The goal of ac analysis (we look only at steady-state response for a sinusoidal forcing function) is to find these amplitudes and phase angles!

- ω is of no concern \rightarrow is the same.

\Rightarrow we need a notation which focuses on ampl. & phase alone!

- This is provided by phasor!

⚡ time domain representation


$$x(t) = X_m \cos(\omega t + \phi)$$

⚡ freq. domain representation

$$X = X_m$$

$$\angle \phi$$
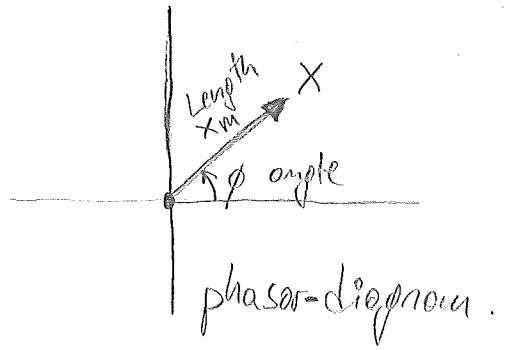
$$X = X_m \angle \phi \quad \text{polar-form}$$



5) Relationship with the complex form/notation

① HW assignment: write a report on section 10.3!

Complex forcing function:

$$X_m \cos(\omega t + \phi) + jX_m \sin(\omega t + \phi) = X_m e^{j(\omega t + \phi)}$$

compact representation exponential/polar form

$$= \text{Re}(X_m e^{j(\omega t + \phi)}) = \text{Im}(X_m e^{j(\omega t + \phi)})$$

Real part Imaginary part

(by EULER'S formula)
BTW: beautiful
 $e^{j\pi} + 1 = 0$
↑ Euler's number

Obs: instead of working with only real part, it is convenient to work with complex quantities, which directly relate to the phasor notation!!!

So, instead of applying for example: $v(t) = V_m \cos(\omega t + \phi_v)$
we can apply $v(t) = V_m \cos(\omega t + \phi_v) + jV_m \sin(\omega t + \phi_v) = V_m e^{j(\omega t + \phi_v)}$
and interpret the response also as a complex entity!
with real part being the response to the real part of the forcing function!!!



② HW assignment: Read Appendix 5

$$X_m \angle \phi \quad \text{known as the polar form.}$$

↑ The abbreviated complex representation is the phasor representation.

Phasor relationships for R, L, & C

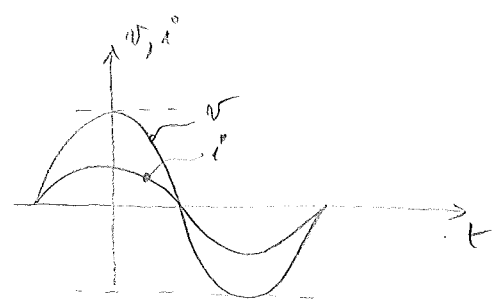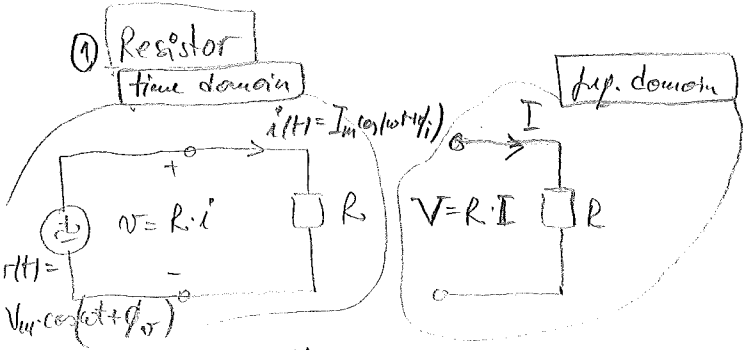⚠ The power of the phasor-based analysis is in that it's possible to define algebraic relations between voltage or current for L, C like for R.




$$v(t) = R \cdot i(t)$$

$$i(t) = \frac{v(t)}{R} = \frac{V_m}{R} \cos(\omega t + \phi_v)$$

$$= I_m \cdot \cos(\omega t + \phi_i)$$
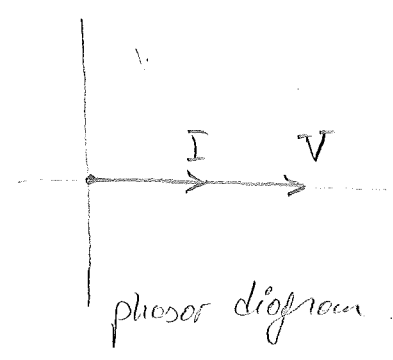
$$I_m = \frac{V_m}{R} \quad \phi_i = \phi_v$$



obs:
▶ voltage & current are in phase!

To derive the phasor relation, we use complex entities (see verso:)

$$v(t) = R \cdot i(t)$$

$$v(t) = V_m e^{j(\omega t + \phi_v)} = R \cdot I_m e^{j(\omega t + \phi_i)} = R \cdot i(t)$$



$$V_m e^{j\phi_v} = R I_m e^{j\phi_i}$$

or in phasor form:

$$\boxed{V_m \angle \phi_v} = R \cdot \boxed{I_m \angle \phi_i}$$

hence, the phasor relation:

$$\boxed{V = R \cdot I}$$

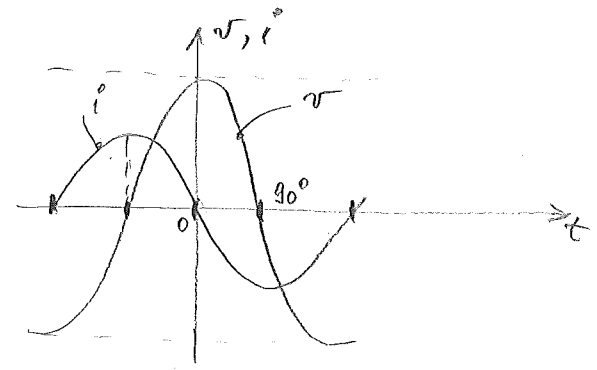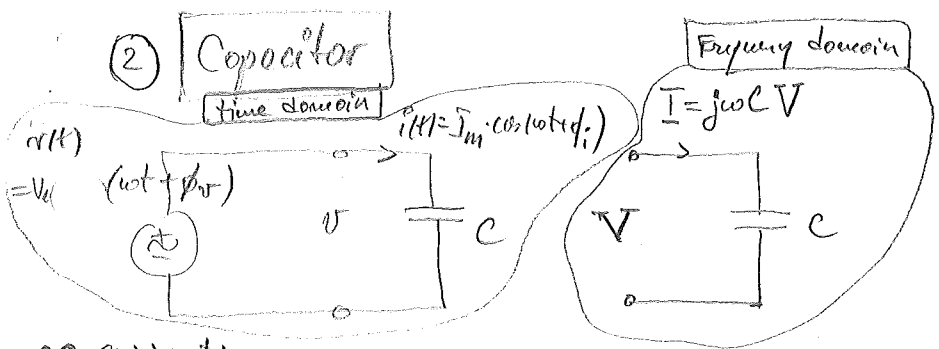


ac current:

$$i(t) = C \frac{dv(t)}{dt} = -\omega C V_m \sin(\omega t + \phi_v)$$

$$= \omega C V_m \cos(\omega t + \phi_v + 90^\circ)$$

$$= I_m \cos(\omega t + \phi_i)$$
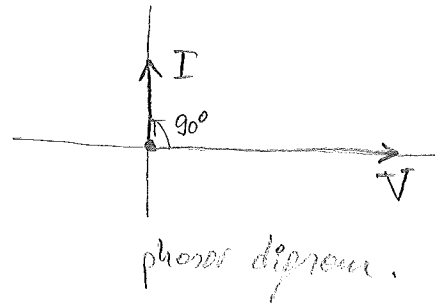
$$I_m = \omega C V_m \quad \phi_i = \phi_v + 90^\circ$$



Obs: amplitudes are still proportional but the constant of proportionality is freq. dependent
 In a capacitance current always leads voltage by 90°

To derive the phasor relation, we start from differential equation:

$$i = C \frac{dv}{dt}$$

and work with complex entities:

$$I_m e^{j(\omega t + \phi_i)} = C \frac{d}{dt} \left[V_m e^{j(\omega t + \phi_v)} \right]$$

$$I_m e^{j(\omega t + \phi_i)} = j\omega C V_m e^{j(\omega t + \phi_v)}$$



$$I_m e^{j\phi_i} = j\omega C V_m e^{j\phi_v}$$

Hence, phasor relation:

$$I = j\omega C \cdot V \quad \text{or} \quad I_m \angle \phi_i = V_m \angle \phi_v + 90^\circ$$

algebraic equation
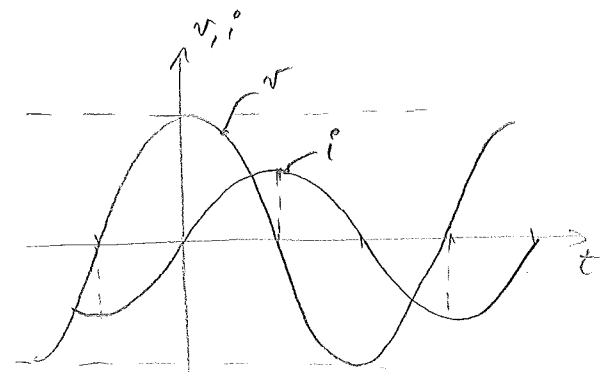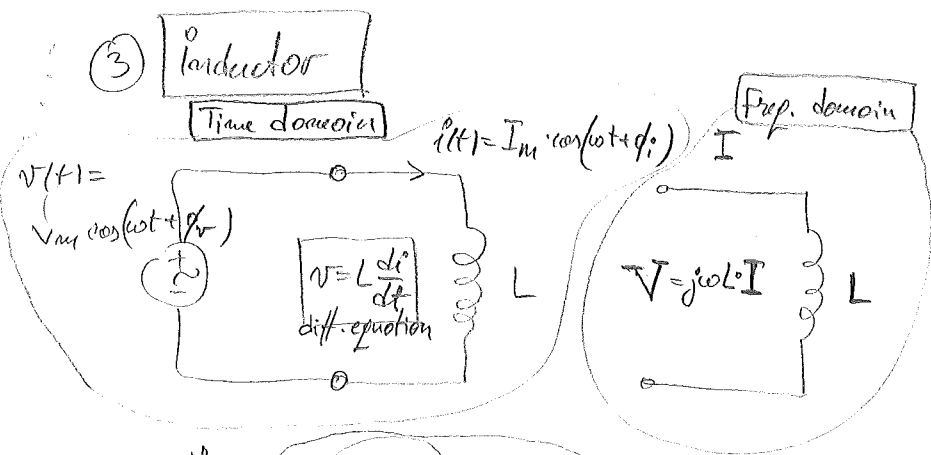
$$V = \frac{1}{j\omega C} I \quad \text{mostly used!}$$




$$v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi_i)$$

$$= \omega L I_m \cos(\omega t + \phi_i + 90^\circ)$$

$$= V_m \cos(\omega t + \phi_v)$$

$I_m = \frac{V_m}{\omega L}$

$\phi_i = \phi_v - 90^\circ$

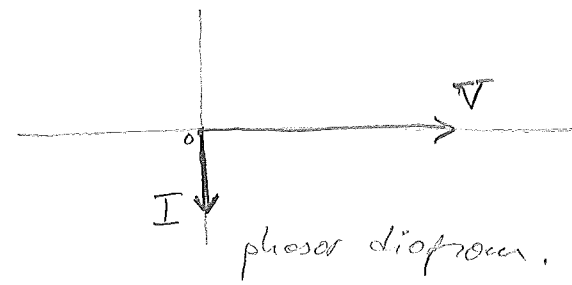

Obs: \blacktriangleright amplitudes proportional; proportionality constant is freq. dependent!
 \blacktriangleright in on inductance, current always lags voltage by 90°!

To derive phasor relation, we work with complex entities:

$$V_m e^{j(\omega t + \phi_v)} = L \cdot \frac{d}{dt} \left[I_m e^{j(\omega t + \phi_i)} \right]$$

$$V_m e^{j(\omega t + \phi_v)} = j\omega L I_m e^{j(\omega t + \phi_i)}$$

$$V_m e^{j\phi_v} = j\omega L I_m e^{j\phi_i}$$

hence, phasor relation: $V = j\omega L I$ or $V_m \angle \phi_v = I_m \angle \phi_i + 90^\circ$

algebraic equation used

$$I = \frac{1}{j\omega L} V$$

(4) Limiting cases

Capacitance: $I_m = \omega C V_m \Rightarrow \omega \rightarrow 0 : I_m \rightarrow 0 : C$ is open at low frequencies and short at high freq.

Inductance: $V_m = \omega L I_m \Rightarrow \omega \rightarrow 0 : V_m \rightarrow 0 : L$ is short at low frequencies and open at high freq.

$I_m = \frac{1}{\omega L} V_m$