
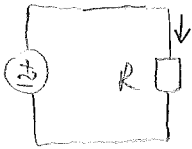
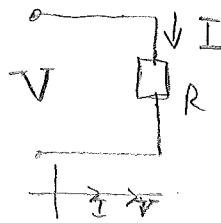
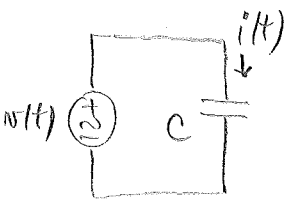
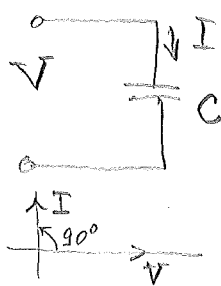
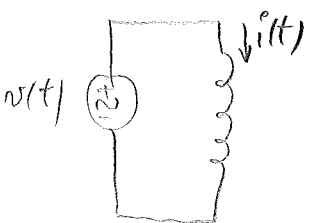
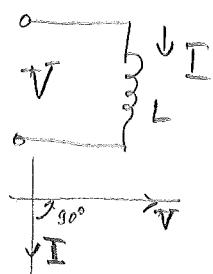


Summary on phasors (so far)

	Time-domain	Frequency-domain	
$v(t) = V_m \cos(\omega t + \phi_v)$ $i(t) = I_m \cos(\omega t + \phi_i)$ 	$v = R i$ $\begin{cases} V_m = R \cdot I_m \\ \phi_v = \phi_i \end{cases}$	$V = (R) I$ 	
	$i = C \frac{dv}{dt}$ $(v = \frac{1}{C} \int i dt)$ $\begin{cases} V_m = \frac{1}{\omega C} \cdot I_m \\ \phi_v = \phi_i + 90^\circ \end{cases}$	$V = \left(\frac{1}{j\omega C} \right) \cdot I$ 	
	$v = L \frac{di}{dt}$ $\begin{cases} V_m = \omega L \cdot I_m \\ \phi_v = \phi_i - 90^\circ \end{cases}$	$V = (j\omega L) \cdot I$ 	

↑
 The power of these phasor relationships is that we can do "phasor-based analysis" techniques which will involve only algebraic equations, similar to how we did it for circuits with only R, indep, & dep. sources!

Example

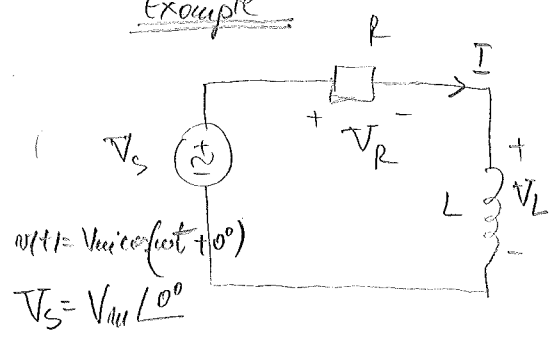

$$V_s = V_R + V_L$$

$$V_s = R I + j\omega L I \leftarrow \text{algebraic equation.}$$

$$I = \frac{V_s}{R + j\omega L}$$

$$V_s \text{ is given } V_s = V_m \angle 0^\circ \quad [v_s(t) = V_m \cos(\omega t + 0^\circ) = V_m \cos \omega t]$$

- So,
$$I = \frac{V_m \angle 0^\circ}{R + j\omega L}$$

- To get the time-domain expression of the current $i(t)$, we first use the polar notation:

$$I = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \angle -\tan^{-1} \frac{\omega L}{R}$$

- Therefore:
$$i(t) = \underbrace{\frac{V_m}{\sqrt{R^2 + (\omega L)^2}}}_{= I_m} \cdot \cos(\omega t - \underbrace{\tan^{-1} \frac{\omega L}{R}}_{= \phi_i})$$

- Finally:
$$i(t) = I_m \cdot \cos(\omega t + \phi_i)$$
 where
$$\begin{cases} I_m = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \\ \phi_i = -\tan^{-1} \frac{\omega L}{R} = -\tan^{-1} \omega \delta \\ \delta = \frac{L}{R} \end{cases}$$

which is the steady-state component of the complete response to a sinusoidal forcing function (Note: see lecture on Ch. 10)

Impedance

$$R = \frac{V}{I} = Z_R$$

$$j\omega L = \frac{V}{I} = Z_L$$

$$\frac{1}{j\omega C} = \frac{V}{I} = Z_C$$

- complex quantities, which we treat the same way we treat resistances.
- we'll call these, impedance, denoted as Z [Ω]

OBS:

- not a phasor!
- cannot be transformed to the time domain by just multiplying with $e^{j\omega t}$ and taking the real part!

- R, L, C are for time-domain
- Z_R, Z_L, Z_C are for the frequency-domain.

The beauty is that impedances can be combined in series or in parallel the same way as resistances!

Examples:




$$Z_L = j\omega L = j50 \Omega$$

$$Z_C = \frac{1}{j\omega C} = -\frac{j}{\omega C} = -j1 \Omega$$

$$Z_{eq} = Z_L + Z_C = j50 - j1 = j49 \Omega$$

OBS: depends on frequency!

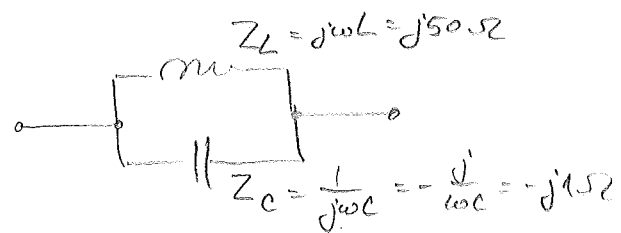

$$Z_L = j\omega L = j50 \Omega$$

$$Z_C = \frac{1}{j\omega C} = -\frac{j}{\omega C} = -j1 \Omega$$

$$Z_{eq} = \frac{Z_L Z_C}{Z_L + Z_C} = \frac{(j50) \times (-j1)}{j50 - j1} = \frac{50}{j49} = -j \frac{50}{49} = -j1.02 \Omega$$

Definitions

$$Z = R + j \cdot X = |Z| \angle \theta$$


\uparrow impedance \uparrow resistance \uparrow reactance [Ω] etc.

$$\begin{cases} Z_R = R & (R \text{ has zero reactance}) \\ Z_L = j\omega L \\ Z_C = \frac{1}{j\omega C} = -j \frac{1}{\omega C} \end{cases}$$


Example: $Z = 50 - j86.6 \Omega$

$\underbrace{\hspace{2em}}$ resistance of 50Ω $\underbrace{\hspace{2em}}$ reactance of -86.6Ω

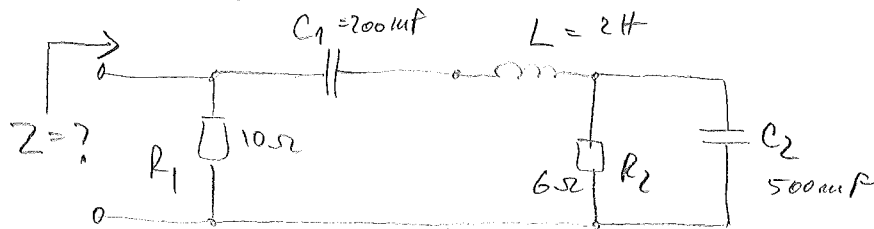Example: Find equivalent impedance of given network for $\omega = 5 \text{ rad/s}$.



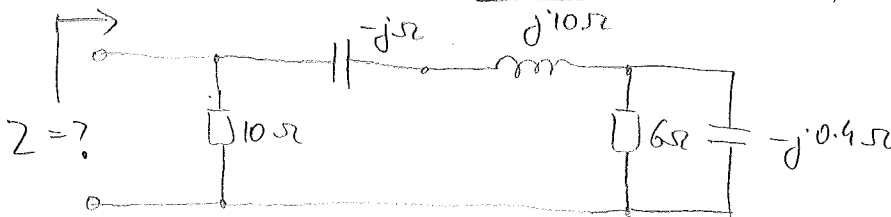$\omega = 5 \text{ rad/s}$ convert R, L, C into impedances.



$$= -j + j^{10}$$

$$= j9 \Omega$$

$$= 6 \parallel (-j0.4) = \frac{6 \times (-j0.4)}{6 - j0.4} = 0.026 - j0.398 \Omega$$

$$= 0.026 - j0.398 + j9 = 0.026 + j8.602 \Omega$$

$$= 10 \parallel (0.026 + j8.602)$$

$$= \frac{10 \times (0.026 + j8.602)}{10 + 0.026 + j8.602}$$

$$= 4.255 + j4.929 \Omega = Z|_{\omega=5 \text{ rad/s}}$$

Alternatively: find $Z(\omega)$ as general solution and then evaluate for desired ω !