

Definitions (more)

Admittance = is the ratio of phasor current to phasor voltage. It is denoted as Y . It is a complex quantity (similar to impedance).

$$Y = \frac{I}{V} = \frac{1}{Z} \quad [S] \text{ siemens.}$$

$$Y = G + jB = \frac{1}{Z} = \frac{1}{R + jX}$$

admittance \uparrow conductance \uparrow susceptance \uparrow resistance \uparrow reactance \uparrow
 impedance

Example:

$$Z = 1 - j2 \Omega$$

$$Y = \frac{1}{Z} = \frac{1}{1 - j2} = \frac{1 + j2}{(1 + j2)(1 - j2)} = \frac{1 + j2}{5} = \frac{1}{5} + j\frac{2}{5} \text{ S}$$


multiply/divide by conjugate

- Connection {

- in parallel \Rightarrow summation of admittances
- in series \Rightarrow similar to resistances in parallel.

Nodal and mesh analysis using phasors to find the steady-state component of the complete response; when the forcing function is a sinusoidal!

Example: Nodal analysis

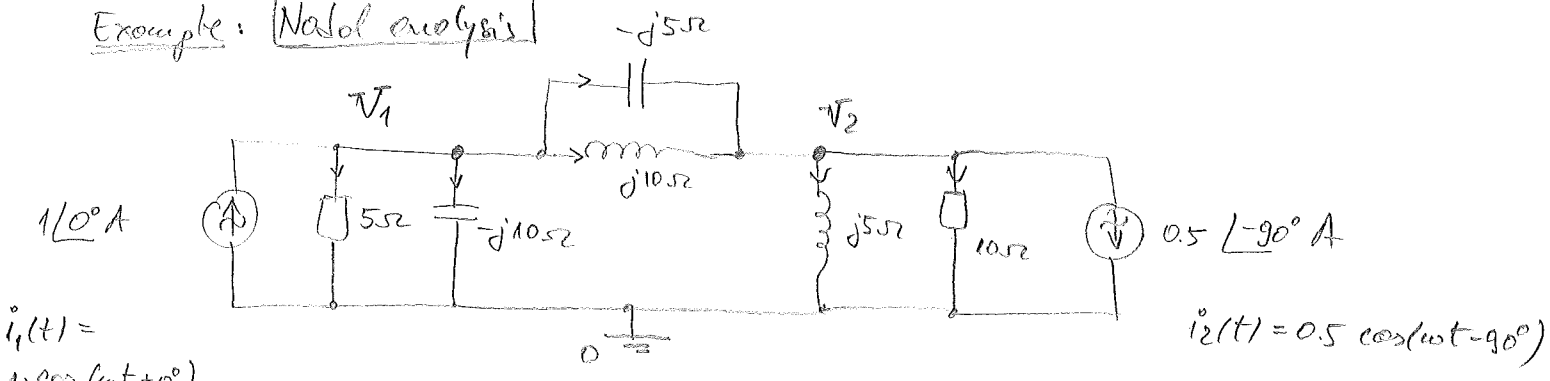

$i_1(t) = 1 \cdot \cos(\omega t + 0^\circ)$
 $= \cos \omega t$

$i_2(t) = 0.5 \cos(\omega t - 90^\circ)$

Obs: $\left\{ \begin{array}{l} - \text{in this figure we work with impedances and phasors!} \\ - \text{AC source have the same frequency!!} \end{array} \right.$

KCL node V_1 : $\left\{ \begin{array}{l} \frac{V_1}{5} + \frac{V_1}{-j10} + \frac{V_1 - V_2}{j10} + \frac{V_1 - V_2}{-j5} = 1 \angle 0^\circ = 1 + j0 = 1 \end{array} \right.$

KCL node V_2 : $\left\{ \begin{array}{l} \frac{V_2}{j5} + \frac{V_2}{10} - \frac{V_1 - V_2}{j10} - \frac{V_1 - V_2}{5\Omega} = -(0.5 \angle -90^\circ) = j0.5 \end{array} \right.$

2 eq.
2 unknown

$\Rightarrow \begin{cases} (0.2 + j0.2) V_1 - j0.1 V_2 = 1 \\ -j0.1 V_1 + (0.1 - j0.1) V_2 = j0.5 \end{cases}$


$\Rightarrow \begin{cases} V_1 = 1 - j^2 \text{ [V]} = 2.24 \angle -63.4^\circ \\ V_2 = -2 + j^4 \text{ [V]} = 4.47 \angle 116.6^\circ \end{cases}$

↑
impolar form

Hence, converting to the time-domain:


$\begin{cases} v_1(t) = 2.24 \cdot \cos(\omega t - 63.4^\circ) \text{ [V]} \\ v_2(t) = 4.47 \cdot \cos(\omega t + 116.6^\circ) \text{ [V]} \end{cases}$

Example : Mesh analysis

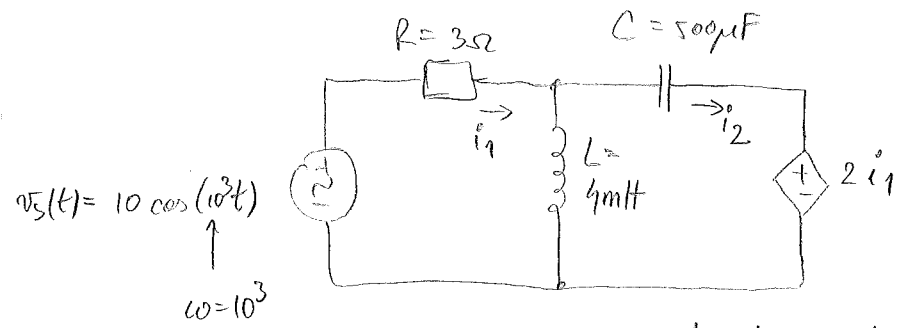

$i_1, i_2 = ?$

convert into impedances and phasors.

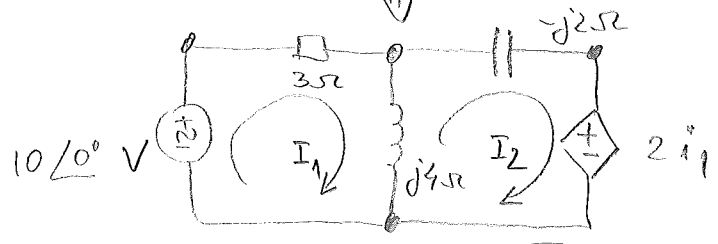

$$\frac{1}{j\omega C} = -j \frac{1}{\omega C} = -j \frac{1}{10^3 \cdot 500 \cdot 10^{-6}} = -j2.5 \Omega$$

$$j\omega L = j \cdot 10^3 \cdot 4 \cdot 10^{-3} \Omega = j4 \Omega$$

$$\begin{cases} \text{Loop } I_1: & 3I_1 + j4(I_1 - I_2) = 10 \angle 0^\circ = 10 + j0 = 10 \\ \text{Loop } I_2: & j4(I_2 - I_1) - j2I_2 + 2I_1 = 0 \end{cases} \quad \left| \begin{array}{l} 2 \text{ eq.} \\ 2 \text{ unknowns.} \end{array} \right.$$

$$\begin{cases} (3 + j4)I_1 - j4I_2 = 10 \\ (2 - j4)I_1 + j2I_2 = 0 \end{cases} \quad \Rightarrow$$

$$\Rightarrow \begin{cases} I_1 = \frac{14 + j8}{13} = 1.24 \angle 29.7^\circ \text{ [A]} \\ I_2 = \frac{20 + j30}{13} = 2.77 \angle 56.3^\circ \text{ [A]} \end{cases}$$



↑
in polar form

Converting to time domain!

$$\begin{cases} i_1(t) = 1.24 \cdot \cos(\omega t + 29.7^\circ) \text{ [A]} \\ i_2(t) = 2.77 \cdot \cos(\omega t + 56.3^\circ) \text{ [A]} \end{cases}$$


Superposition Q. Deter.

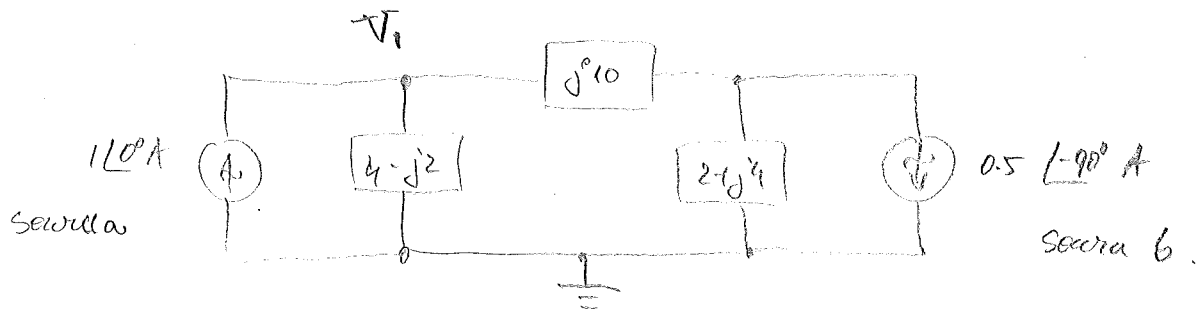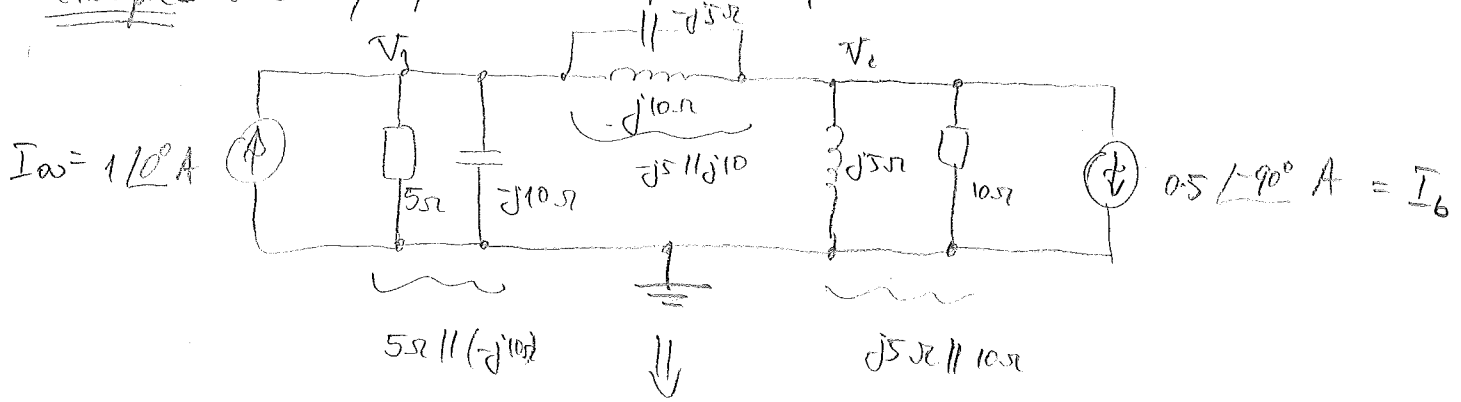Example 4 Use superposition to find V_1 .



$$V_1 = \underbrace{V_{1a}}_{\text{due to source a}} + \underbrace{V_{1b}}_{\text{due to source b}}$$

(a) contribution due to source a:

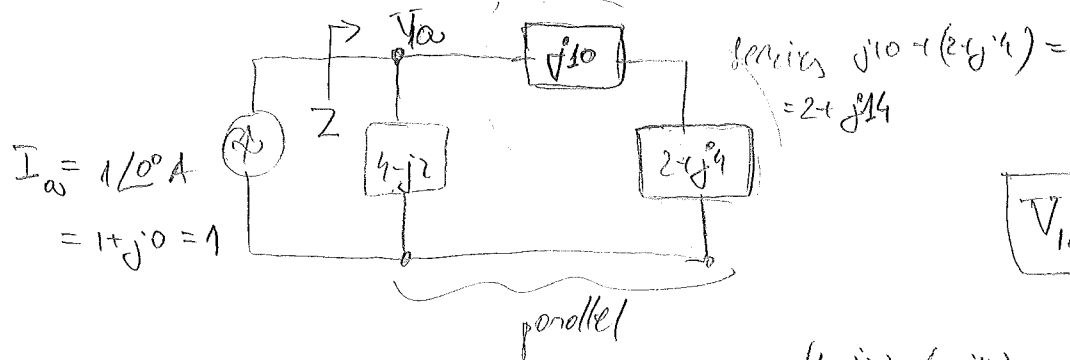


$$I_{\omega} = 1\angle 0^{\circ} A = 1 + j0 = 1$$

series $j10 + (2+j4) = 2 + j14$

$$V_{1a} = Z \cdot I_{\omega} = 2 - j2 \text{ [V]}$$

$$Z_{\text{eq}} = (4-j2) \parallel (2+j4) = \frac{(4-j2) \times (2+j4)}{4-j2 + 2+j4}$$

(b) contribution due to source b:

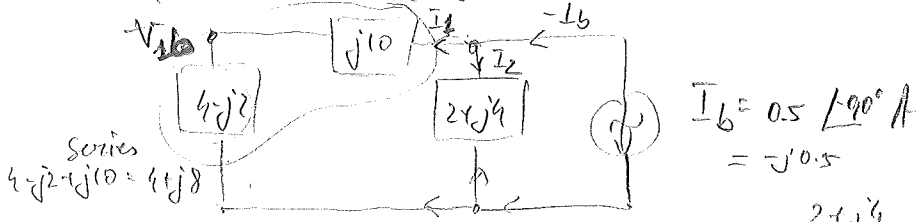

$$I_b = 0.5 \angle -90^{\circ} A = -j0.5$$

$$I_1 = \frac{2+j4}{(2+j4) + (4-j2)} \times (-I_b) = - \frac{2+j4}{6+j2} I_b$$

$$V_{1b} = (4-j2) \cdot I_1 = - \frac{(4-j2)(2+j4)}{6+j2} \times (0.5 \angle -90^{\circ}) = -1 \text{ [V]}$$

$$V_1 = V_{1a} + V_{1b} = 2 - j2 - 1 = 1 - j2 \text{ [V]}$$