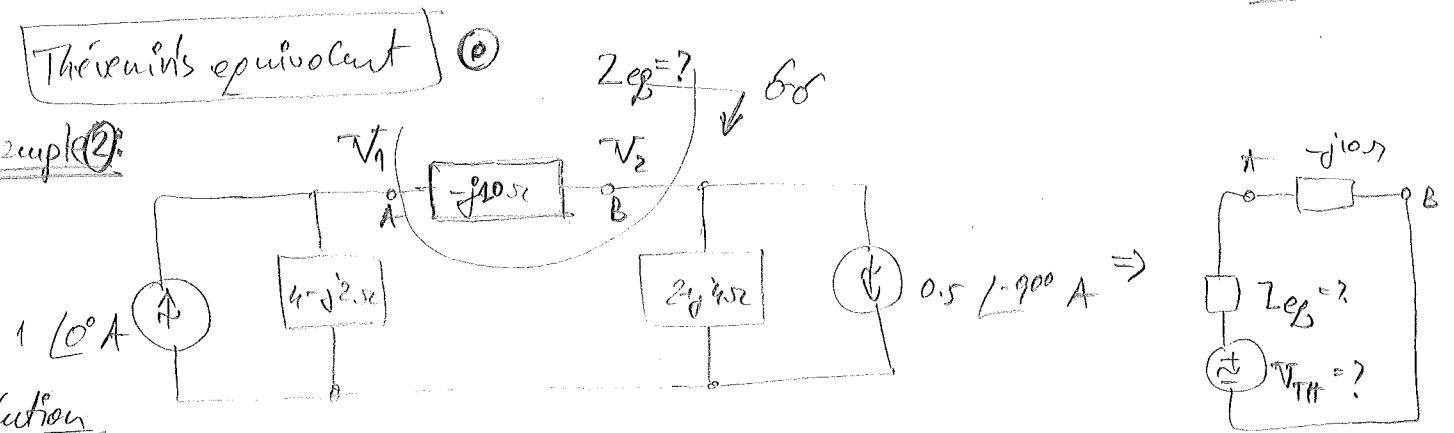


Thévenin's equivalent


(2 up)



Solution

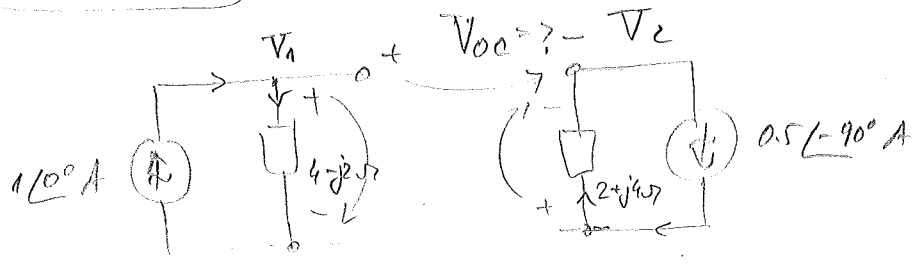(i) $V_{TH} = V_{oc} = ?$

$Z_{eg} = 6 + j2 \text{ } [\Omega]$
 $V_{TH} = 6 - j3 \text{ } [V]$



KVL:


$$V_{oc} = (4-j2) \cdot (1 \angle 0^\circ) + (2+j4) \cdot (0.5 \angle -90^\circ)$$

$$= (4-j2) \cdot (+1) + (2+j4) \cdot (-j0.5)$$

$$= 4-j2 + 2 - 1j = \boxed{6-j3} \text{ } [V]$$

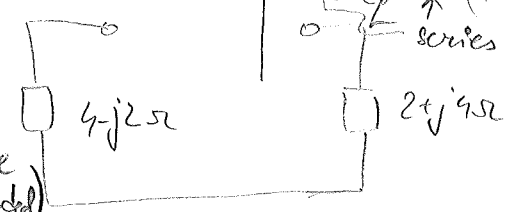
(ii) $Z_{eg} = ?$

$Z_{eg} = (4-j2) + (2+j4) = \boxed{6+j2 \text{ } \Omega}$



Superposition (reloaded)

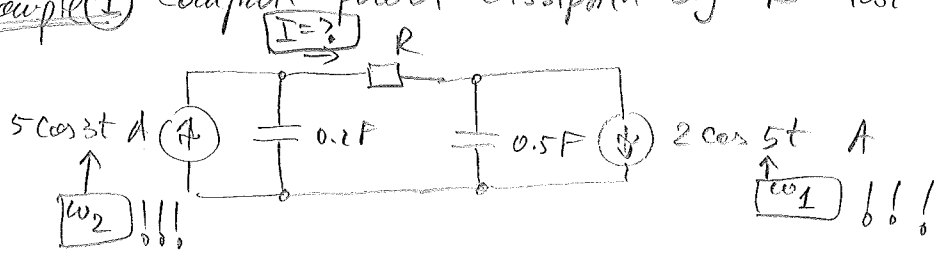
Example (1) Compute power dissipated by $R = 1 \Omega$ (in steady-state!)



Note: we have 2 different frequencies!

Apply superposition to find the contribution of each of the current sources!

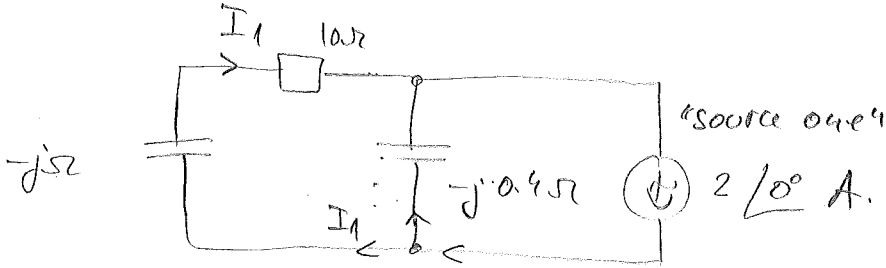
(a) Contribution due to source one: I_1 (phasor current!)



Use current division:

$$I_1 = \frac{j0.4}{j0.4 + (10 - j)} \times (2 \angle 0^\circ) = 79.23 \angle -82.03^\circ \text{ mA}$$

(b) Contribution due to source two: I_2

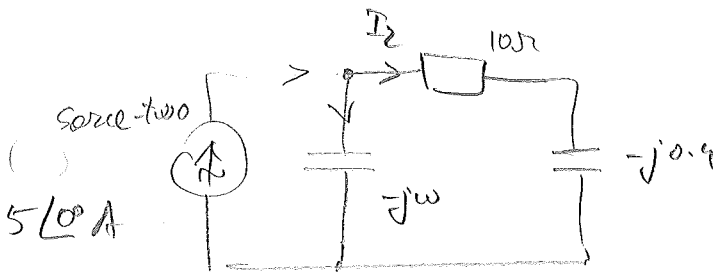

Also by current division:

$$I_2 = \frac{-j\omega}{j\omega + (10 - j0.4)} \times (5 \angle 0^\circ) = 811.7 \angle -76.86^\circ \text{ mA}$$

Finally: $I = I_1 + I_2$ thru impedance of 10Ω .

Converting to the time domain:

$$i(t) = 79.23 \cos(5t - 82.03^\circ) + 811.7 \cos(3t - 76.86^\circ) \text{ [mA]}$$

Power:

$$P(t) = \left(i(t) \right)_{10\Omega}^2 \times 10 = 10 \times \left[\downarrow \right]^2 \text{ [}\mu\text{W]}$$



Give HW #20 the "Phasor diagrams", pp. 404-406.!


Chapte 11: AC Circuit power analysis

① Instantaneous power


= the product of the instantaneous voltage and current:

$$p(t) = v(t) \cdot i(t)$$

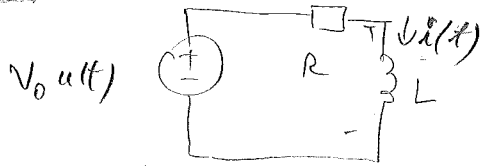② Example ① RL circuit with constant forcing-function V_0 ; $t \geq 0$.



(=)

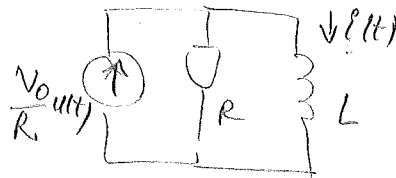

$$v_L(t) = L \frac{di}{dt} = \frac{V_0}{R} \cdot \frac{L}{R} \cdot e^{-\frac{t}{\tau}} = V_0 \cdot e^{-\frac{t}{\tau}}; t \geq 0$$

$$i(t) = \frac{V_0}{R} (1 - e^{-\frac{t}{\tau}}) \cdot u(t)$$

$$i(t) = \begin{cases} \frac{V_0}{R} (1 - e^{-\frac{t}{\tau}}) & ; t \geq 0 \\ 0 & ; t < 0 \end{cases}$$

where: $\tau = \frac{L}{R}$

Power delivered by source (equals the power absorbed by RL network):

$$\begin{aligned} p(t) &= v(t) \cdot i(t) = (V_0 \cdot u(t)) \times \left(\frac{V_0}{R} (1 - e^{-\frac{t}{\tau}}) u(t) \right) \\ &= \frac{V_0^2}{R} (1 - e^{-\frac{t}{\tau}}) \cdot u(t) \end{aligned} \quad (1)$$


Power delivered to R:

$$P_R(t) = R i^2(t) = \frac{V_0^2}{R} (1 - e^{-\frac{t}{\tau}})^2 \cdot u(t) \quad (2)$$

Power delivered to L:


$$P_L(t) = \underbrace{(V_0 e^{-\frac{t}{\tau}} \cdot u(t))}_{=v_L(t)} \times \underbrace{\left(\frac{V_0}{R} (1 - e^{-\frac{t}{\tau}}) u(t) \right)}_{=i(t)} = \frac{V_0^2}{R} e^{-\frac{t}{\tau}} (1 - e^{-\frac{t}{\tau}}) \cdot u(t) \quad (3)$$

(1) = (2) + (3)

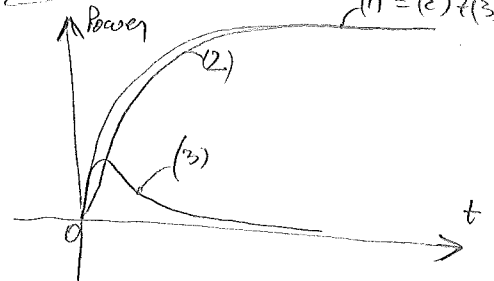

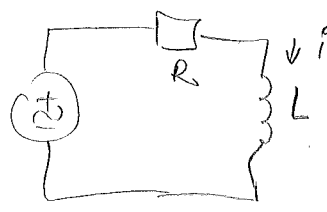6) Sinusoidal forcing-function

$v_s(t) = V_m \cos(\omega t)$
 $\phi_r = 0$



$i(t) = I_m \cos(\omega t + \phi)$
 $\phi = \phi_i$
 $= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$

OBS: This is the steady-state only component.
 (see analysis)

Instantaneous

Power delivered to the network: $p(t) = v(t) \cdot i(t)$

$p(t) = V_m I_m \cos(\omega t) \cdot \cos(\omega t + \phi)$
 $= \frac{V_m I_m}{2} [\cos(2\omega t + \phi) + \cos \phi]$

$p(t) = \underbrace{\frac{V_m I_m \cos \phi}{2}}_{\text{constant}} + \underbrace{\frac{V_m I_m \cos(2\omega t + \phi)}{2}}_{\text{depends on } \omega \text{ and } t}$

depends on ω and t .
 twice the applied frequency.