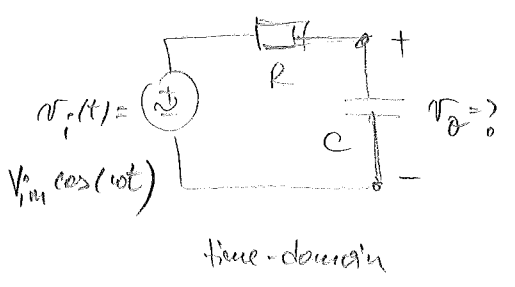



Seminar

More examples of frequency-domain analysis (or phasor analysis)

AC divider



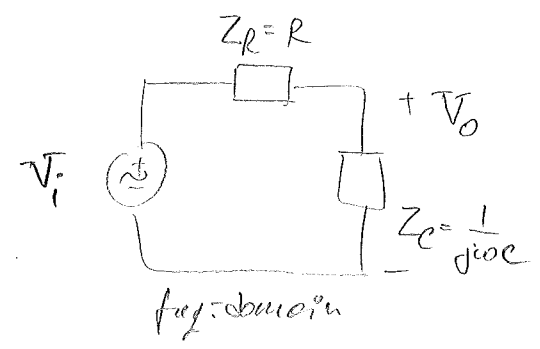get/draw
→
frequency domain
representation of the
circuit.



This is a voltage divider:
$$\boxed{V_o = \frac{Z_C}{Z_C + Z_R} V_i = \frac{1/j\omega C}{R + 1/j\omega C} \cdot V_i = \frac{V_i}{1 + j\omega RC}}$$

$$V_o = |V_o| \angle \phi$$

where:
$$\begin{cases} |V_o| = \frac{|V_i|}{|1 + j\omega RC|} = \frac{V_{in}}{\sqrt{1 + (\omega RC)^2}} \\ \phi = \angle 0^\circ - \tan^{-1} \frac{\omega RC}{1} = (-\tan^{-1}(\omega RC)) \end{cases}$$

$$\boxed{V_o = \frac{V_{in}}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1}(\omega RC)}$$

OBS. 1 Note that this is a low-pass filter!
 - Low frequencies: $\omega \rightarrow 0 \implies |Z_C| \rightarrow \infty$
 - High frequencies: $\omega \rightarrow \infty \implies |V_o| \rightarrow 0$
 - Borderline frequency is the special frequency ω_0 that makes

$$|Z_C(\omega_0)| = |Z_R|$$

$$\frac{1}{\omega_0 C} = R \implies \boxed{\omega_0 = \frac{1}{RC}}$$

which is the **cut off freq.** of the filter!

OBS. 2

In the high-frequency limit, the RC circuit approximates an **integrator**!

$$V_o|_{\omega \rightarrow \infty} \rightarrow \frac{V_i}{j\omega RC} = \left(\frac{1}{j\omega}\right) \cdot \frac{V_i}{RC}$$


Yorks: $x(t) = X_m \cos(\omega t + \theta) \rightarrow X_m \angle \theta$

$$x_{der}(t) = \frac{d}{dt}(x(t)) = \omega X_m \cdot \sin(\omega t + \theta) = \omega X_m \cos(\omega t + \theta + 90^\circ) \rightarrow \omega X_m \angle \theta + 90^\circ$$


So, derivation is multiplication by $\boxed{j\omega}$ and integration is multiplication by $\boxed{\frac{1}{j\omega}}$!

same as: $\rightarrow j\omega X_m \angle \theta$

Example: Find v_1, v_2 .

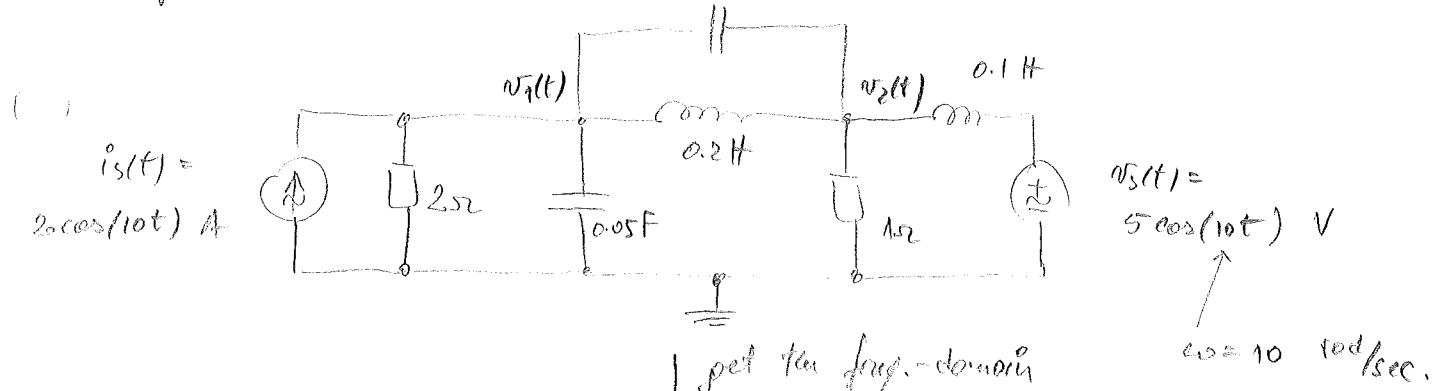


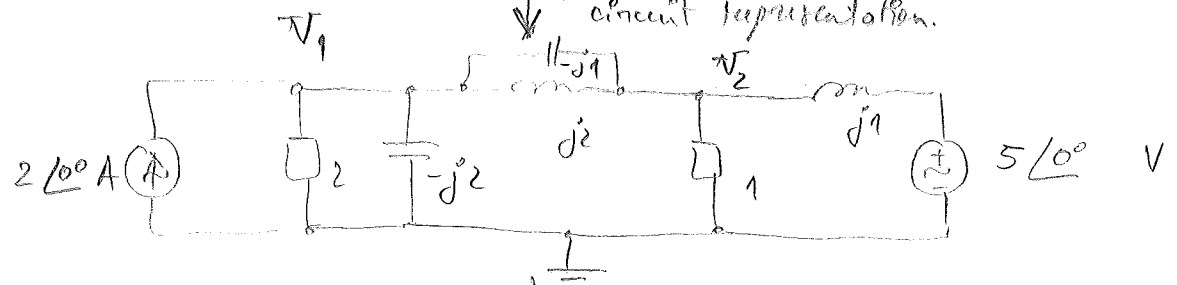get the freq.-domain circuit representation.



simplify by procepting impedances.
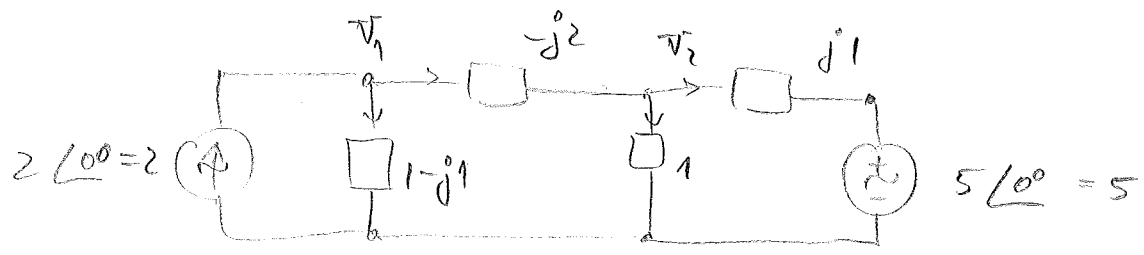
$$\frac{2 \times (-j2)}{2 - j2} = \frac{-j4}{2 - j2} = \frac{-j4(2 + j2)}{8} = 1 - j1$$



Use nodal analysis:

$$\begin{cases} \text{KCL node } v_1: \frac{v_1}{1-j1} + \frac{v_1 - v_2}{-j2} = 2 \\ \text{KCL node } v_2: \frac{v_1 - v_2}{-j2} = \frac{v_1}{1} + \frac{v_2 - 5}{j1} \end{cases}$$

$$\Rightarrow \begin{cases} (1-j3)v_1 + (-1+j1)v_2 = -4-j4 \\ v_1 + (1+j2)v_2 = 10 \end{cases} \quad (\Rightarrow) \boxed{Ax = b}$$

$$A = \begin{bmatrix} 1-j3 & -1+j1 \\ 1 & 1+j2 \end{bmatrix} \quad X = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \quad b = \begin{bmatrix} -4-j4 \\ 10 \end{bmatrix}$$

$$\begin{cases} (1-j3)V_1 + (-1+j1)V_2 = -4-j4 \\ V_1 + (1+j2)V_2 = 10 \end{cases} \quad / \times[-(1-j3)] \oplus$$

$$\Rightarrow (-1+j1)V_2 + (1+j2)(-1+j3)V_2 = -4-j4 -10 + j30$$

$$-1-6-j2+j^3$$

$$(-7+j^9) \cdot V_2$$

$$(-8+j^2)V_2 = -14+j^26$$

$$(-4+j)V_2 = -7+j13$$


$$\Rightarrow \boxed{V_2 = \frac{7-j13}{4-j1} = 3.581 \angle -47.66^\circ \text{ [V]}}$$

$$\boxed{V_1 = 10 - (1+j2)V_2 = \frac{7-j11}{4-j1} = \sqrt{10} \angle -43.49^\circ \text{ V}}$$

Therefore, converting to time-domain:


$$\begin{cases} v_1(t) = \sqrt{10} \cdot \cos(10t - 43.49^\circ) \text{ V} \\ v_2(t) = 3.581 \cdot \cos(10t - 47.66^\circ) \text{ V} \end{cases}$$

Equivalent impedance of ac port

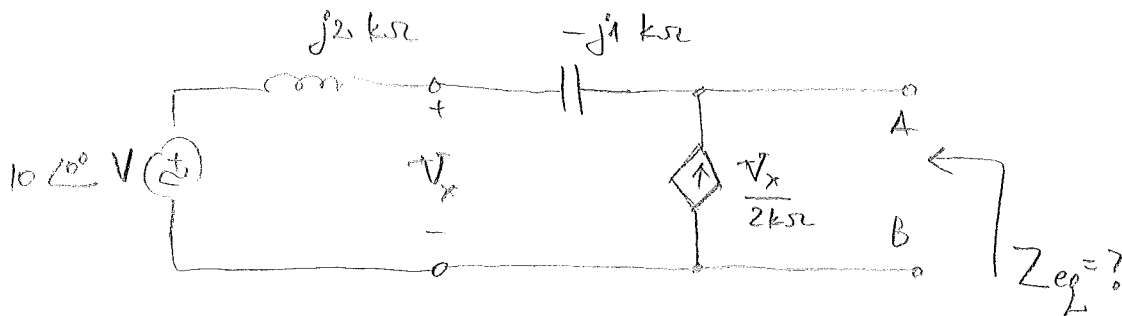

Rule: Take the 2-port network, suppress all independent sources and apply V "arbitrary" current I , then:

$$\boxed{Z = \frac{V}{I}}$$

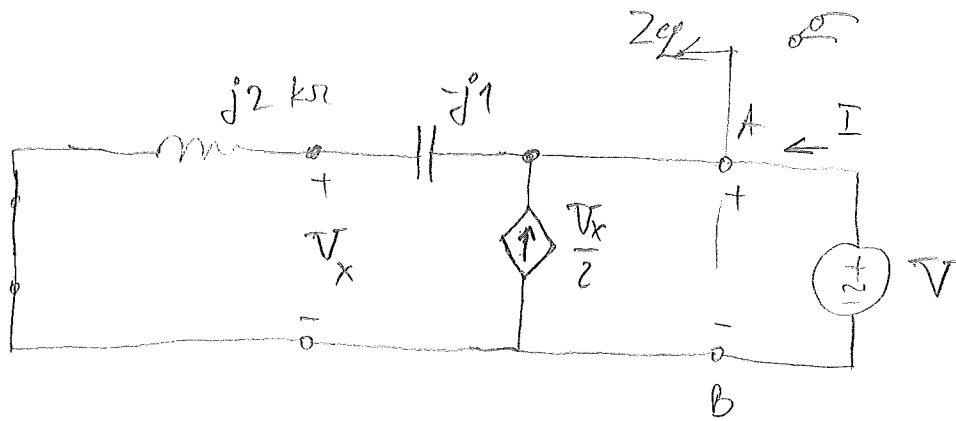

KCL: $I + \frac{V_x}{2} = \frac{V - V_x}{-j1}$

Voltage division: $V_x = \frac{j2}{j2 - j1} V = 2 \cdot V$


$\Rightarrow I + \frac{2V}{2} = \frac{V - 2V}{-j1}$

$I + V = \frac{1}{j} V$


$I = (-1 - j1) V \Rightarrow Z_{ep} = \frac{V}{I} = \frac{1}{-1 - j1} = \frac{-1 + j1}{1^2 + 1^2} = -0.5 + 0.5j \text{ [k}\Omega\text{]}$

$Z_{ep} = -0.5 + 0.5j \text{ [k}\Omega\text{]}$

phasor-diagram

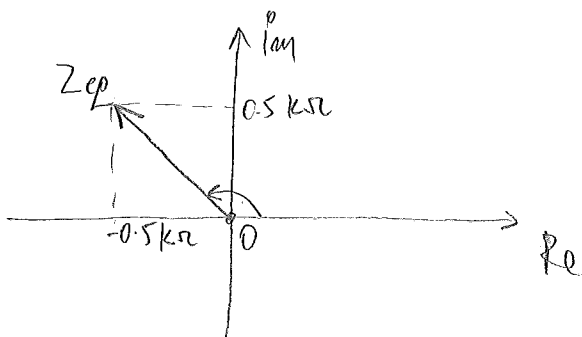

Thevenin equivalent

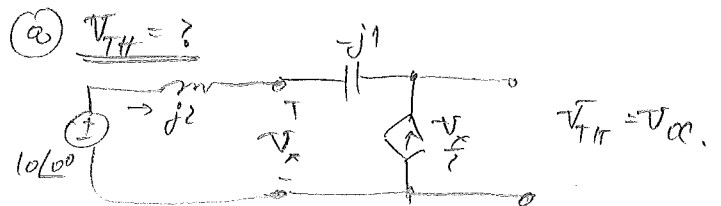

$V_{oc} = V_x + (-j1) \frac{V_x}{2} = (1 - j0.5) \cdot V_x$

$V_x = 10 \angle 0^\circ + (j2) \frac{V_x}{2} \Rightarrow V_x = \frac{10}{1 - j1} = 5 + j5 \text{ V}$

$\Rightarrow V_{oc} = (1 - j0.5)(5 + j5) = 7.906 \angle 18.43^\circ \text{ [V]}$

(b) $Z_{ep} = -0.5 + j0.5 \text{ k}\Omega = 0.707 \angle 135^\circ \text{ k}\Omega$

see above problem

