



Voltage & current sources (pp. 17-22)

Reminder: Please come and ask questions!

Ideal independent voltage sources



A circuit element characterized by a terminal voltage independent of the current thru it.

Symbols:

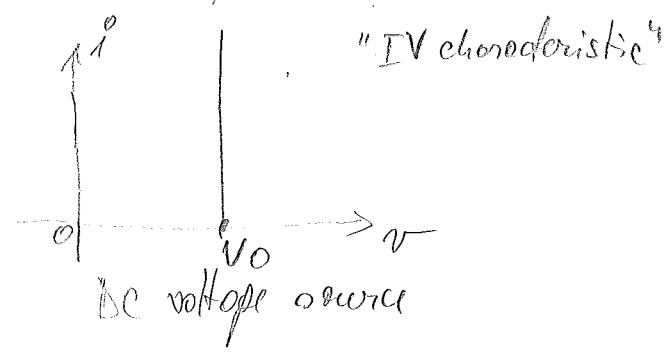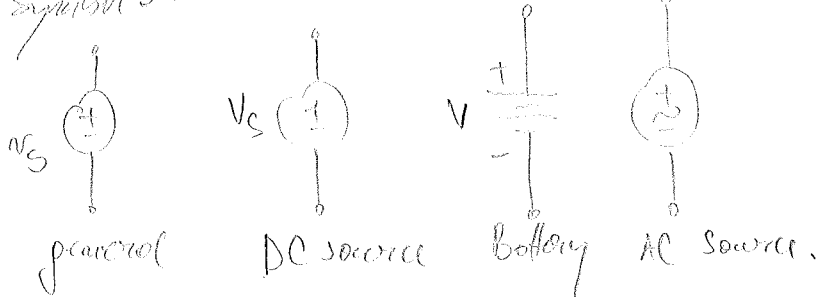


Ideal independent current sources

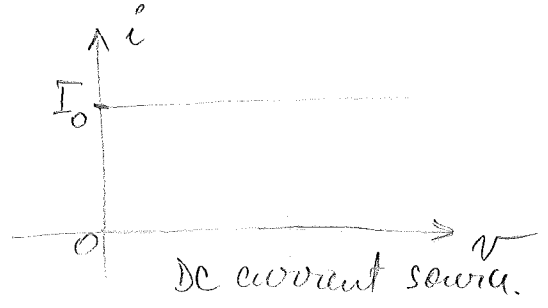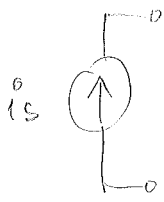The current is independent of the voltage across it.



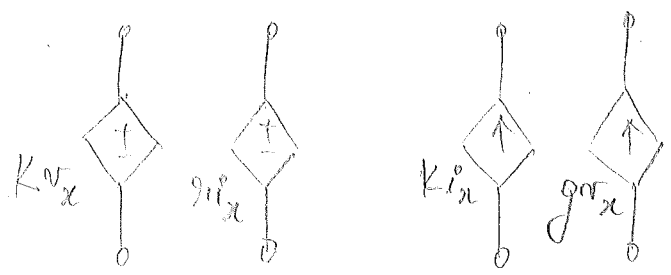Dependent sources (or controlled sources)




Voltage-controlled voltage source -||- -||- -||-
 -||- -||- -||-

- The controlling variable is a different voltage (or current) existing somewhere else in the circuit.
- V, I sources on active elements (opposite of supplying power). Passive elements can only receive power.

Networks and circuits

The interconnection of 2 or more circuit elements \triangleq network.
 A network that has at least a loop \triangleq circuit.

Example:

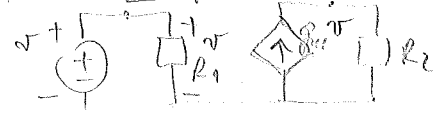

Ohm's Law (pp. 22-28)

When subjected to a test voltage v , a resistance R conducts a current i that is linearly proportional to the applied voltage:


(1) $i = \frac{1}{R} \cdot v$ [Ω]

Ohm [1V] [1A]

and whose direction is always through the resistance out of the positive terminal of the source:


- Alternatively when a current i is forced thru a voltage is developed at terminals.

(2) $v = R \cdot i$

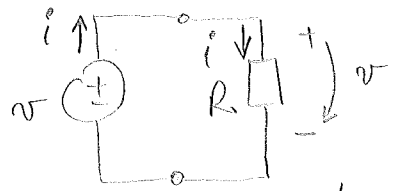


- The IV characteristic is a straight line:

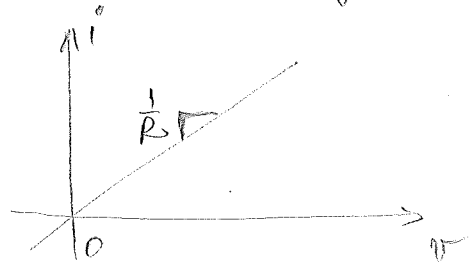Δ This linear relationship between voltage and current is called Ohm's law.




- Example 1: a simple resistor:

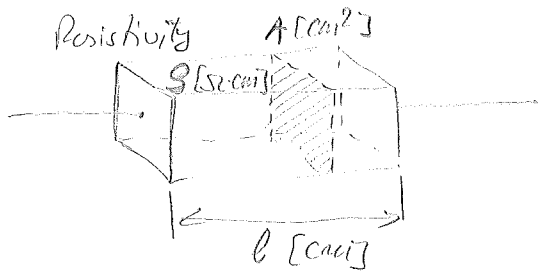

$R = \rho \frac{l}{A}$ [Ω]


Symbol:

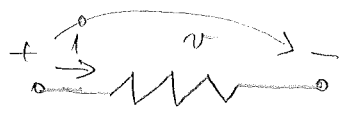

- where resistivity is a "measure" of the easiness with which electrons can travel thru the material.

- OR: R represents the ability to oppose current flow!

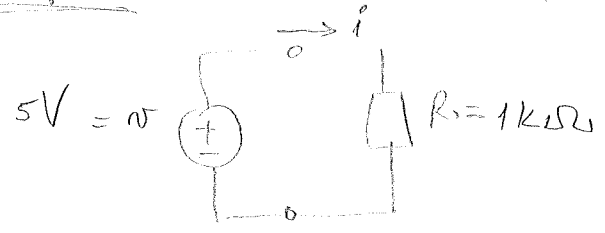- Example 2: Power absorbed by a resistor:



$$p = v \cdot i = v \cdot \frac{v}{R} = \frac{v^2}{R} = \frac{25 \text{ V}^2}{1 \text{ k}\Omega} = \frac{25 \text{ V}^2}{10^3 \Omega} = 25 \cdot 10^{-3} \text{ W} = 25 \text{ mW}$$


(3) $p = v \cdot i = \frac{v^2}{R} = R i^2$

Conductance $G = \frac{1}{R}$ is the inverse of resistance!

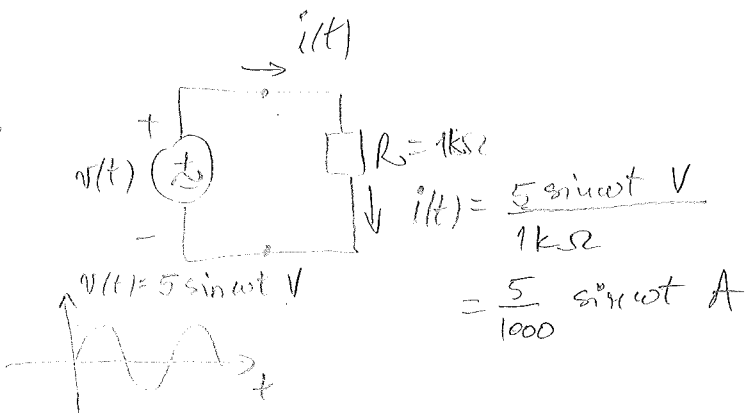(4) $G = \frac{1}{R} = \frac{i}{v}$ [S] Siemens

Final remark:

$p(t) = v(t) i(t)$
 $i(t) = \frac{v(t)}{R}$: example



Reminder You'll get a HW assignment.