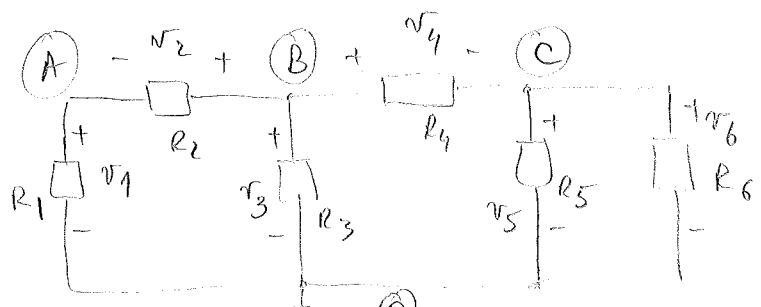


Kirchhoff's Voltage Law (KVL)

- At any instant the sum of voltage risers around a loop must equal the sum of voltage drops around that loop:
- In other words: the algebraic sum of voltages around a loop is zero:

$$(1) \sum v_{\text{RISE}} = \sum v_{\text{DROP}} \quad \text{or} \quad (2) \sum_l v_l = 0$$



- Let's traverse (walk) the loops in clockwise direction:

Loop $R_1 R_2 R_3$: $v_1 + v_2 = v_3$

Loop $R_3 R_4 R_5$: $v_3 = v_4 + v_5$


Loop $R_5 R_6$: $v_5 = v_6$

Loop $R_1 R_2 R_4 R_5$: $v_1 + v_2 = v_4 + v_5$


Loop $R_1 R_2 R_4 R_6$: $v_1 + v_2 = v_4 + v_6$

Loop $R_3 R_4 R_6$: $v_3 = v_4 + v_6$

you already know this:

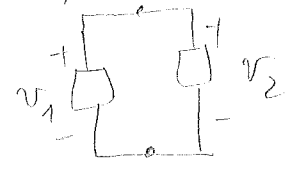

Example

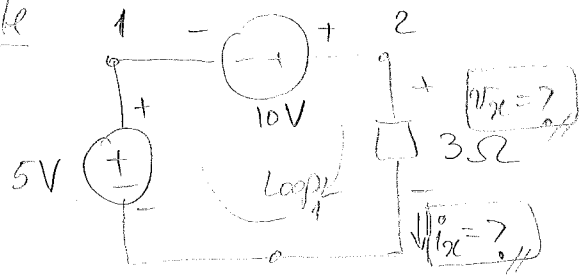


Loop KVL: $5V + 10V = v_x \Rightarrow v_x = 15V$

Ohm's law: $i_x = \frac{v_x}{3\Omega} = \frac{15V}{3\Omega} = 5A$

$i_x = 5A$

Note: Using voltages marked with ones:

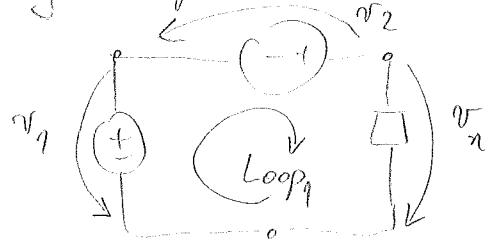


$v_1 + v_2 = v_x$

$-v_1 - v_2 + v_x = 0$


Simple-loop circuit

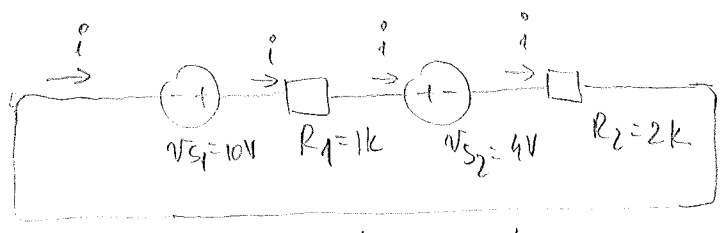- The concept of series connection of circuit elements.



! The current thru each element is the same as series of individual elements.

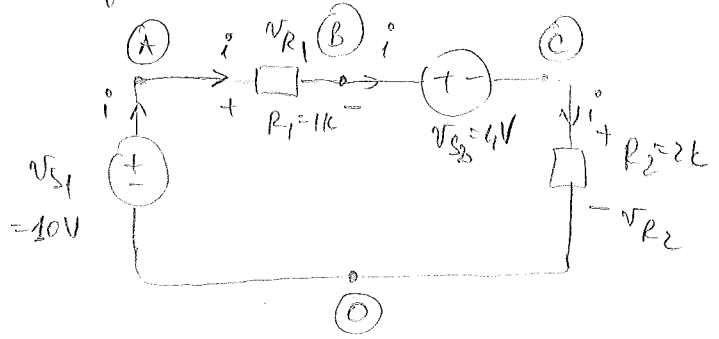- You must prove that this is the same as:



a) $i = ?$

Use KVL and Ohm's law:

$$v_{S1} = v_{R1} + v_{S2} + v_{R2}$$

$$v_{S1} = i \cdot R_1 + v_{S2} + i \cdot R_2$$

$$v_{S1} = i(R_1 + R_2) + v_{S2}$$


$$\Rightarrow i = \frac{v_{S1} - v_{S2}}{R_1 + R_2} = \frac{(10-4)V}{3k\Omega} = \frac{6V}{3k\Omega} = 2 \text{ mA}$$

b) Power consumed by R_2 , $P_{R2} = ?$


$$P_{R2} = v_{R2} \cdot i = (R_2 \cdot i) \cdot i = R_2 i^2 \text{ : observed!}$$

what is power consumed by v_{S1} ?

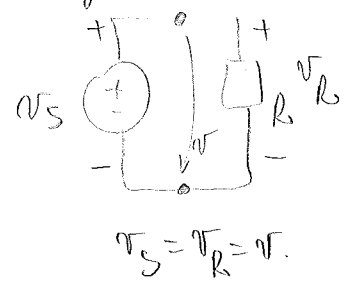- In the particular case of only 2 circuit elements we get for example:




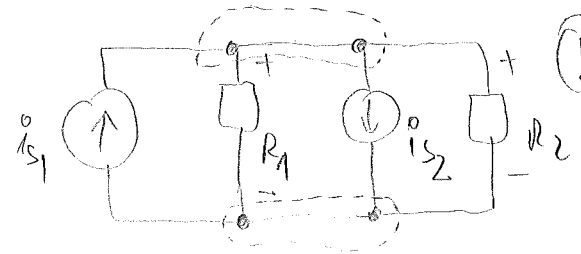This can be generalized to connecting any number of elements between this single-pair of nodes:



! The voltage across all elements is the same!

Example 1:

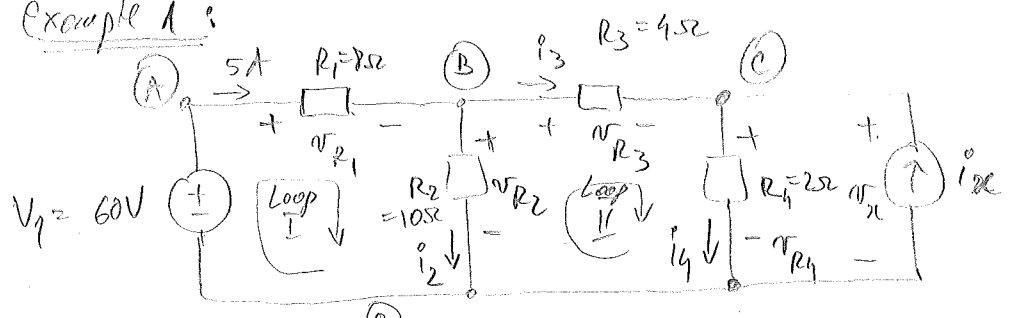

The approach is to contemplate for a little the circuit!

$$v_x = ?$$

$$v_{R4} = v_x$$

but we do not know v_{R4} yet.

- We note that in the left side we have $V_q = 60V$.

- Also: $v_{R1} = R1 \cdot 5A = 8\Omega \cdot 5A = 40V$

- Applying KVL for loop I: $V1 = v_{R1} + v_{R2}$

$$60V = 40V + v_{R2} \Rightarrow v_{R2} = 20V$$

- Having v_{R2} , we could keep moving on with KVL for loop II:

$$v_{R2} = v_{R3} + v_{R4} \Rightarrow v_{R4} = v_{R2} - v_{R3} = 20V - v_{R3}$$

$$\Rightarrow v_{R4} = 20V - R3 \cdot i3$$

- Use KCL for node (B): $5A = i2 + i3 \Rightarrow i3 = 5A - i2$

$$= 5A - \frac{v_{R2}}{R2} = 5A - \frac{20V}{10\Omega} = 3A$$

$$\Rightarrow v_{R4} = 20V - 4\Omega \cdot 3A = 8V$$

$$v_x = v_{R4} = 8V$$