
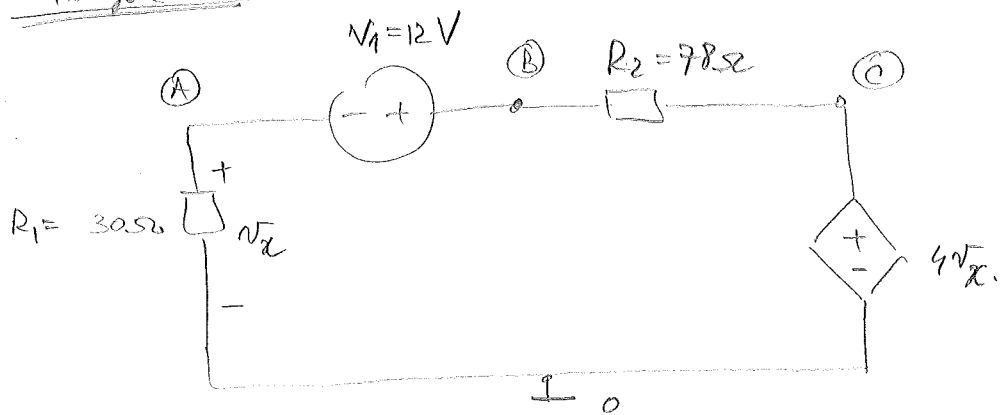


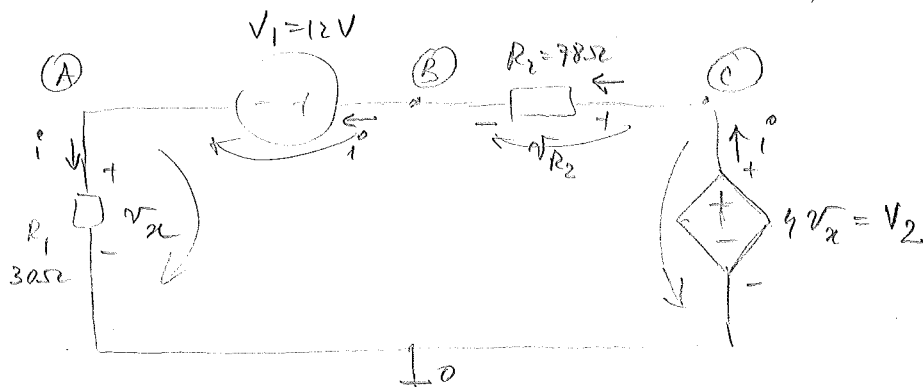Example 2.1

Find the power absorbed by each element in the circuit.



- KVL in the single loop:  $v_x + V_1 + v_{R_2} = 4v_x$

$$R_1 i + V_1 + R_2 i = 4R_1 i$$

$$V_1 = (3R_1 - R_2)i \Rightarrow i = \frac{V_1}{3R_1 - R_2} = \frac{12\text{V}}{(90 - 78)\Omega} = \frac{12\text{V}}{12\Omega} = 1\text{A}$$

- Therefore the power absorbed by:

$$R_1: P_{R_1} = v_x \cdot i = R_1 i^2 = 30\Omega \cdot (1\text{A})^2 = 30\text{W}$$

$$V_1: P_{V_1} = V_1 \cdot i = 12\text{V} \cdot 1\text{A} = 12\text{W}$$

$$R_2: P_{R_2} = v_{R_2} \cdot i = R_2 \cdot i^2 = 78\Omega \times (1\text{A})^2 = 78\text{W}$$


controlled voltage source:  $P = (4v_x) \times (-i) = (4 \times 30\text{V}) \times (-1\text{A}) = -120\text{W}$  : this is actually delivered!

Note: Sum of all power delivered equals the sum of all power absorbed!

Sources connected in series and parallel


Series

(a) Voltage sources:

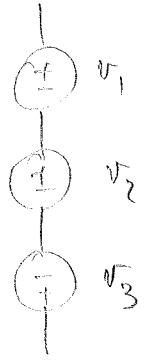


$\equiv$   $\left( \begin{matrix} + \\ - \end{matrix} \right) v_1 + v_2 - v_3$  : generalized to  $n$  number of series connected voltage sources.

(b) current sources:

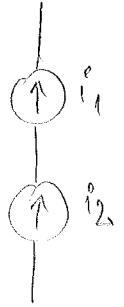


$i_2$  and  $i_1$  must have the same direction & the same value.

Example:

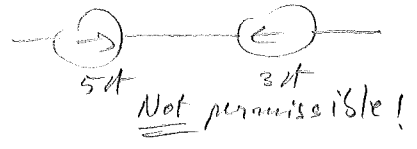


Parallel

(a) current sources:

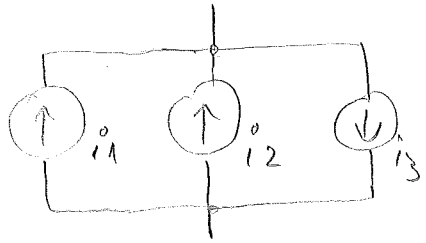


$\equiv$   $\left( \begin{matrix} + \\ - \end{matrix} \right) i_1 + i_2 - i_3$

(b) voltage sources:



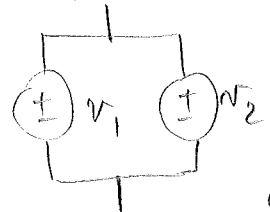


$v_1$  and  $v_2$  must have the same value and polarities.


Example:

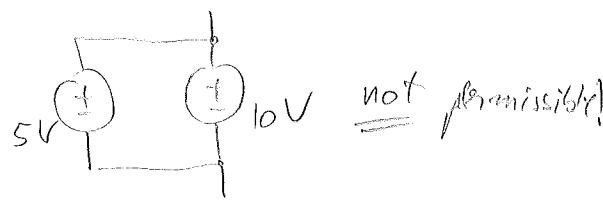

Remarks

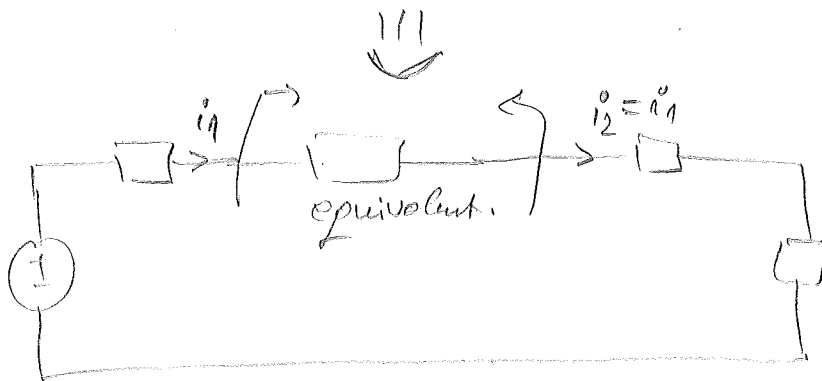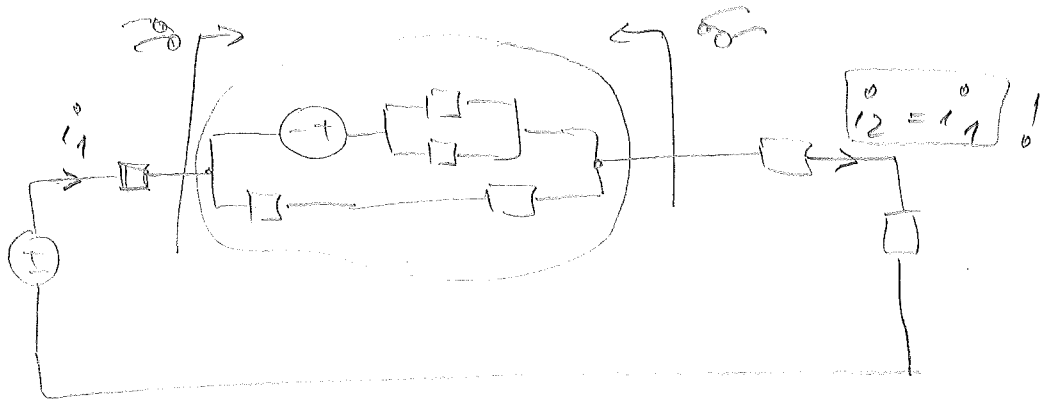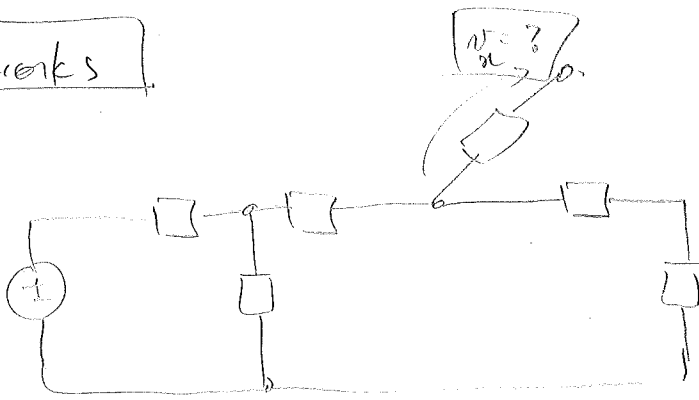

But:

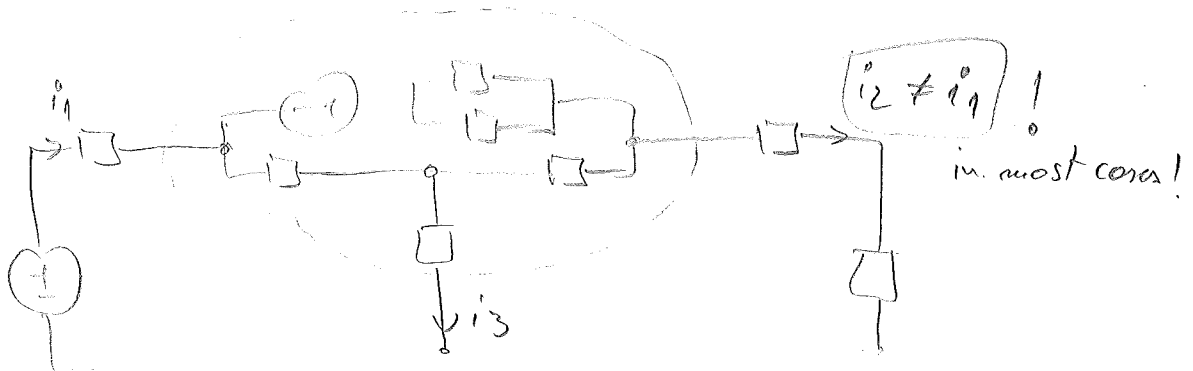

$i_1 = i_2 + i_3$  (!) Think about it!