
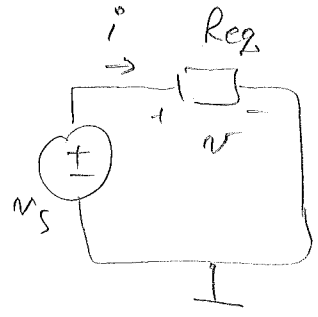


# Resistor combinations

## (1) Series

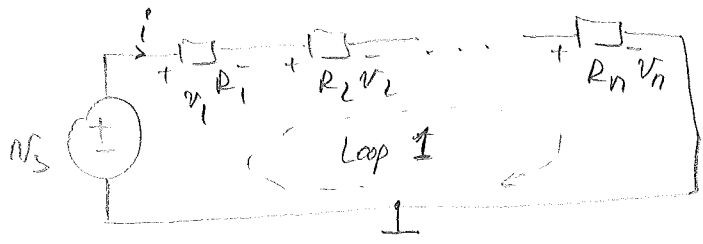


KVL for loop 1:  $v_s = v_1 + v_2 + \dots + v_n$   
 $v_s = i(R_1 + R_2 + \dots + R_n)$

$v_s = v$   
 $v_s = i R_{eq}$


$\Rightarrow R_{eq} = R_1 + R_2 + \dots + R_n$

$R_{eq} = \sum_{i=1}^n R_i$  (1)

Example:

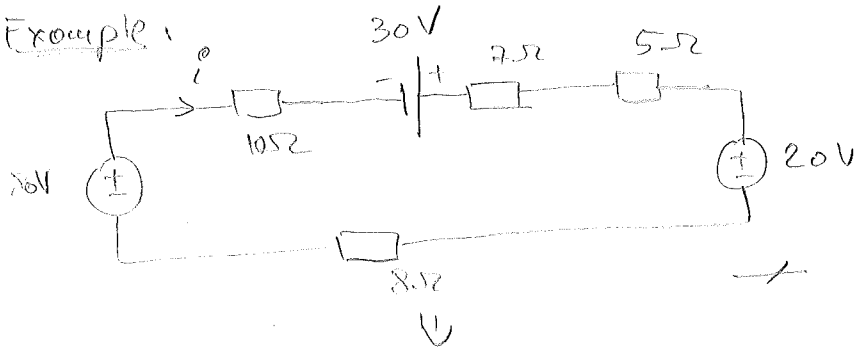


$i = ?$

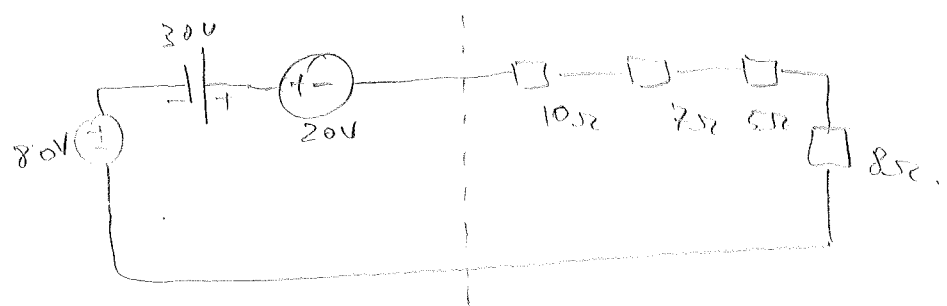


$v_{eq} = 20V + 30V - 20V = 30V$

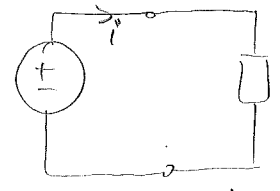$R_{eq} = (10 + 7 + 5 + 20) \Omega = 42 \Omega$



$i = \frac{v_{eq}}{R_{eq}} = \frac{30V}{42\Omega} = 0.714 A$

(2) Parallel connection of resistors

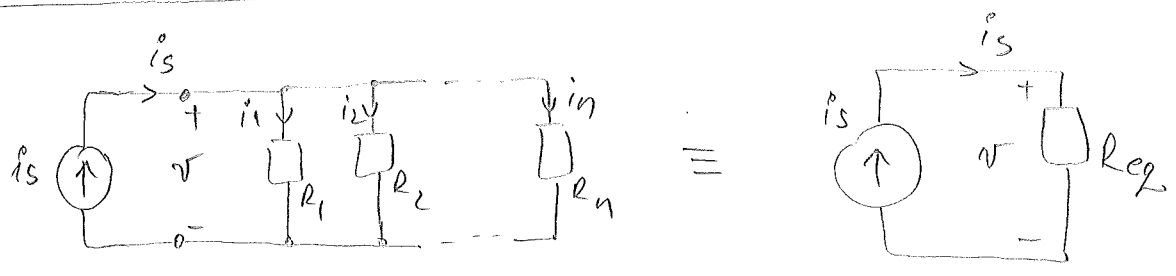

KCL for top node:

$$i_s = i_1 + i_2 + \dots + i_n$$

$$i_s = \frac{v}{R_{eq}}$$

$$i_s = \frac{v}{R_1} + \frac{v}{R_2} + \dots + \frac{v}{R_n}$$

$$i_s = \frac{v}{R_{eq}}$$


$$\Rightarrow \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} = \frac{1}{R_{eq}}$$

$$\Rightarrow R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}} = \frac{1}{\sum_{i=1}^n \frac{1}{R_n}} \quad (2)$$


in terms of conductances:

$$G_{eq} = G_1 + G_2 + \dots + G_n \quad (3)$$

Example:

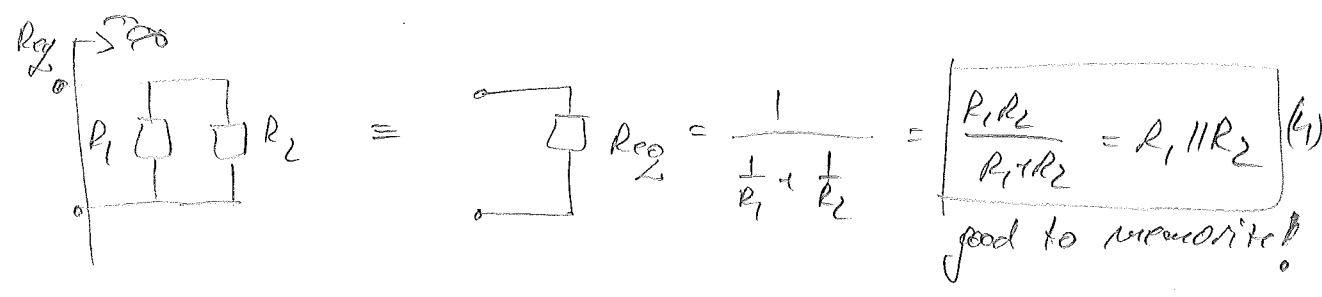

Example:

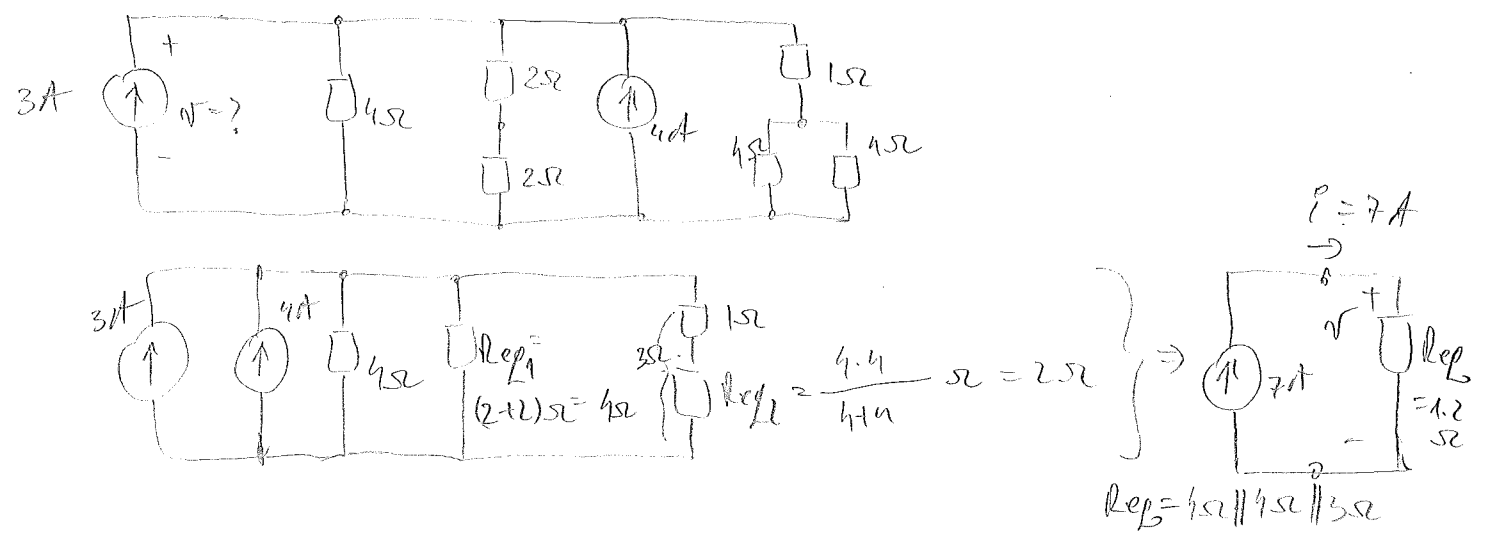

$$R_{eq} = \frac{1}{\frac{3}{4} + \frac{3}{4} + \frac{3}{3}} \Omega = \frac{12}{10} \Omega = 1.2 \Omega$$



$$V = R_{eq} \cdot i = 1.2 \Omega \times 7 A = 8.4 V = v$$

Reference Node

- because only potential differences (or voltages) have practical meaning, it is convenient to reference all node potentials in a circuit to the potential of a common node called the reference node.

- This node is identified by the symbol  $\underline{\underline{0}}$  and its potential is zero by definition!

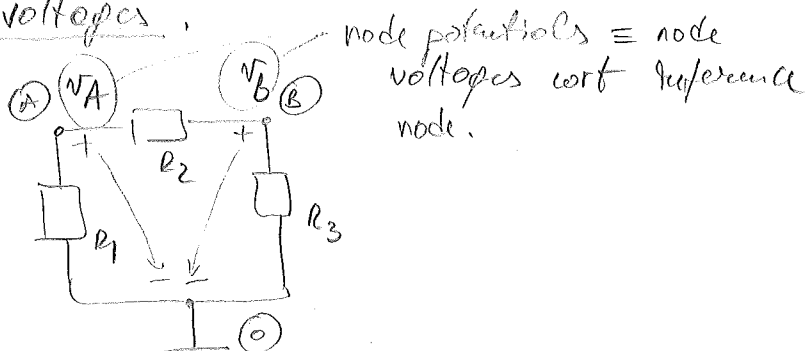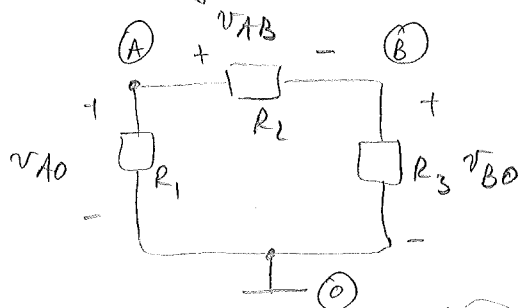- Therefore, when referenced to the reference node, node potentials are simply referred as node voltages.



$$v_{AB} = v_A - v_B$$

$$v_{A0} = v_A - \underbrace{v_0}_{=0} = v_A$$


$$v_{B0} = v_B - \underbrace{v_0}_{=0} = v_B$$

branch voltage drops

node potentials = node voltages.

Note: while  $v_{A0}$ ,  $v_{B0}$  happen to be node voltages,  $v_{AB}$  is not!  $v_{AB}$  is a branch voltage!

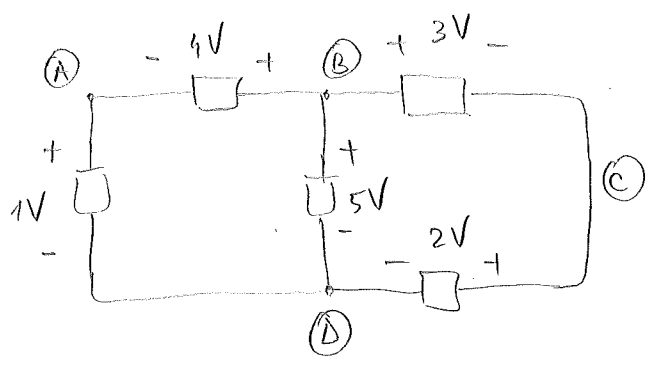- Reference node is not necessarily the bottom-most node in a circuit. It is rather the node with the largest number of connections!



Show node voltages  
for the two different  
choices of node reference!

