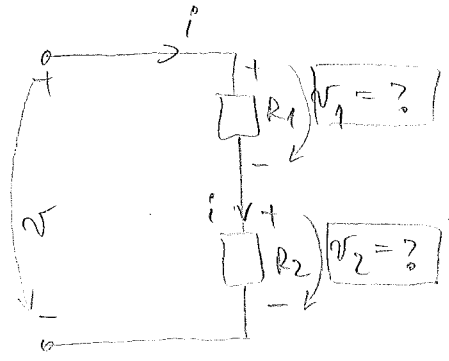


Voltage & current division

(1) Voltage division

- Express voltage across a resistor in series with another resistor as a function of the voltage across both resistors.



KVL: $v = v_1 + v_2$
 $v = iR_1 + iR_2 = i(R_1 + R_2)$


$$i = \frac{v}{R_1 + R_2}$$

Ohm's law for R_1 : $v_1 = R_1 \cdot i$


$$v_1 = \frac{R_1}{R_1 + R_2} v \quad (1)$$

Similarly:
$$v_2 = \frac{R_2}{R_1 + R_2} v \quad (2)$$


Example:

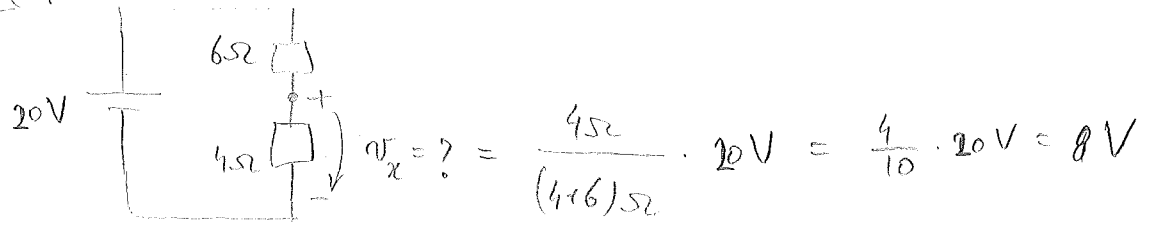

Generalization:

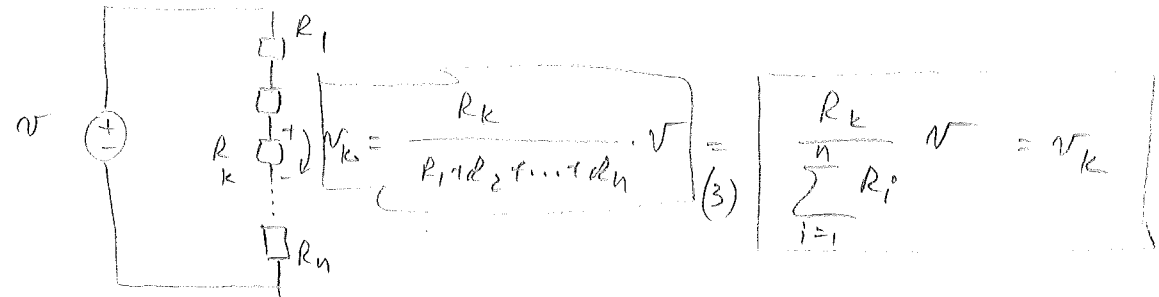


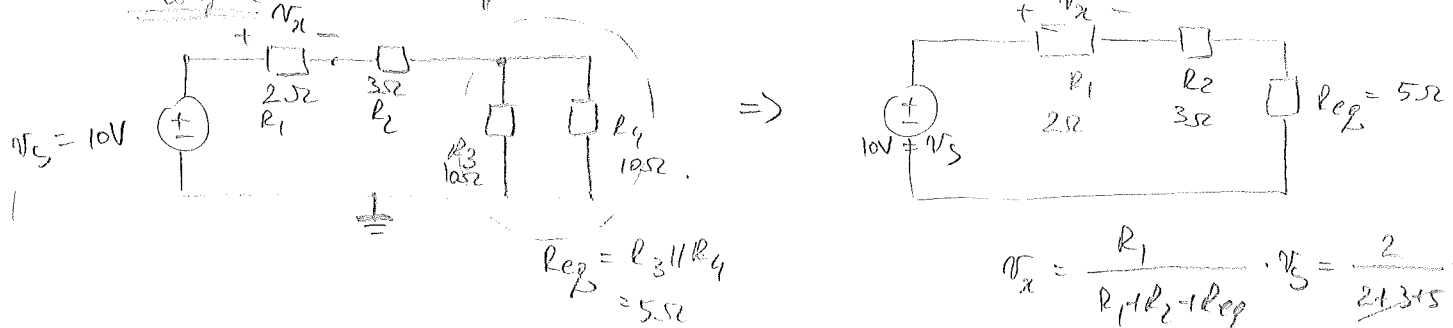Example: use voltage division to determine $v_x = ?$



Note: Could have written $R_{eq} = R_2 + R_3 || R_4$ and simplified to only 2 series resistors.

(2) Current division

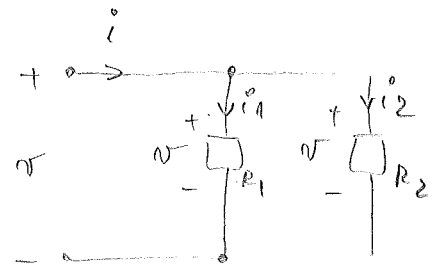

$i_1 = ? = i_1(i)$
 $i_2 = ? = i_2(i)$


KCL: $i = i_1 + i_2 = \frac{v}{R_1} + \frac{v}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \cdot v \Rightarrow v = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \cdot i$

Therefore by Ohm's law again: $i_1 = \frac{v}{R_1} = \frac{1}{R_1} \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \cdot i = \frac{1}{R_1} \cdot \frac{R_1 R_2}{R_1 + R_2} \cdot i$
 $i_1 = \frac{R_2}{R_1 + R_2} \cdot i$ (4)

Similarly: $i_2 = \frac{R_1}{R_1 + R_2} \cdot i$ (5)



Note: 3 differences from (1) & (2) equations!

Generalization:

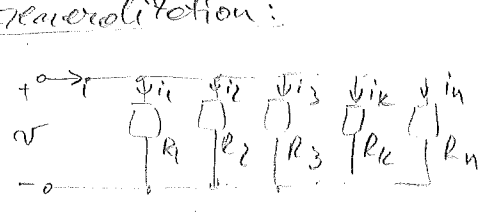


$i_k = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}} \cdot i$ (6)

Example: Find i_x and v_x :

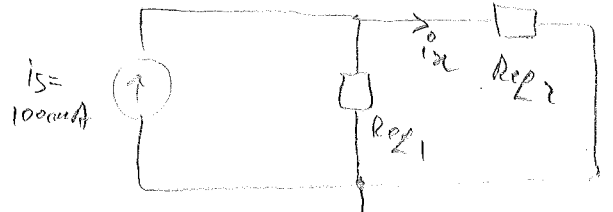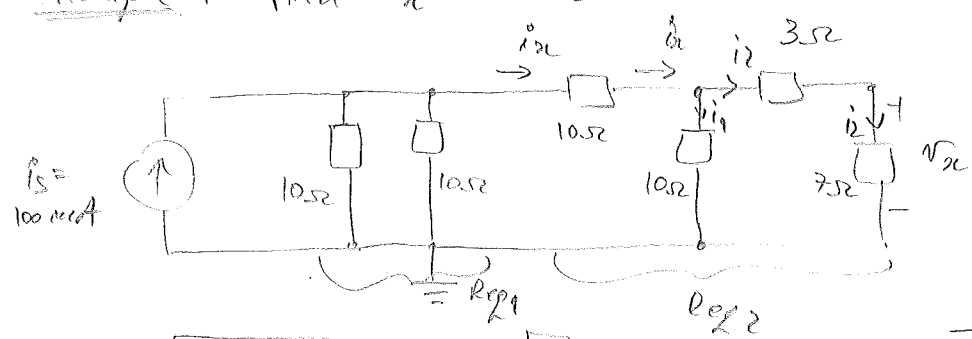

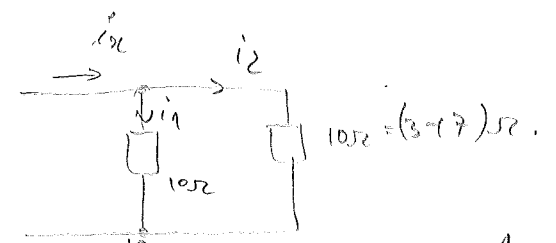$R_{eq1} = 10.5 \parallel 10.5 = 5.25$
 $R_{eq2} = 10.5 + \left[10.5 \parallel (3.5 + 7.5) \right] = 15.5$



$i_2 = \frac{10}{10 + 10} \cdot 25 \text{ mA} = 12.5 \text{ mA}$
 Ohm's law: $v_x = 7.5 \times 12.5 \text{ mA}$

$i_x = \frac{R_{eq1}}{R_{eq1} + R_{eq2}} \cdot i = \frac{5}{5 + 15} \cdot 100 \text{ mA} = 25 \text{ mA} = i_x$