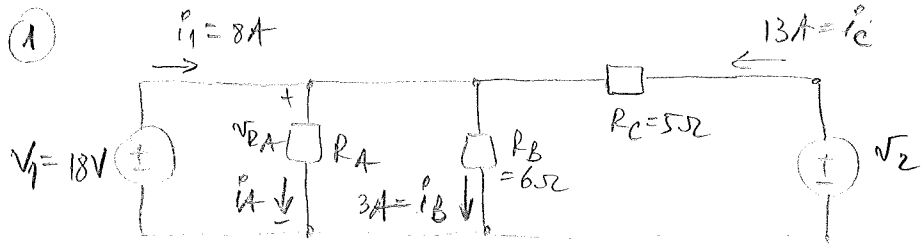


Review for Exam 1

Solved Don → 0 → 10/20

EE-206
 week #5
 Monday



nodes = ?
 # branches = ? , # loops = ?
 RA = ?

nodes = 3
 # branches = 5
 # loops = 6.


$$i_1 + i_c = i_A + i_B$$

$$i_A = i_1 + i_c - i_B = (8 + 13 - 3) A = 18 A$$

$$V_{RA} = V_1 = 18V$$

$$\Rightarrow R_A = \frac{V_{RA}}{i_A} = \frac{18V}{18A} = 1\Omega$$

② Find i_A, i_B, i_C ⊗ do this

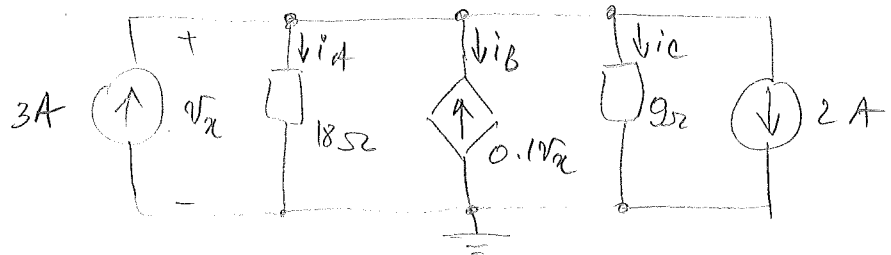

KCL for upper node:

$$3A = i_A + i_B + i_C + 2A$$

$$3A = \frac{v_A}{18\Omega} - 0.1v_A + \frac{v_A}{9\Omega} + 2A$$

$$1 = \frac{v_A - 1.8v_A + 2v_A}{18}$$


$$18 = 1.2v_A \Rightarrow v_A = \frac{18}{1.2} V$$

$$i_A = \frac{v_A}{18\Omega} = \frac{18}{1.2} \cdot \frac{1}{18} A = \frac{1}{1.2} A$$

$$i_B = -0.1v_A = -0.1 \times \frac{18}{1.2} A = -\frac{1.8}{1.2} A$$

$$i_C = \frac{v_A}{9\Omega} = \frac{18}{1.2} \cdot \frac{1}{9} A = \frac{2}{1.2} A$$

3

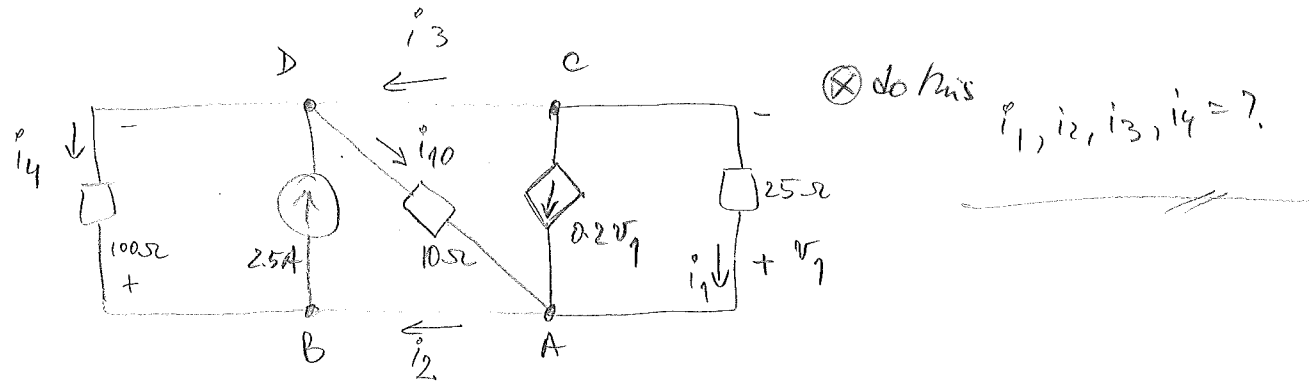

$i_1, i_2, i_3, i_4 = ?$

KCL B: $i_2 + i_4 = 2.5A \Rightarrow i_2 = 2.5A - i_4$

KCL A: $i_1 + i_{10} + 0.2v_1 = i_2 = 2.5A - i_4$

$$-\frac{v_1}{25} - \frac{v_1}{10} + 0.2v_1 = 2.5 - \left(-\frac{v_1}{100}\right)$$

$$-4v_1 - 10v_1 + 20v_1 = 250 + v_1$$

$$5v_1 = 250 \Rightarrow v_1 = 50 [V]$$

$$i_1 = -\frac{v_1}{25} = -\frac{50}{25} A = -2A$$

$$i_4 = -\frac{v_1}{100} = -\frac{50}{100} A = -0.5A$$


$$i_{10} = -\frac{v_1}{10} = -\frac{50}{10} A = -5A$$

$$i_2 + i_4 = 2.5A \Rightarrow i_2 = 2.5A - i_4 = 2.5A - (-0.5A) = 3A$$

$$i_3 + i_1 + 0.2v_1 = 0$$

$$i_3 = -i_1 - 0.2v_1 = 2A - (0.2 \times 50)A = (2 - 10)A = -8A$$

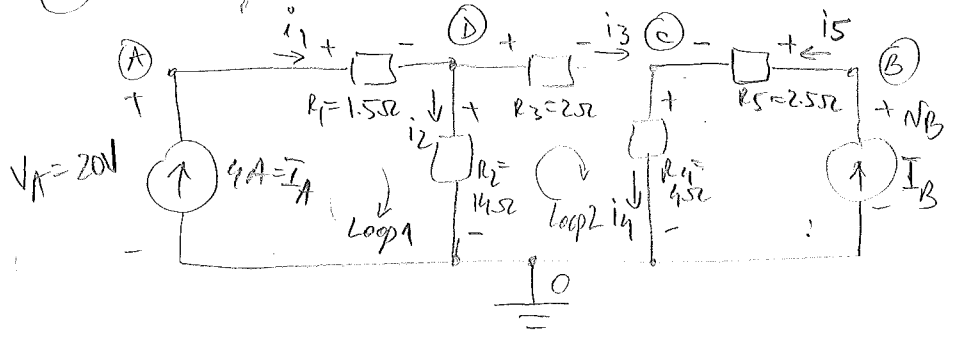4) Find power absorbed by each of the circuit elements: ~~do this~~



Note that:
 $v_A = V_A = 20V$
 $v_D = v_{R2}$
 $v_C = v_{R4}$

KVL Loop 1:

$$V_A = v_{R1} + v_{R2}$$

$$20V = i_1 R_1 + v_{R2} = \underbrace{4A \times 1.5\Omega}_{6V} + v_{R2} \Rightarrow \boxed{v_{R2} = 14V}$$

$$\boxed{v_{R1} = 6V}$$

$$i_2 = \frac{v_{R2}}{R_2} = \frac{14V}{14\Omega} = \boxed{1A = i_2}$$

KVL Loop 2: $v_{R2} = v_{R3} + v_{R4} = R_3 i_3 + v_{R4}$ ↓ KCL node D

$$= R_3 (i_1 - i_2) + v_{R4} = 2(4-1)V + v_{R4}$$

$$= 6V + v_{R4} \Rightarrow v_{R4} = v_{R2} - 6V = (14-6)V = 8V$$

$$\boxed{i_3 = 3A}$$

$$\boxed{v_{R3} = 6V}$$

$$\boxed{v_{R4} = 8V}$$

$$\boxed{i_4 = 2A}$$

$$i_4 = \frac{v_{R4}}{R_4} = \frac{8V}{4\Omega} = 2A$$

KCL node C: $i_3 + i_5 = i_4$

$$i_5 = i_4 - i_3 = 2A - 3A = \boxed{-1A = i_5} = \boxed{-I_B}$$

$$v_B = v_{R5} + v_{R4} = \underbrace{-1A \times 2.5\Omega}_{=v_B} + 2A \times 4\Omega = (8-2.5)V = 5.5V$$

Power absorbed:

I_A : $P_A = v_A \times (-I_A) = -20V \times 4A = -80W$ (delivered!)

I_B : $P_B = v_B \times (-I_B) = 5.5V \times (+1A) = 5.5W$

R_1 : $P_1 = v_{R1} \cdot i_1 = 6V \cdot 4A = 24W$

R_2 : $P_2 = v_{R2} \cdot i_2 = 14V \cdot 1A = 14W$

R_3 : $P_3 = v_{R3} \cdot i_3 = 6V \cdot 3A = 18W$



R_4 : $P_4 = v_{R4} \cdot i_4 = 8V \cdot 2A = 16W$

R_5 : $P_5 = v_{R5} \cdot i_5 = (-2.5V) \times (-1A) = 2.5W$

absorbed:

$$\begin{array}{r} 5.5 \\ 24 \\ 14 \\ 18 \\ 16 \\ 2.5 \\ \hline 80.0 \end{array} W = 80W \text{ delivered!}$$

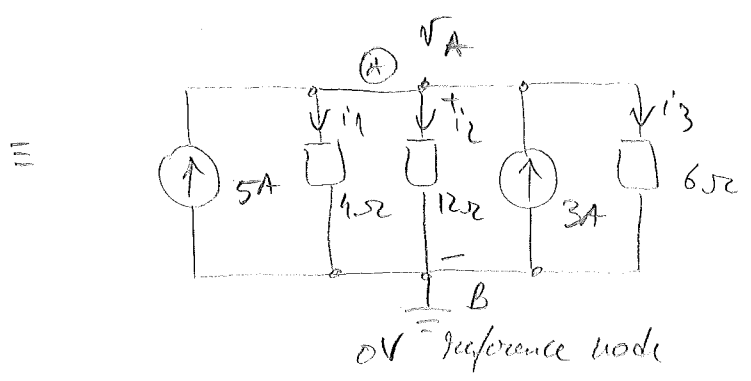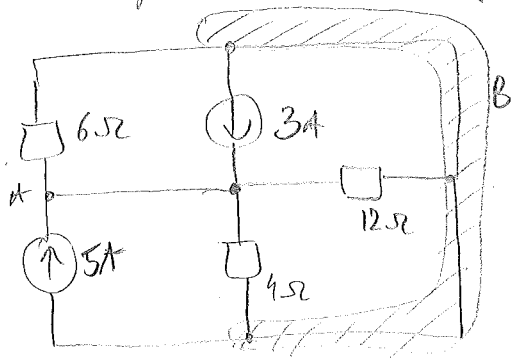5) Find the power absorbed by each of the circuit's elements:





$$5A + 3A = i_1 - i_2 + i_3$$

$$= \frac{3\sqrt{A}}{4\Omega} + \frac{\sqrt{A}}{12\Omega} + \frac{3\sqrt{A}}{3\Omega}$$

$$8A = \frac{8\sqrt{A}}{12\Omega} \Rightarrow \sqrt{A} = 12V$$

The rest is easy...

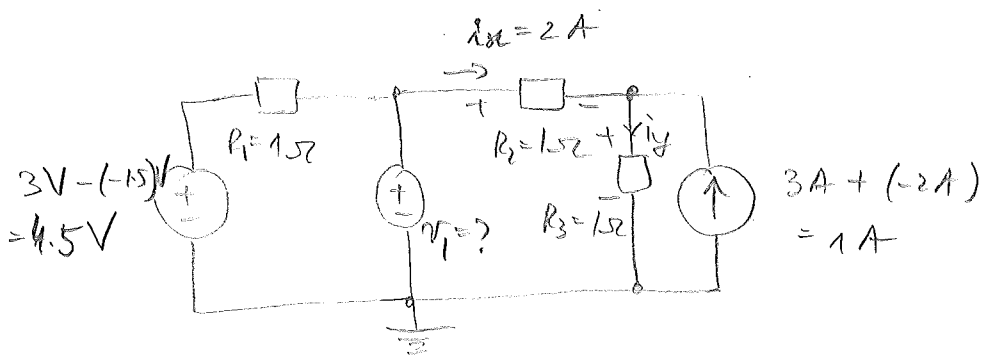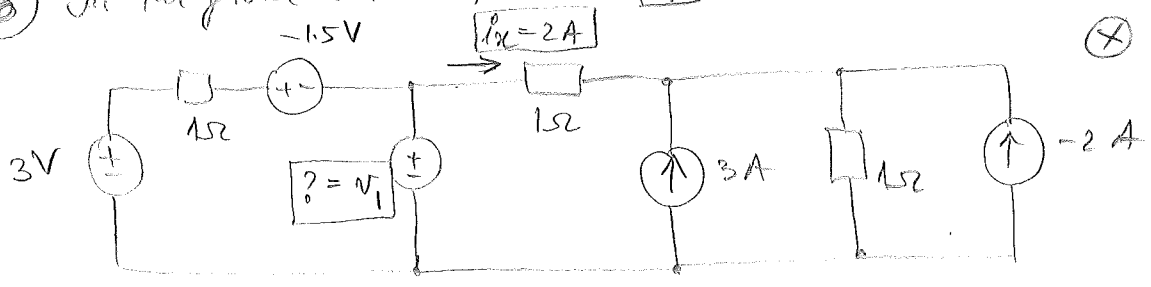6) In the given circuit, choose v_1 to obtain a current i_x of 2A.




$$v_1 = v_{R_2} + v_{R_3} = i_x \cdot R_2 + R_3 \cdot i_y$$

$$= i_x R_2 + R_3 (i_x + 1A)$$



$$v_1 = \underbrace{(R_2 + R_3)}_{2\Omega} \underbrace{i_x}_{2A} + \underbrace{R_3}_{1\Omega} \cdot 1A = 4V + 1V = 5V$$

$$v_1 = 5V$$

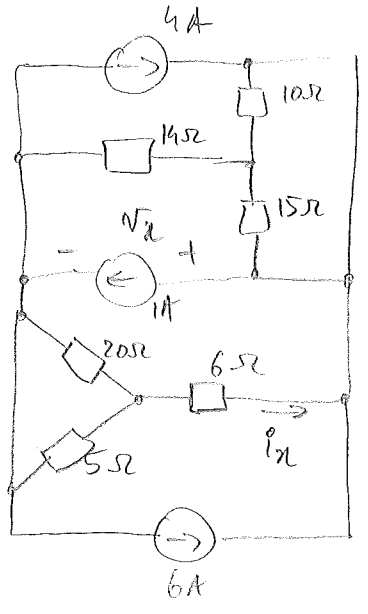7 Use source or resistor combination techniques to find v_x and i_x .



≡

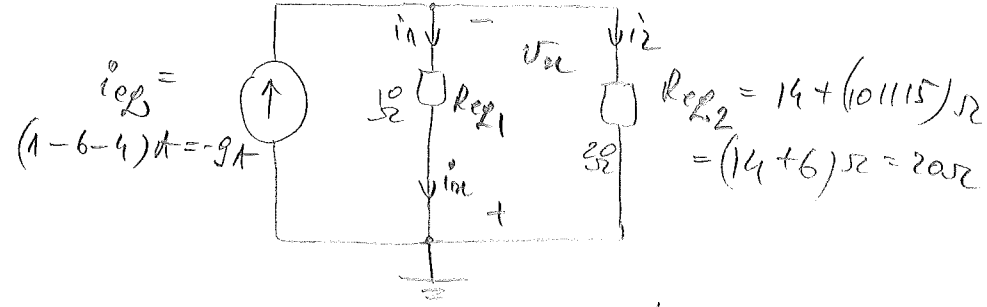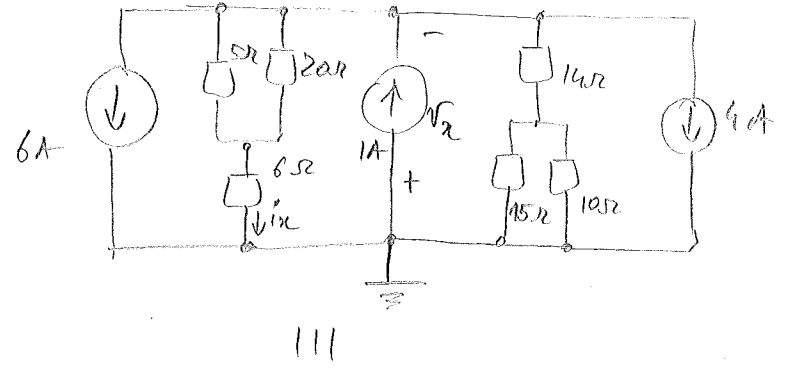

$$i_{eq} = i_1 + i_2 = i_{x1} + i_{x2} \Rightarrow$$

$$i_{eq} = -\frac{v_x}{R_{eq1}} - \frac{v_x}{R_{eq2}}$$

$$-9A = -\frac{2v_x}{10\Omega} - \frac{v_x}{20\Omega} = -\frac{5v_x}{20\Omega}$$

$$\boxed{v_x = 60V}$$

$$i_x = -\frac{v_x}{10\Omega} = -\frac{60V}{10\Omega} = \boxed{-6A = i_{x0}}$$